


Electrical Distribution System Analysis
Dr. Ganesh Kumbhar
Department of Electrical Engineering
Indian Institute of Technology, Roorkee

Lecture – 34
Sequence Component Based Short Circuit Analysis

In the last lecture, we have seen or we have finished load flow analysis and in particular in load flow analysis we have seen 2 3 methods, one is based on backward forward sweep algorithm another is based on direct approach for load flow analysis ah. Initially we have used a direct approach for radial system and then we have extended same approach for weakly meshed system and then finally, we have seen one more method that is gauss implicit Z matrix method.



Today onwards we will start Short Circuit Analysis, so before going to the short circuit analysis let us see why we need a short circuit analysis. So, we know that in normal operating condition the current which is flowing to the various part of distribution system is within the limit specified limit. However, whenever there is short circuiting distribution system the magnitude of current is very large as compared to your rated current or normal limit of your equipment.

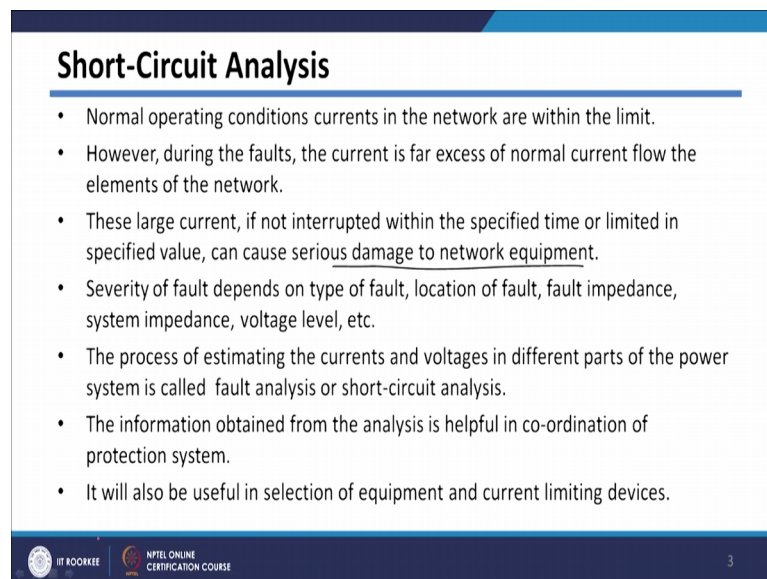(Refer Slide Time: 01:39)



Short-Circuit Analysis

- Normal operating conditions currents in the network are within the limit.
- However, during the faults, the current is far excess of normal current flow the elements of the network.
- These large current, if not interrupted within the specified time or limited in specified value, can cause serious damage to network equipment.
- Severity of fault depends on type of fault, location of fault, fault impedance, system impedance, voltage level, etc.
- The process of estimating the currents and voltages in different parts of the power system is called fault analysis or short-circuit analysis.
- The information obtained from the analysis is helpful in co-ordination of protection system.
- It will also be useful in selection of equipment and current limiting devices.

 IIT ROORKEE  NPTEL ONLINE CERTIFICATION COURSE

3

And if this large current if it is not interrupted or it is not within the limit of magnitude ah; it will cause serious damage to the network equipment, so I just written it here it may

cause the serious damage to your network equipment and the severity of this fault depends on your type of fault location of fault, fault impedance, system impedance and system voltage level.

So, depending upon this fault current may vary and the process of estimating these currents and voltages in the distribution system whenever fault is occurring is called a short circuit analysis or fault analysis. And whatever information we are of obtaining from this fault analysis that is voltage voltages or currents after fault, they will be used for various purposes like they may be required; if you are actually coordinating your protective system. So, for coordinating your relays or protective system we need these information of fault currents and post fault voltages.

We also need this information for selection various equipments, so various equipment will be having some short circuit ratings. And to select par particular equipment in particular location of distribution system, we may need this information like fault current value or post fault voltage values. We also need it for selecting say if you want to put some kind of current limiting device into your distribution system, then also this information will be required. So, if you see or if you classify the faults in the distribution system.

(Refer Slide Time: 03:14)

Symmetrical Components

- Symmetrical Fault: Three-phase fault (LLL) and Three-phase to ground fault LLLG.
- Unsymmetrical Faults: Line to ground (LG), Double line to ground (LLG) and Line-to-Line (LL)

Type of Fault	LG ✓	LL	LLG	Other
Percentage	70 %	15	4	11

LG

LL

LLG

LLL

NPTEL ONLINE CERTIFICATION COURSE
4

The faults can be classified into 2 there is symmetrical faults and unsymmetrical faults. So, symmetrical faults whenever there is three phase faults, that is three phase faults that is LLL faults it is called as or three phase to ground fault that is LLLG fault.


Unsymmetrical faults are 3 types that is line to ground fault where 1 line is falling on the ground, double line to ground faults 2 lines are in contact with ground and then there is third type which is line to line fault where 2 lines are getting short circuited. And if you observe the percentage of these faults probability or percentage of this fault occurrence; the 70 percent faults which are occurring in the distribution system they are LG fault.

So, this is percentage so line to ground fault has a maximum probability of happening; then second is LL fault which is having probability of 15 percent LLG fault is having probability of 4 percent and other faults including your 3 phase fault that is triple L fault or triple LG fault or open conductor fault, they are having probability of 11 percent all other faults. And we know that for our fault studies say in case of line to ground fault as I told you we consider if there are 3 lines, one line will be in contact with ground it may be through some fault impedance, so this is your fault impedance say this is phase a, b and c.

So, here we I can say that there is line to ground fault on phase a, then in case of line to line fault you will be having said these through line 3 lines a b c phases and if you say b phase and c phase getting short circuited through some impedance or directly this ZF may be 0 or some value it is called as line to line fault. So, this is your LG fault, this is your LL fault and in case of LLG fault again these are the 3 phases a b c and I am talking about LLG fault.

So in this case 2 lines will be in contact with the ground through some impedance or directly and then in case of 3 phase fault 3; s, in case of three phase faults all the 3 conductors will be in contact together so it is called as triple L fault and if there is ground be involved it will be triple LG fault so this is LLLG fault.

(Refer Slide Time: 06:03)

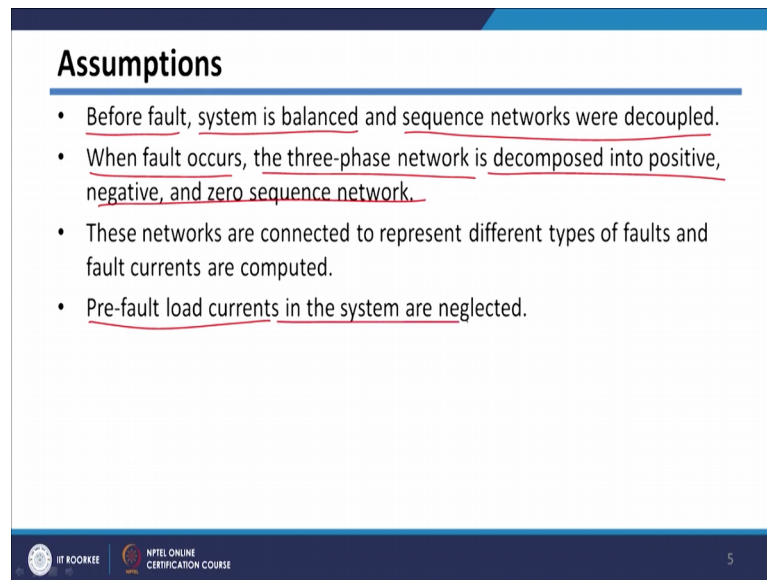

Assumptions

- Before fault, system is balanced and sequence networks were decoupled.
- When fault occurs, the three-phase network is decomposed into positive, negative, and zero sequence network.
- These networks are connected to represent different types of faults and fault currents are computed.
- Pre-fault load currents in the system are neglected.

IIT ROORKEE NPTEL ONLINE CERTIFICATION COURSE 5

So, the basic of method which is used for short circuit analysis which you might have used in your B Tech course; that is symmetrical component based analysis. So, we know that whenever there is unsymmetrical fault, so we use symmetrical components based method to analyze this one.

So, here the assumptions for symmetrical component based system is; we assume that before fault, the system is completely balanced one and sequence networks were decoupled. Basically we assume that since it is balanced only positive sequence network will be existing before fault.

But when the fault occurs the 3 phase networks will be connected and this connection will depend upon what type of fault is existing. So, depending upon your fault there will be different connections of these sequence networks . In this case pre fault load currents of the system will be neglected. So, we are not considering the load current because, the fault current is considered as very large as compared to your load current; so pre fault load current will be considered as negligible.

Now, let us see review your symmetrical component theory, so before going to symmetrical component theory let us revise what we have studied.

(Refer Slide Time: 07:33)

Review of Symmetrical Component

$$\begin{bmatrix} V_a \\ V_b \\ V_c \end{bmatrix} = \begin{bmatrix} 1 & 1 & 1 \\ 1 & a^2 & a \\ 1 & a & a^2 \end{bmatrix} \begin{bmatrix} V_{a0} \\ V_{a1} \\ V_{a2} \end{bmatrix} \quad \left. \begin{array}{l} a = e^{j120^\circ} \\ a^2 = e^{j240^\circ} \\ a^3 = 1 \\ 1 + a + a^2 = 0 \end{array} \right\}$$

$$\begin{bmatrix} I_a \\ I_b \\ I_c \end{bmatrix} = \begin{bmatrix} 1 & 1 & 1 \\ 1 & a^2 & a \\ 1 & a & a^2 \end{bmatrix} \begin{bmatrix} I_{a0} \\ I_{a1} \\ I_{a2} \end{bmatrix}$$

$$\begin{bmatrix} I_{a0} \\ I_{a1} \\ I_{a2} \end{bmatrix} = \frac{1}{3} \begin{bmatrix} 1 & 1 & 1 \\ 1 & a & a^2 \\ 1 & a^2 & a \end{bmatrix} \begin{bmatrix} I_a \\ I_b \\ I_c \end{bmatrix}$$

$$\begin{bmatrix} V_{a0} \\ V_{a1} \\ V_{a2} \end{bmatrix} = \frac{1}{3} \begin{bmatrix} 1 & 1 & 1 \\ 1 & a & a^2 \\ 1 & a^2 & a \end{bmatrix} \begin{bmatrix} V_a \\ V_b \\ V_c \end{bmatrix}$$

IIT ROORKEE NPTEL ONLINE CERTIFICATION COURSE 6

So, you have studied that symmetrical component, so voltages V_a , V_b and V_c 3 phase voltages can be written in terms of 3 symmetrical components, those are V_{a0} which is 0 sequence component, V_{a1} positive sequence, V_{a2} negative sequence and the matrix which converts this sequence component to the phase component is given like this is $\begin{bmatrix} 1 & 1 & 1 \\ 1 & a^2 & a \\ 1 & a & a^2 \end{bmatrix}$. And where we know that your a is e raised to $j 120^\circ$ and a^2 will be then e raised to $j 240^\circ$ and then a^3 we know that it is equal to 1 and one more identity we know that $1 + a + a^2$ is actually equal to 0.


We also this side this relation in case of current that is current I_a , I_b and I_c all the 3 currents phase currents can be written in terms of their sequence component, those are I_{a0} , I_{a1} and I_{a2} . And there were same matrix that exists here that is $\begin{bmatrix} 1 & 1 & 1 \\ 1 & a & a^2 \\ 1 & a^2 & a \end{bmatrix}$ and if you want to you better studied this and then if you want to back convert this, you will be having this relation.

So, you want to calculate sequence components I_{a0} , I_{a1} and I_{a2} , sequence component we want to calculate from your phase components that is V_a sorry I_a , I_b and I_c . So, this current here is I_a and here we are having this inverse of this matrix. So, it will come $\frac{1}{3}$ here and then $\begin{bmatrix} 1 & 1 & 1 \\ 1 & a & a^2 \\ 1 & a^2 & a \end{bmatrix}$ and then $\begin{bmatrix} I_a \\ I_b \\ I_c \end{bmatrix}$.

Similarly, for voltages also we can write voltage V_{a0} , V_{a1} , V_{a2} sequence voltages will be equal to $\frac{1}{3}$ the same matrix $\begin{bmatrix} 1 & 1 & 1 \\ 1 & a & a^2 \\ 1 & a^2 & a \end{bmatrix}$ into your phase voltages that is V_a , V_b and V_c . So, this is how we convert from phase quantities to the sequence

quantities and from the sequence quantities to the phase quantities and the variable which we are using it here is a which is e raised to $j 120$ degree.

(Refer Slide Time: 10:34)

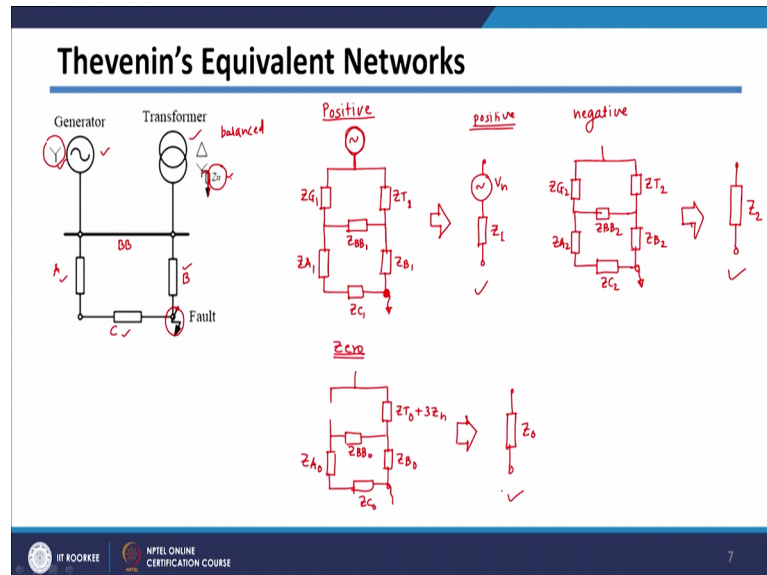

Now, let us see if you are having any distribution system, how we can convert this distribution system into various sequence networks. But this sequence networks we want something like Thevenin's equivalent network. So, let us consider this particular distribution system very simple distribution system I have taken it here, let us say this is generator here the transformer, which is delta and y grounded with some impedance there is this 3 lines which are forming the loop and let us say your fault has taken place at this location.

In this case also we can easily draw a positive sequence, negative sequence and 0 sequence diagrams for this, let us say we are drawing positive sequence network. So, positive sequence network will be something like this, so the both the source can be clubbed together into one source, then there will be impedance of your generator, this is impedance of your transformer, then this is impedance of your bus bar, and this is say this is say line A, this is say line B and this is say line C. So, this will be impedance of line A, this is impedance of line B, and this is impedance of line C and your fault has taken place at this location.

So, in this case this is your source of this network, this impedance will be since it is positive sequence network I can say it is Z_{G1} , Z_{T1} positive sequence transformer

impedance, this will be Z_{BB1} this is, so this is bus bar I can say Z_{BB} this is Z_{A1} , Z_{B1} and this is Z_{C1} and we can actually using series parallel combination of impedances or sometimes you may need to convert are you to use star delta conversion and by after doing that, we can convert this network into this network, equivalent Thevenin's equivalent to a positive sequence network.

So, this is your positive sequence Thevenin's equivalent network which will be having source say this source is V_n Thevenin's equivalent source, and this is your Z_1 equivalent theories Thevenin's equivalent impedance, which at this fault location point.

Exactly similar way we can draw negative sequence network also, so if you also considering negative sequence network, it will be similar only thing is there will not be source here because, as I told you we are considering source which is perfectly balanced. So, the sources which are coming from both the sides are perfectly balanced.

So, therefore they will not be source negative sequence source into the network, only positive sequence source will be existing. So, this is related to generator so Z_{G2} , this will be Z_{T2} , this is Z_{BB2} , this is Z_{A2} , this is Z_{B2} , and this is Z_{C2} and fault is taken place at this location.

Now, this network also we can simplify using series parallel combination or star delta conversion, we can have a simple impedance network, which will be converted into single impedance and this impedance I am calling it Z_2 . So, negative sequence network will be converted into single impedance here, it will not be having any kind of source.

Similarly, in case of 0 sequence network, so in case of 0 sequence network since the neutral of the generator is not grounded, there will not be 0 sequence current path for this network through generator. So, here if you draw this network since there is no path for 0 sequence through generator this will be open here, then there will be impedance of transformer will come here, plus there is some impedance, which is in the neuta in the grounded circuit or arc circuit of this transformer.

So, this impedance will be Z_{T0} transformers 0 sequence impedance, plus 3 times your Z_N that is impedance in ground path and then this will be your other things will remain same. So, and the fault I will taken plate at this location, so this will be 0 sequence impedance of bus bar. So, I can Z_0 Z_{B0} V_0 this is Z_{A0} , Z_{B0} and Z_{C0} .

So, this all this 0 sequence network also we can simplify and this network can be converted into single impedance and this single impedance will be called as Z_0 . So, we have got all the 3 of Thevenins equivalent sequence network, this is positive sequence network, negative sequence network and 0 sequence network and using this network.

For a different types of fault depending upon which fault is there on the system we can connect these network accordingly and do the fault analysis. So, in case of this sequence component analysis based analysis, we first get this sequence network till fault point and then according to fault, we connect this network to get the fault current.

(Refer Slide Time: 16:43)

LG Fault

Boundary condition

$$V_a = 0 \quad V_a = Z_f I_f$$

$$I_f = I_a$$

$$I_b = 0$$

$$I_c = 0$$

$$I_{a1} = \frac{V_n}{Z_1 + Z_2 + Z_0}$$

$$I_f = I_a = I_{a0} + I_{a1} + I_{a2}$$

$$= 3 I_{a1}$$

$$= \frac{3 V_n}{Z_1 + Z_2 + Z_0}$$

$(Z_f \text{ and } Z_n \text{ present})$

$$Z_0 = (Z'_0 + 3Z_f + 3Z_n)$$

$$I_b = I_{a0} + a^2 I_{a1} + a I_{a2} = 0 \quad \text{--- (1)}$$

$$I_c = I_{a0} + a I_{a1} + a^2 I_{a2} = 0 \quad \text{--- (2)}$$

Subtract (1) from (2)

$$(a - a^2) I_{a1} + (a^2 - a) I_{a2} = 0$$

$$I_{a1} = I_{a2} \quad \text{--- (3)}$$

from equation (1)

$$I_b = I_{a0} + (a^2 + a) I_{a1} = 0$$

$$I_{a0} - I_{a1} = 0$$

$$I_{a0} = I_{a1} \quad \text{--- (4)}$$

$$I_{a1} = I_{a2} = I_{a0}$$

So, let us say you are analyzing LG fault, so in case of LG fault as I told you let us say there is fault on phase A, which is getting faulted. So, in this case you are the boundary conditions, so we can see that since this is getting grounded your voltage V_a will become equal to 0 ah, if there is some fault impedance it will not be exactly 0 if there is fault impedance this V_a will be equal to $Z_f I_f$ if so there is some fault impedance in this path.

Another boundary condition this fault current will be equal to your current I_a because, this current I_a is actually basically become your fault current. And then other currents in that case will be negligible as compared to I_a . So, I_b will be equal to 0 and I_c will be equal to 0.

Now, we can get your sequence networks, your sequence networks are something like this is your positive sequence network, this is your negative sequence network and this is your 0 sequence network. So, this is your Z_1 this is your Z_2 and this is your Z_0 and we want to check how they are getting connected to check that let us see what we can do.

So, you are we have seen that I_b is actually equal to from the sequence component point of view, you see it will be I_{a0} plus a square I_{a1} plus $a^2 I_{a2}$. Similarly if you write the equation for I_c it will be I_{a0} plus $a^2 I_{a1}$ plus a square I_{a2} and we have seen that I_b and I_c both are 0, so they will be equator.

So, say this is equation 1 and equation 2 subtract 1 from 2, so I_{a0} I_{a0} cancelled out. So, it will be a minus a square into I_{a1} plus it will be a square minus a into I_{a2} is equal to 0 and if you put the values of a square minus a or a minus a square it is just opposite of each other then we can just say I_{a1} will be equal to your I_{a2} and if you put this equation into equation number 1.

So, from equation 1 we can write by putting I_{a1} is equal to I_{a2} . So, I can say I_b will be equal to I_{a0} plus a square plus a into I_{a1} will be equal to 0 and we have seen that this is nothing but minus 1. So, I_{a0} minus I_{a1} will be equal to zero. So, I can say I_{a0} will be equal to I_{a1} .

So, you can see this from equation number 3 and 4, your I_{a1} is equal to I_{a2} is equal to your I_{a0} . So, means since all the 3 currents are equal, so this is your current I_{a1} , this is your current I_{a2} and this is current I_{a0} and since they are equal your network should be connected in series like this then only these currents will become equal.

So, these networks will be connected in series and you can easily calculate now all these currents which are I_{a1} will be equal to whatever source voltage V_n . So, this will be V_n divided by your Z_1 plus Z_2 plus your Z_0 and we know that your fault current is actually your fault current I_a , which is basically equal to I_{a0} plus I_{a1} plus I_{a2} all of them are equal. So, I can say 3 times I_{a1} and therefore your fault current will be 3 V_n divided by Z_1 plus Z_2 plus your Z_0 .

Ah Now if there is so this we have derived if there is of fault impedance is 0. So, if there is some fault impedance Z_F also, if there is some impedance in neutral circuit of your generator that will get added into this Z_0 .

So, in that case whenever there is ZF and Zn present. So, ZF is nothing, but your fault impedance and Zn is nothing but your impedance with which your source is grounded. So, in that case your Z0 will be consisting of Z0 dash plus 3 times of ZF plus 3 times of your Zn.

So, this is nothing but your 0 sequence impedance of network and this is nothing but fault impedance, which is no getting multiplied by 3 and this is nothing, but your impedance with which your source is grounded that is Zn multiplied by 3. So, this is how we can calculate your fault current in case of LG fault. Now, if there is say LL fault so in case of LL fault.

(Refer Slide Time: 23:06)

LL Fault

$$I_a = 0$$

$$I_f = I_b$$

$$I_c = -I_b$$

$$V_b - V_c = 0$$

if z_F

$$V_b - V_c = z_F I_f = z_F I_b$$

$$I_{a1} = \frac{V_n}{z_1 + z_2}$$

$$I_{a2} = -\frac{V_n}{z_1 + z_2}$$

$$I_f = I_b = I_{a0} + a^2 I_{a1} + a I_{a2}$$

$$= (a^2 - a) I_{a1}$$

$$= -j\sqrt{3} \frac{V_n}{z_1 + z_2}$$

$$I_{a1} = \frac{V_n}{z_1 + z_2 + z_F}$$

$$\begin{bmatrix} I_{a0} \\ I_{a1} \\ I_{a2} \end{bmatrix} = \frac{1}{3} \begin{bmatrix} 1 & 1 & 1 \\ 1 & a & a^2 \\ 1 & a^2 & a \end{bmatrix} \begin{bmatrix} 0 \\ I_b \\ -I_b \end{bmatrix}$$

$$I_{a1} = \frac{1}{3} (a I_b - a^2 I_b) \quad \text{--- (1)}$$

$$I_{a2} = \frac{1}{3} (a^2 I_b - a I_b) \quad \text{--- (2)}$$

$$I_{a1} = -I_{a2} \quad \text{--- (3)}$$

$$I_{a0} = 0 \quad \text{--- (4)}$$

Let us say again this is true let us say your this is phase a b and c your phase b and c they are short circuited. So, in this case yeah the boundary conditions are like this so your Ia will be equal to 0, your Ib so this current is nothing but your current Ib and this current is nothing but current Ic n. So, fault current will be nothing but current Ib and current Ic will be opposite of your current Ib Ic ah. So, Ic will be opposite of current Ib.

Also one more boundary condition when you can get that is Vb minus Vc will be equal to 0, if there is no fault impedance in the fault; if there is some impedance into this fault we can say Vb minus Vc is equal to ZF into Ib. But initially we are not considering this impedance here.

So, therefore it is directly short circuited like this. If you consider now these 2 equations that is so this equation I will take will later. So, it is V if ZF present then $V_b - V_c$ will be equal to ZF multiplied by your I F, which is multiple basically ZF multiplied by your I_b .

Now, let us see this I_{a1} or I_{a0} , I_{a1} and I_{a2} , it is actually equal to we have seen that is $1 \text{ by } 3 \text{ } 1 \text{ } 1$, 1 a a square , $1 \text{ a square a into this currents}$ that is $I_a I_b$ and I_c we are seeing actually minus I_b . So, instead of I_c I can put minus I_b into this case and I_{a0} . So, instead of I_a also I can put 0 here, so I_a is 0. So, I can put it like this.

So, I can say that I_{a1} will be equal to $1 \text{ by } 3 \text{ into a into } I_b \text{ minus a square into } I_b$ and I_{a2} also, it is $1 \text{ by } 3 \text{ into a square into } I_b \text{ minus a into } I_b$ and if you see this equation 1 and equation 2, I can easily see that I_{a1} is equal to minus I_{a2} .

So, from this equation we can easily find out also we know that actually I_{a0} will be equal to 0 because, ground is not involved here it is a LL fault, since the ground is not involved your 0 sequence a current will be equal to 0. So, from this equation say 3 and 4 we can easily draw the connections for this network connection. So, sequence again I am taking this 3 networks. So, it is positive sequence network and then this is your 0 sequence network and this is your current I_{a1} and this is current I_{a2} and I_{a1} and I_{a2} just opposite of each other means we need to connect these circuits like this, then only they will be in opposite direction.

So, from this equation 3 and 4 we can draw equivalent circuit and from this we can easily find out the current I_{a1} . So, current I_{a1} I can just write if the source is V_n here v_n and this impedance is Z_1 this impedance is Z_2 because, this is negative sequence network here. So, V_n divided by Z_1 plus Z_2 ah.

Similarly I_{a2} will be equal to minus V_n divided by Z_1 plus Z_2 and then we know that your fault current is basically your current I_b which is equal to I_{a0} plus a square into I_{a1} plus a into I_{a2} . So, in this case I_a it is already 0 and they are just minus of each other. So, it will be a square minus a into I_{a1} , which is basically minus $j \text{ root } 3$ and I_{a1} we have got V_n divided by your Z_1 plus Z_2 .

So, this is nothing but your fault current equation, which is basically I_b . So, we can get the fault current using this equation here. If there is some impedance in fault path then

this impedance will get connected. So, in this case the new connection of your sequence network will be something like this. So, this is your V_n this is your Z_1 this is your Z_2 0 negative sequence network and this is your Z_F .

So, in this case your I_{a1} for this network your I_{a1} will be equal to V_n divided by Z_1 plus Z_2 plus Z_F and then similarly I_f will be calculated using the same relation. So, this is how actually we can get the fault currents in LL faults.

(Refer Slide Time: 29:24)

LLG Fault

$I_a = 0$
 $I_f = I_b + I_c$
 $V_b = V_c = 0$
 if p z_f present $V_b = V_c = Z_f I_f = Z_f (I_b + I_c)$

$I_{a1} = \frac{V_n}{Z_1 + \frac{Z_2 Z_0}{Z_2 + Z_0}}$
 $I_{a2} = \left(-\frac{Z_0}{Z_0 + Z_2} \right) I_{a1}$
 $I_{a0} = \left(-\frac{Z_2}{Z_0 + Z_2} \right) I_{a1}$

$I_b = I_{a1} + a^2 I_{a2} + a I_{a0}$ — (5)
 $I_c = I_{a1} + a I_{a2} + a^2 I_{a0}$ — (6)
 $I_f = I_b + I_c$ — (7)

$V_b = 0 = V_{a0} + a^2 V_{a1} + a V_{a2}$ — (1)
 $V_c = 0 = V_{a0} + a V_{a1} + a^2 V_{a2}$ — (2)

Subtract (1) from (2)

$(a - a^2) V_{a1} + (a^2 - a) V_{a2} = 0$
 $V_{a1} = V_{a2}$ — (3)

$0 = V_{a0} + a^2 V_{a1} + a V_{a1}$
 $= V_{a0} + \frac{(a^2 + a)}{1} V_{a1}$
 $V_{a0} = -V_{a1}$ — (4)

from (3) and (4)

$V_{a0} = V_{a1} = V_{a2}$

In case of LLG fault, so in case of LLG fault let us consider there are 3 abc phases and line to line to ground fault is occurring inside b and c phases. So, b and c phases they are getting shorted and they will be grounded it here, so initially I am considering the fault with 0 fault impedance.

So, in this case boundary conditions are something like this one boundary condition is that I_a is equal to 0 because, fault is not occurred on phase a. Then a fault current total fault current will be equal to I_b plus I_c . So, this is nothing but your current I_b and this is nothing but current I_c and I_b plus I_c will be nothing but this total fault current.

Another boundary condition we can have that is V_b will be equal to V_c will be equal to 0 because, they are actually both of them have grounded. If Z_F is present if Z_F present in that case V_b will be equal to V_c will be equal to Z_f multiplied by your fault current and that is equal to Z_F multiplied by fault current is actually I_b plus your I_c .

Now, let us see what we can get in this case, so we have actually V_b which is equal to 0 and V_b we know that $V_a 0$ plus a square $V_a 1$ plus a $V_a 2$ similarly V_c which is equal to 0. So, I can say $V_a 0$ plus a $V_a 1$ plus a square $V_a 2$ and if you subtract this equation 1 and 2 from each other. So, from subtract 1 from 2, so if you subtract this this will get cancelled out. So, it will be a minus a square into $V_a 1$ plus a square minus a into $V_a 2$ which will be equal to 0 and we have seen that these 2 quantities are just opposite of each other means sign will be is negative, in that case $V_a 1$ will be equal to your $V_a 2$.

After this same equation which is 3 if I put into equation number 1 I can get 0 is equal to $V_a 0$ plus a square $V_a 1$ plus a into $V_a 1$. So, in this case $V_a 0$ plus a square plus a into $V_a 1$ and a square is nothing, but minus 1. So, in that case $V_a 0$ will become equal to $V_a 1$, so what we are getting it from this is say equation number 4. So, we are getting from 3 and 4 we can say that $V_a 0$ will be equal to $V_a 1$ will be equal to $V_a 2$.

So, this 3 and 4 which will give us how these networks are connected. So, in this case these 3 networks I am just drawing it here. So, this is positive sequence network this is negative sequence network and this is 0 sequence network and this is current $I_a 1$ $I_a 2$ and $I_a 0$ and the voltage across all the 3 it is coming same means all these 3 networks will be connected in parallel. So, this is I will just say Z_1 Z_2 and Z_0 they will be connected in parallel like this.

So, since they are connected in parallel we can write equation for $I_a 1$ which will be equal to say this is V_n , so it will be v_n divided by total impedance of this circuit. So, this is the Z_2 and Z_0 they are coming in parallel and in series with Z_1 . So, it will be Z_1 plus this parallel combination of Z_2 and Z_0 will be Z_2 multiplied by Z_0 divided by Z_2 plus Z_0 .


So, this will give me $I_a 1$ and once I get $I_a 1$ your $I_a 2$ will be equal to minus because, signs they are opposite minus Z_0 divided by Z_0 plus Z_2 into $I_a 1$. So, depending upon a current division the current will get divided into $I_a 2$ and $I_a 0$. So, $I_a 2$ will be proportional to the Z_0 divided by Z_0 plus Z_2 and $I_a 0$ will be proportional to minus Z_2 divided by Z_2 divided by Z_0 plus Z_2 into $I_a 1$.

So, once you get all the 3 current that is $I_a 1$, $I_a 2$, $I_a 0$ we can get the fault current which is basically I_b plus I_c . So, we can just say I_b will be equal to $I_a 0$ plus a square $I_a 1$ plus a $I_a 2$. So, I_b can I can get because $I_a 1$, $I_a 2$, $I_a 3$, $I_a 1$, $I_a 2$, $I_a 0$ already calculated and

then I_c will be equal to I_{a0} plus a into I_{a1} plus a^2 into I_{a2} . So, once you get this I_b and I_c your fault current total fault current in system will be equal to I_b plus I_c .

And if there is any fault impedance which present in the ground path. So, if there is a fault impedance Z_F present here, then you need to connect 3 times of Z_F in series with of Z_0 impedance. So, in this case this $3 Z_0 Z_F$ impedance will be connected here and then analysis will remain same.

(Refer Slide Time: 36:25)

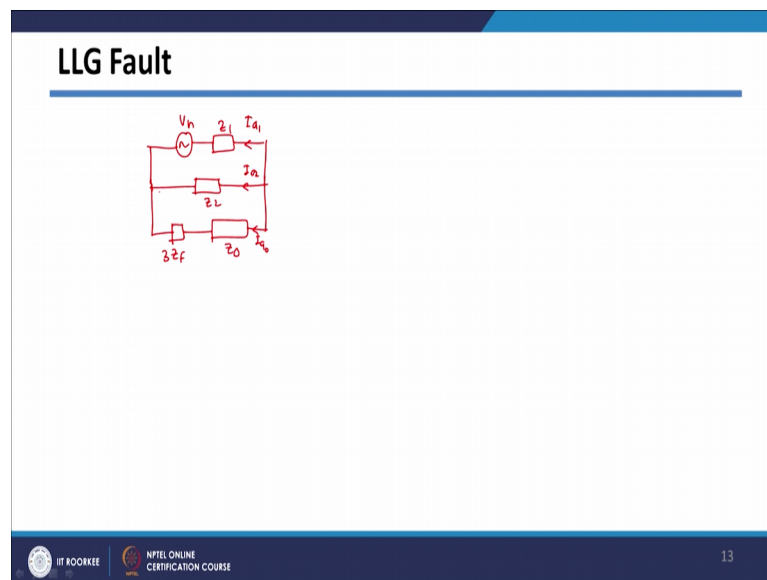

So, new network with impedance will be something like this. So, you are having this positive sequence impedance then negative sequence impedance and this is 0 sequence impedance. But if there is fault impedance in the path, so it will be $3 Z_F$ this will be Z_0 this is Z_2 and the Z_1 and V_n and this is nothing but I_{a1} I_{a2} and this is I_{a0} .

So, we can easily get the values of I_{a1} I_{a2} and I_{a0} after solving this circuit and you can get value of I_F I_{a1} I_{a2} I_{a0} will be from this 1 and only thing is in Z_F , you need to add actually plus $3 Z_F$ there otherwise equation will remain same and you can get the fault current also which is basically I_b plus I_c .

So, in this particular lecture we have started with short circuit analysis and in the short circuit analysis we have started with symmetrical component based analysis because, we already studied it in power system analysis course basically it is used for transmission system widely because it is balanced. However, there are limitations of its use in

distribution system all these limitations of symmetrical component we have study we will see in the next lecture.

Thank you.