

**Flexible AC Transmission Systems (FACTS) Devices**  
**Dr. Avik Bhattacharya**  
**Department of Electrical Engineering**  
**Indian Institute of Technology Roorkee**


**Lecture – 30**  
**Voltage and Phase Angle Regulator Device - II**

Thank you for your kind attention. We shall continue our discussions with the FACTS Devices. This is will be a second lectures on the voltage and the phase angle regulator devices where we have left, we start from that point that is actually that tap changer is feeding highly inductive load, so this is the recapitulation of our previous class.

(Refer Slide Time: 01:13)
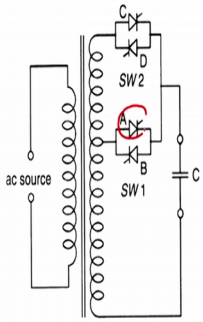
### Continuous Voltage Control regulator (Cont...)

- As the load power factor approaches unity, the interval for  $\alpha_1$ ,  $0 < \alpha_1 < \phi$  diminishes
- The interval for  $\alpha_2$ ,  $\phi < \alpha_2 < \pi$  stretches over the whole half-cycle, from zero to  $\pi$ .
- i.e at a unity power factor (resistive) load,  $\alpha_1 = 0$  and  $\alpha_2 = \alpha$   
Thyristor tap changer has a purely capacitive load
- The capacitive load here is assumed to be capacitive at supply frequency only, and
- Highly inductive to all harmonics, in order not to terminate the thyristor controller with a voltage source at both terminals




As the load power factor approaches unity, so that is for the resistive load that interval for in case of the inductive load you know, it is approaching to the resistive load, alpha should be form actually from actually change from 0 to phi, and it is diminishes. And the interval for alpha 2 will be actually phi to actually till pi, and stretches over the whole half cycle, for the pre at 0 to pi so that is the actually the changes.

That mean what happened in for in resistive kind of power factor you know at unity power factor, the load alpha 1 should be equal to 0, and alpha 2 will be equal to actually alpha. So, that is the actually, then the inductive loads actually goes to the resistive load.

Now, let us take another option, if the load is purely capacitive, the thyristor tap changer has a purely capacitive loading, it is quite difficult to analyze, because you know that these capacitor is dangerous. Their required the DID deputation and all those things, but since there is a leakage inductance across it so there is a series in that you already inserted so you can use it.

Capacitor load here is assumed to be capacitor, and the supply frequency only. Please note that of course, the according to the frequency the system become omega l or omega C can be capacity 1 negative. Highly inductive for all the harmonics, in order to actually terminate the thyristor control with the voltage source of the both the terminal, this is the configuration. So, upper half cycle actually when so of the lower thyristor will be named as A same as the what we have done in case of the inductive one; and lower is B, and upper is C and low is D.

(Refer Slide Time: 03:19)

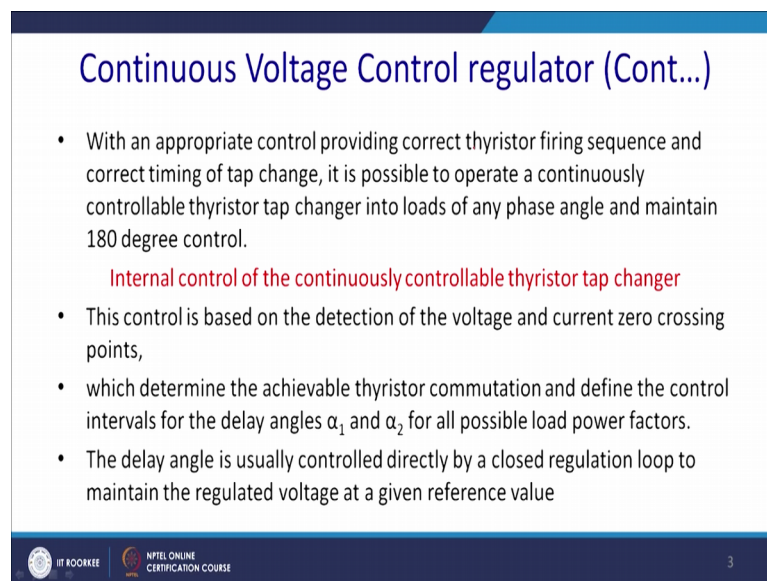

**Continuous Voltage Control regulator (Cont...)**

- With an appropriate control providing correct thyristor firing sequence and correct timing of tap change, it is possible to operate a continuously controllable thyristor tap changer into loads of any phase angle and maintain 180 degree control.

**Internal control of the continuously controllable thyristor tap changer**

- This control is based on the detection of the voltage and current zero crossing points,
- which determine the achievable thyristor commutation and define the control intervals for the delay angles  $\alpha_1$  and  $\alpha_2$  for all possible load power factors.
- The delay angle is usually controlled directly by a closed regulation loop to maintain the regulated voltage at a given reference value


IIT ROORKEE NPTEL ONLINE CERTIFICATION COURSE 3

So, what happened, with an appropriate control providing the direct thyristor firing sequence, and correct timing tap change. This possible to operate a continuously controllable thyristor tap changer into the load to any phase angle, and you can maintain the 180 degree control. The internal control of this continuously control thyristors, will be discussed on.

This control is based on detections of the voltage, and the zero crossing point of the current, because here current will lead the voltage which determines the achievable

thyristor commutations. And define the control interval for the delay angle  $\alpha_1$  and  $\alpha_2$  for all possible load factors. The delay angle is usually controlled directly by a close regulations loop to maintain the regulated voltage and a high reference value. So, this is the way actually it is being controlled.

(Refer Slide Time: 04:31)

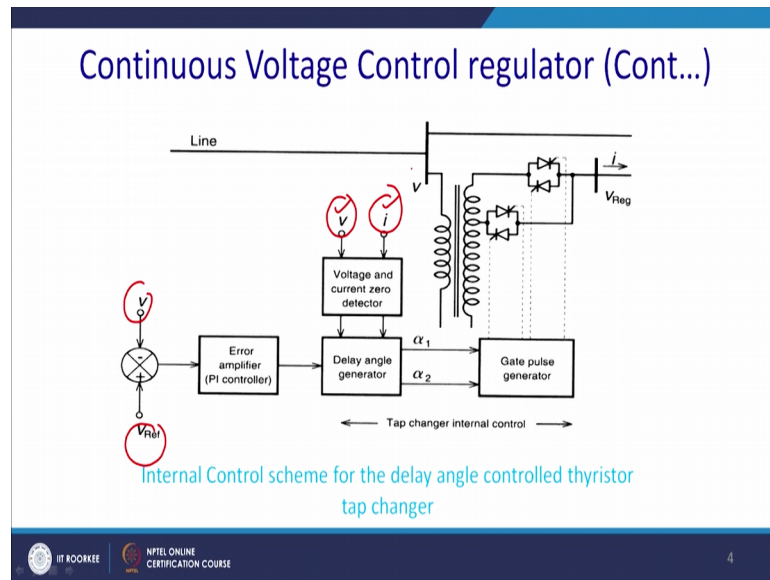

So, do you got a  $V$  and you got a  $V_{ref}$ . See you got and P i controller from P i controller actually error can be calculated. And this is actually the information about the zero crossing of voltage and current. And they will be a delay angle estimation of  $\alpha_1$  and  $\alpha_2$  an accordingly actually you change the thyristors according to the load. So, these information  $v_1$  and  $v_2$ ,  $v_1$  and  $i_1$  will depend on the type of load you will have.

(Refer Slide Time: 04:56)

### Continuous Voltage Control regulator (Cont...)

Major disadvantages of a delay angle controlled thyristor tap changer to achieve continuous control

- First, the fundamental component of the terminal voltage is phase shifted from the source (bus) voltage by an amount depending on the gating angle  $\alpha$  and  $\phi$  the load phase angle, and the direction of this phase shift depends on the load phase angle
- This can lead to significant problems in transmission applications where even small arbitrary phase shifts can have serious consequences in an interconnected ac network

IIT ROORKEE NPTL ONLINE CERTIFICATION COURSE 5

So, continuous voltage control regulation, major disadvantage of the delay angle control of the thyristor tap changer actually to harmonics, it injects harmonics. And for this we actually go towards this continuous angle control method.

First, the fundamental component of the terminal voltage is phase shifted from the source voltage by amount depending on the getting angle  $\alpha$  and the  $\phi$ , the load phase angle. And the direction of the phase shift depends on the load phase angle, whether it is inductive or capacitive, it depends on it. This can lead to significant problem in transmission line application, where small arbitrary phase shift can have a serious consequence in the interconnected network. So, you have we have discussed in our previous class, there is a circulating current. If there is a little phase angle delay, so it least to the phase angle delay, and thus we cannot do that.



(Refer Slide Time: 06:11)

**Continuous Voltage Control regulator (Cont...)**

- The thyristor tap changer with delay angle control is more likely to be applied as a voltage regulator in distribution systems than as a more general, voltage and angle regulator in transmission systems.
- Second drawback is, the low-order harmonics can have magnitudes, even for small values of inter-tap voltages, which may be unacceptable in many utility applications.
- Thus, an output harmonic filter is almost certainly required for a continuously controlled thyristor tap changer applied in a utility environment.

IIT ROORKEE NPTL ONLINE CERTIFICATION COURSE 6

The thyristor tap changer with delay angle control is more likely to be applied as a voltage regulator in distribution system, than has a more general, voltage and the angular (Refer Time: 06:25) in transmission system. Second drawback is, the lower order harmonic actually have a quite sufficient magnitude, we have same the harmonic spectrum in our previous discussions. Low-order harmonic can have a magnitude, even small value of inter-tap voltages, which may be unacceptable in many utility applications.

So, for this results we have to actually get rid of this disturbance. Thus what happened to have to find the solution, and output harmonic filter is almost certainly required for continuously control thyristor tap changer applied to the utility environment that adds to the extra cost to the system.

(Refer Slide Time: 07:19)

The slide features a blue header with the title "Thyristor Tap Changer with Discrete Level Control" in white. Below the title, there are three bullet points in black text. The slide has a dark blue footer containing logos for IIT ROORKEE and NPTEL ONLINE CERTIFICATION COURSE, along with the number 7.

### Thyristor Tap Changer with Discrete Level Control

- The problems associated with a continuously controllable thyristor tap changer can be avoided with the application of discrete level voltage control conventional electromechanical tap changers.
- With discrete level control tap changing function can be achieved without introducing harmonic distortion or undesirable phase shifts and without the control complexities
- The choice of power circuit is decided by performance requirements and cost (two possible circuit configurations).

IIT ROORKEE NPTEL ONLINE CERTIFICATION COURSE 7


The problem associated with the continuously controlled thyristor tap changer can be avoided with the application of the discrete level voltage control conventional electromechanical tap changer that will see now.

With discrete level control tap changing function can be achieved without introducing harmonic distortion or undesirable phase shift without with any control complexities. So, it is just mechanical tap changer. So, it was previously connected to the  $n$  number of tons, thereafter it will be  $n + 1$  number of tons for  $n + 1$  is greater than in something like that. The choice of the power circuit is decided by performance requirement and the cost, two possible circuit configuration can be actually observed here.

(Refer Slide Time: 08:12)
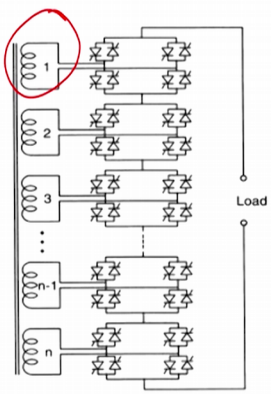
### Discrete Level Control(Cont...)

- A conceptually simple tap-changing configuration, In this scheme each winding section is bridged by four bi-directional thyristor valves,
- Thus may be inserted in the outside (transmission line) circuit in either polarity or bypassed, giving  $0$  to  $\pm V$  volts availability in  $V/n$  steps.
- If 16 equal sections are used to give 33 steps capability over  $V$  volts with current rating  $I$ , then the total required thyristor valve rating is  $(V/16 \times 64)I = 4VI$



IIT ROORKEE    NFTEL ONLINE CERTIFICATION COURSE    8

So, this is the case of discrete level voltage regulator. What happened, you can have a number of actually secondary, and they have in cascaded. So, you have a, but you have a different level of it, and you can bypass a particular level, or you can take the level through the magnetics and thus you can step it or step it down. And in this case, either this actually 1 or 2 or any level is not used and thus actually turns ratio of primary to secondary get decreased or increase according to the requirement.

Conceptually, the simple tap changing configuration, in this scheme each winding section is bridged with four bi-directional thyristor valves. So, this is the four bi-directional thyristor valve. You can allow current to pass through this switches, pass through this magnetics, or you can simply bypass this magnetics, you have a choice.

Thus maybe inserted in the outside transmission line, the circuit either polarity or bypassed, noise] giving angle 0 or plus minus 0 volt to this  $V$  by  $n$  number of steps. If 16 equal sections are used, so that any 16 to give 33 capability over  $V$  volts, then thyristor will be consider below with the current rating  $i$ , then the total required thyristors will be actually thyristor rating is  $V$  by 16 into 64. So, that is actually quite high value of that is quite actually low voltage. So, that rating of the thyristors is practically available in our existing network.

(Refer Slide Time: 10:28)

### Discrete Level Control(Cont...)

- With this rating the actual voltage control range is 2 V and thus the ratio of controlled VA range to valve VA rating is only two
- The thyristor tap changer, in contrast to the previously considered shunt and reactive compensators, can neither generate nor absorb reactive power.
- The reactive power supplied to or absorbed from a line when it injects in phase or quadrature voltage must be absorbed by or supplied to it by the ac system.
- Due to this reason, both the series insertion and shunt regulating transformers must be fully rated for the total VI product

IIT ROORKEE | NFTEL ONLINE CERTIFICATION COURSE 9

So, for this session this kind of modular kind of solution discrete level control is quite popular compare to that what we have discussed previously. The rating with this rating of the actual rating voltage control range is 2 V, and thus the ratio of the control VA range to the valve VA rating is only two. The thyristor tap changer, in contrast to the previously consider shunt or the reactive compensator, can either generate nor absorb reactive power. So, there cannot control the real power.

The reactive power supplied or absorbed form the line, where it injects in phase or quadrature voltage must be absorbed or supplied by the ac system or load. Due to this reason, both series in session insertion, and the shunt regulating transformer must fully rated to this actually the VI product of the rating. So, rating is quite high, in case of the both, shunt and the series solution.

(Refer Slide Time: 11:38)

**Discrete Level Control(Cont...)**

- The circuit configuration shown also has some **practical disadvantages**.
- The winding must be broken into  $n$  equal sections for  $2n + 1$  total number of required steps, and  $4n$  thyristor valves are used.
- A major problem with this is the difficulty of producing a transformer with  $n$  small and isolated winding sections, with  $2n$  leads coming from the winding structure.
- Another disadvantage of this configuration is that at lower system voltages, (smaller controlled voltage  $V$ ) the voltage per winding section becomes much lower than the minimum economic voltage application point of power thyristors currently available (typically available high rating thyristor )

IIT ROORKEE NIEL ONLINE CERTIFICATION COURSE 10


But here, this configuration has some practical disadvantage. The circuit configuration also has some practical disadvantages. The winding must be broken into  $n$  equal section for this kind of configurations required in steps, and  $4n$  thyristors level as used as shown in the previous figure; The major problem with this difficulty of producing a transformer with  $n$  small and isolated winding section, with  $2n$  leads coming from the winding structure. So, complexity is available with a manufacturing of such unique kind of transformer.

Another disadvantage of this configuration is that lower system voltage. Smaller controlled voltage  $V$ , the voltage per winding section becomes much lower, and the minimum economic voltage applications point of power thyristors available; Typically available power rating of the thyristors.

(Refer Slide Time: 12:51)
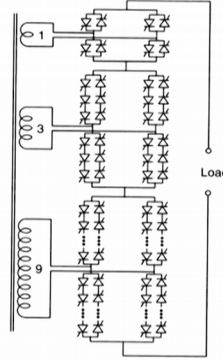
### Discrete Level Control(Cont...)

- A possible approach to solving the above practical problems by no identical winding sections with winding turns increasing in geometrical progression
- With the previously introduce ternary windings, proportioned 1 :3:9, a total of 27 steps can be obtained with only 12 bi-directional thyristor valves (of different voltage ratings).



IIT ROORKEE NPTEL ONLINE CERTIFICATION COURSE 11

So, a possible approach to solve this problem, the above practical problem by no identical winding section with winding turns increasing in a geometrical progression that is what you have shown in the previous slide. So, it has got 1 ton or the ratio is 1 3 and 9, and subsequently what happened that thyristors, will be actually change.

So, with the previously introduce the ternary winding, the proportioned 1 is to 3 is to 9 a total of 27 steps is obtained only by 12 bi-sectional thyristor valve of different voltage ratings. So, this kind of configuration may solve, the previously discussed problem.

(Refer Slide Time: 13:48)

### Discrete Level Control(Cont...)


- The total rating of the valves is the same as that of the previous scheme, 4 VI, and also half of the total number of valves(6 out of 12), operating at any given time
- The thyristors for higher voltage sections are fully utilized, while those for the smallest voltage section may still be operating below the minimum economic voltage level.
- The practical problems of transformer winding are also much reduced.
- The structure of a thyristor controller with progressively larger (higher voltage) valves increases both complexity and cost.

IIT ROORKEE NPTEL ONLINE CERTIFICATION COURSE 12

The total rating of the valve is the same as that of the previous scheme, 4 VI, and also the half of the total number of valves. So, 6 out of 12, is operating any given time that reduces the conduction losses also. Thyristor of the higher voltage section are fully utilized, while those of the smallest sections may still be operating below the minimum economic voltage level.

The practical problem of the transformer winding is also reduced, because you do not need that much of the leads to come out from your core. The structure of the thyristor control with progressively large, higher voltage increases both complexity and the cost both.

(Refer Slide Time: 14:45)

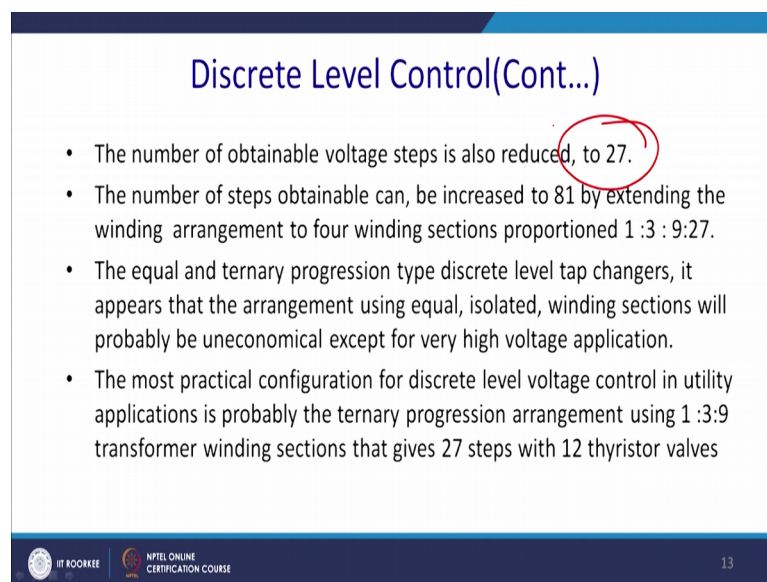

**Discrete Level Control(Cont...)**

- The number of obtainable voltage steps is also reduced, to 27.
- The number of steps obtainable can be increased to 81 by extending the winding arrangement to four winding sections proportioned 1 : 3 : 9 : 27.
- The equal and ternary progression type discrete level tap changers, it appears that the arrangement using equal, isolated, winding sections will probably be uneconomical except for very high voltage application.
- The most practical configuration for discrete level voltage control in utility applications is probably the ternary progression arrangement using 1 : 3 : 9 transformer winding sections that gives 27 steps with 12 thyristor valves

IIT ROORKEE | NPTEL ONLINE CERTIFICATION COURSE | 13


The number of obtainable voltage steps here also reduced, to 27, so that is something that we have to keep in mind. The number of steps obtainable can be increase to 81, so we have to make another section to 27 that is all, so 1 is to 3, 9, 27; By extending, the winding arrangement for the four winding section proportional to 1, 3, 9, 27.

The equal and the ternary progression type discrete level tap changers, it appears that the arrangement using equal, isolated, winding section probably be uneconomical except for a very high voltage application. So, previous this kind of actually splitting is been preferred. Most practical configuration for the discrete level voltage control utility application is probably the ternary progression arrangement using 1, 3, 9 something like




that transformer winding section that gives you 27 steps with 12 thyristors valve that is one of the biggest advantage of the discrete level control.

(Refer Slide Time: 16:11)

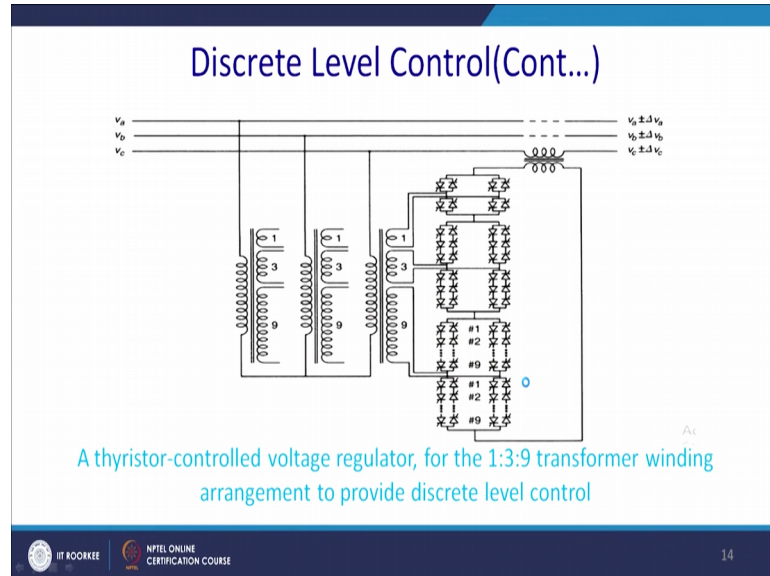

So, this is the case here. So, actually total circuit is shown in the phase 3. So, we can inject different kind of voltage in phase with  $\Delta V$ , so that can be this, that can be this, or that can be this. So, this is the beauty of the discrete level transformer with 27 steps. The thyristor-controlled voltage regulator with 1, 3, and 9 transformer winding arrangement provides 27 discrete level steps.

(Refer Slide Time: 16:46)

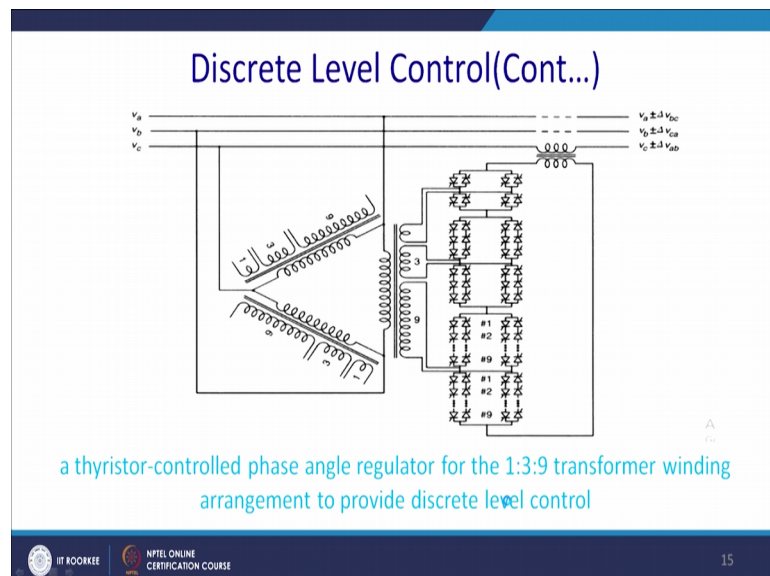



Similarly, the thyristor control phase angle, why we have to inject the voltage in quadrature. So, we can we have already seen that you know, if you want to inject in 90 degree with a phase a, we have to apply the voltage b c. So, thus this kind arrangement gives you the quadrature phase angle in only one phase has been shown.

So, this is with the a, and this is with the b, and the c. So, you know the delta, it will gives you 30 degree phase shift. A particular vector group is to be chosen, it is basically d 1 delta star 11 or 1. So, in this configuration, we can have a same thing and where voltage will be added with the quadrature that is b c, c a, and a b with the phase voltage that is will be the port, and that will be the actually the phase angle regulation. You inject the voltage in quadrature; the thyristor-controlled phase angle regulator for 1, 3, 9 transformer winding arrangement to provide discrete level control.

(Refer Slide Time: 18:11)

**Switching Converter Based Voltage And Phase Angle Regulators**

- In series compensation discussed, synchronous voltage source is applied as a series reactive compensator to inject a controllable voltage in quadrature with the line current.
- It is shown that such a compensator, when appropriately supplied with dc power, can also provide compensation for the resistive voltage drop across the line by injecting a voltage component that is in phase with the line current.
- Therefore it should be possible that a converter-based SVS with controllable amplitude  $V$ , and phase angle  $\phi$  can be used for voltage and phase angle regulation.

IIT Koorkee NPTEL ONLINE CERTIFICATION COURSE 16

So, a switching converter based voltage and the phase angle regulator, let us have a comparison between these two. Series compensation discussed, synchronous voltage sources applied as a series reactive compensator to inject the controllable voltage in quadrature with the current. So, this is the principle of operation.

It is shown that such compensator, when appropriately applied supplied with the dc source or dc power, can also provide compensation for the resistive drop across the line by injecting the component that is in phase with the current. Therefore, it should be possible that a converter-based SVS with controllable amplitude  $V$ , and the phase angle

phi can be used for voltage and the phase angle regulation. So, it can control both. So, this is the converter-based regulator.

(Refer Slide Time: 19:19)

### Switching Converter Based Regulators(Cont...)

- Where the in-phase and quadrature components of an assumed load current with respect to the voltage inserted for voltage regulation, quadrature boosting and ideal phase angle control are shown together with the corresponding expressions for the real and reactive power the SVS exchanged

Voltage regulation

$P_c = V_c I_{cd} = V_c I \cos \phi$   
 $Q_c = V_c I_{cq} = V_c I \sin \phi$

Quadrature boosting

$\psi = \frac{\pi}{2}$

$P_c = V_c I_{cd} = V_c I \sin \phi$   
 $Q_c = V_c I_{cq} = V_c I \cos \phi$

Ideal phase angle control

$P_c = V_c I_{cd} = V_c I \cos(\psi - \phi)$   
 $Q_c = V_c I_{cq} = V_c I \sin(\psi - \phi)$

IIT ROORKEE    NFTEL ONLINE CERTIFICATION COURSE    17

Where in-phase and the quadrature component of an assumed load current with respect to the voltage inserted in voltage regulation, quadrature boosting that we have discussed in previous class, and ideal phase angle control are shown together with corresponding expressions of the real and the reactive current and the power exchange by SVS. So, this is basically the supply voltage, and this is the interest component, and this is high and you add up by c. So, this is essentially the voltage regulation what happened then, since you have applied a real current, and then voltage.

So, what happened actually  $V_c$  into  $I_{cd}$ , so ultimately the that particular component of the power will be  $I_c V \cos \phi$ . Similarly,  $I_c q \sin \phi$  will be the  $Q_c$ , and this is for the voltage regulation. Same way, we have a quadrature boosting you have you inject actually the current perpendicular to the  $V_s$ . So, what happened then, actually  $c d$  will come in this way, and  $i q$  will be coming this way.

And thus that actually new  $P_c$  compositing power, real power will  $P_c$  into  $I_c d$  that will be  $I$  in  $\sin \phi$ , and similarly it will be  $\cos \phi$ . But, in real angle control you know, there what you can do, you can inject basically  $V_c$  with any angle  $\phi$ . And in that way, you can also compensate real power as well as the active power.

So, this is the ideal phase angle control, because you have to inject current into arc. So, this one is  $V_1$ , this one is  $V_2$ , and this one is actually  $\phi$ . So, you have to inject in this way, not in this quadrature or in-phase. So, how can you inject in a arc, this can be this is ideal phase angle regulator, where actually you have to find it out this  $\phi$ , and from their actual there is will be a calculations of shy.

So, form there you actually inject is voltage as regulated by this particular power angle regulator, not exactly at phase, not exactly at quadrature. So, then expressions becomes, in this case from this phasor it is  $V_c$  into  $I_c d$  should be the real power. So, it is  $V_c I_c \cos \phi$  minus  $\psi$  that should be the angle and  $Q_c$  will be  $P_c I_c \sin \phi$  should be you see  $I \sin \phi$  minus  $\psi$  minus  $\phi$ .

(Refer Slide Time: 22:18)

**Switching Converter Based Regulators(Cont...)**

- The SVS, in contrast to a thyristor tap changer, has the inherent capability to generate or absorb the reactive power
- it must be supplied at its dc terminals with the real power portion of the total VA demand resulting from the voltage or angle regulation.
- Depending on the application, the voltage regulation or phase angle control may require either unidirectional or bi-directional real power flow.

IIT ROORKEE NPTEL ONLINE CERTIFICATION COURSE 18

Now, switching off the converter based on the SVS. What is the actually difference between the discrete component based thyristor. SVS, in contrast to the thyristors tap changers, has the inherent capability to generate or absorb the reactive power, this is one of the biggest advantage of it.

It must be supplied, and it is and dc terminal with the real power that is one of the requirement you required to a power source. Real power portion of the VA demand resulting from the voltage or angle regulation. Depending on the applications, voltage regulation or the phase angle control may require either unidirectional or bi-directional

flow of the real power. So, that is something we required to keep in mind, while designing that SVS base P r.

(Refer Slide Time: 23:16)

### Switching Converter Based Regulators(Cont...)

- In the case of unidirectional real power flow (the voltage injection at the ac terminals only supplies real power), the real power could be supplied from the ac system by a relatively simple line-commutated ac-to-dc thyristor converter

Line-commutated converter Rating:  $P_c$       Voltage-sourced converter Rating:  $\sqrt{P_c^2 + Q_c^2}$

So, this is the case of SVS base P r. So, this is a switching converter based regulator. In case of the unidirectional real power flow, the voltage injection at the, terminal voltage injection at the ac terminal only supplies the real power. The real power could be supplied from the ac by a simply a line commutated ac-to-dc thyristor converter. So, thus in this way, the real power will go, and this will maintain the dc bus voltage, and from there this is a voltage source converter, this will compensate the requirement of this  $Q_c$  and the  $P_c$  as result.

(Refer Slide Time: 24:15)

### Switching Converter Based Regulators(Cont...)

- If the application requires bi-directional power flow (the ac voltage injection supplies and absorbs real power under different operating conditions),
- The power supply must be "regenerative," capable of controlling the flow of current in and out of the dc terminal of the injection converter.

Rating:  $P_c$       Rating:  $\sqrt{P_c^2 + Q_c^2}$

IIT ROORKEE      NPTEL ONLINE CERTIFICATION COURSE      20

So, if the application required the bi-directional flow bi-directional power flow, the ac voltage injection supplied or absorbed, the real power under the different operating condition. Then power supply should be regenerative, capable of controlling flow of the current and out of the dc terminal of the injection converter. So, power has to be bi-directional.

(Refer Slide Time: 24:36)

### Switching Converter Based Regulators(Cont...)

- The dc power supply for the voltage source type implementation of the voltage and angle regulator fulfil the same function as the excitation transformer for its more conventional counterparts employing a thyristor tap changer.
- It should also be noted that the rating of the dc power supply (shunt transformer and ac-to-dc converter) is, particularly for angle regulators, appreciably lower than that of the ac excitation transformer.
- The internal capability of the voltage-sourced converter to generate reactive power is a significant advantage in both voltage and phase angle regulation applications.


IIT ROORKEE      NPTEL ONLINE CERTIFICATION COURSE      21

So, in this case, we have to change some kind of topological aspect. So, what happened, the dc power supply for the voltage source type implementation of the voltage and the

angle regulator fulfill same function as the excitation transformer for its more conventional counterparts employing a thyristor tap changer.

It should be noted that the rating of the dc power supply, and the shunt and ac-to-dc converter is, particularly for a angle regulators. Appreciably lower than that of the ac excitation transformer. The internal capability of the voltage-sourced converter to generate, the reactive power is significant advantage of both voltage and the phase angle applications.

(Refer Slide Time: 25:43)

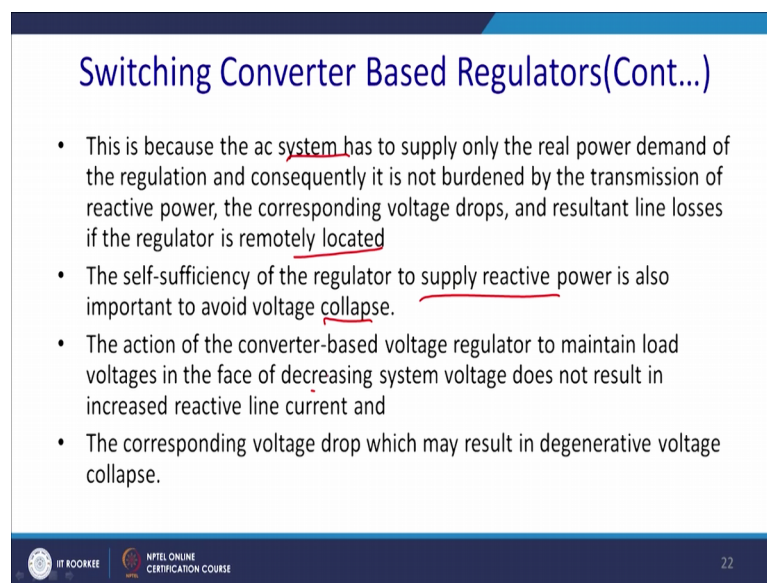

**Switching Converter Based Regulators(Cont...)**

- This is because the ac system has to supply only the real power demand of the regulation and consequently it is not burdened by the transmission of reactive power, the corresponding voltage drops, and resultant line losses if the regulator is remotely located
- The self-sufficiency of the regulator to supply reactive power is also important to avoid voltage collapse.
- The action of the converter-based voltage regulator to maintain load voltages in the face of decreasing system voltage does not result in increased reactive line current and
- The corresponding voltage drop which may result in degenerative voltage collapse.

IIT ROORKEE NPTEL ONLINE CERTIFICATION COURSE 22

This is because the system has to supply only the real power demand of the regulations, and consequently it is not burdened by the transmission of the reactive power. The corresponding voltage drops, thus what happened, and result in the line loss give the regulator is remotely located, this is actually one of the drawback. The self-sufficient sufficiency of the regulator to supply the reactive power is also important to avoid voltage collapse. That is something it has a self-healing mechanism.

The action of the converter-based voltage regulator to maintain the load voltage, in the phase of the decreasing system voltage does not result in increase reactive line current. The corresponding voltage drop, which may result in degenerative voltage collapse that is something we required to take care of it.

(Refer Slide Time: 26:50)

### Switching Converter Based Regulators(Cont...)

- The arrangement of the back-to-back voltage-sourced converter has broad possibilities for the implementation of extremely powerful FACTS Controllers with multiple and convertible functional capabilities.
- These include voltage regulation and phase-angle control in addition to combined real and reactive series and shunt compensation of transmission lines.

IIT ROORKEE NPTEL ONLINE CERTIFICATION COURSE 23

So, for the session the arrangement of the back-to-back voltage-sourced converter has broad possibilities of implementation of the extremely powerful FACTS controller, which multiply with multiple convertible functional capabilities. And what happened you know, here this converter essentially will hold this dc link voltage. And thus, the another converter in right hand side, can do work very well, and these include the voltage regulations, phase-angle control in addition to the combined real and the reactive power, and series compensation of the transmission line.

(Refer Slide Time: 27:33)

### Hybrid Phase Angle Regulators

- The hybrid phase angle regulator is a combination of two (or more) different types of phase angle regulators to achieve specific objectives at a minimum cost
- For example, a mechanical tap-changer type phase angle regulator may be combined with a continuously controllable, fast voltage source type angle regulator
- In this arrangement the mechanical tap changer would provide the quadrature voltage injection as needed to maintain the required steady-state power flow
- The voltage source converter would provide superimposed dynamic phase angle control during system disturbances.

IIT ROORKEE NPTEL ONLINE CERTIFICATION COURSE 2




So, phase angle regulator, this is called hybrid phase angle regulator. We have seen that you know, most of the cases, the voltage injected in quadrature to shift the change, then can we do something. So, that you know, we can inject in any phases, and optimal compensation can be achieved. In that case, we consider a hybrid phase angle regulator. Hybrid phase angle regulator, it is a combination of may be the one, it is injecting in phase, another you injecting in quadrature or any other angle; Two or more different type of phase angle regulator to achieve the specific objective at minimum cost.

For example, a mechanical tap changer type phase angle regulator may be combined continuous combined with the continuously controllable, fast voltage source type angle change regulator. There we can use a phase factor, so that will be actually very correctly calculate that magnitude of the voltage and phase require and inject that. So, this is the actually the mechanical version of it will be actually the mechanical tap changer type phase angle regulator.

In this arrangement, the mechanical tap changer would provide the quadrature voltage injection, we know that if you wish to inject quadrature with phase a, we required to inject b c needed a maintain the required the steady state power flow. The voltage source converter of instead of the mechanical switch devices, would provide superimpose dynamic phase angle controlled during the disturbances, and thus it is preferred.

(Refer Slide Time: 29:43)

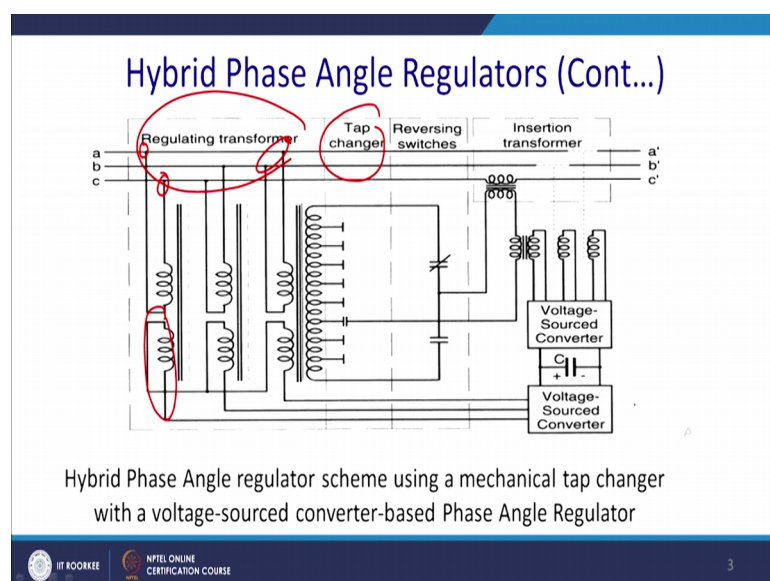



So, see that you know, this is actually the regulating transformer. And these are the tap changer. And the reversing switches, and it is a insertion transform. So, you got a different phases, for example, this is a b c. So, these and these is a c and this will is be sensed and similarly a c a b b c, c a. And accordingly, these are the taps, so we can change the number of taps as an where it is required. So, based on that for example, you know this is the a b phase, and so it will be linked with some voltage of a b to compensate the voltage in this phase c.

Similarly, you have a voltage source converter, which exactly actually calculate the amount of the voltage require. So, you may require to compensate let us say 35 degree, then some portion will be quadrature, and some portion will be your actually in phase, instead of applying in quadrature and phase. These are the property you know, if it is a phase vector, it can inject in the phase types of the two level inverter of 60 degree.

So, you can make, the combination of the voltage that is 65 degree you required to inject that can be that can come from the quadrature, as well as by this. So, these two voltage will be added in series, and will give you the these are voltage. And this converter x very fast for this reason, the compensation will be very accurate.

(Refer Slide Time: 31:41)

**Hybrid Phase Angle Regulators(Cont...)**

- This hybrid arrangement can be highly cost effective if the steady-state flow control requires only relatively large
- The above concept can be extended to the combination of thyristor tap-changer type and voltage source converter type angle regulator to achieve a different objective.
- For example, the discrete level voltage regulator with n identical transformer windings and thyristor valve arrangements can be made simple and economically attractive by reducing n to a manageable number

IIT ROORKEE
 NPTEL ONLINE CERTIFICATION COURSE


So, what are the advantages of this hybrid phase angle regulator. This hybrid phase angle regulator can be highly cost effective. (Refer Time: 31:46) one part is actually mechanical, and thus you compensate the bulk power and the power handling capability

of this of this part of the converter actually voltage source inverter, can be of the low rating low power rating. And thus you can actually reduce the cost of the component. If the steady state flow power control require only the reactive, only the relatively large form. So, you require only inject the quadrature power. So, transformer itself will be sufficient to do that.

The above concept can be extended to the combination of the thyristor tap changer type, voltage source converter type. The thyristor and the voltage source converter type angle regulator to achieve different objective. Different objective means, you required to inject the particular voltage and the phase. So, that can also be achieved by this hybrid phase angle regulator.

For example, the discrete level voltage regulator with an n identical transformer winding, and thyristor valve arrangement can be made a simple economically attractive, it reducing the n manageable number. For this is we can student may actually refer to the contrast, this kind of transformer is called sense transformer, is one of the versatile phase angle regulator. We shall give it to this sense transformer in the reference.

(Refer Slide Time: 33:40)

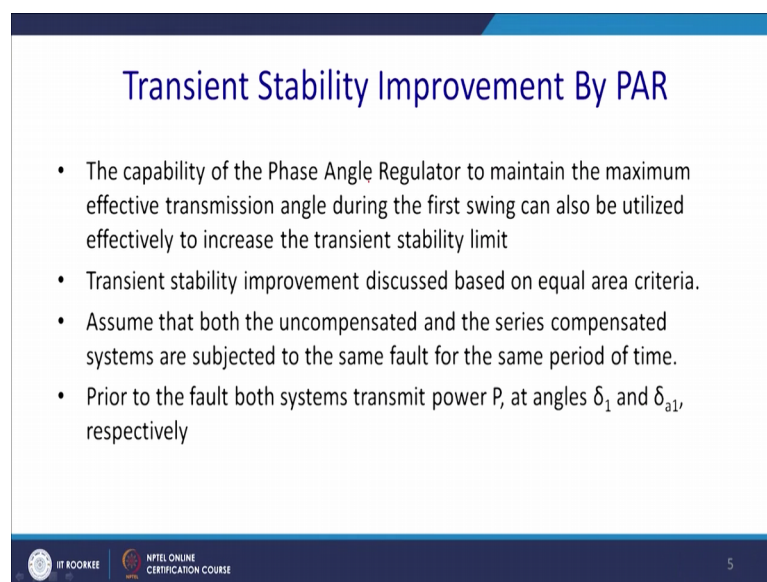

The slide features a blue header and footer. The main content is white with a blue border. The title 'Transient Stability Improvement By PAR' is in blue. The bullet points are in black. The footer contains logos for IIT ROORKEE and NPTEL ONLINE CERTIFICATION COURSE, along with the number 5.

### Transient Stability Improvement By PAR

- The capability of the Phase Angle Regulator to maintain the maximum effective transmission angle during the first swing can also be utilized effectively to increase the transient stability limit
- Transient stability improvement discussed based on equal area criteria.
- Assume that both the uncompensated and the series compensated systems are subjected to the same fault for the same period of time.
- Prior to the fault both systems transmit power  $P$ , at angles  $\delta_1$  and  $\delta_{s1}$ , respectively


IIT ROORKEE NPTEL ONLINE CERTIFICATION COURSE 5

Now, let us discuss about the enhancement of the transients by phase angle regulator. So, the capability of the phase angle regulator, to maintain the maximum effective transmission angle during the first swing, can also be utilize effectively to increase the transient stability limit. So, by changing delta, it enhances the power handling capability,

and thus in the first swing, it can increase the power flow through this transmission network.

Transient stability improvement discussed, we will be again take on the equal area criteria. And we will be show that how the transient stability is enhanced by the presence of PAR. And let us take the same equal area criteria, and assume that both the uncompensated, and the series compensated systems are subjected to the same fault for the same period of time; Prior to the fault, both system transient power, at an angle delta 1, and delta 2 respectively.

(Refer Slide Time: 34:49)

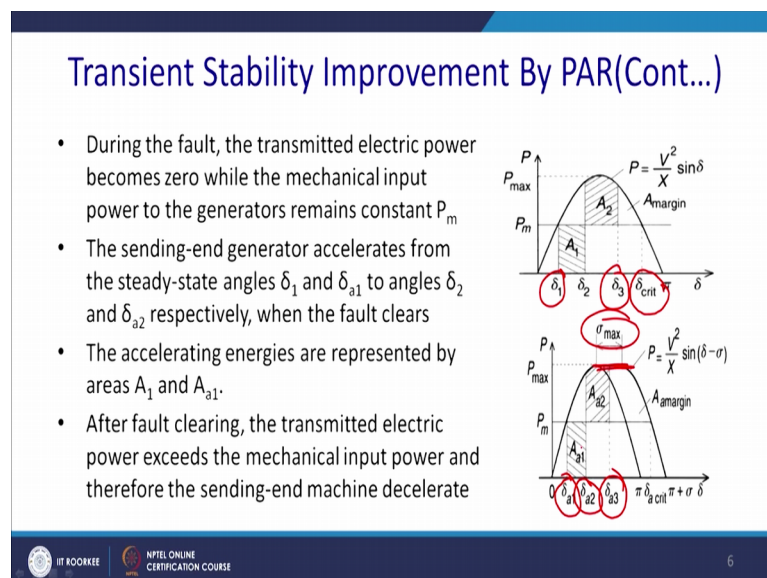

Let us referred to the figure so, you know, this is the this is the equal area criteria and uncompensated one. Delta 1 was the was the delay angle, and then you got a accelerating area A 1, and ultimately due to that you know, you got other deceleration area A 2. And a and you know that actually fault required to be cleared. And let us assume that fault been cleared at del del 3 and how was this critical fault clearing angle is delta critical.


On the other hand, you know with the PAR, let us assume that it is the same delta 1, we shall market as a delta A 1, and the exhilarating area is actually change to delta A 2. But, here you know, you have a range you have actually change to the value, and you can add sigma may be 45 degree, in this direction as well as this direction.

Thus you know, the maximum power handling capability  $P_{max}$  will vary with the huge amount of range. And thus what happened, even though you actually clear out the fault, and  $\delta_{a3}$  you have  $\delta_{crit}$  is been shifted by shifted by this angle, that is  $\pi + \sigma$ . So, your so this actually breakers another system, what enhance time to actually mitigate the fault as well as enhances the transient stability.

So, let us take one by one. During the fault, the transmitted electric power becomes zero, and thus it is a cost of the accelerating area. While the mechanical input power to generate it remains the  $P_m$  constant, that is  $P_m$ . So, this is given by this value. The sending-end generator thus accelerates from the steady-state value  $\delta_1$ , and  $\delta_{a1}$ , in case of the presence of the PAR to  $\delta_2$  to  $\delta_{a2}$  respectively, and when fault is cleared.

The accelerating result energies are represented by  $A_1$  and  $A_{a1}$ . So, both area are essentially same, there is no difference. After fault what happen, after clearing the fault, the transmitted electric power exceeds the mechanical power. And therefore, sending-end machine decelerates, and this is basically the deceleration area.

(Refer Slide Time: 37:38)

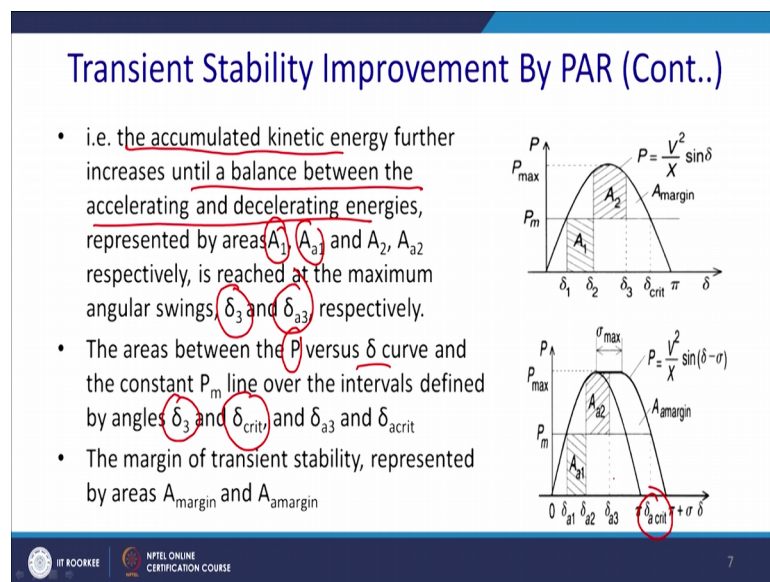



That mean, the accumulated kinetic energy further increases, until the balance between the accelerating and the decelerating energies are established. Energies, and it represented by  $A_1$ , and  $A_1$  and  $A_2$ , and  $A_2$  respectively, is reached at the maximum angle of swings  $\delta_3$  and  $\delta_{a3}$ , respectively.

The constant between the areas between the P versus delta curve, and the constant P m line over the interval is defined as delta 3, and delta critical, and delta a 3, and delta a critical. So, this is actually delta a critical. The margin of transient stability is represented by the area, A margin and A a margin. So, this is basically the A margin. So, this is basically A margin, you can see that this is the limit of the stability. And here, this big area is A a margin, which is actually quite enhanced.

(Refer Slide Time: 39:01)

**Power Oscillation Damping with PAR**


- Transmission angle control can also be applied to damp power oscillations.
- Power oscillation damping is achieved by varying the active power flow in the line so as to counteract the accelerating and decelerating swings of the disturbed machine.
- That is, when the rotationally oscillating generator accelerates and angle  $\delta$  increases ( $\frac{d\delta}{dt} > 0$ ), the electric power transmitted must be increased to compensate for the excess mechanical input power
- when the generator decelerates and angle  $\delta$  decreases ( $\frac{d\delta}{dt} < 0$ ) the electric power must be decreased to balance the insufficient mechanical input power.



8

Thus similarly, it can mitigate the oscillation. Transmission line power can also be applied to damp the power oscillation. We have seen in case of the series, against of the shunt, and it is also applicable for the power angle regulator. The power oscillation damping is achieved by varying the active power flow in the line. So, to counteract accelerating and the decelerating swing of the disturb machines on line.

That is what happened, when the rotationally oscillating generator accelerates at an angle delta increases, then  $\frac{d\delta}{dt}$  should be greater than 0 that will be (Refer Time: 39:53) and acceleration sorry. The electric power transmitted must be increased to accommodate the enhanced extra power, to compensate the excess mechanical power. When generated decelerates, the angle decreases and the electric power must be decreased to balance the insufficient mechanical input power.

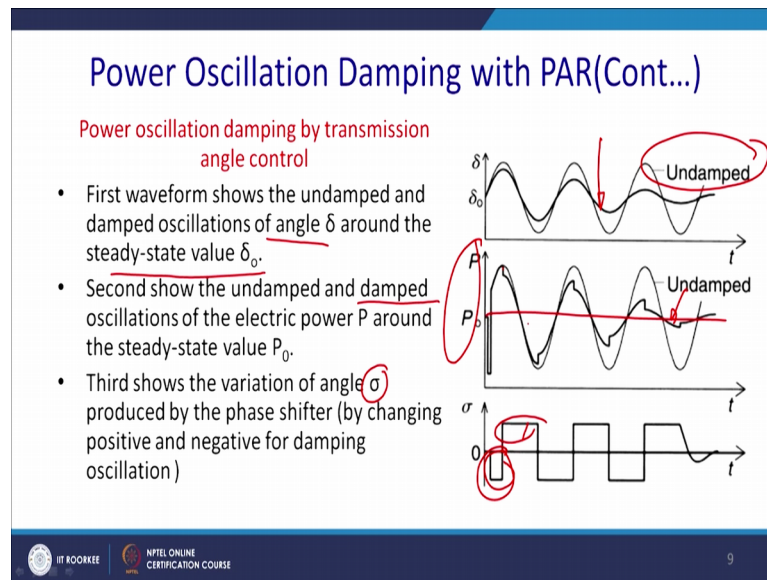(Refer Slide Time: 40:21)



So, this is the case. Now, this is basically the uncompensated delta. And with this damping ultimately this way from become this, this is the compensator delta. First waveform shows the undamped, and the damped oscillation of angle delta around the steady-state value delta 0.

The second shows, the damped and undamped oscillation of the electrical power, since it is oscillating. So, electrical power also will have a main dc that is  $P_0$  over it, it will oscillate, and quiet dangerous. Oscillation of the electric power  $P$ , around the steady-state value  $P_0$ ; so, this one is undamped, and when it is being damped you will have this kind of features.

The third shows, the variation of angle del sigma produced by the phase shifter, gradually what you will do you will actually. Change the phase of it generally, it is started a quadrature and accordingly will change. And generally, what you can see that. So, since it is actually positive, so you inject the negative phase, so bring it down. And you inject the positive phase to actually bring it down, the negative change in delta.

So, by phase shifter by changing the positive and the negative damping oscillation, you gradually actually by changing sigma, you gradually bring down the delay angle to this steady-state value. So, thus this can deliver damp power effectively the power oscillation.

Thank you for your attention. This thus we conclude our discussions of our third topic that is the voltage and phase angle regulator. We shall now, we shall continue now, the next topic that is on UPFC and UPQC, while series, and shunt, and the PAR been combined into the single entity. And for this session term universal or unified is added. We shall continue to our discussions.

Thank you for your attention.