


**Computer Aided Power System Analysis**  
**Prof. Biswarup Das**  
**Department of Electrical Engineering**  
**Indian Institute of Technology – Roorkee**

**Module No # 07**  
**Lecture No # 35**  
**Line Outage Sensitivity Factor**

Hello welcome to this lecture on the particular course on computer aided power system analysis in the last lecture we have discussed about the generation outage sensibility factor. In this lecture we will start talking about the line outage sensitivity factor. Now to before we discuss about what is mean line outage sensitivity factor ahh rather how to calculate this particular line outage sensitivity factor we should first look into the concept of Thevenin equivalent circuit as observed from any particular bus in a large power system.

So first let us look at the concept of Thevenin equivalent circuit so we have Thevenin so you are talking about Thevenin equivalent circuit.

**(Refer Slide Time: 01:22)**

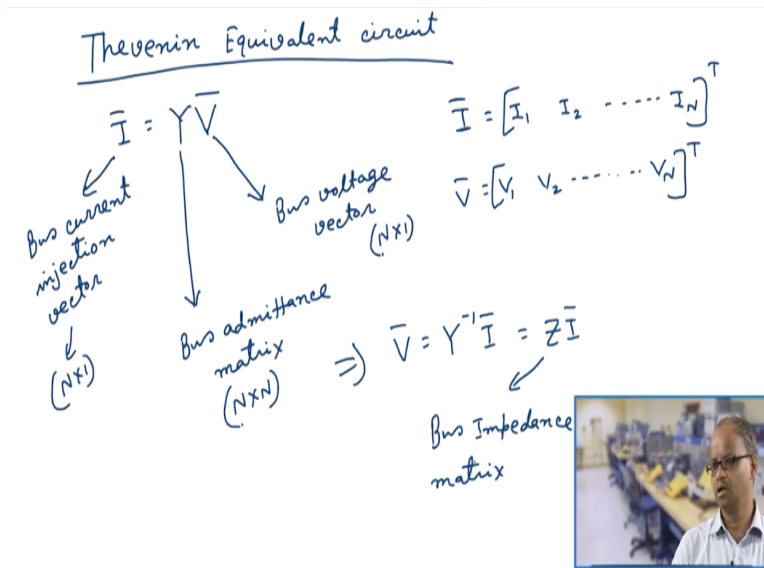

So Thevenin equivalent circuit now we know from our basic power system analysis whatever we have done that we know that  $I$  vector  $I =$  matrix  $Y$  into vector  $V$  vector  $I$  is the bus current injection vector. Vector  $V$  is bus voltage vector and this is bus admittance matrix now if there is  $n$  number of buses in my system so then in that case this is  $N$  cross  $1$  this is  $N$  cross  $N$  and this is  $N$

cross 1 and we note that we just recollect that I vector is essentially I1, I2, IN transpose T, V is V1, V2, VN and transpose T.

Here we also have to note that all to this currents I1, I2, IN V1, V2, VN they are all essentially complex quantities but taking a rather doing an abuse of notation we not putting in over power over any of this quantities because we have already put an over power to denote I and V are two vector anyway. So now from this we can write down that V = Y inverse into I or in other words V = ZI where Z is the recall bus impedance matrix. Now suppose due to some reason this vector I is being part out by a vector delta I.

**(Refer Slide Time: 04:37)**

$$\bar{I} + \Delta \bar{I} = [I_1 + \Delta I_1 \quad I_2 + \Delta I_2 \quad \dots \quad I_N + \Delta I_N]^T$$


$$\bar{V} + \Delta \bar{V} = Z(\bar{I} + \Delta \bar{I}) \Rightarrow \bar{V} + \Delta \bar{V} = Z\bar{I} + Z\Delta \bar{I}$$

$$\Rightarrow \Delta \bar{V} = Z\Delta \bar{I} \quad [\text{as } \bar{V} = Z\bar{I}]$$

$$\Delta \bar{V} = [\Delta V_1 \quad \Delta V_2 \quad \dots \quad \Delta V_N]^T$$

$$\begin{bmatrix} \Delta V_1 \\ \Delta V_2 \\ \vdots \\ \Delta V_N \end{bmatrix} = \begin{bmatrix} z_{11} & z_{12} & \dots & z_{1N} \\ z_{21} & z_{22} & \dots & z_{2N} \\ \vdots & \vdots & \ddots & \vdots \\ z_{N1} & z_{N2} & \dots & z_{NN} \end{bmatrix} \begin{bmatrix} \Delta I_1 \\ \Delta I_2 \\ \vdots \\ \Delta I_N \end{bmatrix}$$

Now, suppose  $\Delta I_j = 0$   
 $\forall j \neq k \quad j=1, \dots, N$



So that means the injected current at bus 1 is I1 is being part out from I1 to delta I1. Similarly injected current at bus 2 is being part out from I2 to delta I2 and so on and hence so forth and injected current at bus N is being part of from IN to delta IN right. So then therefore so then if this is part out so then we can say that this is nothing but I + delta I vector why this particular delta I vector is obvious that this delta I vector is nothing but delta I1, delta I2, delta IN transpose.

Now because this I vector is being part out from its original value to I + delta I so then therefore as a result this V vector will also be part out from its original value to V + delta V so then therefore we can write down that V + delta V = Z into I + delta I. Please note that this V is change from V to V + delta V because of this change of I from I to I + delta I. So from this we

know that  $V + \Delta V = Z \text{ into } I + Z \text{ into } \Delta I$  or in other words  $\Delta V = Z \text{ into } \Delta I$  as  $V = ZI$ .

So then therefore I can write down of course here in that of course here that  $\Delta V$  vector would be is nothing but  $\Delta V_1, \Delta V_2, \Delta V_N$  transpose so then now we can write down this relationship as  $\Delta V_1, \Delta V_2$  to  $\Delta V_N$  in that would be equal to here it is  $\Delta I_1, \Delta I_2$  to  $\Delta I_N$ . Please again note that all this quantities are complex quantities and similarly  $Z_{11}, Z_{12}$  to  $Z_{1N}, Z_{21}, Z_{22}$  to  $Z_{2N}$  and so on and hence so forth  $Z_{N1}, Z_{N2}$  to  $Z_{NN}$ .

Please note that this elements  $Z_{11}, Z_{12}$  up to  $Z_{NN}$  etc all this are also complex quantities but just to ease of notation we are not putting any bar or over any of them. Now suppose that they current injection is changed only at a particular bus  $K$  so that means now suppose that for a  $\Delta I_j = 0$  for all  $j$  not equal to  $k$  and  $j$  of course  $j = 1$  to  $N$  and it has got some value at bus  $k$  which is equal to  $\Delta I_k$ .

**(Refer Slide Time: 09:14)**

$$\begin{bmatrix} \Delta V_1 \\ \Delta V_2 \\ \vdots \\ \Delta V_k \\ \vdots \\ \Delta V_N \end{bmatrix} = \begin{bmatrix} Z_{11} & Z_{12} & \dots & Z_{1N} \\ Z_{21} & Z_{22} & \dots & Z_{2N} \\ \vdots & \vdots & \ddots & \vdots \\ Z_{k1} & Z_{k2} & \dots & Z_{kN} \\ \vdots & \vdots & \ddots & \vdots \\ Z_{N1} & Z_{N2} & \dots & Z_{NN} \end{bmatrix} \begin{bmatrix} 0 \\ 0 \\ \vdots \\ \Delta I_k \\ \vdots \\ 0 \end{bmatrix}$$

$\Delta V_i = Z_{ik} \Delta I_k$   
 $\forall i = 1, \dots, N$   
 $\Delta V_k = Z_{kk} \Delta I_k$   
 If initial voltage at bus 'k' is  $V_k^{(0)}$ , then the new voltage is


$$V_k = V_k^{(0)} + \Delta V_k = V_k^{(0)} + Z_{kk} \Delta I_k$$



So then therefore in that case what we will happen so we can write down that  $\Delta V_1, \Delta V_2$  to  $\Delta V_k$  to  $\Delta V_N$  so it would be  $Z_{11}, Z_{12}$  to  $Z_{1N}, Z_{21}, Z_{22}$  to  $Z_{2N}, Z_{k1}, Z_{k2}$  to  $Z_{kN}$  and 1 to  $Z_{NN}$  and it would be everywhere it would be 0, 0 dot  $\Delta I_k$  and 0. So then from here we can write down that  $\Delta V_i = Z_{ik} \Delta I_k$  that is very straight forward  $\Delta V_i$  would be  $Z_{ik}$  into  $\Delta I_k$  for all  $i = 1$  to  $N$ .

So then therefore  $\Delta V_k$  would be  $Z_{kk}$  into  $\Delta I_k$  now so this is the change in the voltage at bus  $k$  due to the change in the injection current at bus  $k$  so then therefore if the initial voltage at bus  $k$  is  $V_k$  say  $V_k^0$  then the new voltage is so then this new voltage would be equal to  $V_k$  would be equal to  $V_k^{\text{naught}} + \Delta V_k$  that would be equal to  $V_k^{\text{naught}} + Z_{kk} \Delta I_k$ . So now we have got this equation that  $V_k = V_k^{\text{naught}} + Z_{kk} \Delta I_k$  so we have got the equation as.

**(Refer Slide Time: 12:29)**

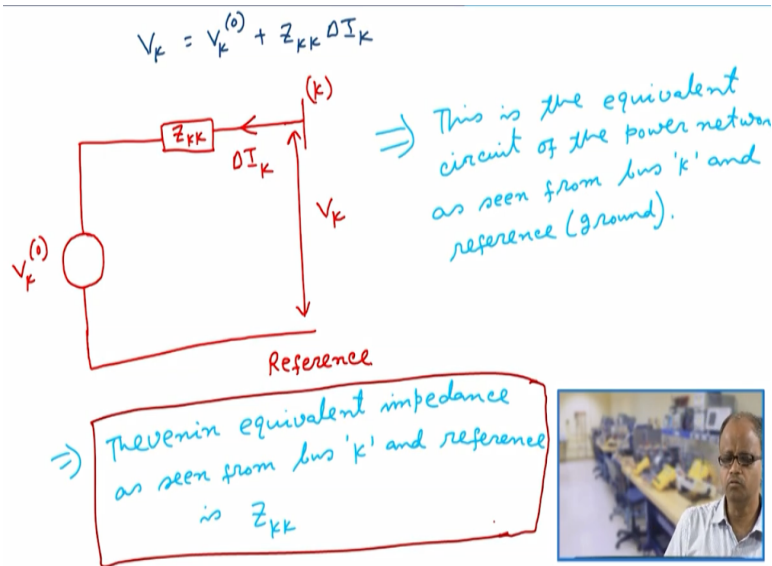

So we have got the final equation as  $V_k = V_k^{\text{naught}} + Z_{kk} \Delta I_k$  now the question is that how do we represent this particular equation as an equivalent circuit. So now we can represent this particular equation as an equivalent circuit and this would look like something like this so we have got some source some impedance then this is bus  $k$  this is the reference and this is  $V_k$  this is  $V_k^{\text{naught}}$  this is  $Z_{kk}$  and the current injector is  $\Delta I_k$ .

So then therefore this particular equivalent circuit very easily very conveniently represent this particular equation. So  $V_k =$  this drop  $Z_{kk}$  into  $\Delta I_k$  + this drop so  $V_k =$  this drop + this one that is fine so then therefore this is the equivalent circuit of the entire power grid as perceived from bus  $k$  and ground. So we can write down that this is the equivalent circuit so this is the equivalent circuit of the power network as seen from bus  $k$  and reference.

So reference is nothing but ground so it is ground now if I wish to find out that what is the Thevenin equivalent impedance of the entire grid as observed from bus  $k$  and ground. So then from our very basic understanding of the network theory we know that whenever we are trying to

calculate the Thevenin equivalent impedance what you have to do we have to simply short circuit all the voltage sources and simply open circuit all the current sources and then simply calculate the equivalent impedance as perceived from the given two terminals.

Now in this case there is no open now in this case there is no current source there is only voltage source that is this we cannot so then therefore if we wish to calculate this equivalent Thevenin impedance so then what you have to do some can be shot it once we shot it so therefore the equivalence impedance between this and this as perceived from bus k would be nothing but  $Z_{kk}$  so then therefore you can write down when therefore Thevenin equivalent impedance as seen from bus k and reference is  $Z_{kk}$ .


So this is the very interesting result so this is a very interesting concept okay now the question is well we have found out the Thevenin equivalent impedance of the entire power grid as perceived from bus k and ground but whatever would be Thevenin equivalent impedance of the entire network as perceived from between two buses let us the bus m and bus n so let us look at that. So now we are now trying to find out that what would be the Thevenin equivalent impedance of the power grid as perceived from bus m and bus n.

**(Refer Slide Time: 17:50)**

Now, we assume that  $\Delta I_x = 0 \quad \forall x = 1, \dots, N; \quad x \neq m, x \neq n$

$$\begin{bmatrix} \Delta V_1 \\ \Delta V_2 \\ \vdots \\ \Delta V_N \end{bmatrix} = \begin{bmatrix} z_{11} & z_{12} & \dots & z_{1N} \\ z_{21} & z_{22} & \dots & z_{2N} \\ \vdots & \vdots & \ddots & \vdots \\ z_{N1} & z_{N2} & \dots & z_{NN} \end{bmatrix} \begin{bmatrix} 0 \\ 0 \\ \vdots \\ \Delta I_m \rightarrow \text{m}^{\text{th}} \text{ position} \\ \vdots \\ \Delta I_n \rightarrow \text{n}^{\text{th}} \text{ position} \\ \vdots \\ 0 \end{bmatrix}$$

$$\Delta V_m = z_{mm} \Delta I_m + z_{mn} \Delta I_n$$

$$\Delta V_n = z_{nm} \Delta I_m + z_{nn} \Delta I_n$$


So towards that goal we assume that now we assume that  $\Delta I = 0$  for  $i = 1$  to capital M and  $i$  is not equal to m and  $i$  is not equal to n. So therefore what we have simply trying to say that only at

bus M and bus N there are some power turbation in the injected current at all the other buses there is no power turbation in the injected currents.

So then in that case what we have is we can write down the delta V1, delta V2 up to delta VN and then Z11, Z12 to Z1N, Z21, Z22 to Z2N this is ZN1, ZN2 to ZNN and we have 0, 0 something called delta Im and let us say then delta In and then all are 0. So this is the mth position and this is the nth position and position so then from this what we can write down about delta Vm and delta Vn so we can write down about delta Vm and delta Vn so we can write down as delta Vm = Zmm delta Im + Zmn into delta In.

And similarly we can write down delta Vn = Znm into delta Im + Znn into delta In so these are the power turbation due to the so then these are the power turbation of the voltage due to the power turbation in the injected currents at bus m and n.

**(Refer Slide Time: 21:25)**

$$\begin{aligned}
 V_m &= V_m^{(0)} + \Delta V_m = V_m^{(0)} + Z_{mm} \Delta I_m + Z_{mn} \Delta I_n \\
 V_n &= V_n^{(0)} + \Delta V_n = V_n^{(0)} + Z_{nm} \Delta I_m + Z_{nn} \Delta I_n \\
 V_m &= V_m^{(0)} + (Z_{mm} - Z_{mn}) \Delta I_m + Z_{mn} (\Delta I_m + \Delta I_n) \\
 V_n &= V_n^{(0)} + Z_{nm} (\Delta I_m + \Delta I_n) + (Z_{nn} - Z_{nm}) \Delta I_n
 \end{aligned}$$

So then therefore we can write down Vm final Vm is as usual Vm0 + delta Vm so then Vm0 is the initial voltage + Zmm into delta Im + Zmn into delta In. Similarly Vn = Vn0 that is initial voltage of bus n + delta Vn that would be equal to Vn0 + Znm delta Im + Znn delta In. So we have got these two equations now we will do some simple algebraic manipulations of these two equations as follows right that Vm = from here Vm0 + Zmn - Zmn into delta Im.


So what I have done we have done I am simply subtracting Zmn into delta Im now because I am subtracting Zmn into delta Im so then I must also add it and if I add it so then what I will get is

so I get  $Z_{mn}$  into  $\Delta I_m + \Delta I_n$  this is very simple what i have done I have simply subtracted  $Z_{mn}$  into  $\Delta I_n$  and I have added  $Z_{mn}$  into  $\Delta I_m$  so these two cancel out and the original system remains same.

Similarly  $V_n$  would be equal to  $V_n$  naught + here what we do here is first  $Z_{nn} - Z_{nm}$  into  $\Delta I_m$  so what I have done we have simply subtracted  $Z_{nm}$  into  $\Delta I_m$  so that therefore I have to add this  $Z_{nm}$  into  $\Delta I_n$  to make this ahh I mean  $(\Delta I_m)$  (24:13) system so then therefore if we do that so we have got  $Z_{nn}$  into  $\Delta I_m + \Delta I_n$  so this is the equation. So now we have got these two equations of course this equation comes from this.

Now how do we represent this two equations can we represent this two equations so in an equivalent circuit so we would now like to represent this equations in equivalent circuit so when we represent this equations in an equivalent circuit what we get is so we.

**(Refer Slide Time: 24:59)**

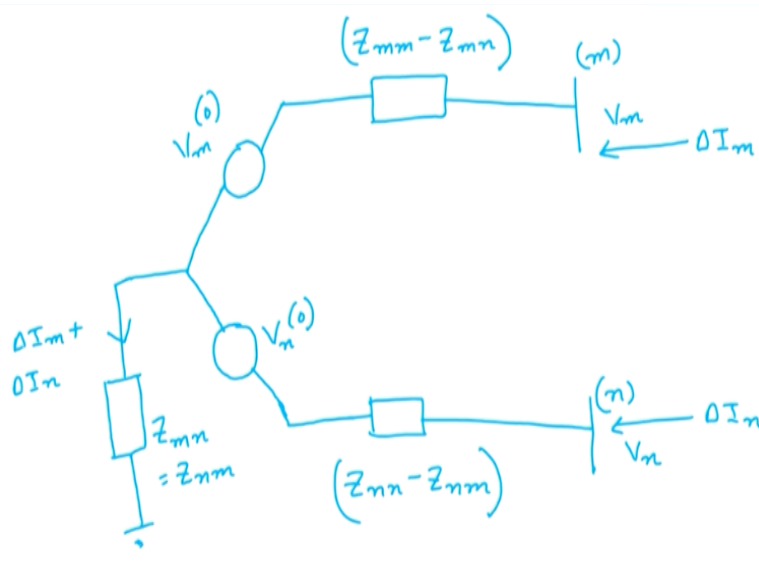

So what we do is so we say that it is an bus m this is bus n so this is bus m this is bus n and we have here so you have the voltages is  $V_m$  here this voltages is  $V_n$  injected current here is  $\Delta I_m$  injected current here is  $\Delta I_n$  and this current goes from here this current goes from here they meet together so then here the total current is  $\Delta I_m + \Delta I_n$  and this impedance is  $Z_{mn} = Z_{nm}$ .

Please note that because why was matrix is a symmetric so then therefore the inverse of it so that is nothing but the bus impedance matrix will also be a symmetric matrix so as a result  $Z_{mn}$

would be is equal to  $Z_{nm}$  this would be  $V_{m0}$  this would be  $V_{n0}$  this would be  $Z_{mm} - Z_{mn}$  and this would be  $Z_{nn} - Z_{nm}$ . So this would be the equivalent circuit so from this equivalent circuit what we get that  $V_m = \Delta I_m \text{ into } Z_{mm} - Z_{mn}$  last  $V_m \text{ naught}$  so let us see so  $V_m = V_m \text{ naught} + \Delta I_m \text{ into } Z_{mm} - Z_{mn} + Z_{mn} \text{ into } \Delta I_m \text{ into } \Delta I_n$ .

And  $V_n = V_n \text{ naught} + Z_{nm} \Delta I_m + \dots$  so then this circuit faithfully represents these two equations so then this is nothing the equivalent as perceived from bus m. So this is the equivalent circuit as perceived from bus m and n. Now from here i can find out practically everything now if I want to find out the equivalent impedance as perceived from bus m to ground so what I get so first thing what we have to do you have to make this two sources short circuited so once you do this short circuit and then if I wish to find out that what is the equivalent Thevenin impedance as perceived from bus m and ground.

So then what it would be this would be  $Z_{mm} - Z_{mn} + Z_m Z_{mn}$  so this and this cancels out so  $Z_{mm}$  remains so then therefore from this the equivalent Thevenin impedance between bus m and n sorry bus m and ground would be  $= Z_{mm}$  which we have already seen. Similarly as observed from bus m to ground we can find out that the Thevenin equivalent impedance would be  $Z_{mn} - Z_{nm} + Z_{nm}$  so then this particular  $Z_{nm}$  cancels out and so then therefore the Thevenin equivalent impedance as perceived from bus n and ground would be  $= Z_{nn}$  which is absolutely correct as we have already observed.

Now what would be the Thevenin equivalent impedance as perceived from bus m to n so then for that what we have to do you have to simply make our journey from bus m and then we have simply finish our journey at bus n and then we have to simply add and then we have simply see that I mean what are the impedance we get so then when we start our journey at bus m and then finish our journey at bus n we find that this impedance and this impedance are in series so then therefore the Thevenin equivalent impedance as perceived from so Thevenin equivalent impedance as seen between bus m and n is this is denoted as  $Z_{\text{Thevenin } mn}$  that is given by  $Z_{mm} - Z_{mn} + Z_{nn} - Z_{nm}$ .

**(Refer Slide Time: 31:29)**



$$\Rightarrow Z_{n,mn} = Z_{mm} + Z_{nn} - 2Z_{mn}$$

as

$$Z_{mn} = Z_{nm}$$

So then therefore as  $Z_{mn} = Z_{nm}$  so then therefore  $Z$  Thevenin between bus  $m$  and  $n$  is given by  $Z_{mm} + Z_{nn} - 2Z_{mn}$  so this is a very powerful and interesting result so then therefore you can find out that once you know the bus admittance matrix of a system then we will simply take the inverse we will find out the bus impedance matrix and once we point out the bus impedance matrix from that bus impedance matrix elements we can readily calculate the Thevenin equivalent impedance of the entire power grid as perceived from bus  $m$  and  $n$ .

Of course here we have we have actually written down this particular expression due to this fact that  $Z_{mn} = Z_{nm}$  right and this is due to this fact that my bus impedance matrix is basically a symmetric matrix so in this lecture we have looked into the Thevenin equivalent impedance of the entire power network first we have looked into the Thevenin equivalent impedance as perceived from any particular bus to ground and then we have looked into Thevenin equivalent impedance as perceived between any two given buses. So in the next lecture we would be continuing this particular discussion thank you.