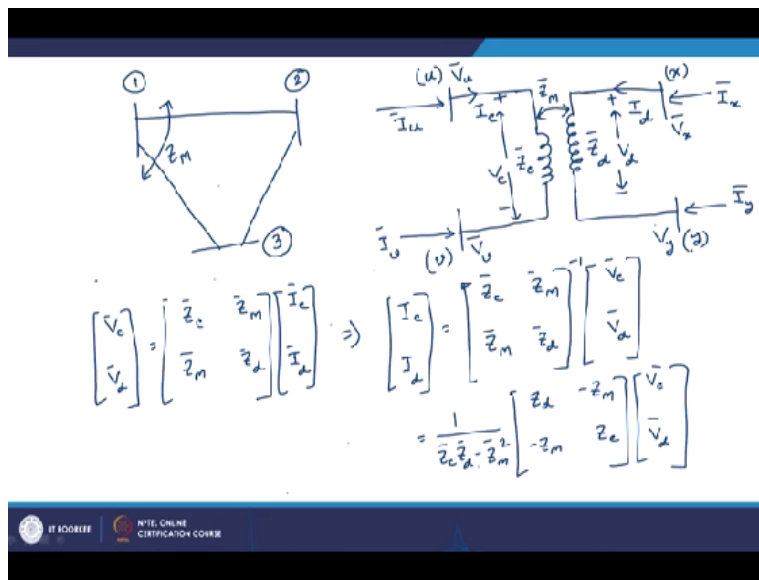


Computer Aided Power System Analysis
Prof. Biswarup Das
Department of Electrical Engineering
Indian Institute of Technology - Roorkee

Lecture – 04
Bus Admittance Matrix with Mutual Impedance

Welcome to this module of this course, Computer Aided Power System Analysis. Up to the last class, we have discussed about the formation of the bus admittance matrix of any general large power system. But in that formulation, we have not considered the mutual impedance between the lines. So here in this lecture as well as in the next lecture, we would be looking into the fact that how do we take into account the mutual impedance between any 2 lines into account while forming the bus admittance matrix. So what we are trying to do is as actually follows.

(Refer Slide Time: 01:09)



Suppose I do have, so this is let us say bus 1, this is bus 2, this is bus 3 and let us say there is 1 transmission line between all these buses and suppose that these 2 line have got some mutual impedance connecting between these 2 lines. So now what we are trying to do is as follows. Now suppose I do have let us say bus u, bus v, it is a bus x, bus y. So it is bus u, bus v, bus x, bus y. Between u and v, there is an element connected.

Between x and y, also there is an element connected. The current through this element, let us say, I_c . The current through this element is I_d . The impedance of this element is Z_c . The impedance

of this element is Z_d and these 2 elements are interconnected or rather they do have a mutual impedance between them as Z_m . And let us say that the current which is being injected here I_u , I_v .

These are all complex quantity. This is I_x . This is I_y . So this is the setup. So what we are actually trying to do is, essentially we are trying to formulate or rather find out an equivalent circuit between bus u, bus v, bus x and bus y such that after we form the equivalent circuit connecting all these 4 buses, we would be able to apply the standard rules of forming the bus admittance matrix.

So essentially that is our goal. So to do that, so now let us see we have that and let us say that this voltage across this is V_c . Voltage across this element is, let us say, V_c . Voltage across this element is V_d . So we can write down $V_c V_d = Z_c Z_m Z_m Z_d I_c I_d$. So a complex quantity because after all V_c would be $Z_c I_c + Z_m I_d$ and also V_d would be $Z_m I_c + Z_d I_d$. So therefore, $I_c I_d$ would be $Z_c Z_m Z_m Z_d$ inverse $V_c V_d$. Now it would be, so this would be equal to $1/Z_c Z_d - Z_m^2 Z_c Z_d - Z_m Z_c V_c V_d$.

(Refer Slide Time: 05:42)

$$\Rightarrow \begin{bmatrix} \bar{I}_c \\ \bar{I}_d \end{bmatrix} = \begin{bmatrix} \bar{Y}_c & \bar{Y}_m \\ \bar{Y}_m & \bar{Y}_d \end{bmatrix} \begin{bmatrix} \bar{V}_c \\ \bar{V}_d \end{bmatrix} \quad \text{--- (1)} \quad \text{where } \Delta = \bar{Z}_c \bar{Z}_d - \bar{Z}_m^2$$

$$\begin{bmatrix} \bar{I}_u \\ \bar{I}_v \\ \bar{I}_x \\ \bar{I}_y \end{bmatrix} = \begin{bmatrix} 1 & 0 \\ -1 & 0 \\ 0 & 1 \\ 0 & -1 \end{bmatrix} \begin{bmatrix} \bar{I}_c \\ \bar{I}_d \end{bmatrix} = [C] \begin{bmatrix} \bar{I}_c \\ \bar{I}_d \end{bmatrix} \quad \text{--- (2)} \quad \text{where } [C] = \begin{bmatrix} 1 & 0 \\ -1 & 0 \\ 0 & 1 \\ 0 & -1 \end{bmatrix}$$

$$\begin{bmatrix} \bar{V}_c \\ \bar{V}_d \end{bmatrix} = \begin{bmatrix} 1 & -1 & 0 & 0 \\ 0 & 0 & 1 & -1 \end{bmatrix} \begin{bmatrix} \bar{V}_u \\ \bar{V}_v \\ \bar{V}_x \\ \bar{V}_y \end{bmatrix}$$

Or in other words, so we can write $I_c I_d = Y_c Y_m Y_m Y_d V_c V_d$ where Y_c is given by Z_d by this, Δ Y_m is given by $-Z_m/\Delta$ and Y_d is given by Z_c/Δ where $\Delta = Z_c Z_d - Z_m^2$. Now from this circuit, we can write down that $I_u I_v I_x I_y =$, if I try to represent it all this injected current

I_u, I_x, I_y in terms of these branch currents, so we get some matrix now. What this matrix, clearly here I_u would be equal to I_c and I_v would be equal to $-I_c$.

Similarly, I_x would be equal to I_d and I_y would be equal to $-I_d$. So then therefore, I_u would be equal to I_c , so it is 0 1 0. I_v is $-I_c$, so it is -1 0. $I_x=I_d$, so it is 0 1. And $I_y=-I_d$, it is 0 -1. So let us say this is matrix C, some matrix $C \cdot I_c, I_d$. Where matrix C is, this matrix 1 0 -1 0 0 1 0 -1. Also $V_c=V_u-V_v$ and $V_d=V_x-V_y$. So then therefore, if I write down V_c, V_d , you have something called here V_u, V_c, V_x, V_y .

So it would be something like this. So $V_c=V_u-V_v$. So it would be 1 -1 and others would be 0 and $V_d=V_x-V_y$, so it would be 0 0 1 -1. So we can clearly see that this matrix is nothing but transpose of this matrix C. So this row, sorry this column becomes this row and this column becomes this row.

(Refer Slide Time: 09:52)

From eqn 1

$$\begin{bmatrix} \bar{I}_c \\ \bar{I}_d \end{bmatrix} = \begin{bmatrix} \bar{Y}_c & \bar{Y}_m \\ \bar{Y}_m & \bar{Y}_d \end{bmatrix} \begin{bmatrix} \bar{V}_c \\ \bar{V}_d \end{bmatrix} \Rightarrow [C] \begin{bmatrix} \bar{I}_c \\ \bar{I}_d \end{bmatrix} = [C] \begin{bmatrix} \bar{Y}_c & \bar{Y}_m \\ \bar{Y}_m & \bar{Y}_d \end{bmatrix} \begin{bmatrix} \bar{V}_c \\ \bar{V}_d \end{bmatrix}$$

Substituting eqn 3 into eqn 4 we have

So then therefore, we can write down that $V_c, V_d =$ matrix C transpose V_u, V_v, V_x, V_y . Now we have $I_c, I_d =$ this, so now we would be, let us say that this is equation 1. We should set equation 1. We should say that this is equation 2 and we should say that this is equation 3, suppose. From equation 1, $I_c, I_d = Y_c, Y_m, Y_m, Y_d \cdot V_c, V_d$. Now I premultiply everything by the matrix C. So I premultiply everything by matrix C, so then I get premultiplying everything by matrix C, I get $C \cdot I_c, I_d =$ matrix C $\cdot Y_c, Y_m$.

Now in this equation, we will now put equation 3. So this is, let us say this equation 4. So substituting equation 3 into equation 4, we have.

(Refer Slide Time: 12:45)

$$[C] \begin{bmatrix} \bar{I}_c \\ \bar{I}_a \end{bmatrix} = [C] \begin{bmatrix} \bar{Y}_c & \bar{Y}_m \\ \bar{Y}_m & \bar{Y}_a \end{bmatrix} [C]^T \begin{bmatrix} \bar{V}_c \\ \bar{V}_b \\ \bar{V}_a \\ \bar{V}_y \end{bmatrix}$$

$$\Rightarrow \begin{bmatrix} \bar{I}_u \\ \bar{I}_b \\ \bar{I}_a \\ \bar{I}_y \end{bmatrix} = [C] \begin{bmatrix} \bar{Y}_c & \bar{Y}_m \\ \bar{Y}_m & \bar{Y}_a \end{bmatrix} [C]^T \begin{bmatrix} \bar{V}_c \\ \bar{V}_b \\ \bar{V}_a \\ \bar{V}_y \end{bmatrix} \rightarrow \text{utilizing eqn. (2)}$$

That $C \cdot I_c I_d = \text{matrix } C$, and then it is $V_c V_d$ and $V_c V_d$ is C transpose this, C transpose $V_u V_v V_x V_y$. Now $C \cdot I_c I_d$, now from $C \cdot I_c I_d$ is nothing but $I_u I_v I_x I_y$. So if I utilize equation 2 here, so then therefore, we have $I_u I_v I_x I_y = \text{matrix } C \cdot Y_c Y_m Y_m Y_d \cdot C$ transpose V_u , all are complex quantities, $V_u V_v V_x V_y$. So this is utilizing equation 2. Now we have to look at that what is this matrix? $C \cdot Y_c Y_m Y_m Y_d \cdot C$ transpose.

(Refer Slide Time: 15:06)

$$\text{Now, } [C] \begin{bmatrix} \bar{Y}_c & \bar{Y}_m \\ \bar{Y}_m & \bar{Y}_a \end{bmatrix} [C]^T = \begin{bmatrix} \bar{Y}_c & -\bar{Y}_c & \bar{Y}_m & -\bar{Y}_m \\ -\bar{Y}_c & \bar{Y}_c & -\bar{Y}_m & \bar{Y}_m \\ \bar{Y}_m & -\bar{Y}_m & \bar{Y}_a & -\bar{Y}_a \\ -\bar{Y}_m & \bar{Y}_m & -\bar{Y}_a & \bar{Y}_a \end{bmatrix}$$

$$= \begin{bmatrix} 1 & 0 \\ -1 & 0 \\ 0 & 1 \\ 0 & -1 \end{bmatrix} \begin{bmatrix} \bar{Y}_c & \bar{Y}_m \\ \bar{Y}_m & \bar{Y}_a \end{bmatrix} \begin{bmatrix} 1 & -1 & 0 & 0 \\ 0 & 0 & 1 & -1 \end{bmatrix}$$

$$\begin{matrix} (4 \times 2) \leftarrow & & & \rightarrow (2 \times 4) \end{matrix}$$

So now let us look at. Now $C \cdot Y_c Y_m Y_d C^T$. That would be equal to? C matrix is $\begin{bmatrix} 1 & 0 & -1 & 0 \\ 0 & 1 & 0 & 0 \\ 0 & 0 & 1 & 0 \\ 0 & 0 & 0 & 1 \end{bmatrix}$, this is $Y_c Y_m Y_d$. And C^T matrix C^T is, this is just $\begin{bmatrix} 1 & -1 & 0 & 0 \\ 0 & 1 & 0 & 0 \\ 0 & 0 & 1 & 0 \\ 0 & 0 & 0 & 1 \end{bmatrix}$. So what I would get? So I would get here from here $\begin{bmatrix} 1 & 0 & -1 & 0 \\ 0 & 1 & 0 & 0 \\ 0 & 0 & 1 & 0 \\ 0 & 0 & 0 & 1 \end{bmatrix}$ and this would be $Y_c - Y_c Y_m - Y_m$, it would be $Y_m - Y_m Y_d - Y_d$. So this is a 4×2 matrix and this is a 2×4 matrix.

So then therefore, there product would be a 4×4 matrix and this product would be, so it is $Y_c - Y_c Y_m - Y_m$. This is $-Y_c Y_c - Y_m Y_m$. This plus is not required. Then what we have? We have $Y_m - Y_m Y_d - Y_d$. Then we have $-Y_m Y_m - Y_d Y_d$. So this is the matrix. So this matrix is this. So then therefore, what we have?

(Refer Slide Time: 19:08)

Therefore,

$$\begin{bmatrix} \bar{I}_u \\ \bar{I}_v \\ \bar{I}_x \\ \bar{I}_y \end{bmatrix} = \begin{bmatrix} \bar{Y}_c & -\bar{Y}_c & \bar{Y}_m & -\bar{Y}_m \\ -\bar{Y}_c & \bar{Y}_c & -\bar{Y}_m & \bar{Y}_m \\ \bar{Y}_m & -\bar{Y}_m & \bar{Y}_d & -\bar{Y}_d \\ -\bar{Y}_m & \bar{Y}_m & -\bar{Y}_d & \bar{Y}_d \end{bmatrix} \begin{bmatrix} \bar{V}_u \\ \bar{V}_v \\ \bar{V}_x \\ \bar{V}_y \end{bmatrix}$$

$$\Rightarrow \bar{I}_u = \bar{Y}_c \bar{V}_u - \bar{Y}_c \bar{V}_v + \bar{Y}_m \bar{V}_x - \bar{Y}_m \bar{V}_y$$

$$= \bar{Y}_c \bar{V}_u - \bar{Y}_c \bar{V}_v + \bar{Y}_m \bar{V}_x - \bar{Y}_m \bar{V}_y$$

$$= \bar{Y}_c (\bar{V}_u - \bar{V}_v) + \bar{Y}_m (\bar{V}_u - \bar{V}_x) - \bar{Y}_m (\bar{V}_u - \bar{V}_y)$$

Therefore, we have $I_u I_v I_x I_y =$, this big matrix 4×4 and it would be $V_u V_v V_x V_y$. So this would be all complex quantity, this would be all complex quantity. So $Y_c - Y_c Y_m - Y_m$. So it is $Y_c - Y_c Y_m - Y_m$. $-Y_c Y_c$, so it is negative, $-Y_c Y_c - Y_m Y_m$. Then $Y_m - Y_m Y_d - Y_d$, so $Y_m - Y_m Y_d - Y_d$. This is $-Y_m Y_m$. This is just the negative of it. $-Y_m Y_m - Y_d Y_d$. So what we got?

We got a bus, you know admittance matrix connecting the injected currents. So what we have got? So you see here what I have got? $I_u I_v I_x$ and I_y , these are nothing but the injected current at bus u bus v bus x and bus y respectively. And these voltage is V_u , sorry I should have mentioned either, this is voltage V_v . This is V_x and this voltage is V_y . So I have got this voltages $V_y V_v V_x$

and V_y .

So what we have got? We have essentially connected this injected, 4 injected currents, I_u I_v I_x and I_y . With these 4 bus voltages, V_u V_v V_x and V_y . So then therefore, so it may appear that we have done our job but the problem is now, so then therefore, this is nothing but the bus injected current. This is the bus voltage vector and this is the bus admittance matrix as far as these 4 buses are concerned.

Now it may appear that we have done our job. But the point is, we really cannot utilize this, because this particular bus admittance matrix cannot be directly incorporated into our normal standard bus admittance matrix. So then therefore, we need to do something else. So what we will do is, so now, we will now utilize these equations and we will go through this. Now here, there are, so I_c I_d V_c V_d .

So now let us write down these equations. So now these equations are, so now we have to write down the equations, are $I_u = Y_c V_u - Y_c V_v + Y_m V_x - Y_m V_y$, these are. To this, we simply add $Y_m V_u$ and then also subtract $Y_m V_u$, so what we get is $Y_c V_u - Y_c V_v + Y_m V_x - Y_m V_y + Y_m V_u$ and $-Y_m V_u$. So we have simply added and subtracted $Y_m V_u$ from these expressions. So we got these.

So from here, what I get? I take Y_c as $V_u - V_v$ from these 2 terms. Then we take $Y_m V_u$, this minus this $-Y_m V_u$ and then $-Y_m V_u - V_x$. So this is the expression of I_u . So then if this is the expression of I_u , so then what we can have that for this, so now we have got I_v x y . So this is bus u , this is bus v , this is bus x , this is bus y . And we have got injected current I_u and now, so now we can see that this injected current I_u is actually constitutes of these 3 terms.

So if we can represent these 3 terms by means of some equivalent impedance or admittance, so then therefore, we can express this first row of this equation or rather first row of this particular matrix relation by an equivalent circuit. So now let us see how do we do this? So from this, so I have got I_u . So now if I put Y_c here and then I put $V_u - V_v$, so this is, I put here Y_m , this is Y_m . And between these 2, I put another admittance $-Y_m$.

So now what we have? This current which is entering this bus is constituting of 3 currents, this current+this current+this current. This current is obviously $V_u - V_v$ *this admittance. This current is obviously $V_u - V_y$ *this admittance. And this current is actually $V_u - V_x$ *this Y and this is precisely this particular relation shows this current is nothing but $Y_c * V_u - V_v$. This current is actually nothing but $Y_m * V_u - V_y$.

And this current, this third current is nothing but equal to $-Y_m * V_u - V_x$. So then therefore, what we have done that we have represented the first row of this matrix equation by an equivalent circuit. So then similarly we can also represent the, all the other rows of this equation by some other equivalent circuit and then we have to actually add those 4 equivalent circuits together and we have to arrive at the compact equivalent circuit representing this particular network. So this we will do in the next lecture. Thank you.