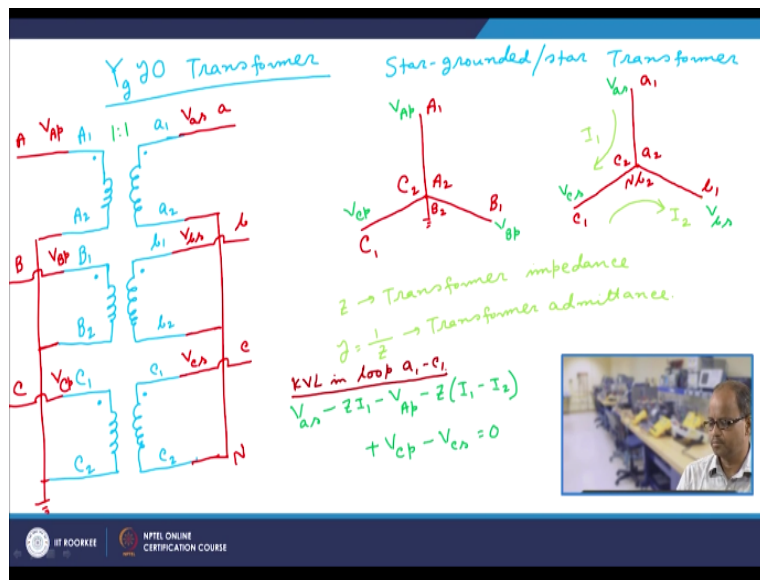


**Computer Aided Power System Analysis**  
**Prof. Biswarup Das**  
**Department of Electrical Engineering**  
**Indian Institute of Technology – Roorkee**

**Lecture - 59**  
**Fault Analysis (Contd.)**

Hello friends. Welcome to this lecture on computer aided power system analysis. We have been looking into the aspect of transformer modeling. In the last lecture, we have looked into the modeling of YgYg transformer of corresponding to two different vector groups. Today, we would be looking into the aspect of modeling in Ygy transformer.

**(Refer Slide Time: 01:02)**



So therefore today what we are going to do is modeling of Ygy transformer, so it is Ygy transformer, so let us say Ygy0 transformer. So that means it is basically star-grounded star transformer and there is no phase difference between the phase A voltage of the primary side and the phase a voltage of the secondary side. So then therefore, we again draw, so we have got as we have done so have got 3 winding, as you have done in the earlier case you are doing exactly the same case.

So I have got A1 A2, B1 B2, C1 C2 then small a1 small a2, small b1 small b2, small c1 small c2 and the dots are here, here, here, here, here and here. So as usual this is star-grounded, so this is phase A, this is phase B, this is phase C and because this vector diagram would be the same, so we have already seen so then obviously we also have to star ground them but only difference is that they will not be grounded.

So you are creating a star connection but they will not be grounded. So this is phase a, this is phase b, this is phase b, this is phase small c. So the voltage let us say we denote that it is  $V_A$  now and  $V_B$  and  $V_C$ . Now it is  $V$  small c, it is  $V$  small b, it is  $V$  small a. To distinguish between the primary side and secondary side, we can possibly write  $V_{Ap}$ ,  $V_{Bp}$ ,  $V_{Cp}$  and let us say this is  $V_{as}$ ,  $V_{bs}$ ,  $V_{cs}$ .

Otherwise, sometimes this capital C and small c they are not (()) (04:33) recognizable with each other. So the current is  $I_A$ ,  $I_B$  and  $I_C$  etc. So now we draw the vector diagram. Vector diagram we already know, so this is grounded, this is  $A_1$   $A_2$ , this is  $B_1$ , this is  $B_2$ , capital  $C_1$ , capital  $C_2$  and in the secondary side also we have got the same. So this is  $a_1$   $a_2$ ,  $b_1$   $b_2$ , small  $c_1$  small  $c_2$ .

Only difference is that that this point is not grounded. So now the point is that how do we calculate the current? Now in the earlier case, when this was grounded and when this was grounded, so then we could only say that essentially the voltage across this particular winding is  $V_{Ap}$  only but here in this case the voltage across this winding is not equal to  $V_{as}$ , it is actually  $V_{A1}-V_{A2}$ .

So then therefore, if I say that this point is neutral so it is actually  $V_{A1}-V_N$ , similarly the voltage across this is  $V_{B1}-V_N$  and then similarly the voltage across this winding is actually  $V_{C1}-V_N$  but here we do not know what is the capital N, we just do not know what is capital N. So then therefore, what we can do is so then therefore we really cannot write that  $I_A$  is  $=V_{Cp}-V_{cs}/z$  and etc.

So then so to get around this problem what we do is we take some circulating current like this let us say  $I_1$  and we take some circulating current like this say  $I_2$  at the secondary side that is at the y side and we also say that  $z$  is the transformer, small  $z$  is the transformer impedance. So then therefore we can say  $y$  is  $=1/z$  is transformer admittance. Now what we will do is so let us denote these potentials, so these potentials are  $V_{as}$ ,  $V_{bs}$ ,  $V_{cs}$  and this is say  $V_{Ap}$ ,  $V_{Bp}$ ,  $V_{Cp}$ .

Now we would like to write down the KVL across this loop, so then if we consider this loop so then what will happen? Now in this loop, if I start from this point and if I go to this point,

what are the electrical quantities we will get? Now when I go in this direction, so then we get the equation  $V_{as}$ , so this voltage-the drop due to this current  $I_1$ , so  $z \cdot I_1$  and there also would be a drop.

Now because these two windings are actually magnetically coupled with each other, so then therefore when we would travelling in this direction, we will also get one reflected voltage here, so then therefore that reflected voltage will also be from this to this. So then therefore, this reflected voltage would be  $V_{Ap}$ . Here we are assuming that this is 1:1 transformer, so  $V_{Ap}$ . So  $V_{as}$ -this drop and then the voltage drop due to this reflected voltage of the primary side to the secondary side.

Then, we are moving in this direction and in this direction what is the amount of current in this direction, in this direction the current is  $I_1 - I_2$ , so it is minus, so then the drop is  $z (I_1 - I_2)$  - the drop in this direction due to the voltage, due to the voltage corresponding to this branch. Now here when you are moving in this direction, so then therefore we are here encountering the C phase, so then therefore here also you will be encountering C phase.

But then this potential  $V_{Cp}$  is actually from this to this, so then therefore when we would be moving from this side to this side here, it would be actually rise so then it would be  $V_{Cp}$  right, so it would be  $V_{Cp}$  and then  $-V_{Cs}$  is  $=0$ . I repeat, so then therefore we start so as if at this point as if that time there is a rising voltage  $V_{as}$ -the drop and this is nothing but the impedance drop due to the flow of current  $I_1$  in this branch that is  $z I_1$ .

Then, there will be another drop due to this reflected voltage of phase A, see this is phase A and this is phase a. Then, there is another drop because in this direction net current is  $I_1 - I_2$ , so then therefore there is a drop  $z \cdot (I_1 - I_2)$ . Now the reflected voltage of the primary side of phase C is actually from this side to this side, so then therefore when you are moving from this side to this side, it would be nothing but a rising voltage.

So then we will get  $V_{Cp}$  and then of course then it will be the drop  $V_{Cs}$ . So this is the equation. So this equation is actually you should actually write that KVL in loop a1-c1, so we are writing KVL in loop a1-c1.

**(Refer Slide Time: 12:12)**

$\Rightarrow zI_1 + z(I_1 - I_2) = V_{a_n} - V_{Ap} + V_{Cp} - V_{Cn}$   
 $\Rightarrow 2zI_1 - zI_2 = V_{a_n} - V_{Ap} + V_{Cp} - V_{Cn} \dots\dots\dots ①$   
KVL in the loop c1-b1  
 $V_{Cn} - z(I_2 - I_1) - V_{Cp} - zI_2 + V_{Bp} - V_{A_n} = 0$   
 $\Rightarrow z(I_2 - I_1) + zI_2 = V_{Cn} - V_{Cp} + V_{Bp} - V_{A_n} \dots\dots\dots ②$   
 $\Rightarrow -zI_1 + 2zI_2 = V_{Cn} - V_{Cp} + V_{Bp} - V_{A_n} \dots\dots\dots ③$   
 $② \times 2 \Rightarrow -2zI_1 + 4zI_2 = 2(V_{Cn} - V_{Cp} + V_{Bp} - V_{A_n}) \dots\dots\dots ③$   
 $① + ③ \Rightarrow 3zI_2 = V_{a_n} - V_{Ap} + V_{Cp} - V_{Cn} + 2V_{Cn} - 2V_{Cp} + 2V_{Bp} - 2V_{A_n}$   
 $\Rightarrow 3zI_2 = -V_{Ap} + 2V_{Bp} - V_{Cp} + V_{a_n} - 2V_{A_n} + V_{Cn}$

So then therefore we can write down the equation as from this you can write down that  $zI_1 + zI_1 - I_2$  so  $zI_1 + z \cdot I_1 - I_2$  is  $= V_{as} - V_{Ap} + V_{Cp} - V_{cs}$  or in other words it is  $2zI_1 - zI_2 = V_{as} - V_{Ap} + V_{Cp} - V_{cs}$ . So this is equation number 1. Now we consider another loop. Now we consider the loop c1-b1. So now we write the KVL equation in the loop c1-b1. So we write KVL in the loop c1-b1.

So when I write down the KVL in the loop c1-b1, so we start from this point and we reach at this point. So when we start at this point, so my voltage is  $V_{cs}$  so my first voltage is  $V_{cs}$ . Then, the current in this direction is  $I_2 - I_1$ , so then the drop due to the current in this direction is  $zI_2 - I_1$ . So then the drop  $z \cdot I_2 - I_1$ , then there would be a drop due to the reflected voltage of phase C here.

So then this reflected voltage is also from this point to this point and then essentially the instantaneous polarity of this reflected voltage would also be from this point to this point. So there will be  $-V_{Cp}$  so it is  $-V_{Cp}$ . Then, the drop when the drop in this direction in this branch the current is only  $I_2$ , so then the drop is  $-zI_2$ , so  $-zI_2$ . Then, now we should also have now here in this branch the reflected voltage is  $V_{Bp}$ .

But again this  $V_{Bp}$  is actually rising from this point to this point, so then therefore the reflected voltage here at this branch would also be rising from this point to this point. So then therefore, this is a rising voltage, so then therefore it should be  $+V_{Bp}$  and then -we reach this voltage  $-V_{bs}$  is  $= 0$  right. So it is  $-V_{bs}$  is  $= 0$ , so then therefore we write  $zI_2 - I_1 + zI_2$  is  $= V_{cs} - V_{Cp} + V_{Bp} - V_{bs}$ .

So then therefore  $-zI_1 + 2zI_2$  is  $=V_{cs} - V_{Cp} + V_{Bp} - V_{bs}$  is equal to so this is the second equation. So now what happen, so you have got so now therefore what you have done so far because at the secondary side I do not know this voltage of this point N, so this point is N or b2 the same. So we have created two-loop current  $I_1$  and  $I_2$  and by writing KVL equations in two loops, so we have got two loop equations.

These loop equations are given by 1 and 2. So now we need to solve these two equations and find out the expression of  $I_1$  and  $I_2$ . So to do this, so what we do is we do multiplication of 2 x 2 so now is actually  $-4I_1$  it is  $-2zI_1 + 4zI_2$  is  $=2 * V_{cs} - V_{Cp} + V_{Bp} - V_{bs}$ . So this is equation 3. Now we do 1+3, if we do 1+3 so then what happens, this this cancel out and this becomes  $3zI_2$  is actually  $V_{as} - V_{Ap} + V_{Cp} - V_{cs} + 2V_{cs} - 2V_{Cp} + 2V_{Bp} - 2V_{bs}$  or in other words  $3zI_2$  will be now take all these things common.

So what we get,  $V_{as} - 2V_{bs}$  so first  $-V_{Ap} + 2V_{Bp}$  and so it is I have got  $-V_{Ap} + 2V_{Bp} - V_{Cp} + V_{as}$  then  $-2V_{bs} + V_{cs}$ . So again let us cross check so let us cross check this  $V_{Ap} + 2V_{Bp} - V_{Cp} + V_{as}$  then  $-2V_{bs}$  and  $+V_{cs}$ .

**(Refer Slide Time: 20:30)**

Handwritten mathematical derivation on a whiteboard:

$$\Rightarrow I_2 = \frac{2}{3} (-V_{Ap} + 2V_{Bp} - V_{Cp} + V_{as} - 2V_{as} + V_{cs}) \dots \text{--- (4)}$$

$$\text{By } \textcircled{1} \times 2 \Rightarrow 4zI_1 - 2zI_2 = 2(V_{as} - V_{Ap} + V_{Cp} - V_{cs}) \dots \text{--- (5)}$$

$$\text{By } \textcircled{5} + \textcircled{2} \Rightarrow 3zI_1 = V_{cs} - V_{Cp} + V_{Bp} - V_{as} + 2V_{as} - 2V_{Ap} + 2V_{Cp} - 2V_{cs}$$

$$\Rightarrow 3zI_1 = -2V_{Ap} + V_{Bp} + V_{Cp} + 2V_{as} - V_{as} - V_{cs}$$

$$\Rightarrow I_1 = \frac{2}{3} (-2V_{Ap} + V_{Bp} + V_{Cp} + 2V_{as} - V_{as} - V_{cs}) \dots \text{--- (6)}$$

Now,  $I_{an} = I_1$ ;  $I_{as} = -I_2$ ;  $I_{cs} = I_2 - I_1$

$$I_{as} = \frac{2}{3} (V_{Ap} - 2V_{Bp} + V_{Cp} - V_{as} + 2V_{as} - V_{cs}) \dots \text{--- (7)}$$

The whiteboard also features a small inset image of a classroom setting and logos for IIT Roorkee and NPTEL Online Certification Course at the bottom.

So then therefore  $I_2$  is  $=y/3 * \text{what is } y/3, y/3 * \text{what is } y/3? y/3 * (())$  (20:42)  $-V_{Ap} + 2V_{Bp} - V_{Cp}$  when writing all of them  $+V_{as} - 2V_{bs} + V_{cs}$ . So this is the expression of  $I_2$ . So let us so this is the equation. So I have got the expression of  $I_2$ . Now we have to also get the expression of  $I_1$ . So to get the expression of  $I_2$ , what you do is we multiply this equation by 2, so by

equation 1\*2 so what does it give us, this give us  $4zI_1 - 2zI_2$  is  $= 2*V_{as} - V_{Ap} + V_{Cp} - V_{cs}$  so this is also equation say 5.

Now what you do is we add 5 and 2, so if I add 5 and 2 so what you get is if I add 5 and 2 so we do by 5+2 so what you get so 5 and 2 we get is  $3zI_1$  is  $= V_{cs} - V_{Cp} + V_{Bp} - V_{bs} + 2V_{as} - 2V_{Ap} + 2V_{Cp} - 2V_{cs}$ . So then therefore what we get is  $3zI_1$  we collect everything first we collect  $V_{Ap}$  so when we collect  $V_{Ap}$  so we get  $-2V_{Ap}$  there is only  $-2V_{Ap}$  so  $-2V_{Ap} + V_{Bp}$  so  $-2V_{Ap} + V_{Bp}$  and then  $+V_{Cp}$  and then what we get is  $+2V_{as}$  and then what we get is  $-V_{bs}$  and  $-V_{cs}$ . Let us cross check.

So let us cross check, so cross check with  $-2V_{Ap}$  that we have got,  $+V_{Bp}$  that we have got,  $+V_{Cp}$  this and this  $+2V_{Cp}$ ,  $2V_{as}$  so this gives me  $2V_{as}$ ,  $-V_{bs}$  this gives me  $-V_{bs}$  and only this two are remaining, everything else has been taken care of so these two remaining  $-V_{cs}$  so then therefore  $I_1 = \frac{1}{3} (-2V_{Ap} + V_{Bp} + V_{Cp} - 2V_{as} - V_{bs} - V_{cs})$ , 6 and 4 are the equations of  $I_1$  and  $I_2$ . So with these equations of  $I_1$  and  $I_2$ , now we are ready to write down the equation.

**(Refer Slide Time: 26:55)**

The image contains two hand-drawn circuit diagrams and associated mathematical notes. The left diagram is labeled 'YgΔ0 Transformer' and shows a three-phase transformer with primary windings A1, B1, C1 and secondary windings a1, b1, c1. The right diagram is labeled 'Star-grounded/star Transformer' and shows a similar three-phase transformer with primary windings A1, B1, C1 and secondary windings a1, b1, c1. Handwritten notes include: 'Z -> Transformer impedance', 'Y = 1/Z -> Transformer admittance', and a KVL equation: 'KVL in loop a1-c1: V\_a1 - Z I\_1 - V\_A1 - Z(I\_1 - I\_2) + V\_c1 - V\_c1 = 0'. A small video inset shows a person speaking.

Now from here what I can do, now I a1 or rather I small a or now let us say that these currents are denoted as now let us say these currents are denoted as let us say  $I_{as}$ , this current is  $I_{as}$ , this current is  $I_{bs}$ , this current is  $I_{cs}$ . So this current is  $I_{bs}$ , this current is  $I_{cs}$ , this current is  $I_{as}$ . So then therefore what we can do write  $I_{as} = I_1$ . So now from this equation I can write down that now we can write down  $I_{as} = I_1$ ,  $I_{bs} = -I_2$  and  $I_{cs} = I_2 - I_1$ .

So then therefore  $I_{as}$  is  $I_1$  is this,  $I_{bs}$  is  $-I_2$  so then therefore  $I_{as}$  is equal to so then therefore  $I_{as}$  is  $I_2 - I_1$ . So  $I_{bs}$  is actually is  $-I_2$  so then therefore  $y/3 * V_{Ap} - 2V_{Bp} + V_{Cp} - V_{As} + 2V_{Bs} - V_{Cs}$ . So this is equation 7 and  $I_{cs}$  is  $I_2 - I_1$ .

**(Refer Slide Time: 29:22)**

$$I_{cs} = I_2 - I_1 = \frac{y}{3} \left[ -V_{Ap} + 2V_{Bp} - V_{Cp} + V_{As} - 2V_{Bs} + V_{Cs} + 2V_{Ap} - V_{Bp} - V_{Cp} - 2V_{As} + V_{Bs} + V_{Cs} \right]$$

$$\Rightarrow I_{cs} = \frac{y}{3} \left[ V_{Ap} + V_{Bp} - 2V_{Cp} - V_{As} - V_{Bs} + 2V_{Cs} \right] \dots \text{--- (8)}$$

So  $I_{cs}$  is  $I_2 - I_1$  that is  $y/3 * V_{Ap} + 2V_{Bp} - V_{Cp} + V_{As} - 2V_{Bs} + V_{Cs}$  so this is  $I_2 - I_1$  so it is  $+2V_{Ap} - V_{Bp} - V_{Cp}$  and  $-2V_{As} + V_{Bs} + V_{Cs}$ . So then therefore  $I_{cs}$  is  $y/3 * V_{Ap} + V_{Bp} - 2V_{Cp}$  then  $-V_{As} - V_{Bs} + 2V_{Cs}$ . So this is equation 8. So now what we have got, we have got the 3 equations at the secondary side. Now we have to get the 3 equations at the primary side and then we have to write down the inter Y bus matrix right. So this we will do in the next lecture. Thank you.