

Microelectronics: Devices to Circuits
Prof. Sudeb Dasgupta
Department of Electronics and Communication
Indian Institute of Technology, Roorkee
Module 02: Microelectronics: Devices to Circuits
Lecture 09: BJT: Small Signal Circuit Model-II

Hello and welcome to NPTEL Online Certification course on Microelectronics: Devices to Circuits. In our previous lecture, we had discussed with you the π model and the T model. We have also discussed with you the condition for small signal model and we have seen that the requirement for small signal model has been that, if your input signal is small enough so that your bias point does not change too much and you are in the linear region of operation of the device where amplification is almost independent of the input voltage, we define that to be as smallest signal. We have also understood that if I have a BJT in a common emitter configuration then the amplification is typically very large, of the order of few hundreds in Voltage Amplification.

Whereas common collector does not give me voltage amplification directly, right? We also understood about the relationship between α and β , where β is basically the current gain and α is also a current gain in common emitter configuration and β is common current gain in common emitter configuration and α is the current gain in common base configuration. We have seen the functionality and the operation of BJT. What we will do today is, have a look at small signal circuit model we will extend that to *CE*, *CB* and *CC* which means common emitter, common base and common collector.

(Refer Slide Time: 2:07)

Common-emitter configuration

$R_{in} = r_{\pi}$

$v_o = -(g_m v_{\pi})(R_C \parallel r_o)$

$R_o = (R_C \parallel r_o)$

Fig. 7. Common-emitter amplifier

Source: Microelectronics Circuits, Sedra and Smith, Fifth edition

So, just to continue with yesterday's talk, we will come to this point that if you have a common emitter configuration which you see then, as I discussed with you in the yesterday's discussion or slide that, you do have a BJT here which is an NPN transistor looking at the direction of the arrow, this is basically an NPN right? So I have a p-type base, an n-type emitter and we have got a collector which is n-type, there is also a resistance ' R_c ' which primarily is a resistance which is seen at the collector side right? And you have an input resistance also referred to as ' R_{sig} ' here and we define ' R_m ' as the input resistance or input impedance and ' R_o ' as the output resistance or impedance and ' V_o ' as the output voltage whereas ' V_{sig} ' is my input voltage, input voltage.

Now you see that the two aspects which should be very clear at this stage, V_{sig} is not equal to ' V_i ' right, so your input voltage to the BJT will be slightly less as compared to the actual signal voltage and the reason being the presence of this R_{signal} right? Because these are all voltage sources right, and these voltage sources will have a finite output impedance and as a result, this output impedance will, there will be some drop across that output impedance and therefore the actual potential applied to the base emitter junction of a BJT will be relatively smaller, smaller than what is expected from here, right?

Now so we have therefore if you so this BJT is broken up into equivalent small signal model as you can see the blue box here, where you have r_{π} , r_{π} is basically nothing but the value of R_{in} and the reason being r_{π} is nothing but the resistance between the base emitter junction, right so when the base emitter junction is forward biased this r_{π} will be of the order of few ohms right to the order of ohms right, because it is a forward bias device characteristics.

(Refer Slide Time: 4:08)

Common-emitter configuration

(a)

(b)

Fig. 7. Common-emitter amplifier

Source: Microelectronics Circuits, Sedra and Smith, Fifth edition

2

Now so....so.... the voltage across this r_{π} is the voltage which is basically V_{be} happens to be r_{π} so V_{π} is the voltage across across r_{π} right? So this is sort of an input voltage which is visible to us and that when multiplied by transconductance (g_m) gives me the output current, right? And that is the count, so g_m times r_{π} or V_{π} is my output current, that if you multiply with the effective resistance seen from the output sign. What is the effective resistance? R_C parallel to R_o , right? R_C parallel to R_o and therefore I get V_o equals to minus g_m times V_i into R_C parallel to R_o .

(Refer Slide Time: 5:05)

The slide displays a handwritten derivation in red ink. It starts with the equation $-g_m v_\pi (R_C \parallel R_o) = v_o$. Below this, the parallel resistance is expressed as a fraction: $-g_m v_\pi \left[\frac{R_C R_o}{R_C + R_o} \right] = v_o$. The next step shows the fraction being multiplied by $\frac{R_C + R_o}{R_C + R_o}$ to get $-g_m v_\pi \left[\frac{R_C + R_o}{R_C + R_o} \right] = v_o$. Finally, the fraction is simplified to $\frac{1}{R_o} + \frac{1}{R_C}$, resulting in the equation $-g_m v_\pi \left[\frac{1}{R_o} + \frac{1}{R_C} \right] = v_o$.

At the bottom of the slide, there is a footer with the IIT ROORKEE logo and the text "NPTEL ONLINE CERTIFICATION COURSE". A small number "2" is visible in the bottom right corner of the slide area.

So if you look very carefully or understand it, then it is basically minus g_m times V_π , right? R_C parallel to R_o , this is the value of your V_o , right? See if you if you break it down V_π this will be $R_C R_o$ upon R_C plus R_o , right? This will be your so, basically the 1 upon this so minus $g_m V_\pi$ into R_o , R_o , fine? So you see therefore if you break it up, I get 1 by R_o plus 1 by R_C , right? This is equals to your V_o for our practical purposes.

(Refer Slide Time: 6:28)

Handwritten mathematical derivation on a whiteboard:

$$A_v \approx g_m \quad -g_m v_o (R_C \parallel r_o) = v_o$$

$$-g_m v_o \left[\frac{R_C r_o}{R_C + r_o} \right] = v_o$$

$$-g_m v_o \left[\frac{R_C + r_o}{R_C r_o} \right] = v_o$$

$$(high) \quad -g_m v_o \left[\frac{1}{r_o} + \frac{1}{R_C} \right] = v_o$$

Now you see where R_o at R_C is the external potential, R_C is the external bias which you have given and R_o is basically the, the output impedance of the BJT, right? So the parallel combination of R_o and R_C gives you the net output impedance seen by the device and therefore I have written here that R_o is equal to R_C parallel R_o , right? And that gives you a fair idea about the type of voltages which you will get. Since g_m is relatively high right, so g_m is high. Even if this quantity is low quantity right, even if it is low I will get V_o which quiet high, right?

(Refer Slide Time: 7:12)


Common-emitter configuration

BJT \rightarrow BJT
signal
 $v_{sig} \neq v_i$
 $\sum (r_{\pi} g_m)$
 $R_{in} = r_{\pi}$
 $v_o = - (g_m v_{\pi}) (R_C \parallel r_o)$
 $R_o = (R_C \parallel r_o)$

Fig. 7. Common-emitter amplifier
 Source: Microelectronics Circuits, Sedra and Smith, Fifth edition


So therefore, we can safely assume that that the gain is directly proportional to g_m which is an understood phenomena, that it is actually depending on the value of g_m , so higher the sensitivity is for a BJT to work, more will be the gain and therefore more will be the output voltage with the same amount of input voltage but please keep in mind that the V_{sig} which you are using the signal input signal voltage is basically a small signal, right? Please keep this in mind for all practical purposes. This is basically small signal right and therefore these are all small signal models.

(Refer Slide Time: 7:43)

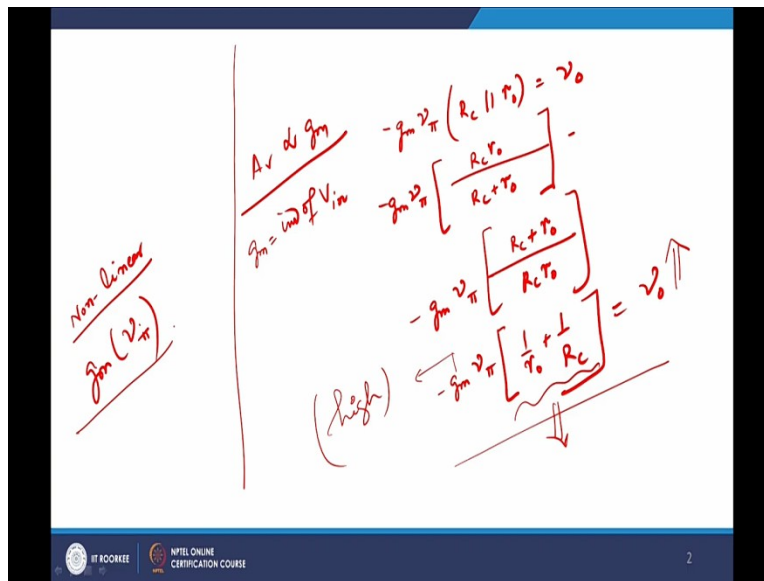

Now if your signal is large then you entail a non-linearity into your g_m , so assuming g_m to be constant will be an over assumption, right? So one important point when you do a non-linear analysis or a non-linear profiling which is which we are not doing here, non-linear. Then g_m will be actually a function of V_{in} , in this case V_{π} , right? But in reality or at least for the all understanding purposes basic purposes, we assume that g_m is sort of independent of independent of V_{in} , right? In reality g_m might be also a function of V_{π} and therefore you will entail a non-linearity into the whole system. So...so... therefore we have understood that you do have a problem of nonlinearity also coming into picture, but if we sustain a small value of input voltage there will be no nonlinearity and I would expect to see a gain which is totally independent of V_{in} and linear gain will be available.


(Refer Slide Time: 8:26)

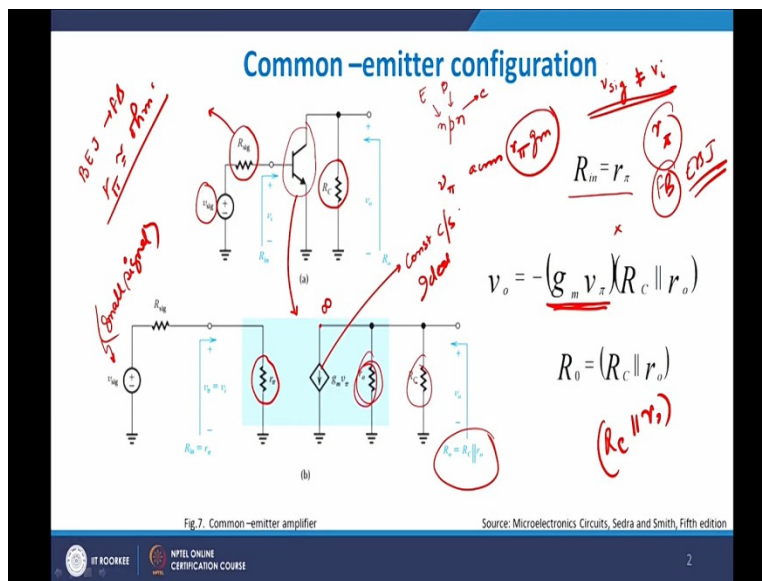

Two things we therefore, we take out from this slide is that my input impedance is R_π and output impedance is basically R_C parallel to R_o right? Now so your input impedance is basically R_π which is nothing but the forward biased EBJ right, Emitter Based Junction. The resistance offered by that is basically my EBJ, right? Second thing is, there is also assumption that this is behaving like a constant current source right, constant current source and we are also assuming it to be ideal. So the voltage, so the impedance offered by this is infinity. But since this is parallel of course therefore this does not play into the picture. I think it is clear to you right?

So, what we have therefore assumed is that the current source is basically an ideal current source as a result, the output impedance is infinity and, Since it is a constant current source and the output impedance is infinity, when it is parallel to R_o and R_C right, so that vanishes off because it is quite high a quantity, right. So in parallel combination that does not stay to a large extent right, obviously because in parallel you remember it is less than the least in the series and it is larger than the largest. In this case it is less than the least and therefore we just neglect that particular case, right? Okay.

(Refer Slide Time: 9:57)

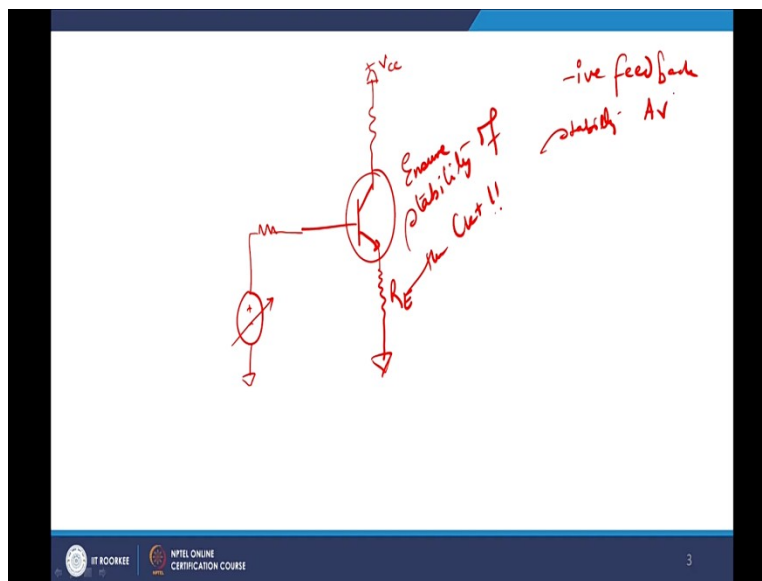


We now move into the next slide and see what happens with emitter resistance. Let me see why do you at all needed emitter resistance, very important issue is there when we are having an emitter. Till now if you remember we were actually looking from the point of view or the fact that we had a BJT right? And there was a resistance here, fine and you had a bias here and this bias was varying and you did it like this, like this and then we have a plus V_{CC} and then we are doing like this sorry, we are doing like this, this is R_E .

Now what we are trying to tell you is, that no let me do small, a change here and the change is that we try to do some change in emitter configuration and what is the change, change is that we try to put a resistance here, why we will see that later on. So let me put a resistance R_E here right, emitter resistance, all right. Now see, the reason we want to do it is to ensure what is known as stability, ensure stability of the circuit and I will explain that to you how I get it.

See if you remember from your basic class tenth even undergraduate days that or you can understand that whenever you have a negative feedback right? Whenever you have a negative feedback, you automatically have a more stable system, right. The (pay) the price you pay for it is here, gain starts to fall down, right?

So if I do a negative feedback in voltage domain which means that the output feedback, the output voltage is fed into the input voltage, input side with a 180 degree phase shifted value then, I can safely assume that my overall gain will reduce because obviously there will be principle of superposition can be applied and the two voltages will be added algebraically as a result the overall voltage bit falls down but then, we also ensure that by doing a negative feedback that the overall gain is more stabilized which means that the gain with respect to change in the input is much smaller.

(Refer Slide Time: 12:13)

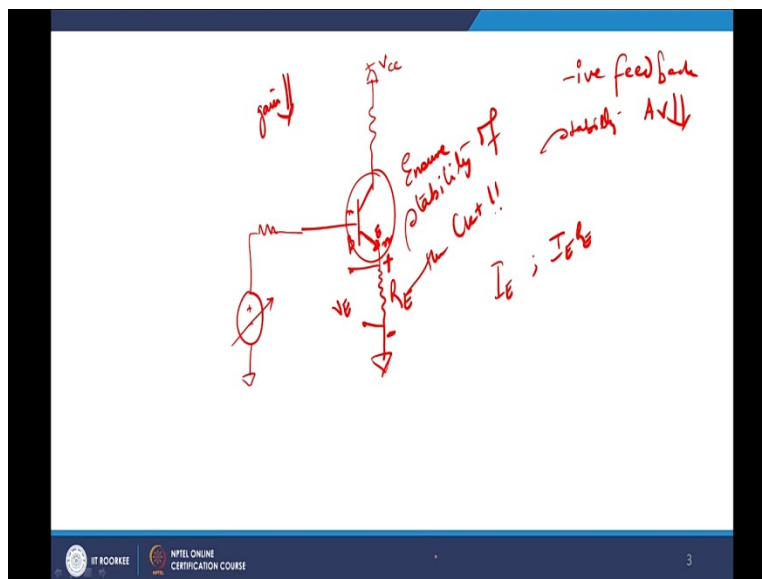

So, negative feedbacks actually gives you a stable system that is what we have learnt and we know all of us possibly know this basic concept. Now if this R_E is in series to this external emitter resistance, emitter resistance is applied to, to the side of emitter then when a current I_E flows through it then there is a voltage drop which is I_E times R_E in which this is positive and this is negative, right? So the voltage across this which is let us suppose we assume it to be as V_E appears because of I_E, R_E .

This V will start to reverse bias my this base emitter junction right, as it starts to reverse bias it is because you are applying positive side to n-type and maybe a negative side to p-type right, or even a positive bias to the n-side and as a result what is happening is that the emitter is getting

more and more positive which means it is trying to reverse bias the emitter base junction and therefore majority current carrier is reducing and you have a large amount of minority carrier which appears.

Therefore, when you apply R_E your gain starts to fall down, right? And it starts to go down and down. So when you put an emitter resistance R_E in series to the BJT we end up having a reduced gain right, a reduced gain but a more stabilized, stabilized circuit. So I have a reduced gain but more stabilized is with me. So that is the reason why we do, we bias with emitter resistance.

(Refer Slide Time: 13:49)

Common-emitter configuration with emitter resistance

$$R_m = (\beta + 1)(r_e + R_E)$$

$$A_v = -\frac{g_m R_C}{1 + g_m R_E}$$


$$R_o = R_C$$

Fig. 7. Common-emitter amplifier with emitter resistance Source: Microelectronics Circuits, Sedra and Smith, Fifth edition

Now if you look very carefully therefore, in this case we have an R_E here which is basically this one and therefore R_{in} is given as β plus 1, R_E plus r_e , plus R_E right, where capital R_E is basically the resistance, external resistance and r_e is the internal resistance. So this so if you go from this point to this point, it is basically R_E plus R_E which you see in front of you right, that you multiplied with β plus 1 you get total R_{in} value right, because that is the basic definition of a β now. β will be very much larger than 1 and therefore I can safely write down R_{in} to be equals to β times r_e plus R_E which appears as βr_e plus β times R_E , right?

So if your β is typically very high let us say, it is about 150-200 then the resistances offered by the BJT right and the circuitry gets amplified drastically, right? And the input (temp) and the input resistance becomes very-very large because you can see here, you are multiplying β to both r_e , small r_e and capital r_e and as a result you will have a large amount of voltage across this terminal right, not only that you will also have to reduce the gain of the MOS device which you are using, other FET device of the MOSFET, sorry BJT which you are using.

(Refer Slide Time: 15:27)

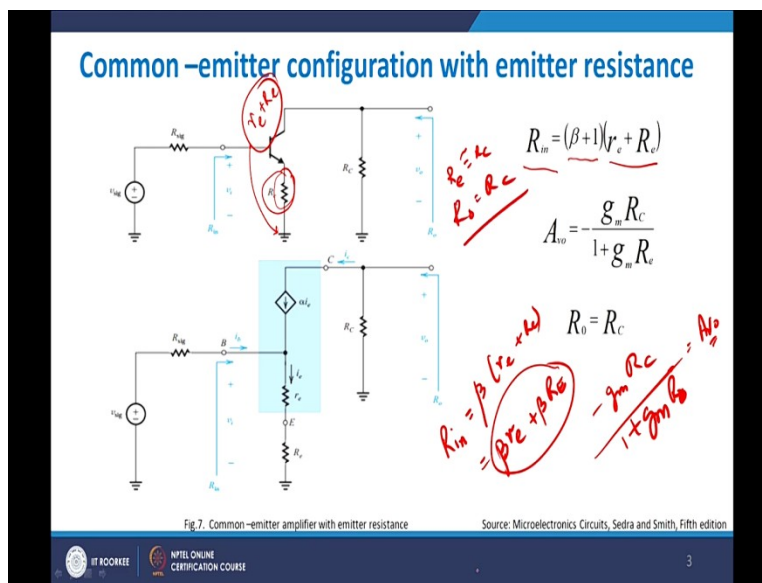

Now therefore I get A_{v0} to be equals to minus g_m times R_C divided by 1 plus $g_m R_E$, right? So it is basically gain is equals to minus $g_m R_C$ divided by 1 plus g_m times R_o , fine. And this your voltage gain A_{v0} . We also assume for all practical purposes that R_E is so large as compared to R_C that R_E is R_C is approximately equal to R_E and as a result R_o equals to R_C , right? So the output impedance or output resistance seen by the device is approximately equal to the collector resistance offered by the BJT, right. These two things we will be assuming for all practical purposes.


If this is true we can look at the left hand side figure, the down figure here, then we see that I have got V_{sig} , I have got R_{sig} which is the signal specifications which terminates at this particular point and you have α times I_E as the collector current source right, assuming that the emitter current is fully biased and only depends upon the input bias and not on anything else. I can safely

say that the collector current here is equal to α times I_E , right? The I_E also flows to the bottom side so I_E times R_E is basically the voltage drop which you see on the bottom side of the channel, right. And that is what you get from all of these regions, right. Okay.

We now come to the common base amplifier and the common base amplifier you will see that the base is grounded right, so the previous was basically your base emitter grounded, now we are entering into base grounded. So when the base is grounded I get my, I am applying signal to the input side on the emitter side and let us see how it works out. The problem with this is technically is when you apply a signal on the emitter side right, when you apply a signal on the emitter side, you end up having a large parasitic capacitance being extracted even at relatively small voltages, right and as a result what will happen is that the speed of the operation will get reduced, right.


So one has to be very cautious when we design a common base amplifier in a small confined domain. Now with this knowledge we can safely right down or we can actually give an instruction that R_m is equal to R_E , no doubt because of the previous discussion we can just remove it.

(Refer Slide Time: 18:00)

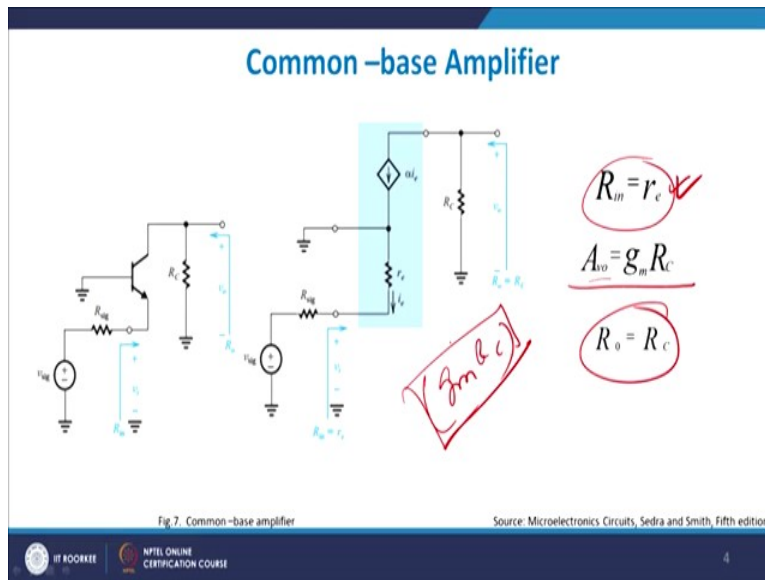

So if you see R_{in} is equal to R_E , which is given here, so I get R_{in} equals to R_E . That is what you get R_{in} equals to r_e why, because input resistance right, input resistance which you feed here is exactly equals to R_E . R_E is the output impedance of a BJT at this stage. So I get A_{v0} equals to g_m times R_C and R_o equals to R_C , right? So you can understand that, your R_o is typically very large quantity and therefore g_m times R_C is very large and that is the reason you do have a large amplification in their case, in their this thing that is compared to other experiments or other this thing because the same reason is that your g_m is relatively independent of the applied currents, right.

(Refer Slide Time: 19:01)

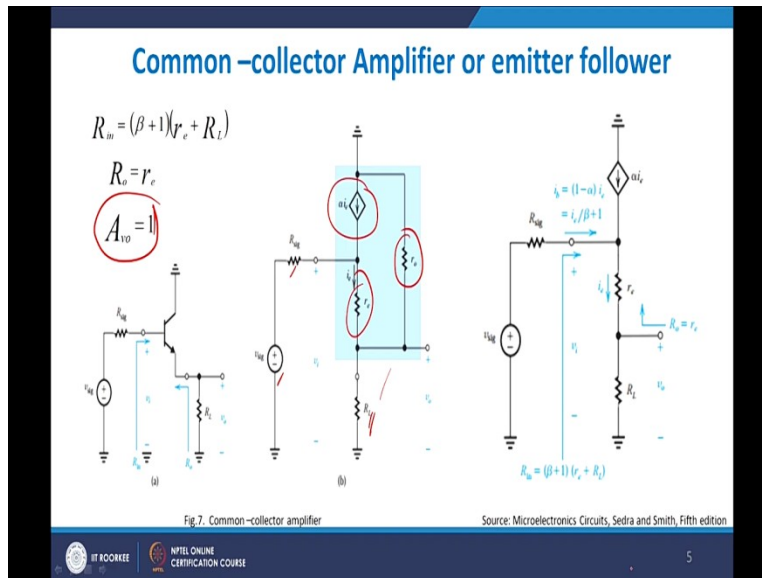

Common Collector Amplifier as the name suggests is also referred to as Common emitter or emitter follower amplifier and is given by this formula. In this case please understand the voltage gain is approximately equals to zero and that is what we all understand that common collector is not a very good amplifier or it cannot amplify small signals to large values, right and that is quite important that they cannot do it and since they cannot do it, they are used for some other purposes but not for amplification purposes, right.

And that is what we come to know right, because A_{v0} equals to 1 so, it is basically phase change which is looking into and nothing else and is given by α times I_E which is basically the actual current source which is available to us. R_L is already there, R_{signal} and V_{signal} is also available. Output impedance of current and resistances are also available with me and gives me quite interesting results as far as common collector or a common this is given.

(Refer Slide Time: 19:55)

Recapitulation

- ❑ The CE configuration is the one best suited for realizing the bulk of gain required in an amplifier.
- ❑ The CB amplifier use as a high frequency amplifier due to low input resistance.
- ❑ The emitter follower finds application as a voltage buffer for connecting a high source to a low-resistance load.

Source: Microelectronics Circuits, Sedra and Smith, Fifth edition

NPTEL ONLINE CERTIFICATION COURSE


6

So let me recapitulate what we did. Common emitter configuration is the most easiest and the most high gain, can be obtained from common emitter configuration. The common base amplifier user high frequency amplified it with low input signal, right? Input signal is quite low and therefore you use a high amplifier design. The emitter follower finds application as a voltage buffer right, for connecting high source and passes it onto right source.

So if you do a common collector, you are actually, though you amplification will be low voltage to voltage but your transits will be very-very fast which means that if you want to compare the output impedance of a particular system with your system. On the collector side if you put the resistance is small and therefore you can easily match the low input impedance and their design. So the emitter follower finds application as voltage buffer for connecting a higher source to a load resistance source, right?


So emitter follower generally used, typically used for the purpose of buffering or the purpose of connecting between two points through a network right and that is what is emitter follower is all about. It is basically we require it the power it to be low and it is excessively low right and that that is what is very important. With this we have almost finished this section but before we move forward let me give you a brief questionnaire or a question maybe, right?

(Refer Slide Time: 21:27)

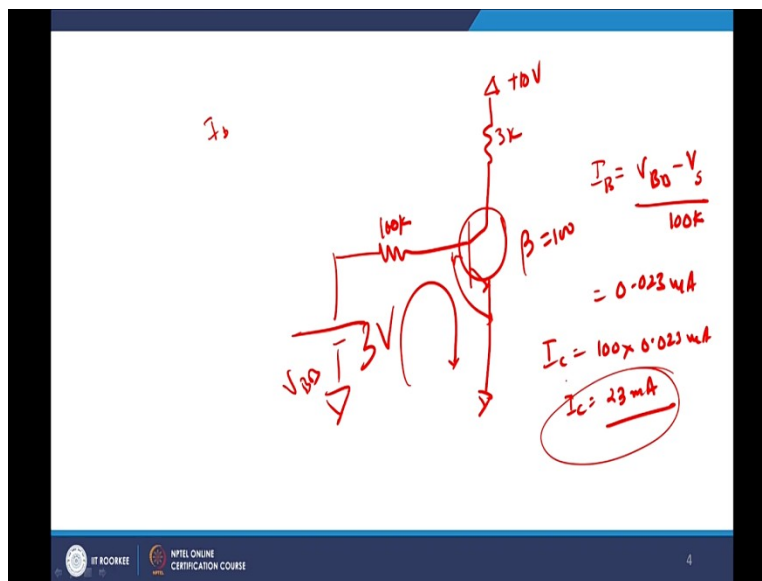

So I have a question, so I have a transistor whose beta is equals to 100 right and applied voltage is 10 volts so I get I_C , so I need to find out first of all beta, this is 3 volts, so we need to find out I_B first. So to do that in this loop, let me find out that this is 0.7, right? And you are given 3 volts, so what you get from here is that I_B will be equals to V_{BB} minus V_s right? This just drop divided by r which is 100 k and if you solve it comes out to 0.023 mA, right?

(Refer Slide Time: 23:12)

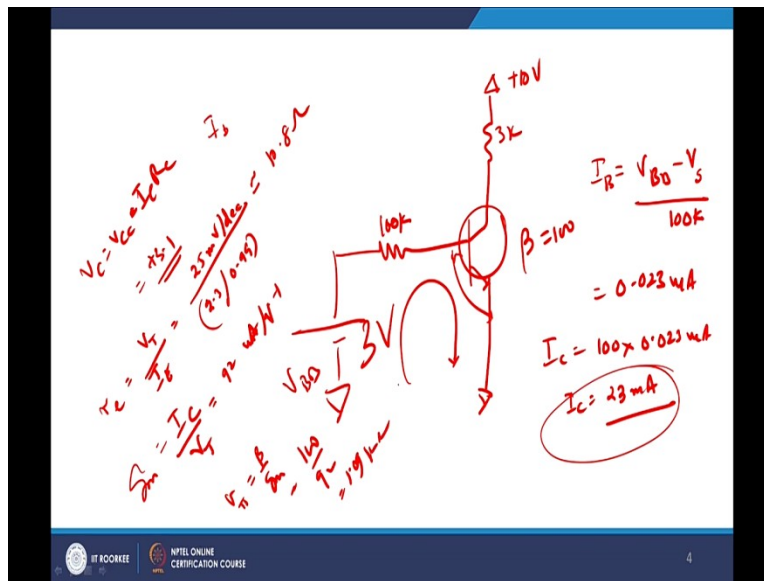

So the amount of current which flows is typically very small. So therefore I_C will be equals to 100 times 0.023 mAs so I_C will be there for approximately 23 mAs, fine. So typically this much amount of current will be required for all practical purposes.


Now, if you again go back and explain the relative slides here we can (show), we can safely show that V_C is equals to V_{CC} minus $I_C R_C$, right? In this case we find out this to be as plus 3.1 volt. Now if you find out the value of R_E it is V_T by I_E . V_T is 25 mV/decade divided by V_T , V_T is divided by I_E actually. I_E will be V_T divided by 2.3 divided by 0.99 and this comes out to be approximately close to 10.8 Ω , which means that 10.8 Ω is the is the emitter resistance offered by the emitter to the input system , right?

Transconductance (g_m) can be written as I_C by V_T and therefore this can be written as 92 mA per voltage minus, right? $R_\pi \beta$ by g_m , we get 100 by 92, fine. So this is how we do a small signal analysis as far as this course is concerned and gives you an idea about how a small signal analysis works even for a single transistor or for a BJT. A transistor wherein BJT starts to find out new methodologies to destabilize itself, right?

So therefore these are the few areas in which people are working and quite interesting work is going on. Now, so, what we did was, we used a common emitter configuration for the best configuration and we and then what we saw was that for if your gain is typically very large, bulk gain is very-very large and your actual gain or the device gain is relatively small we can still have that as the best suited amplifier.

The common base is used for high frequency due to low input resistance is used for high frequency amplifier, right? The emitter follower finds applications of voltage buffer for connecting a high source to a low resistance path, right. And this we have done for emitter follower, we have done and we do for common base as well, right?

(Refer Slide Time: 25:42)

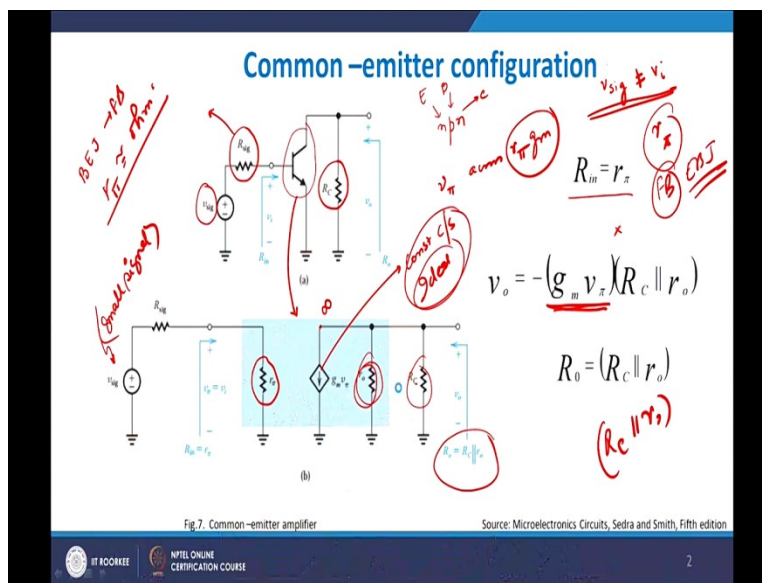

We will therefore in this stage, recapitulate what we did, we did collector common collector emitter base configuration, we also looked into the fact that given a result or given this thing which one is the best form of configuration and for that common emitter is the best form of configuration as far as the results are confirmed. Thank you very much for your patient hearing. We will come back to you next time with more information.