

Basic Electrical Technology
Prof. L. Umanand
Department of Electrical Engineering
Indian Institute of Science, Bangalore

Lecture - 28
DC Motor - 2

Hello everybody. In the last session we had started our discussion about the DC motors. Principally the DC motors and the DC generators belong to the same class with the structure of the machine or the structure of the equipment being similar in both the cases. The structure of a DC generator can be used even for a DC motor only that the flow of power is reversed. In the case of the DC generator the power flows from the mechanical side to the electrical side and in the case of the DC motor the flow of the power is from the side of the electrical to the mechanical side. All the equations and the principles involved are exactly similar to the case of the DC generator.


The DC motor's back emf which is equivalent to the lower end force in the case of the DC generator the induced emf in both the cases that is the back emf here and the generator emf in the case of the generator are having the same equations that is $p N \Phi Z \omega$ by 60 volts the only difference being the flow of power; in the case of the DC motor it flows from the electrical to the mechanical side whereas it is the other way the round in the DC generator. So, in this session we shall continue our discussion of the DC motor. First let us review what we have learnt till now about the DC motor. We have the DC motor which is represented as a circle and it has two brushes. So the armature makes contact with the electrical world by the means of these two brushes and the armature winding resistance is represented as an equivalent resistance R_a as shown here. There is a source which is applied a source voltage which is applied and we call that one as E_a across the terminals of the motor and the armature as the motor is connected to a shaft and which may be coupled to a mechanical load.

Now this DC motor when it is rotating will generate a back emf or a counter emf E_b which we discussed in the last class and on the mechanical side we have two variables which we need to consider that is one is the torque which is the potential variable and the other is the omega in radians per second which is the kinetic or the flow variable on the mechanical side and the flow variable on the electrical side is I_a .

Now E_b into I_a is the power which gets into the armature power delivered to the armature and that is going to deliver the rotational power to the mechanical side. Now the torque here..... we saw that the torque here is given by $p \phi Z I_a$ by 2π **this you saw in the last session** and we know the induced emf is $p N \phi Z$ by 60. So we see here that the induced emf is dependent on this speed of the rotation the torque is dependent on I_a .

If we rewrite this here E_b equals p , now if it had been ω in radians per second I have to convert them into rpm so ω which is in radians per seconds to convert it into rpm 60 by 2π where this is in rates per second. Now this whole thing is in rpm into ϕ into Z **number of** total number of conductors in the armature, ϕ is the flux per pole, p is the number of pole pairs divided by 60 which gives you $p \omega \phi Z$ by 2π and torque is also given by $p \phi Z I_a$ by 2π .

(Refer Slide Time: 7:50)

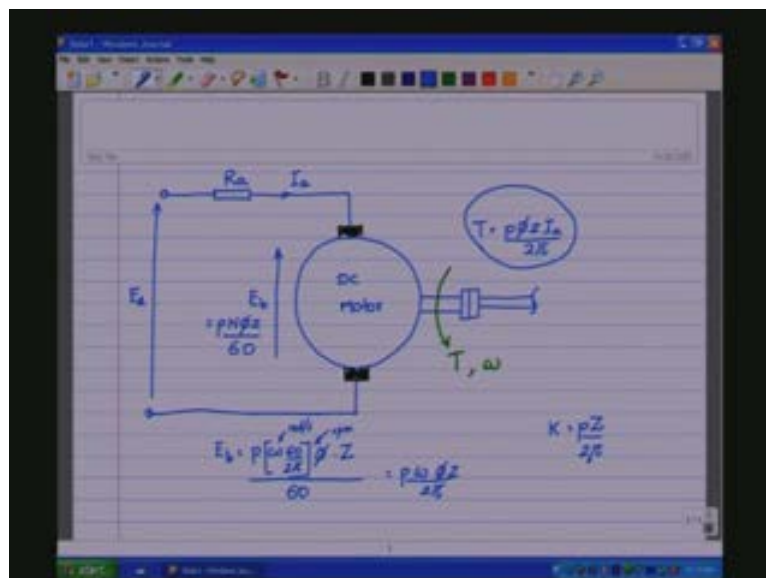


Now let us have a constant K which is defined as $p Z$ by 2π . This constant k is number of pole pairs, total number of conductors and 2π which is a constant and therefore it is a constant for a machine **constant for a machine**. So therefore torque is equal to $k \phi I_a$ and E_b is equal to $k \phi \omega$.

Now these two are the important equations in modelling the motor and also in determining the flow of the power **and the flow of the power** and relations between the two sets of


variables the potential variable on the electrical side to the potential variable and the flow variable on the mechanical side and vice versa.

(Refer Slide Time: 8:56)

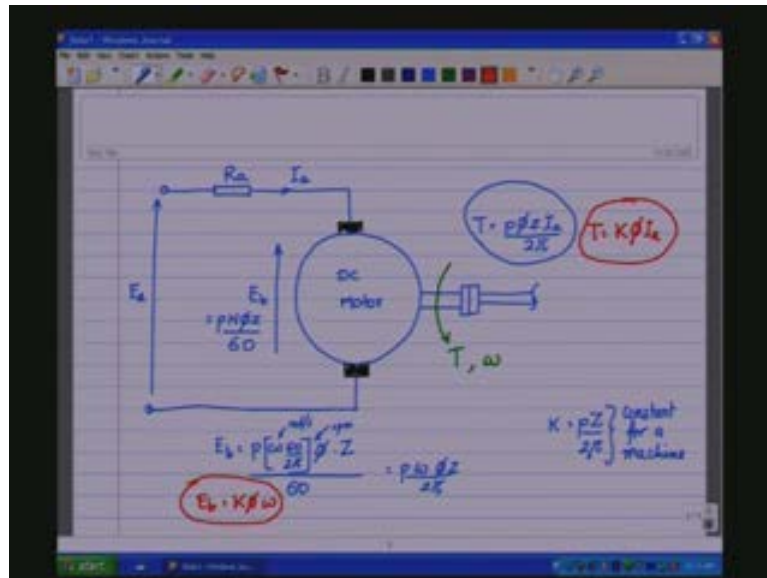

So we now have a motor with brushes as shown here and the mechanical port in the form of the shaft and the electrical port in the form of the black wires being taken out from the brushes.

(Refer Slide Time: 9:36)

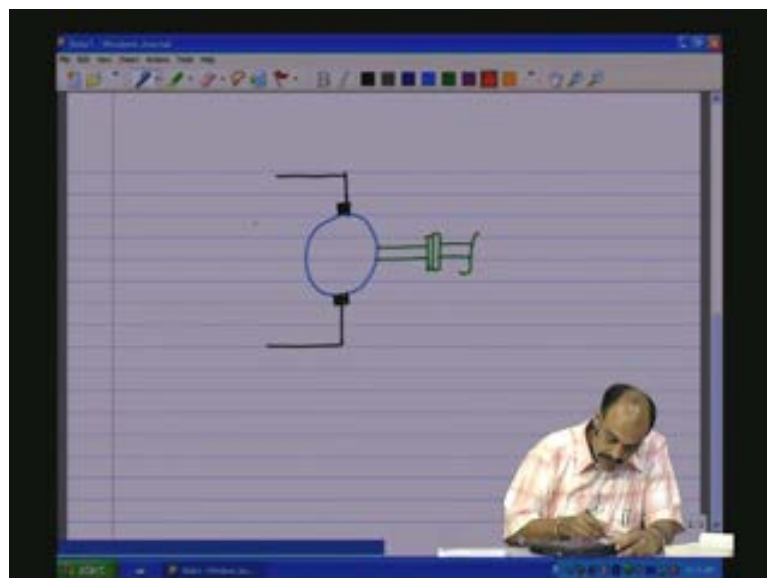


Now E_b , back emf which is induced here is $K \phi \omega$ torque **torque okay** **sorry I will use** **that** is given by generated torque is given by $K \phi I_a$ is it not? That is what we just now, saw in the previous discussion.

Now what is I_a ?

I_a is the current that is flowing into the armature or the armature current and what is ω here; ω is the speed in a radians per second and where k is equal to $p Z$ by 2π . Now you see that we have E_b and I_a on one direction on one side on the electrical side and you have generated torque and ω on the mechanical side.

Now E_b is linked, the back emf E_b is linked with the speed of rotation on the mechanical side angular speed of rotation in radians per second that is ω and I_a is linked with the generated torque as shown by the equations here and the linking variable is $K \phi$ is same for both the cases. So therefore this is a GYRATOR. We have already said that the motors, generators are GYRATORS but this equation here emphasis our point that it is a GYRATOR and not a transformer.


(Refer Slide Time: 12:06)

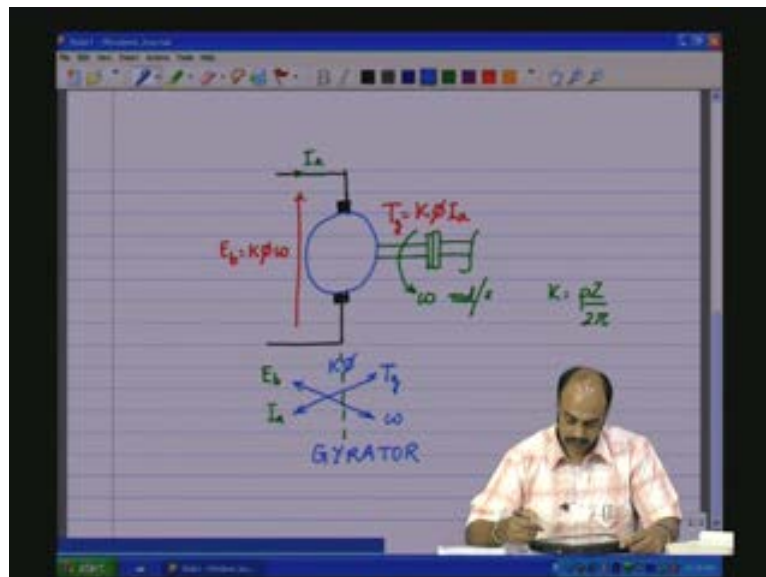

Now, looking at this equations here the torque generated torque is proportional to two quantities ϕ and I_a the armature current; ϕ the flux the excitation in the machine. So if we vary I_a the armature current the generated torque is going to change and for a given load if


the generated torque changes the speed is also going to change. So one could control the speed by changing I_a or one could also control the speed by changing the generated torque by changing the excitation or control in the excitation.

(Refer Slide Time: 13:10)

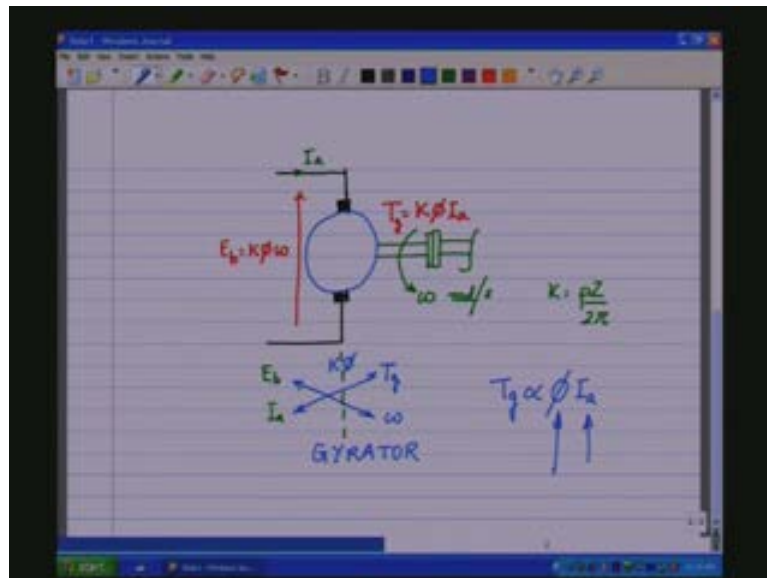


So, generated torque **generated torque which in turns** which in turn is going to affect the speed of rotation is affected by two variables main variables which is the field or excitation ϕ and the other variable is armature current I_a . So, by controlling the armature current I_a or by controlling the field or the excitation ϕ or both one can change or control the generated torque and for a given load that is going to change this speed. This means that the speed of the DC motor can be controlled by changing these two parameters by controlling these two parameters to achieve speed control.

(Refer Slide Time: 14:50)

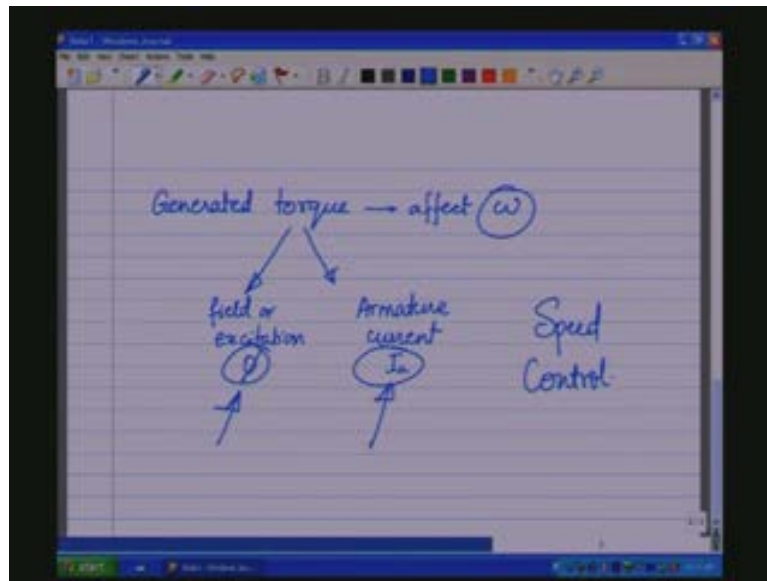

So let us get back to the equivalent circuit and see how we go about achieving speed control. So first let us do control from the armature side armature side speed control. So we have the motor, we have the brushes here (Refer Slide Time: 15:35) and the brushes are connected to the terminals of the motor, they are brought out to the terminals of the motor and we have a resistance R_a which is the equivalent resistance that we apply to the motor.


(Refer Slide Time: 16:01)

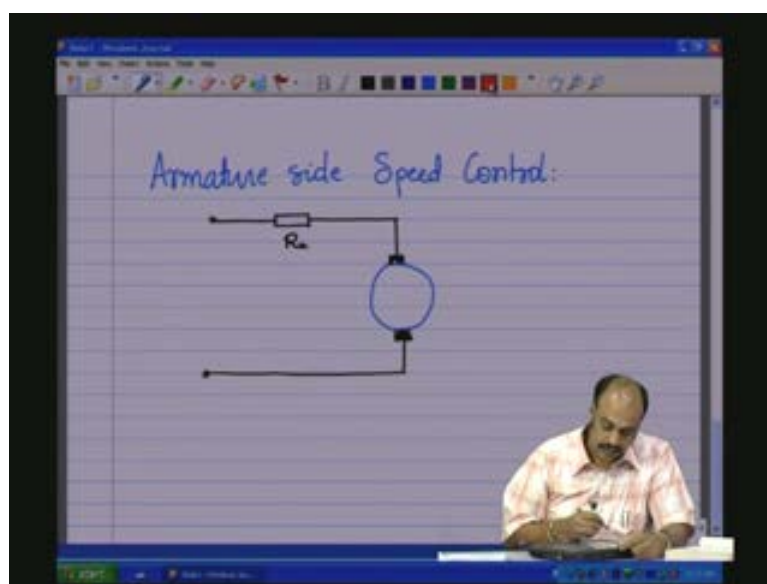

Now **this** to this motor we are applying a source E_a and this motor mechanical shaft is connected to whatever load mechanical load that one wants to connect and this has the generated torque and ω the two parameters, and on this side we are having E_b the back emf and I_a the armature current which are two corresponding variables the potential and the kinetic variables and this is the DC motor.

Now, to control the speed we need to change E_b . Of course the speed is going to affect the induced emf E_b and we saw that T_g was proportional to these two main things the main parameters ϕ and I_a . Let us first look at how we go about changing ϕ I_a .

(Refer Slide Time: 17:28)

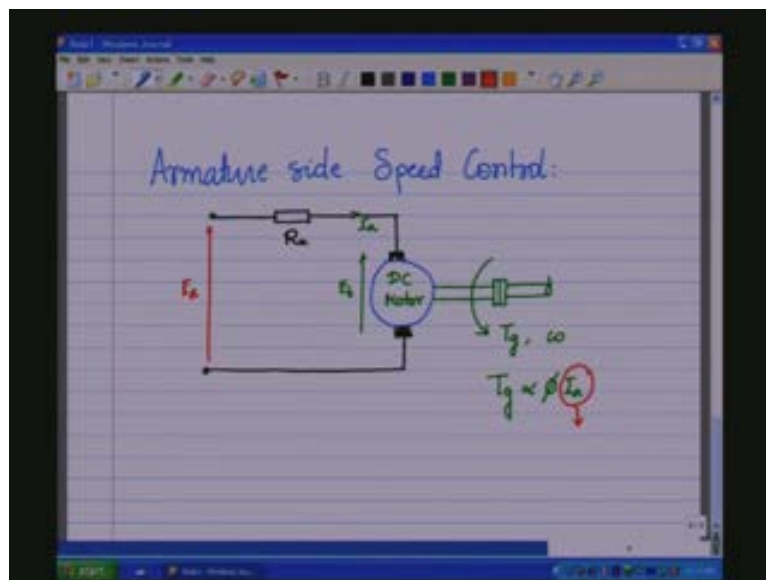


Now the armature current can be changed by either changing this or by changing I_a itself by interposing a resistance in series with R_a and making that variable as R_s that is the R_s **series**. So therefore when E_a is varied I_a is equal to E_a minus E_b by R_a R_s is still not **put** come in to the picture. Now if R_s is put then it is plus R_s .

So let us say right now R_s is equal to 0. So if R_s is equal to 0 we have this equation. Now as E_a is decreased **as E_a is decreased** what is going to happen E_b is still not decreased, I_a is going to reduce because E_a minus E_b is going to reduce and as I_a reduces T_g the generated torque is going to reduce because it is proportional to ϕI_a and all this while ϕ we are keeping constant and because the generated torque has decreased for the same load ω the

rotational speed also reduces and because the rotational speed has reduced this is going to affect E_b and E_b is going to reduce because E_b is proportional to ω so it will come and settle at the new equilibrium point or the new operating point. So this is how the sequence of parameters that will get affected if you reduce E_a .

(Refer Slide Time: 20:06)

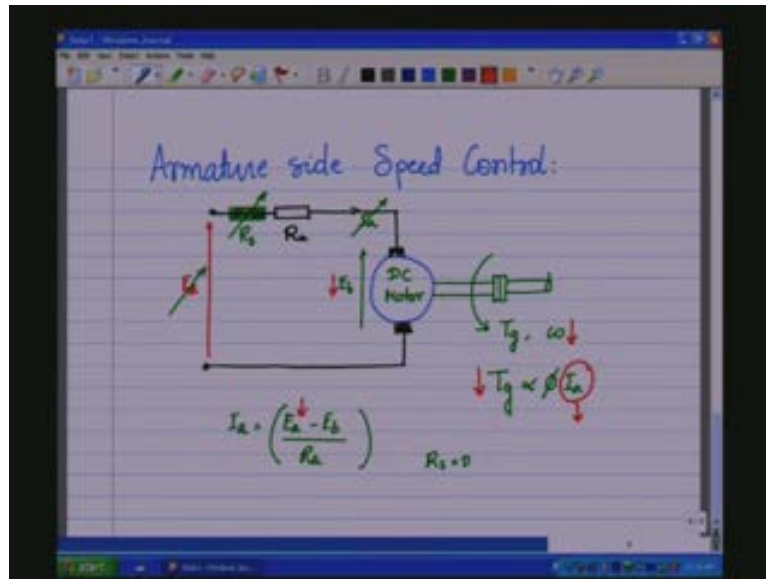

Now if E_a is not reduced E_a is just gets fixed which means we introduce a series resistance R_s . if a series resistance R_s is introduced here R_s is finite no longer zero. So E_a is fixed E_b is fixed for now we are increasing R_s , moment R_s is increased I_a is going to reduce, reduction in I_a is going to result in reduction in the torque T_g generated torque which is going to reduce the speed ω for the same load and that is going to reduce the back emf E_b and that will come and get settled in a new operating point. So now E_a minus E_b is going to get distributed between R_s and R_a by their values by the ratio of the values. So in this way the speed can be controlled by either controlling the armature voltage or by controlling the armature current by way of a series resistance or rheostat connected in series with the armature.

Now, between the two methods if you see if we introduce a series resistance the whole I_a current the armature current is going to flow through the series resistance and there is going to be a $I_a^2 R_s$ drop. So, for a power which is E_a into I_a that is going to be taken from the source and E_b into I_a that is going to be delivered to the armature $I_a^2 R_s$ and I_a


everywhere so we will use E_f so this is the field coil coming from a separate source. So this is the separately excited motor **this is a separately excited motor** just like in the case of the generator a separately excited generator case.

Now we need to apply an armature voltage E_a that is capable of being varied, a DC voltage. So to the terminals here let us connect a generator here which has its own R_a which comes from again **another machine** another similar machine but it is being operated in the generator mode, so this is a DC gen DC generator and this is a DC motor and the shaft of the generator is being driven by a prime mover and this generator also has a field coil **of course as explained before**, there could be a resistance, there could be of course a battery some other separate source so you have an R_f and an I_f which is going to generate ϕ and this is an E_f . So this is going to excite the generator this is also a separately excited generator. So the speed of the shaft or the torque supplied or the energy supplied through the mechanical domain this could be moved by a prime mover, it could be an AC motor or some other prime mover like a IC engine that is the internal combustion engine or any of those things. This prime over is going to supply the mechanical energy through the generator generates the E_g here across the generator then after the drop what you get here is E_0 , E_0 is the armature applied voltage to the motor. So here you have the motor here you have the generator so E_0 and E_a are same.

Now for this generator the load is this motor. So this A is applied to the motor and this is going to deliver again the energy back to the mechanical domain. So if we control the speed of the prime mover the generated voltage here because this is again dependent on the speed here, **if the** this is rotating at N rpm, what you are going to get here is E_g which is equal to $\frac{N \phi Z}{60}$ so N here is going to affect E_g so by changing N E_g changes, E_0 changes and therefore E_a changes which is going to change the **torque** generated torque here which is ϕI_a which is going to affect ω .


So the speed of this mechanical shaft of the motor side is controlled by controlling the speed of the mechanical shaft of the generator. This type of speed control system is called Ward - Leonard system. This is called the Ward - Leonard speed control system. This is for speed control. This is a **very rugged method of** very rugged and useful method of controlling the speed of the DC motor especially high power systems.

(Refer Slide Time: 30:45)

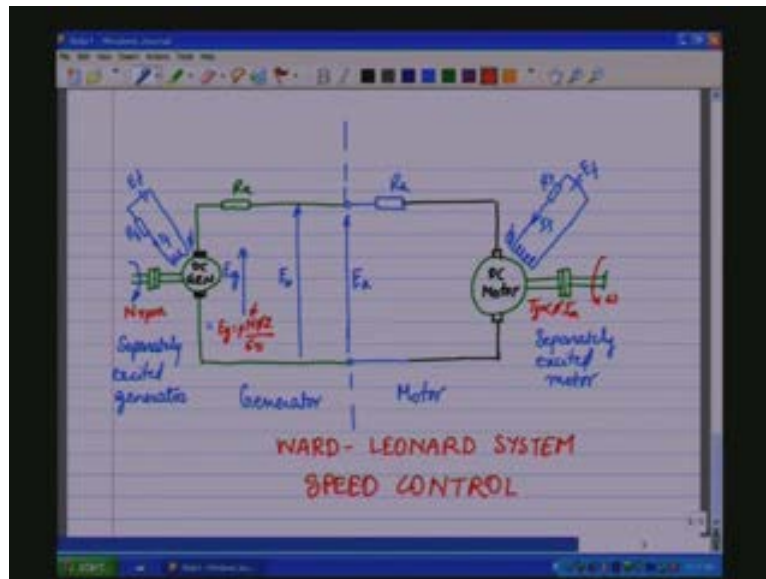

The other method that we saw that we said could affect the speed of the mechanical side and the omega is by controlling the excitation of the flux of the field because T_g is proportional to not only I_a but also to ϕ . So if we are able to change ϕ then we should be able to affect T_g and thereby the speed for a given load.

(Refer Slide Time: 31:35)

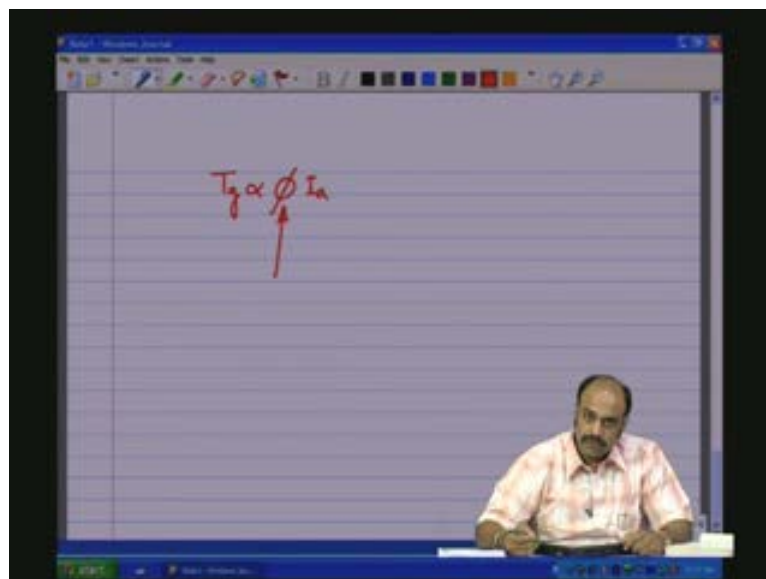


Now how do we change ϕ ?

Changing ϕ is not a difficult issue. You see that we have a circuit here which is generating the field or the excitation (Refer Slide Time: 31:49) so there is a source E_f and that E_f is passed through R_f and the current I_f or the field current is flowing through the field coils. So two possible ways of controlling I_f ; so, if we change I_f because ϕ is proportional to I_f so if we change I_f ϕ is going to change. So I_f can be changed either by adjusting this resistor or by changing this voltage value of this voltage source. Both these will change ϕ which will lead to change in T_g which will go which will affect the speed of the motor. But the manner in which we are going to change ϕ is going to depend also on the way the motor is going to be excited and the motor is excited in the following ways.

Generally we have three main categories for the motor for excitation motor field excitation. So, first method is called the shunt motor. So the name shunt motor is got from the fact that its field is excitation by having the field coil connected in shunt or across the motor terminals. The series motor the series motor is a motor wherein the field coil is connected in series with the armature winding and thereby the armature current flows through the field and third is the compound motor. So in the case of the compound motor as the name suggests it is a mix of both, you have two sets of coils: the shunt coil and the series coil; the shunt coil is connected across the motor armature, the series coil is connected in series with the motor armature. So that is the compound motor and these are the three main types of motor that you would come across, general categories.


(Refer Slide Time: 38:53)

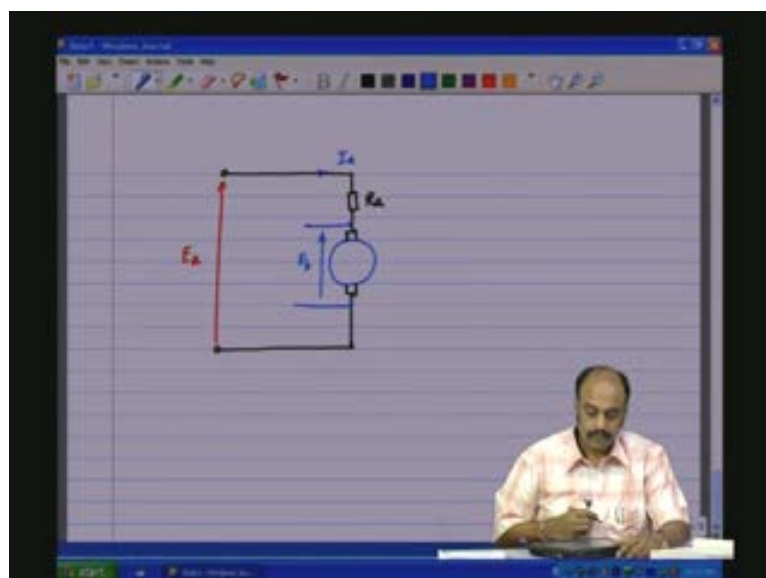

So the field current is generally is very small compared to I_a ; I_f is very small compared to I_a and therefore the field coil can be rated for a lower current and therefore the gauge of it that is the thickness of the field wire will be very small in general compared to the armature winding thickness. By varying R_f that is by making R_f variable the field current can be controlled and therefore I_f can be controlled or the flux can be controlled as a consequence and therefore the T_g can be controlled.

So, in the case of let us say a constant **let me** constant field motor **let us select this, copy, paste** (Refer Slide Time: 40:14). So in the case of a constant field application, ϕ is a constant then T_g becomes proportional to only I_a . So therefore as a result as T_g is proportional to only I_a the torque varies linearly with a load. So let us have a graph of torque versus I_a and let us say torque, so the torque would vary linearly with the load so this is T_g versus I_a this would give you the load characteristic.

(Refer Slide Time: 41:33)

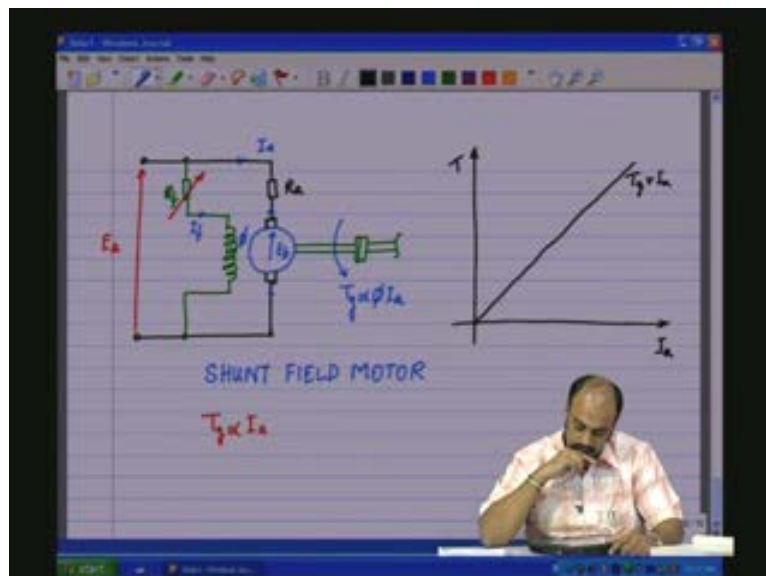


Now if we look at the **shunt motor curve with respect to the** torque with respect to the speed what happens?

Now $T_g \times \omega$ into the omega will be the power; T_g into omega is the power. Now let us say we want to the keep the power constant **power constant**. So, when the power is constant then T_g is inversely proportional to omega that is T_g is proportional to $1/\omega$. So with speed, so if we have speed as one of the axis then T with respect to speed is going to


decrease, T is inversely proportional to..... so T versus ω . So as ω increases torque is decreasing. So this is T_g generated and let us say this is T_g which is load dependent the T_g value which is load dependent or the torque value which is load dependent therefore we will say this is the load line, this is the load, this is the generated torque by virtue of its rotation and therefore this is the operating point **operating point**.

(Refer Slide Time: 43:29)

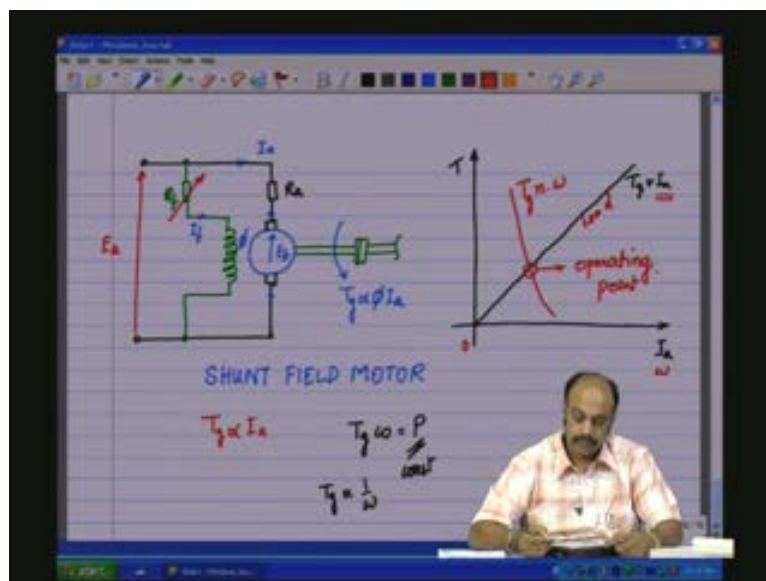


And because the power is constant meaning we are at let us say the maximum power p_{max} let it be constant and let us say P_{max} then this would indicate maximum or rated load this particular operating point. So the torque at rated load and at rated speed or the nominal speed so that would be your I_a rated, ω rated in radians per second.

(Refer Slide Time: 44:20)

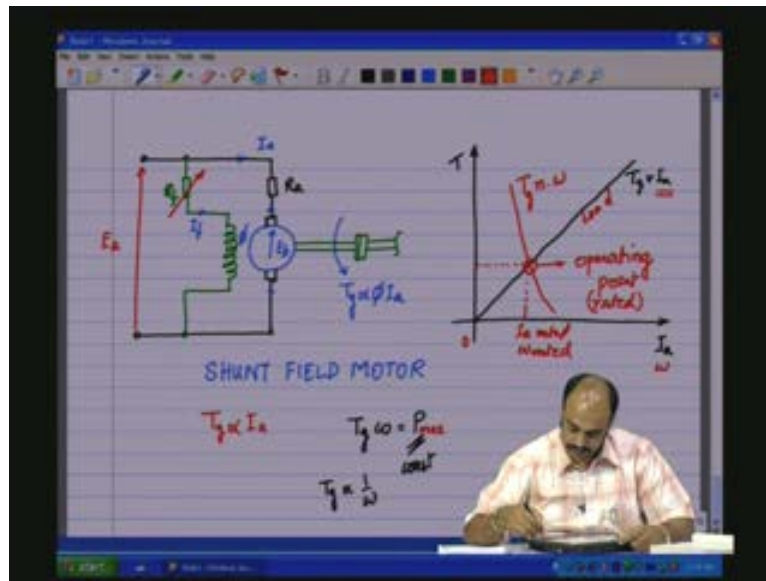

On other hand, what if we are not keeping power constant. So let me draw a graph with respect to the speed ω in radians per second, this is the torque so this is in Newton meter. Now let us say **let us say** I keep on increasing the voltage. As the voltage is being increased the voltage will keep on increasing as shown let us say up to a certain point. So this is the..... beyond that the voltage cannot increase because we would have reached the rated value for the voltage for the machine E_a rated. So this is the E_a curve this is E_a with respect to speed.

(Refer Slide Time: 45:50)

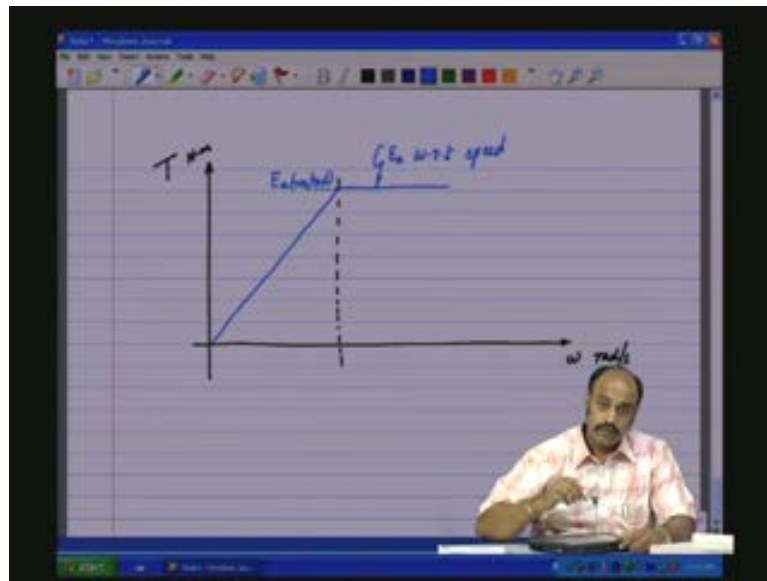


Now let us for the moment take R_a equal to 0 so which means E_a is same as E_b . So this is actual the back emf also because we are saying R_a this is the back emf E_b because R_a is equal to 0. Beyond a particular speed the back emf has reached the same value as rated voltage we cannot apply a voltage more than the rated voltage otherwise the machine will saturate so it has to get clamped at this beyond a particular value of the speed. Now what is happening to the power the power that is delivered to the armature is $E_b I_a$ or $V_a I_a$ because R_a is equal to 0 so the power curve is $E_b I_a$ which is the power which is put into the armature.

Now as E_b is 0 the power here is going to zero and that is going to increase. So let us say the power curve increases in some fashion up to this point. So at this point this is the power curve P in watts. Now at this point torque rated has been reached, ω that is the speed rated or the nominal has been reached whatever is given in the name plate and I_a is also rated beyond let us say we want to still increase the speed, what happens?

E_a cannot increase any further, speed only can change and how can you increase the speed by keeping E_a constant by decreasing flux only because T_g is proportional to flux into I_a , we are not going to change anything in the armature side because armature voltage now reaches its maximum constant so only other parameter to control is ϕ and ϕ you cannot increase more because already the voltage is in the maximum any increase in the voltage will


saturate so therefore you have to only decrease the flux so we decrease the flux so which means T_g starts reducing. So you can still go beyond the rated speed by reducing the torque. So the torque will start reducing in this zone and the maximum that can be available is T_g is $P_{\text{maximum}} / \omega$.

(Refer Slide Time: 49:24)

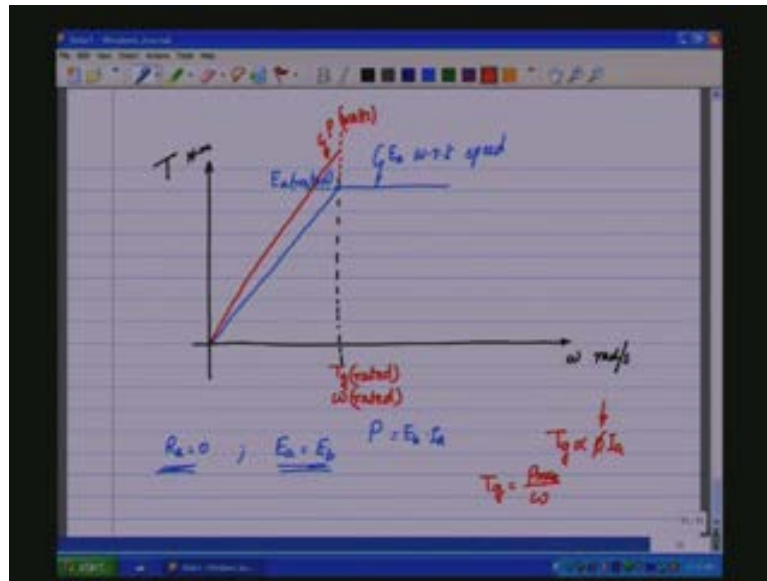

So if you say P_{maximum} is constant for the machine then T_g is inversely proportional to ω . So if I am having the T_g curve so let us say this is $T_g \text{ max}$ so that will start going proportional to $1/\omega$ as ω is increasing. But in this region you could achieve a constant torque up to maximum by changing these two. So there is possibility of obtaining a constant torque here because the speed is less than the rated and as the speed is less than the rated I_a can take a lesser value and therefore for any load one could achieve a constant operating point below the rated. But beyond the rated there is upper limit for the torque **which will take** which will have a proportionality of $1/\omega$. So this would be the achievable maximum torque curve the green line as I am showing here with respect to ω .


(Refer Slide Time: 50:47)

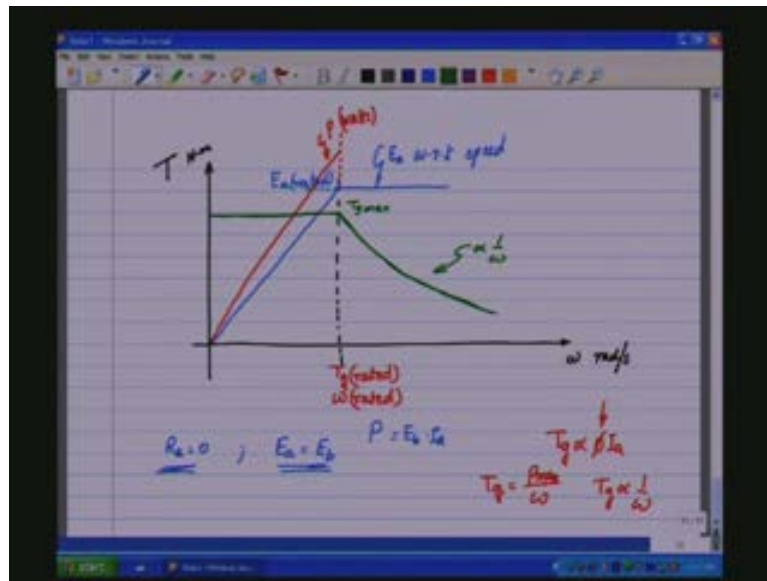

Now in the case of the series motor what happens?


So, in the case of the series motor we have let us say the same machine, we have the brush and I have the armature resistance R_a as shown here across these terminals. This is the brush and this is the DC motor, this is R_a and this is brought out to the terminals here and there is a back emf E_b across the brushes, there is also an applied voltage E_a across the armature and there is a current I_a through the armature windings, there is now a field winding.

(Refer Slide Time: 52:13)

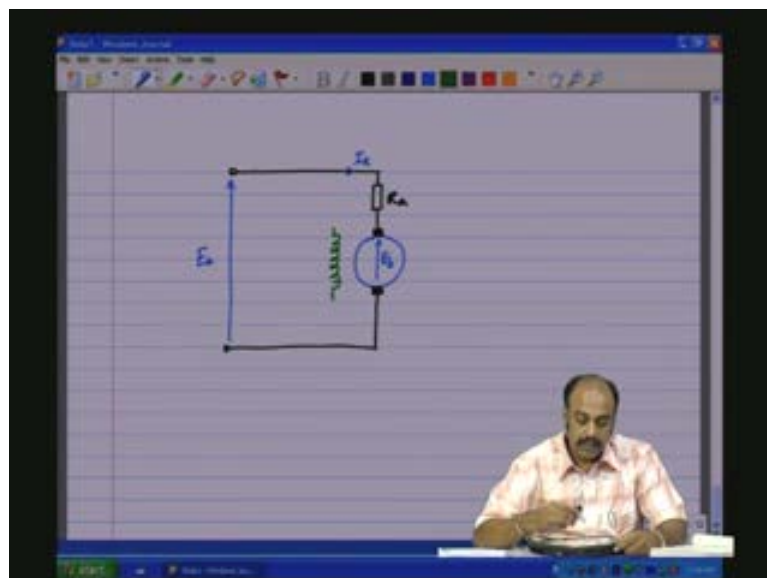

Now this field winding is not going to be connected directly across the terminals but it is going to be brought out here and connected in series with the armature. So what we do we make a cut here and then connect it like..... so which means the I_a flows through the field coil to produce also the flux and also the load and then what happens to the torque and the mechanical side; the torque on the mechanical side that is generated we know it is proportional to the flux into I_a but the flux is proportional to the field current but the field current is same as I_a so flux is proportional to I_a and therefore T_g is proportional to I_a square in the series motor.

(Refer Slide Time: 53:36)

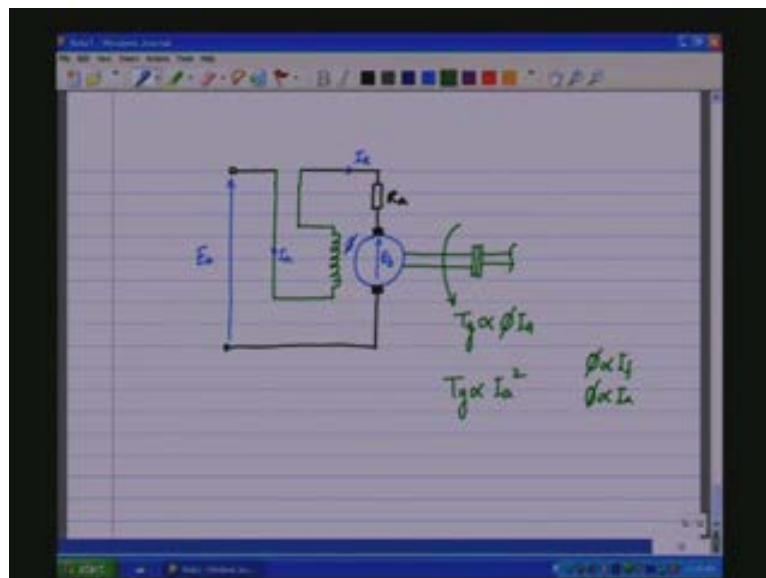


So in the case of the series motor we have the flux which is proportional to I_a and therefore the generated torque T_g is proportional to I_a square. So therefore if we look at if we look at the load torque characteristics with respect to I_a we see that this starts having a hyperbolic; T_g versus I_a in the case of series motor. Now let us see E_b . Now E_b is also proportional to ϕI_a sorry is proportional to $\phi \omega \phi$ into ω or E_b is proportional to I_a into ω because the flux is also proportional to.....

Now E_b into I_a is the power E_b into I_a is the power and therefore the power is proportional to I_a square ω . And let us say we want to keep the power constant, then then I_a square ω will be a constant. Of course I_a square is T_g proportionality is there in the factor and it is proportional to the torque is proportional to $1/\sqrt{\omega}$; in the case of T_g is


proportional to I_a^2 and $1/\omega$ but T_g is already I_a^2 and therefore the armature current of the load current will be proportional to $1/\sqrt{\omega}$ in the case of in the case of the series motor whereas in the case of the shunt motor I_a is proportional to $1/\omega$.

(Refer Slide Time: 57:10)

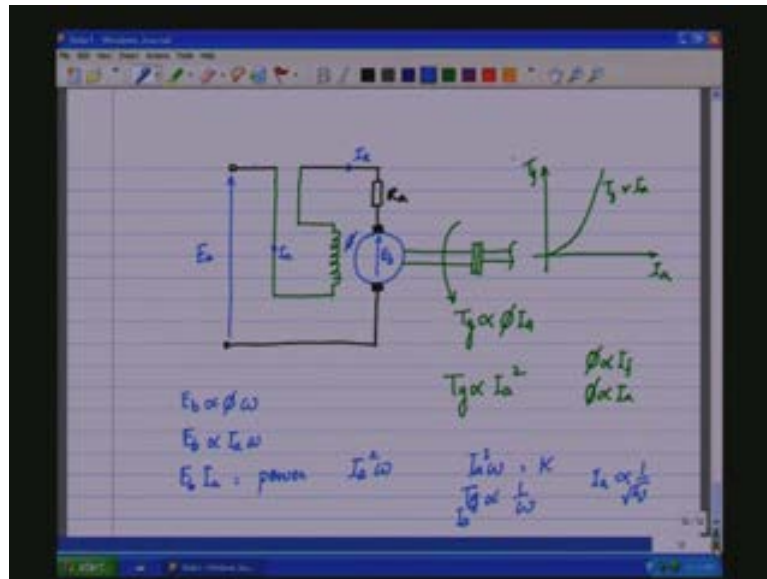

Now if we take this equation E_b which is equal to $p N \phi Z$ by 60 or $p Z$ by 2π into $\phi \omega$ where this is in rpm, this is in radians per second and this is K which we have defined so which is equal to $K \phi \omega$.

(Refer Slide Time: 58:05)

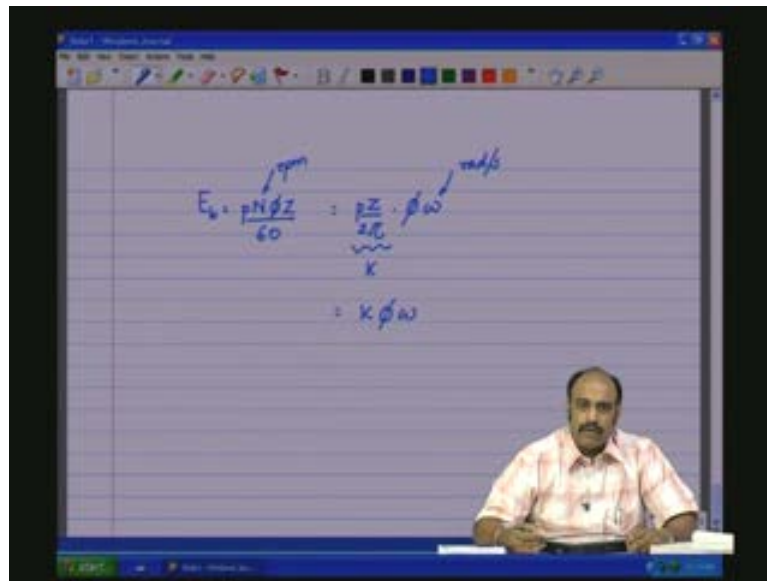

Now let us say in the case of the shunt motor. So in the case of the shunt motor let us say this is given by the applied voltage **which is per** therefore it is connected across the terminals and therefore it is not zero phi is not zero and E b is proportional to omega when omega is equal to 0 the induced emf is 0.

If the flux is brought to zero what happens?

Now E b is let us say approximately equal to E a and let us say for the moment for the discussion R a is equal to 0 then E b equals E a which is proportional to phi into omega. Now this if we keep it constant it is a constant DC source which is applied externally if you reduce the flux the field is going to increase so that the product is a constant. So, if this is suddenly made zero that is the shunt field winding coil is made suddenly zero then under no load conditions the speed here can increase phenomenally high and it may break away and damage the machine. But in the case of **but in the case of** the series motor when the field coil is broken I a is also 0 because I a is 0..... because this is proportional to I a and omega is also proportional to..... because we saw that omega is also a function of I a I a is proportional to 1 by root omega or omega is proportional to I a square. So when I a is made zero both the speed also will become zero because that is a function of speed and the motor does not run away whereas in the case of the shunt motor there is a possibility of running away. We will stop here and continue our discussion in the next session.