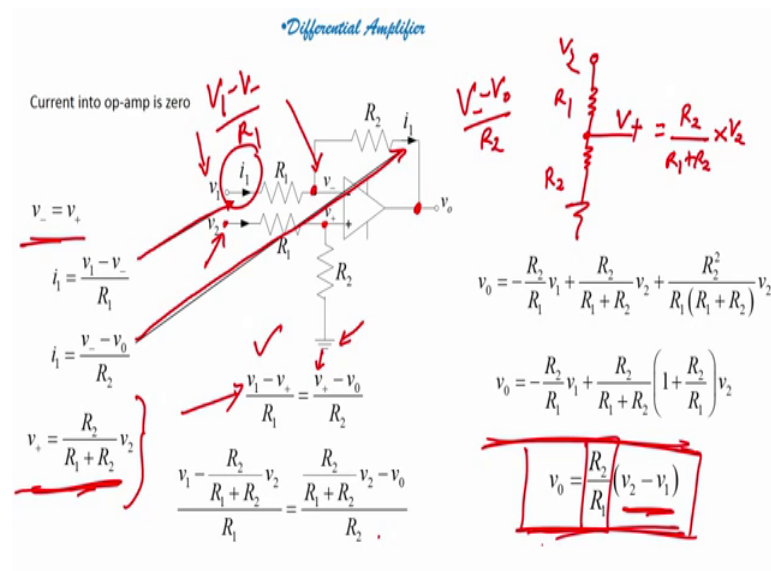


Integrated Circuits, MOSFETs, OP-Amps and their Applications
Prof. Hardik J Pandya
Department of Electronic Systems Engineering
Indian Institute of Science, Bangalore

Lecture – 21
Applications of Operational Amplifier: Differential Amplifier

Welcome to this module. And here today we will see what exactly is a differential amplifier. So, we have seen the opamp as an inverting, we have seen opamp as a non-inverting, and we have seen opamp as a summing amplifier. So, let us see how the operation amplifier can be used as a differential amplifier all right.

(Refer Slide Time: 00:40)



So, if you come back to the screen, so if I have a opamp in the following configuration, in the following schematic or following circuit, then what I see is I am applying input to the inverting as well as non-inverting amplifier correct applying input to the inverting as well as non-inverting terminal of the amplifier. I have values R 1 R 2 right. In this particular configuration, how can I find my output voltage v o. First case is how first I have to find the output voltage v o, the relation between the R 2, R 1, v 1, v 2 with respect to v o.

So, you see these points one is v minus, another one is v plus; one is v minus, another one is v plus. Now what can I see v minus equals to v plus, how, because current into the opamp is 0 or because of the virtual ground concept, v 1 equal to v 2 or v minus equals to


v_1 minus v_2 plus. So, i_1 would be so this one first we are considering this value which is i_1 then we will consider the value which is right over here i_1 . So, this value is nothing but what will be v_1 minus v_2 minus, so v_1 minus v_2 minus divided by R_1 correct.

And if I consider this value then it will be nothing but v_2 minus right because here you can see here and you have to see here, so it will be v_2 minus minus v_0 by R_2 minus v_0 by R_2 . So, what is my v_2 plus, my v_2 plus here, now if I want to measure this value v_2 plus right. What is v_2 plus v_2 plus will be so you see here v_2 plus you have to consider this ground, you have voltage here. So, this is like a potential divider. So, v_2 plus will be R_2 divided by R_1 plus R_2 into v_2 correct, because you see here v_2 and here is a ground. So, it looks like we are measuring we have v_2 , we have R_1 , we have R_2 , and we are measuring the v_2 plus correct. So, v_2 plus would be nothing but R_2 by R_1 plus R_2 , v_2 plus would be nothing but R_2 divided by R_1 plus R_2 into v_2 right.

Now, I know that v_2 plus right because v_1 minus equals to v_2 plus. So, I will also put my value i_1 equals to these both values. So, v_1 minus v_2 minus by R_1 equals to v_2 plus minus v_0 by R_2 correct, this is the value. Now, if I substitute the value of v_2 plus, if I substitute the value of v_2 plus in this equation, what will I write v_1 minus this value divided by R_1 equals to R_2 divided by this whole value again we are substituting here in this place right.

So, if I solve further what will I have, when I solve the complete equation, I will find that my v_0 equals to minus R_2 by R_1 v_1 plus R_2 by R_1 plus R_2 into v_2 plus R_2 by R_1 into v_2 . Or further I solve it then my output voltage will be nothing but R_2 by R_1 into v_2 minus v_1 correct. When you solve it, further you will get nothing but R_2 by R_1 into v_2 minus v_1 . So, what is it doing, it is the differential amplifier, it is amplifying, it is amplifying the difference of voltage at the output. And what is the amplification factor, amplification is done by values of R_1 and R_2 . Amplification is done by substituting the values of or selecting the values of R_1 and R_2 . What is R_1 and R_2 , R_1 and R_2 are my feedback registers, R_1 and R_2 are nothing but my feedback registers. You got it?

(Refer Slide Time: 05:28)

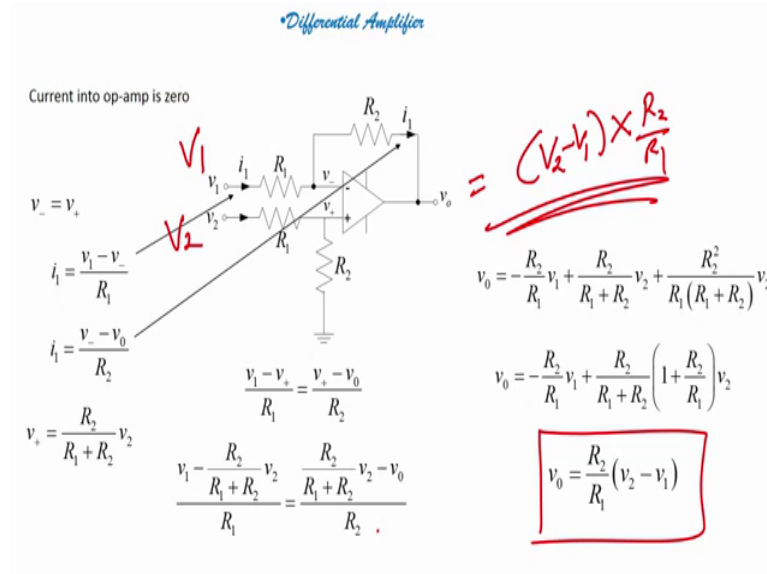

So, this is how my differential amplifier will work that whenever I apply a voltage at both the terminals voltage v_1 and here, v_2 at the another terminal, my output voltage would be nothing but difference of the voltage into R_2 by R_1 . This is the formula that I have to remember. And this will be my differential amplifier, this will be my differential amplifier.

(Refer Slide Time: 05:53)

Example: Differential Amplifier

For the Differential Amplifier configuration shown it is given that $R_1 = R_3 = 10 \text{ k}\Omega$ and $R_2 = R_F = 20 \text{ k}\Omega$. Solve for the output voltage, the input resistance to the v_{I1} terminal, and the input resistance to the v_{I2} terminal for the three cases: $v_{I1} = 0$, $v_{I1} = -v_{I2}$

Solution


Because $R_F/R_3 = R_2/R_1$, the output voltage is given by

$$v_O = \frac{R_F}{R_3} (v_{I1} - v_{I2})$$

$$v_O = \frac{R_F}{R_3} (v_{I1} - v_{I2})$$

Therefore, $v_O = 2(v_{I1} - v_{I2})$

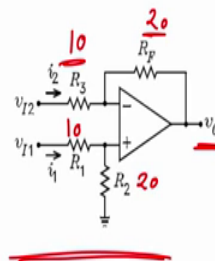As $R_F = 20 \text{ k}\Omega$ and $R_3 = 10 \text{ k}\Omega$



So, let us solve an example, let us solve an example. So, for the differential amplifier configuration shown here; it is given that R_1 equals to R_3 equals to 10 kilo ohms. So,

this is 10, this is 10. R_2 equals to R_f equals to 20; this is 20; this is 20. Solve for the output voltage we have to find v_o right the input voltage v_1 terminal and input resistance to v_1 terminal for three cases v_1 equals to 0 and v_1 equals to minus V_{I2} right. So, let us see one by one. Now, because R_f by R_3 equals to R_2 by R_1 , the output voltage is given by it is very easy right v_o equals to R_f by R_3 into this one V_{I1} minus V_{I2} right. If I substitute the value 20 divided by 10 equals to 2, so 2 times V_{I1} minus V_{I2} . So, as R_f equals to 20 kilo ohm and R_3 equals to 10 kilo ohm, input resistance to terminals V_{I1} and V_{I2} varies as shown here, you can show this here right.

(Refer Slide Time: 07:07)

Example: Differential Amplifier

For the Differential Amplifier configuration shown it is given that $R_1 = R_3 = 10 \text{ k}\Omega$ and $R_2 = R_f = 20 \text{ k}\Omega$. Solve for the output voltage, the input resistance to the v_{I1} terminal, and the input resistance to the v_{I2} terminal for the three cases: $v_{I1} = 0$, $v_{I1} = -v_{I2}$

Solution Contd.

The input resistances to the two terminals v_{I1} , v_{I2} varies as shown in figure aside.

Therefore, input resistance to v_{I1} terminal is $R_1 + R_2 = 30 \text{ k}\Omega$

Input resistance to v_{I2} terminal when $v_{I1} = -v_{I2}$ is

Applying KVL,

$$(v_{I2} + v_{I2}(R_2)/(R_1 + R_2))/i_2 = R_3$$

$$v_{I2}(R_1 + 2R_2)/(R_1 + R_2)/i_2 = R_3 \Rightarrow v_{I2}/i_2 = R_3(R_1 + R_2)/(R_1 + 2R_2)$$

Therefore input resistance into terminal 2, after substituting values is $6 \text{ k}\Omega$




So, what will happen therefore, input resistance to V_{i1} terminal one is nothing but R_1 plus R_2 right. If you see this circuit, what we will find that the input resistance to terminal V_{i1} will be nothing but R_1 plus R_2 right. What is R_1 , R_1 is 10, R_2 is 20, so it is 30 kilo ohm. Input resistance to V_{i2} , when V_{i1} equals to minus V_{i2} will be if we apply the Kirchhoff's voltage law then you will find that V_{i1} V_{i2} plus V_{i2} into R_2 divided by R_1 plus R_2 divided by R_2 equals to R_3 . If we see this circuit, you have to see this circuit, we will find this, how we are solving. Also V_{i2} , so when you further solve it what do you get V_{i2} by i_2 equals to this particular value.

So, therefore, the input resistance into terminal two after substituting the value, so if I this is nothing but my input resistance of the terminal two right V_{i2} by i_2 is nothing but input resistance to the terminal two right whatever the input resistance is. So, substituted

if we substitute the values what will I have 6 kilo ohm, I have value of 6 kilo ohm right. So, this is how we can solve the problem for the differential amplifier. Now, understand that I am little bit getting faster in solving the things, I am little bit speeding up my lectures, the reason is that you have to also try to understand how to go in a frequency with the teacher all right. This is another skill that as a student, as a listener, we should develop that if the speed is increased our capability of understanding the problem should also increase and that can increase only when we are clear with the earlier lectures all right.

So, when I talk suddenly about virtual ground, you do not have to go back and see what is virtual ground right, because you have already seen and you have already know what exactly virtual ground is. Similarly, when I talk about inverting, non-inverting amplifier, immediately you should be able to say there was the case there is a equation; a differential amplifier v_o is nothing but minus R_f by R_1 into V_2 minus V_1 or R_f by R_1 into V_2 minus V_1 . Now, if I talk about solving the in differential amplifier this is how you can solve the differential amplifier. So, we have taken two problems in which we have solved the differential amplifier right.

(Refer Slide Time: 09:54)

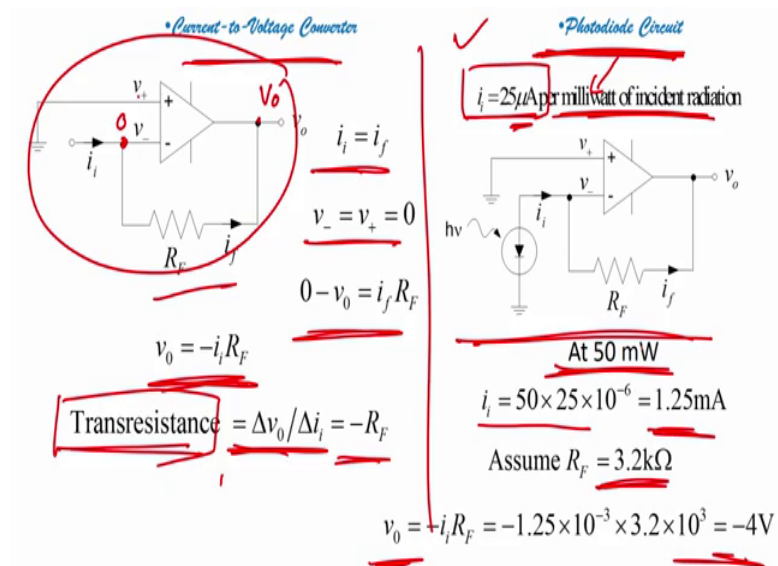

Now, if I want to show you problem where there is a current to voltage converter. So, if you come in the screen, there is a current to voltage converter. What do you see here is the first circuit right. And here if I want to understand then what is it if would be equals

to i_1 right. So, another way is v_1 and v_1 plus equals to v_0 minus equals to 0 that is also true right. So, if I substitute the value and $0 - v_0$, $0 - v_0$ is nothing but minus $i_1 R_f$ because v_1 is what $-v_0$, and here is v_0 . So, $0 - v_0$ is nothing but $i_1 R_f$. So, v_0 equals to minus $i_1 R_f$. The trans resistance is nothing but Δv_0 by Δi_1 is minus R_f .

So, now let us see this particular circuit. Let us see this particular circuit. Now, I am not going to teach you what is transconductance trans resistance that you have to understand how trans resistance can what is how it is defined, and how we have written Δv_0 by Δi_1 right. So, understand what is trans resistance, ok guys, understand something, try to learn by yourself as well.

Now, v_0 equals to minus $i_1 R_f$ correct. So, this is value of output voltage given a circuit to you. Now, let us consider this particular circuit, which is our photodiode circuit. So, if you are given a photodiode, how can you measure the output, how can you measure the output. So, this is a photodiode as you can see. And what is that i_1 is 25 microampere per milliwatt of incident radiation, this much is the current that we can generate. So, at 50 milliwatt, at 50 millivolts, what is the power, what is the current. 50 milliwatt, it will be $50 \times 25 \times 10^{-6}$, because this is microampere 1.25 milliamperere.

Now, if I assume that R_f equals to 3.2 kilo ohm, then my output voltage v_0 would be minus 4 volts, then my output voltage v_0 would be minus 4 volts all right. So, again if I am given a photodiode circuit as shown in figure, and if I am told that i_1 equals to 25 microampere that is the amount of current that the photodiode generates per milliwatt of incident radiation. And at 50 milliwatt, what should be the final voltage a 50 milliwatt, what should be the final voltage, then I had to use this formula that i_1 equals to $50 \times 25 \times 10^{-6}$ will be 1.25 milliamperere. And then I have to assume the value of R_f , assuming the value of R_f to be close to 3.2, I will have output voltage equals to minus 4 volts. So, this is how your current to voltage converter works, and photodiode circuit is an example of current to voltage converter. And we have also seen how the differential amplifier works right. So, this is all about this particular module.

In the next module, let us see the application of an integrator. And then in another module, we will see application of an differentiator. Again you see I am breaking this

module into small modules or breaking the lecture into small modules, so that you can understand the concept, read it, solve the problems get more problems and solve by yourself all right. And also see how what is the application of this amplifiers all right. So, that is why the time I am squeezing down in 20, 25, 30, half an hour whatever the lectures I can bring it to whatever modules I can bring it to so that you have enough time to understand, and then digest and then solve more. And if you have an query you can ask, if you have an query feel free to ask.

So, in the next module, we will see the integrator, till then you learn about this thing; understand what I have taught right, understand how the current to voltage converter works and at solve few more examples by yourself all right.

Till then you take care, I will see you in the next module, bye.