

**Oil Hydraulics and Pneumatics**  
**Prof. Somashekhar S**  
**Department of Mechanical Engineering**  
**Indian Institute of Technology, Madras**


**Pneumatic Circuits: Design and Analysis of Multiple Actuators**  
**Lecture - 78**

**Part 02: Power circuit, Signal conflicts, 3/2 idle-return rollers, Cascade method –  
design and operating principles, Power supply positions in 2 group, 3 group and 4  
group circuits**

(Refer Slide Time: 00:23)

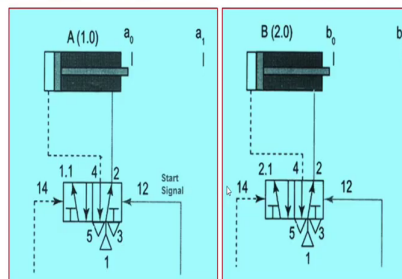**Power Circuit**

- Draw the Power Circuit with the → Cylinders, Final control elements-DCV, and Sensors for end position of cylinders
- Consider Cylinder A(1.0) and Cylinder B (2.0)
- Automatic Operations → is achieved through the sensor positions as →  $a_0$ ,  $a_1$  for Cylinder A and  $b_0$ ,  $b_1$  for Cylinder B
- TWO 5/2-way Double-pilot DCV - 1.1 and 2.1 is used to control Cylinder A and Cylinder. B Exactly below the Cylinder A and Cylinder B as shown in Figure below:



My name is Somashekhar, course faculty for this course. Now, come back to the problem of stamping operation a plus b plus b minus a minus to stamp the workpiece come back to this. The first and foremost thing is we have to represent the task in the power circuit, first while building the pneumatic circuits.

Draw the power circuit with the cylinders final control elements DCV, and sensors for end positions of the cylinders. Has already know it we are two cylinders, we are using A 1.0, B 2.0. Automatic operations is achieved through the sensor positions as a 0, a 1 for the cylinder A a 0 for the retracted position a 1 for the extended position.


Similarly, b 0 and b 1 for the cylinder B. Then, we are using the two 5 by 2 double pilot DCV, we can name it as 1.1 and 2.1 is used to control the cylinder A and cylinder B. But, remember exactly below the cylinder A and cylinder B, you have to place as shown in the figure below here. You will see here friends a cylinder A 1.0 initial position a 0 extended position a 1.

Similarly, B b 0, b 1 exactly below this 1 I am using the 5 by 2 DCV 1.1 exactly below this 1.1, here 2 is there know 2.0 that is why 2.1 is 5 by 2 DCV 1.4 and 1.2 are the signals 1.4 and 1.2 are the signals, this is known as a power circuit. Power circuit is main cylinders beneath this the main control valves 5 by 2 DCV adding this. And, then mentioning the sensor positions of each cylinders.

(Refer Slide Time: 02:59)
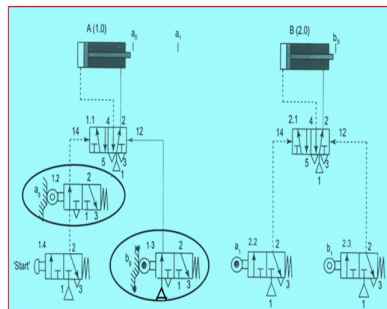
### Complete the Control Circuit → A+ B+ B- A-

- Complete the Control Circuits → by adding Various Valve to the power circuit
  - Make sure that the circuit has at least one start push-button for complete control
- Initially sensors  $a_0$  and  $b_0$  are shown in the actuated position as because the two cylinders are in complete retracted position



- For proper functioning of an entire loop
  - ✓ Identify the presence of Signal Conflicts after pressing the push-button of 3/2 DCV at Cylinder A
  - ✓ If present → remove by some means



Now, complete the control task A plus B plus B minus A minus you already know that how to do this, complete the control circuits by adding the various valves to the power circuits. Make sure that the circuit has at least one start push button, as I have told you now remember this for complete control.

When you will press this stop no energy to any cylinder, when we will press this energy starts moving. One control valve is very very important in the any circuits; initially sensors  $a_0$ ,  $b_0$  are shown in the actuated position. As because the two cylinders are in complete retracted position as I have told, you always retracted position is  $a_0$ ,  $b_0$  should be there. That is why, what I am doing is I am doing here a  $a_0$  position I am making to monitor starting here.

Then,  $b_0$  position you have to sense it please remember friends here, beneath the main 5 by 2 control valve 3 by 2 a valve I am using for controlling the this actuation 14 3 by 2 a valve it

is. But, as I have told you it will always starts with the a 0 and b 0 that is why I am making this position a 0, b 0 please remember. This is I am taking 1.2 1.3 one main control valve is required that is 1.4 again; it is a 3 by 2 a valve.


When, we will push this all the things will start otherwise it is stopped. Always you will remember, always you have to draw it in the retracted position retracted position you will see always. But, this purposely I am doing a 0 and b 0 like this a 0 and b 0, let us we will see now.

For proper functioning of the entire loop, identify the presence of signal conflicts after pressing the push button 3 by 2 a of DCV, this is 1.4. After pressing this one only we will come to know that, because of both cylinders are in the null position. Now, if present remove by some means, otherwise this valve 5 by 2 a valve will not switch over if signal conflicts will occur. If signal conflict is both appeared at the same time, let us will see now here.


(Refer Slide Time: 06:20)
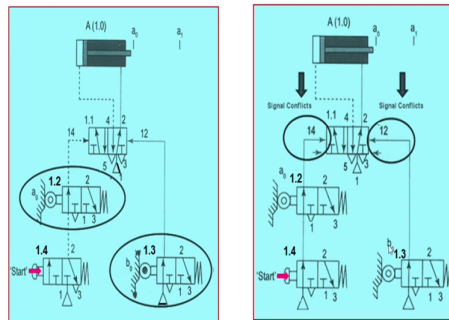
### Complete the Control Circuit → A+ B+ B- A-

- Let us start - when we press the push-button of 3/2 DCV of Cylinder A (1.4) and observe the signal flow at valve 1.1 (pilot-operated valve) through port 14 and port 12



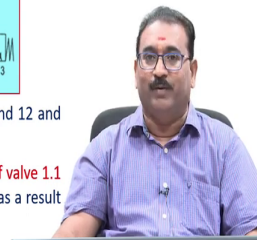- So we have observed the presence of two pilot signals at valve 1.1 → 14 and 12 and hence it is unable to switch over
- The reason for this signal conflict is → the persistence of signal at Port 12 of valve 1.1 because of continuous monitoring of  $b_0$  (retracted position of cylinder B) → as a result of continuous actuation of sensor  $b_0$  at Cylinder B




Let us start when we press the push button of 3 by 2 DCV of a one point this is 1.4 correct. If we will press this observe the signal flow at 1.1 through the port 14 and 12 what is there. See now here when you will press this, what happen energy will pass through this, but we will see now. But, previously we made the  $b_0$  is to monitor continuously I am given this position for the cylinder A correct.

Now, we will see signal is appearing here and appearing here continuous monitoring, meaning valve will not switch over signal conflicts occur because of continuous monitoring of  $b_0$  here,  $b_0$  means cylinder B should be in the retracted position that is a main problem here now what I did, we will see this how to do it, but understand this now. So, we have observed the presence of two pilot signals at valve 1.1 14 and 12.

And, hence it is unable to switch over what we will do now? The reason for this signal conflict is as I have told you, the persistence of signal at port 12 of valve 1.1, because of the continuous monitoring of b 0. As a result of continuous actuation of b 0 at cylinder B both signals are there, then what to do somehow how you have to release this, how to do I will teach you do not need to worry now.

(Refer Slide Time: 08:31)

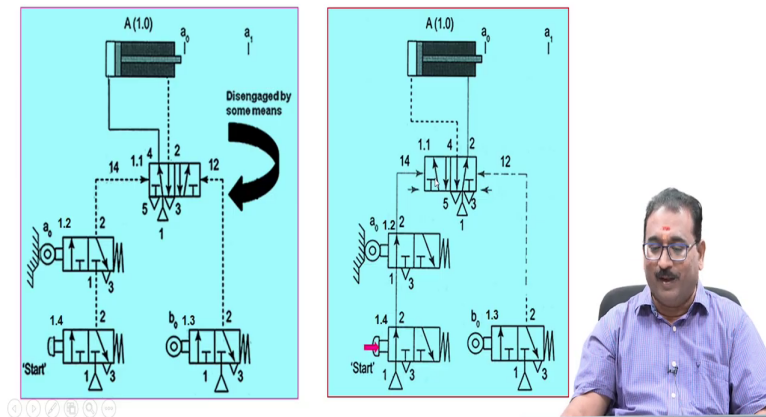- If sensor  $b_0$  can be **disengaged** 'somehow' - later we discuss how to disengage with different methods. Now we will assume we disengaged signal 12. Now the circuit looks like ...
- Now let us start from the beginning - when we press the push-button of 3/2 DCV of Cylinder A ( 1.4) then observe the signal flow at valve 1.1 through ports 14 and 12 as follows...




Now, we will see if sensor  $b_0$  can be disengaged somehow later, but it is required mandatory  $b_0$  should be there, then only  $a$  will extend then  $b$  extend it is require, but you have to disengage now. That is why I am writing here, if sensor  $b_0$  can be disengaged somehow later we discuss how to disengage with different methods. Now, we will assume that I disengaged signal 12.

Now, circuit looks like this I disengaged. How to do it what is a mechanism? I will tell you, but now we will assume it if there is no signal here. Now, we will see friends what happens? Now, correct it is no signals, if we will press this signal. Now, let us start from the beginning when we press the push button of 3 by 2 DCV of cylinder the 1.4, then observe the signals always at the 5 by 2 a 1.


Now, we will see energy will come here it will come, but here no signal we disengaged by somehow, I will teach you how now what happens automatically. It will switch over it will energy will come to this position left position, then what happens cylinder will a will start moving.

(Refer Slide Time: 10:00)

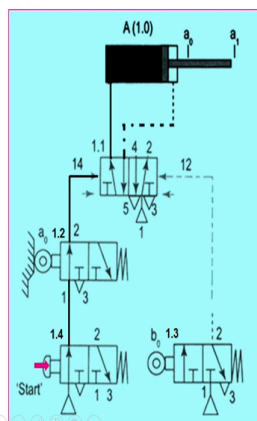➤ Now the Cylinder A can extend (A+) without any difficulty and circuit looks like this....



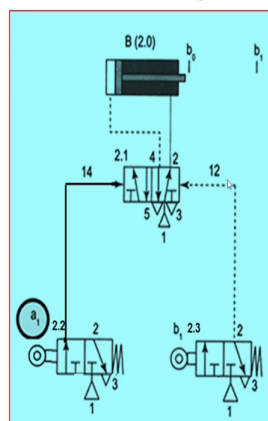➤ As Cylinder A extends (A+) → sensor  $a_1$  actuates, which in turn actuates 3/2 DCV provided at Cylinder B circuit (2.2). So that it sends the pilot signal 14 to valve 2.1 to actuates as shown in Figure below




Now, we will see this now the cylinder now see here when it will come automatically, it will energy will come to the head side. The cylinder A is extending as soon as it will reaches the a

1 sensor will actuated correct. Now, we will see as cylinder A extends A plus sensor a 1 actuates which in turn actuates, after A cylinder extend B should actuates know that is why we will see here, the sensor position is here. The sensor a 1 actuates, which in term actuates the 3 by 2 DCV provided at cylinder B, this is 2.2 get actuated.

So, that it will sense the pilot signal 14 to the valve 2.1 to actuate correct it will actuate, but you will always you will check signal conflict is there at this here, here it is there signal conflict now.

(Refer Slide Time: 11:19)

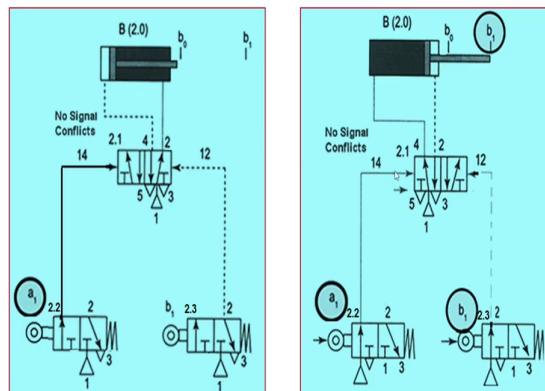- Now check for the presence of the signal conflicts at port 14 and 12 of valve 2.1 ?
- So no signal conflicts and hence the Cylinder B extends (B+) thereby actuates the sensor  $b_1$  and in turn 3/2 DCV (2.3) as shown in Figure below..



Now, check the presence of signal conflicts at 14 and 12 of 2.1. So, friends what happen no signal conflicts. Hence the cylinder B extends B plus will takes place energy automatically it will come here, it will extends. Thereby actuates  $b_1$  after extend  $b_1$  will extends which in




turn after b 1 what happen after extending b minus will takes place, that is why you will see here it will come here.


When, it will extend to b 1 it actuates this valve. What happens friends? The signal will come here, then what is there here, signal is there signal conflict will takes place remember.

(Refer Slide Time: 12:17)

- Once 3/2 actuates (2.3) because Cylinder B is in extended position and sensed by  $b_1$ , a pilot signal 12 appears on 2.1 DCV
- Please check whether 2.1 DCV is responding to pilot signal 12 ?.
- No.. as because already pilot-signal 14 is there because Cylinder A (1.0) is in a actuated position - made continuous actuation of sensor  $a_1$  of cylinder A and hence **there is persistence of signal 14 in 2.1 DCV** → results in Signal Conflict. Please refer Figure

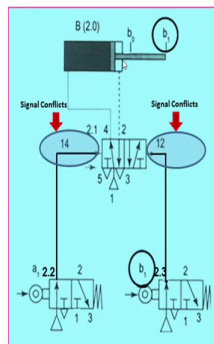

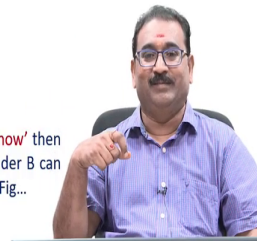
- If sensor  $a_1$  can be disengaged 'somehow' then DCV 2.1 can switch over, in turn cylinder B can retract (B-) automatically as shown in Fig...




Now, we will see friends here once the 3 by 2 actuates meaning 2.3 actuates. Because of the cylinder B is in extended position and sensed by the  $b_1$  a pilot signal 12 appears on 2.1 DCV. Please check the 2.1 DCV is responding to pilot signal 12 no, as I have told you already signal 14 is there why 14 is there, because I want to monitor A extended position afterward, when B retracts A retracts that is why I want to monitor that position.

That is why it is look here signal conflicts correct. What we will do now? If a 1 can be disengaged somehow then DCV 2.1 switch over to this then only it retract otherwise no, because already a I am making it should extend.

(Refer Slide Time: 13:40)

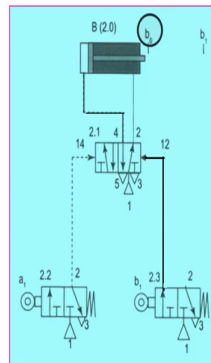

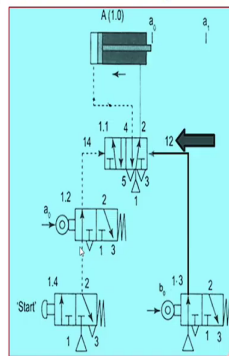- When Cylinder B is fully retracted i.e. when it reaches sensor  $b_0$  (See the figure), which in turn sends the signal to 3/2 DCV (1.3) and in turn send the pilot signal to DCV 1.1 of Cylinder A .
- Check the signal conflict at 1.1.
- Yes. We have not seen signal at pilot port 14 of 1.1.
- So Cylinder A will back to retracted position as shown below



Now, will see friends when I will disengage this by somehow what is that I will tell you. If now I will making assuming that there is no signal here, then it will come energy will come to the road end it will retract. When the cylinder B is fully retracted meaning when it reaches, the position  $b_0$  which in turn after  $b_0$  what happen.

A will retract back that is why we will see which in turn sends the signal 3 by 2 of 1.3 meaning 1.3 or further cylinder A, which in turns sends the signal to DCV 1.1 of cylinder A meaning it is a 5 by 2 valve we will see now. Again you will check the signal conflicts, I will draw this you will see here friends. Now, we will see when the  $b_0$  will takes place here  $b_0$


will takes place, automatically it will signal will come, check the signal conflict no signal conflict because it is dotted.

Then, what happen? Cylinder A will be back energy will go to the tail side whatever the air is there it will go to the atmosphere correct. See now how the signal conflicts will occur, when we are making to monitor continuously. The cylinder retracted positions. And, also we are putting the condition cylinder A is extended position only because, it is holding the workpiece we will do the work, then what happen you have to monitor A is in extended position only. After B will go a will go.


This conditions makes us the signal conflicts to occur at 5 by 2 DCV correct your seen now.

(Refer Slide Time: 15:53)

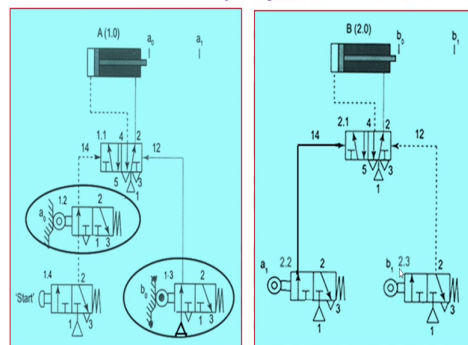- From the above analysis of the designed pneumatic circuit for stamping operation → it can be identified that roller valves  $b_0$  and  $a_1$  are responsible for signal conflicts



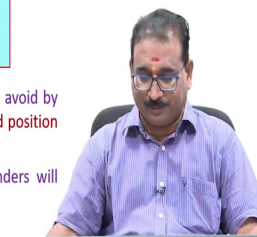- To eliminate the problem of signal conflicts one of the simplest method is avoid by continuous monitoring of retracted position of Cylinder B ( $b_0$ ) and extended position of Cylinder A ( $a_1$ ).
- So we can use 3/2 idle-return rollers for instant monitoring when Cylinders will extend completely or retract completely




So, from the above analysis of the design pneumatic circuit for stamping operation, what we have shown here. It can be identified that the roller valve b 0 correct and a 1 these are the problems correct you have to release I told you then I told you release this. If you will make this instantaneous detection, then no signal conflicts you will see now. Because, this b 0 meaning this side 12 of 1.1 and 14 of 2.1 these are responsible for the signal conflicts.

To eliminate the problem of signal conflicts, one of the simplest method is avoid by continuous monitoring of the retracted position of cylinder B, b 0 and extended position of cylinder A, a 1. Because, these are responsible for signal conflicts you are seen already, there are many methods are there. One among them is we can use 3 by 2 idol return roller valves, for instant monitoring when cylinders will extend completely or retract completely.

Because, valves are like this when it is extent it will sense it is extended. Once it will go out it will inactive this valve is inactive, but it is ensuring that cylinder is extended. If will place in the other direction, when it will come back one instant it will detect afterward no. You have to use 3 by 2 idle return roller valves at b 0 and a 1, but a 0 and b 1 no problem you keep this 3 by 2 roller valve is more than enough.

(Refer Slide Time: 18:21)

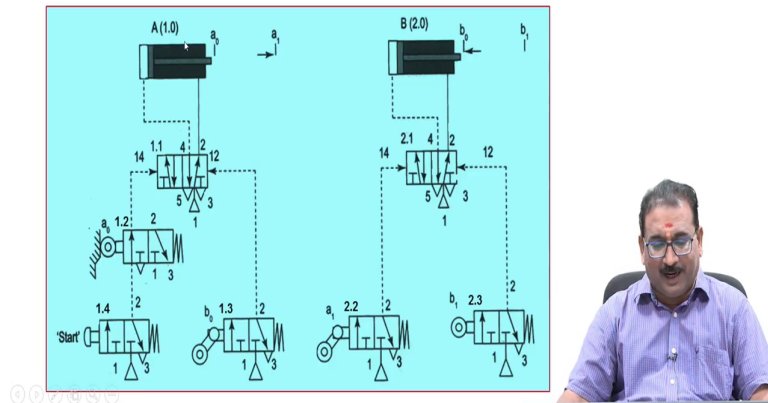- Also please note the signals from the idle-return valves are **not continuous**, and this will help in overcoming signal conflicts
- Also note the 3/2 DCV at positions  $a_0$  (1.2 DCV) and at position  $b_1$  (2.3 DCV) need not be replaced with the idle-return rollers as these valves do not cause signal conflicts for the given control task
- Final Circuit looks like .....



Also please note that as I have told you the signals from the idle return valves are not continuous. And, this will help in overcoming the signal conflicts, also note the 3 by 2 DCV at position  $a_0$  1.2 of DCV and at position  $b_1$  2.3 DCV, need not be replaced with the idle return roller valves. As these valves do not cause any signal conflicts for the given control task.

So, the final circuit looks like this see here I am keeping same here, A is in actuated in the retracted position I am monitoring. But, here how I am relieving I am using the 3 by 2 idle return roller valve. If you will use this what happen the  $b_0$  position when it will retract it will monitors. Instantly not continuous monitoring is not required.

Similarly, here also what is our objective here B is extended are not to monitor that is why you will see here, you will put the 3 by 2 idle return roller valve, then it is disengaged. This is one of the easiest way to overcome the signal conflicts across the 5 by 2 DCV.

(Refer Slide Time: 20:07)

### Cascade method - Design and Operating Principles



- In this method, the sequence of operations of Cylinders → say, A+ B+ B- A- can be divided into appropriate number of groups in such a way that there is no possibility of signal conflicts
- If A+ and A- operations happen to be in one group then → there is a possibility of signals appearing simultaneously at both ends of the final control element- 5/2 DCV of Cylinder A to operate for extension and retraction of Cylinder A → which is the STATE OF SIGNAL CONFLICT
- Similarly for B+ B- and C+ C- cases are leading to → SIGNAL CONFLICT CASES. So they are not in a same group
- Hence the sequence of operations is divided in such a way that → A+ and A- fall into different groups, B+ and B- fall into different groups and so on
- For stamping operations

A+	B+	A-	B-
G1		G2	



Now, we will move onto cascade method design and operating principle, this is also one of the important method, widely usually in industry to overcome the signal conflicts in pneumatic circuits. In this method the sequence of operations of cylinders for example, A plus B plus B minus A minus can be divided into appropriate number of groups. In such a way what there is no possibility of signal conflicts.

If A plus A minus operations happen to be in one group, then there is a possibility of signal appearing simultaneously at both ends of the final control element 5 by 2 DCV of cylinder A to operate for extension and retraction of cylinder A which is the state of signal conflict.

Meaning here, in one group you should not make the group A plus A minus, because it will not understand whether shall I extend or shall I retract that is why A plus A minus should be in the different group.

Similarly, for B plus B minus C plus C minus cases are leading to signal conflict cases, if we will group it in the same group. So, they are not in the same group. An hence the sequence of operations is divided in such a way that A plus and A minus fall into different groups B plus B minus fall into different groups and so on.

For example, we have seen in the previous slides stamping operation A plus B plus B minus A minus correct how to group these things, you will see here how I am grouping A plus cylinder A is extending, then cylinder B is extending no problem it is correct, A minus cylinder A is retracting cylinder B is retracting, you will make a group in such a way that they are in the A plus A minus should be in the different group similarly, B plus B minus in the same group.

(Refer Slide Time: 23:14)

- After dividing the sequence of cylinder operations into a number of groups, then next requirement of the cascade method is to...
- Divide the power supply for the control circuit into the same number of groups as for the sequence operations in such a way that
  - at any given point of time, only one group will have power supply with all other groups connected to the exhaust
- By appropriate interconnection of 5/2 DCV, power supply can be divided into two, three, four or more groups
- Let us we will discuss these power supply groups ...



After dividing the sequence of operations into a number of groups, then next requirement of the cascade method is to divide, the power supply for the control circuit into the same number of groups, as for the segments of operation. In such a way that at any given point of time only one group will have a power supply with all other groups connected to the exhaust.

So, by appropriate interconnection of 5 by 2 DCV power supply can be divided into 2, 3 or more number of groups, based on how you are dividing the sequence of operations to be performed. Let us we will discuss first these power groups, how they will divide.




(Refer Slide Time: 24:29)

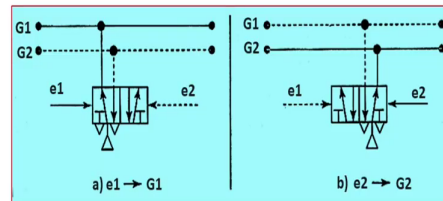
### Power Supply Positions in Two-group Circuit



- Let  $e_1, e_2, e_3 \dots$  are the input signals to the cascade, and  $G_1, G_2, G_3, \dots$  are the output signals from the cascade



- Initially the power supply is in the last group  $G_2$
- When a control signal is applied to input  $e_1$ , the power supply changes to group  $G_1$  from group  $G_2$  and when a control signal is applied to input  $e_2$ , the power supply changes to group  $G_2$  from group  $G_1$
- Therefore, when the control signals are applied to inputs  $e_1$  and  $e_2$  of a 5/2 DCV in that sequence  $e_1 - e_2 \rightarrow$  the power supply changes to groups  $G_1 - G_2$ , across the cascade

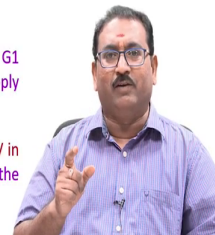

Power supply positions in a two groups circuit, if you are making the to group. For example, in the stamping operation A plus B plus A minus B minus, we made known for this how the power supply positions will looks. Let us we will see now, let  $e_1, e_2, e_3$  what how many want are the input signals to the cascade, and  $G_1, G_2, G_3$  are the output signals from the cascade.

You will see here how I am dividing this  $G_1, G_2, 5$  by 2 a valve  $e_1, e_2$ , here I am showing here  $e_1$  signal is there that is why this port is an active. You will see here the  $e_2$  signal is an active this port is an active meaning  $G_2$  is an active, please remember friends how to draw this circuit.

Meaning the power supply position in two groups circuits two groups are there  $G_1, G_2$  that is why  $e_1$  and  $e_2$  signals are required. To invoke either  $G_1$  group or a  $G_2$  group for this I

am using 1 5 by 2 DCV. How it operates you will see? Initially the power supply is in the last group G 2 please remember this friends. To all the circuits when you are designing using the cascade method, always the power supplies in the last group here, it is a G 2 group we will see it will starts from here G 2.


Meaning G 1 is vented out please see here only G 1 is dark here, because it is receiving the power, but G 1 is vented out. When e 1 is signal is coming that time G 1 is receiving the power G 2 is vented out please understand this very important friends it is. When a control signal is applied to input e 1, the power supply changes from G 2 to G 1 and when the control signal apply to e 2, the power supply changes to group G 2 from group G 1.

Therefore, when the control signals are applied to inputs e 1 and e 2 of a 5 by 2 DCV b in that sequence e 1 e 2 the power supply changes to the group G 1 and G 2 across the cascade. Meaning you will see, remember here friends, when I am grouping the sequence of operation of multi cylinders in each group I am taking care that there should not be a signal conflicts.

For example, A plus A minus should not be in the same group B plus B minus should not be in the same group. That time what happen, what are the sequences of operation you grouped in the G 1 or G 2 or G 3 only that group is on other groups are vented to the atmosphere, they will not receive any signal.

(Refer Slide Time: 28:16)
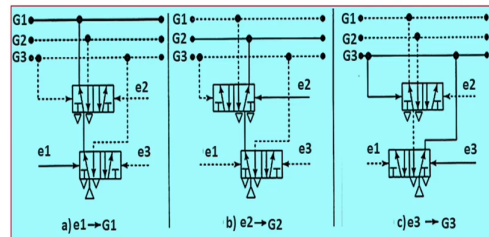
### Power Supply Positions in Three-group Circuit



- Initially the power supply is in the last group G3
- When a control signal is applied to input e1, the power supply changes to group G1 from group G3
- When a control signal is applied to input e2, the power supply changes to group G2 from group G1; and
- When a control signal is applied to input e3, the power supply changes to group G3 from group G2



Similarly, let us we will see the power supply positions in a three group circuit meaning, if I am making the sequence of operation control task G 1, G 2, G 3 for example, if I am operating the three cylinders that time three groups are there. I will make the three groups G 1, G 2, G 3 that time how many signals are require? e 1 e 2 e 3 correct friends, already we know that.

Now, previously we are seen two group only 1 5 by 2 a valve e 1 and e 2. Now, I may required the three control signal to invoke the G 1, G 2, G 3 how many signals e 1, e 2, e 3 are required that is why I am using now, we will see how it is. I am using the 2 5 by 2 DCV. Now, always we will remember what is the null position? Always in the last group meaning you will see e 3, meaning other groups are you will see here vented off other groups are vented off.

When signal e 3 is there, G 3 group whatever you clubbed in the G 3 those cylinders will receive the signal, other cylinders are not receiving any power that is a beauty of cascade method. Now, we will see how it will work. Initially the power supply is in the last group e 3, meaning G 3. When a control signal is apply to e 1, what happens now friends? The power supply changes to group G 1 from G 3, G 2 and G 3 vented to atmosphere you will see here.


Only when I will apply the e 1 signal, you will see the power supply is coming here, only dark this is G 1 group is receiving the energy. Others you will see others are vented off you will see here, others are vented off please remember friends this is a beauty. Similarly, when a control signal is applied to e 2, if I am applying to e 2, then what happens the power supply changes to group G 2 from G 1 correct from G 1.

Then, what happens here? You will see here friends energy is coming here coming here going to G 2 is an active, G 1 is vented off G 3 is also vented off remember very important it is. When, the control signal is applied back to input e 3, what happen the power supply changes to group G 3 from G 2 because previous state is G 2.

Now, we will see here again G 1 and G 2 are vented off e 3 and G 3 are active please remember, how the power supply positions in the three group circuit. Similarly, you have to make a number of groups; I will show you one more if your operations control sequence is more. You are handling the multiple cylinders like a 4 like a 5 6 that time you have to group this in such a way that no signal conflicts in each group.

(Refer Slide Time: 31:37)
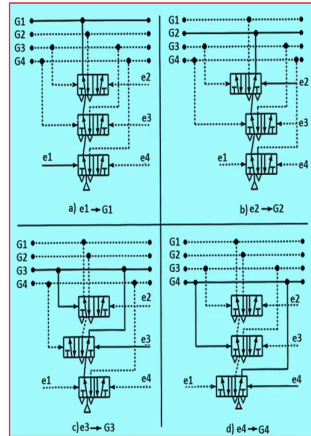
### Power Supply Positions in Four-group Circuit



- Initially the power supply is in the last group G4
- When a control signal is applied to input e1, the power supply changes to group G1 from group G4
- When a control signal is applied to input e2, the power supply changes to group G2 from group G1
- When a control signal is applied to input e3, the power supply changes to group G3 from group G2 and
- When a control signal is applied to e4, the power supply changes to group G4 from group G3



Now, I will show you one more four groups circuit four group means G 1, G 2, G 3, G 4 draw quickly the horizontal lines G 1, G 2, G 3. But, make sure that how many signals are required e 1, e 2, e 3, e 4 correct you will see here e 1, e 2 is required a 3 is required e 4 is required.

As I have told you the null position always power supplies in the last position, meaning when e 3 is there power supply is coming here. You will see G 4 is on all the elements all the actions in G 3 are receiving the signals. Others are vented off you will see others are vented off.

Now, let us we will see how it will work now, initially the power supply is in the last group G 4. When, the control signals applied to input e 1 the power supply changes to group G 1 from G 4 remember, because previous state is a G 4 when you apply the signal G 1.

Immediately it will jump to the G 1 the G 4 is vented off. Similarly, when a control signal is applied to the input e 2, the power supply changes to group G 2 from group G 1, when a control signal is applied to e 3 what happen G 3 is an active G 1, G 2, G 4 are vented off.

Similarly, when a control signal is applied to e 4 the power supply changes to group G 4 from group G 3. Please remember this, even though it increases the number of pi by 2 a valves, but it will never leads to signal conflict place. As we have seen simple operation in stamping operation, you will see here friends when I am operating the multiple cylinders that time if you will not use this cascade method, then difficult task it is, you have to identify every time pi by 2 a valve, where we are getting the signal conflicts.

In which position it is affecting the either you have to use, as I have told you 3 by 2 idle return roller valve. The best method is cascade method, but it require the practice you have to practice the how the circuit will work.