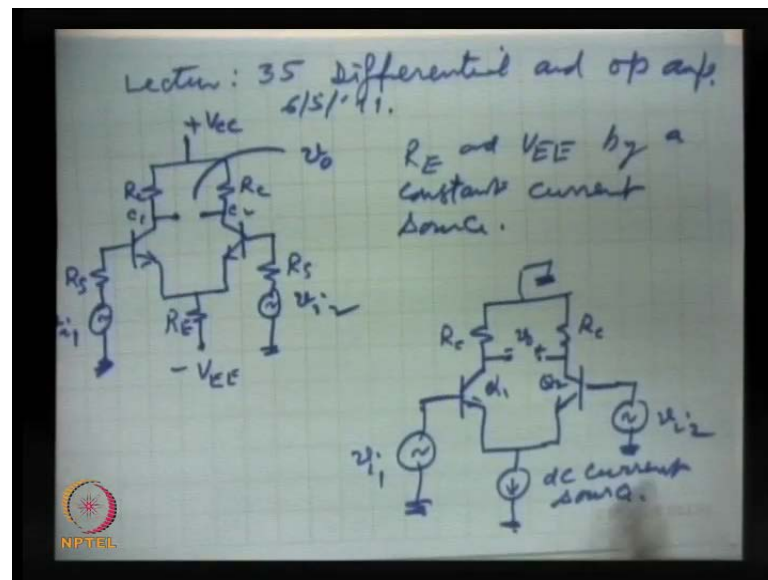


Electronics
Prof. D. C. Dube
Department of Physics
Indian Institute of Technology, Delhi

Module No. # 07
Differential & Operational Amplifiers
Lecture No. # 02
Differential & Operational Amplifiers (Contd.)

(Refer Slide Time: 00:41)




We continue our discussion on ac analysis of differential amplifier. And the basic circuit for the differential amplifier was this, containing two transistors, we are taking v_{j1} and v_{j2} and actually. And finally, we will see that this can be done even with the FET and mosfets and the output is taken normally from that two collectors; this is one collector, this is another collector c_1 and c_2 , this is R_C , this is R_C and this is R_S , which is normally small this is the source resistance. This source which supplies the signal it has impedance and that source resistance; and this is v_{i1} and this is v_{i2} , i for input impedance and here is v_o the output. And we were discussing the in AC analysis of this basic differential amplifier; for that we said that the purpose of this register R_E and this dc source V_{EE} is to supply a constant emitter current.

Now, so for ac analysis, we can replace this arrangement R_E and V_{EE} by a constant current source. And for ac analysis, as we have discussed the several times that there are certain rules, and the rules are dc voltage sources have to be grounded, and dc current sources have to be opened. So, this source is to be grounded, so our ac circuit will become this; Q_1 and Q_2 and this we are replacing with a current source; this is dc current source, constant current source, and supply is the emitter current; and these resistance source resistance we are taking negligibly small, so that we neglect them, and here are these this is v_{i1} , this is v_{i2} , R_C , R_C and the output we take from two collectors here, plus minus this is v_o .

So, this is the equivalent circuit from the basic operational amplifier circuit which we are going to use for ac analysis. Now, I said that dc current sources **sources** have to be grounded. So, dc voltage sources have to be grounded and dc current sources are open for ac that means, they pose are very high resistance and ideally we take infinity that means no ac will pass through this path, this we have to remember. Now, from the analysis which we are going to have these are two sources. So, what we do? We will use super position theorem, we will take one input source as active and we will see and ground the other one we will see, what is the contribution in the output? Then we will ground this and we will activate the second input source, and what is the contribution and then we will the super position theorem says that the net output will be the algebraic sum of these outputs, which will be created by two fine input sources.

From this analysis, one very important point we are going to come out and that is, this two inputs of the differential amplifier, they are **they are** different in one way and that distinguishes them one will be the non inverting input the other will be the inverting input and they are always called like that inverting input and non inverting input. Because I have said it earlier that differential amplifier is the first stage in the multistage amplifier called operation amplifier, which we are going to study just after finishing the differential amplifier. And so this is very essential to know, what is the meaning of inverting input and non inverting input and **and** so on; so we pursue, we **we** continue the analysis, and here this is the circuit and as I said the second input source we will ground and we will see the output of the first one.

(Refer Slide Time: 06:46)

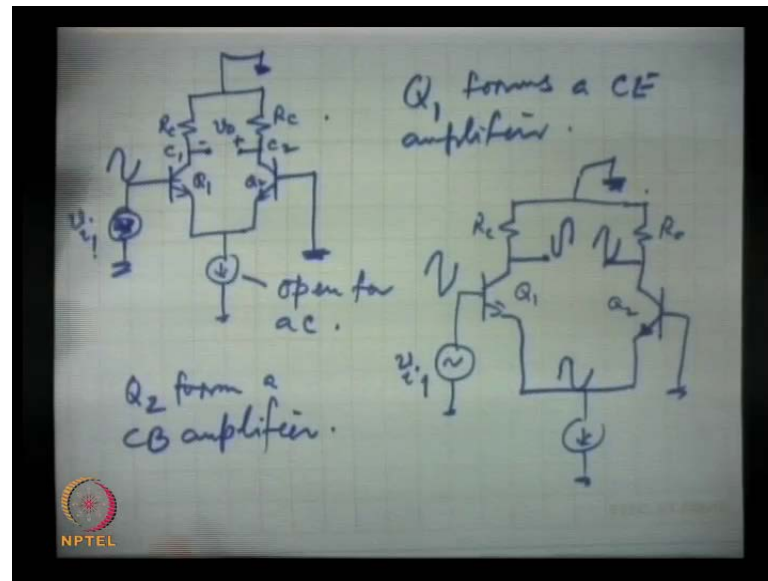


So, here it is this is grounded and here this is active, this is v_{i1} and this is grounded and here this is the dc source. So, open for ac now this is the output which is taken between these two collector c_1 and c_2 of transistor Q_1 and Q_2 and this is v_o . This is the situation when for one of the two input signals is activated is active. So, now see the signals that here we take the input signal is sinusoidal is like that now several very important point will come during this discussion. What is this Q_1 ? Q_1 this is we said earlier forms a common emitter CE amplifier and common amplifier common emitter amplifier shows the output inverted of the input. So, amplified output will appear at the collector and here this will be better out of this I make a bigger figure this is open.

So, we need not to show it no this is the input signal this will appear here in the inverted form wide fully because, we are feeding to the base with respect to ground and we are collecting it at the collector and they are inverted. So, we will get a output here like that now this signal will move here as well and at the emitter when we take the output form then there is no face inversion. So, at the emitter the signal will be available like the original. Now, very important point c_1 forms ac amplifier but now look here this signal will propagate from here to this emitter. So, the that the signal is applied at the emitter and we are taking it at the collector this is Q_2 one see the form Q_2 forms a common base CB amplifier very important point. This is acting Q_2 is acting as a common base amplifier and in common base amplifier there is no inversion, but amplification we will just write the expression this is equal to this hence the signal will be amplified and will,

appear with this polarity and hence this will be here. So, that will be the net output, because of the first signal source input signal source v_{i1} .

(Refer Slide Time: 11:33)

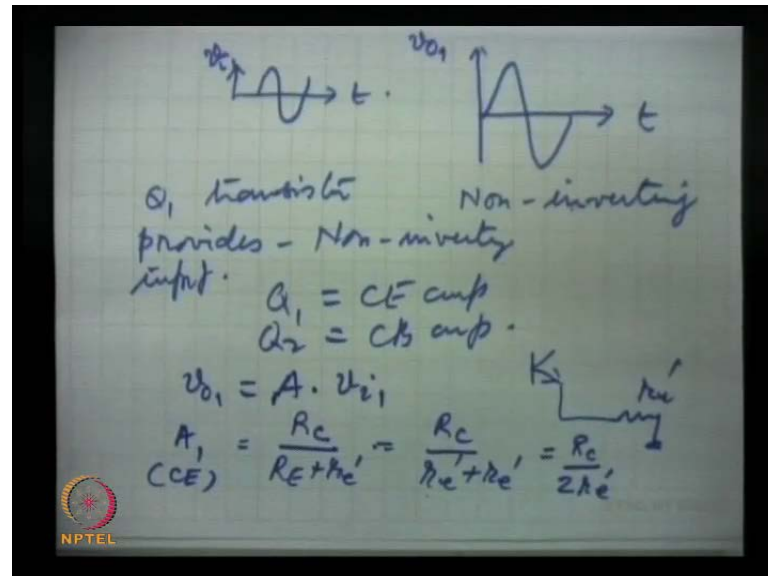

This is this **this** is time and this is v_{o1} output net output because of first input. Now, look here this is the output you may say how the two will be combined now look here that at this point, if head it been safe with respect to ground, this will be the maximum and now instead of ground level which is more negative. So, this will be these two will be added this is like that we measure the height of this point from this table then say this is 20 centimeter, if we measure it from the ground, it will be say 1 meter and 20 centimeter. So, that is to be added and if it still from a deeper point, we measure this height that is to be added so the same thing, this is added up to that. So finally, this is the this is the output, and now see here this output appears for this input this was input v_{i1} with respect to t .

So, obviously this sin non inverting this is non inverting and this input is called non inverting input; non inverting and Q_1 is Q_1 transistor provides non inverting input it is called non inverting input. Now, we will see the other way we can find even the amplification actually, and as I said Q_1 forms CE amplifier Q_2 forms CB amplifier and the amplification will be the output v_{o1} is A is the gain into v_{i1} . If is the general expression for the voltage gain, where a is the voltage gain of the amplifier. Now, how much is that we can it is very simple because we have done it in the analysis of a small

signal b j t amplifiers. So, A 1 the gain because of CE amplifier this is R C by R E plus r e prime, where R E is the resistance with the emitter, where it is simply the I draw another figure to illustrate this point here.

So, the signal is going to the emitter and hence this will act as r e prime r e prime desire I R I I r e prime is the dynamic emitter resistance that is the emitter resistance of the junction dynamic a c resistance and here this will come for Q 2 but the two transistors are identical hence they are the same. So, this will be A 1 is equal to R C r e prime plus r e prime this is from the transistor, one is from Q 1, the other is from Q 2, and hence this is equal to R C by 2 r e prime and this is because of CE instead.

(Refer Slide Time: 16:35)

The image shows handwritten mathematical derivations on a grid background. The equations are as follows:

$$A_2 = \frac{R_c}{2r_{e'}} \quad (\text{CB amp})$$

$$A_1 = \frac{R_c}{r_{e'}} = \frac{R_c}{2r_{e'}}$$

$$A = A_1 + A_2 = \frac{R_c}{2r_{e'}} + \frac{R_c}{2r_{e'}}$$

$$A = \frac{R_c}{r_{e'}}$$

$$v_{o1} = A v_{i1} \quad \text{--- (1)}$$


An NPTEL logo is visible in the bottom left corner of the slide.

And similarly, it will be for the voltage gain in CE and CB are identical and hence this will be A 2 for CB amplifier this is at also this comes out to be 2 r e prime because, for CB CB the gain is R C by r e prime but there are 2 R C R C here R C here. So, they have we combine they are in parallel and hence this will also be R C by 2 r e prime therefore, A in this expression which gives the output A voltage gain due to Q 1 plus Q 2 this is simply A 1 plus A 2 and this is R C 2 r e prime plus R C 2 r e prime and A is equal to R C by r e prime this is the gain.

Differential gain and remember this is that v output because, of first input will be A v i1 this is equation one. Similarly, you will get the equation when the second input is a second input source is active we will get another output and then we will apply the super

position theorem. Always remember one very important point that we are always in the differential amplifier when we take output from the two collectors.

(Refer Slide Time: 18:37)

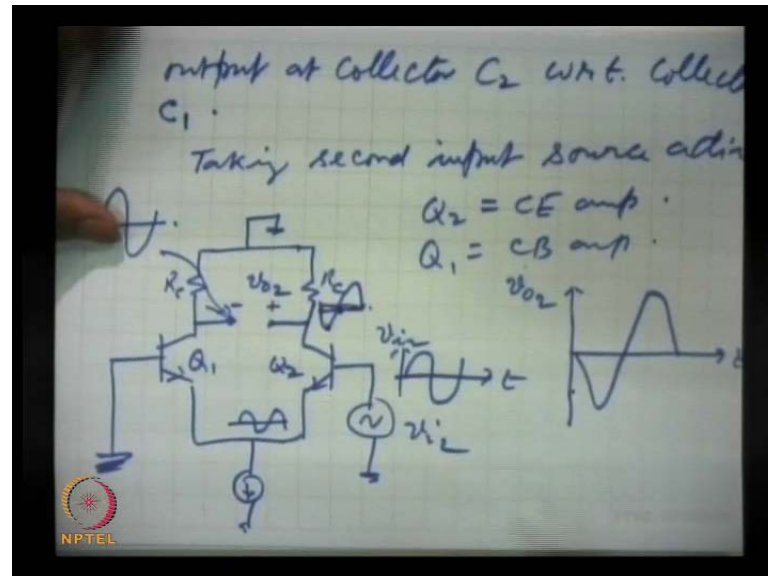


Then always we are taking at C_2 with respect to C_1 , output at collector C_2 with respect to collector C_1 is very important that is why I said that at when this output was maximum when we measure with respect to this point this two will be added. Now, when second source taking second input source active and here the situation will be this **this** is active this is grounded here and this is R_C , R_C and this is minus plus at that instant when input has maximum like that the signal is like the t verses this v_{i2} this is v_{o2} when this input is active and this is grounded.

Now, the rows will reverse here feed in the signal at Q_2 at the base taking it at collector. So, Q_2 will be is CE amplifier and inverted output will appear here. So, here the out the output will be inverted that means like that CE amplifier this is the input just 5 phase will appear at the output. So, output will be like that and this signal this signal goes here and now Q_1 will be CB amplifier. So, without any inversion amplified signal will appear here so at this collector here at this collector it will be like that. So, when we sum up the two remember this is C_2 so this with respect to this therefore, the output v_{o2} as a function of time this will be as I have said up to earlier in the first case this will be like that when the two this is measure with respect to this then this is that and this now


compare these two this is the inverted output here for this input this is v_{i2} as a function of time this gives output like this v_{o2} .

(Refer Slide Time: 22:26)

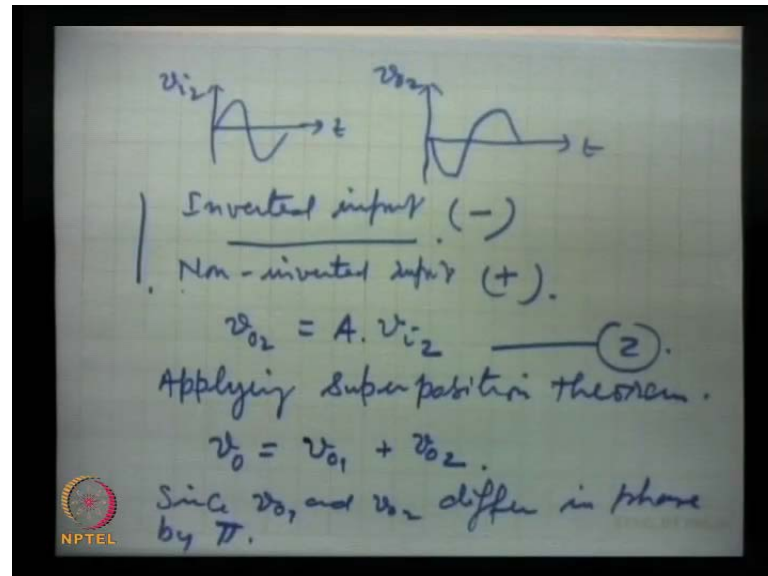

So, this is inverted **inverted inverted** the input one is non inverted input out of that two input this input is non inverted input this is inverted input this you remember and there are mod actually the inverted input with a minus sign and a circuit diagram it is shown and the logic circuit diagram also on the device it is minus and non inverted input with a plus sign. So, these are the two input now we return back that these are the contributions v_{o1} and v_{o2} these are the contributions from individual sources when the first v_{i1} was activated we got the output here. Now, v_{o2} is a as the same because the same thing is been repeated Q 2 forms the CE amplifier Q 1 forms the CB amplifier so we get the same gain and this is v_{i2} this is equation two now we apply super position. So, applying super position theorem v_o the when both are both inputs are active that means when both signals are present then the output will be algebraic sum of the two and they differ in phase by π since v_{o1} and v_{o2} differ in phase by π .

(Refer Slide Time: 25:28)

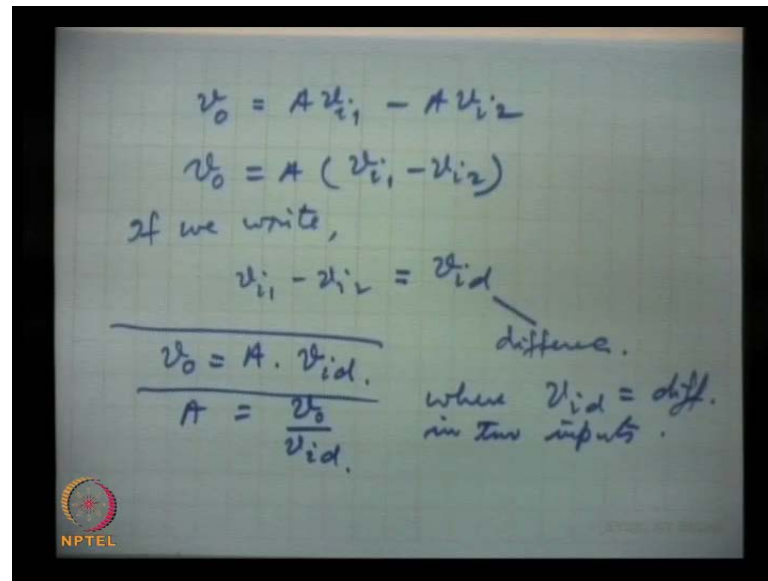
$$v_o = A v_{i1} - A v_{i2}$$
$$v_o = A (v_{i1} - v_{i2})$$

if we write,


$$v_{i1} - v_{i2} = v_{id}$$
$$v_o = A \cdot v_{id}$$
$$A = \frac{v_o}{v_{id}}$$

difference.

where v_{id} = diff. in two inputs.

Therefore, v_o will be equal to $A v_{i1}$ minus $A v_{i2}$ or v_o is A times common $v_{i1} - v_{i2}$. If this difference, if we write **if we write** the difference $v_{i1} - v_{i2}$ as v_{id} for difference d for difference then v_o is A times v_{id} or A is v_o by v_{id} . That means this is what earlier we said as a statement now mathematically by the ac analysis this is coming true that in differential amplifier differential amplifier amplifies the difference of the two signals. So, we can write like this the output where v_{id} is a difference in two inputs. So, this is very important analysis and this has brought out several important features of the differential amplifier that this acts as a differential amplifier plus the two inputs one is the inverting and other is non inverting input. Then we take another parameter from this is analysis and that is input impedance for every amplifier input impedance is very important parameter.

(Refer Slide Time: 27:51)

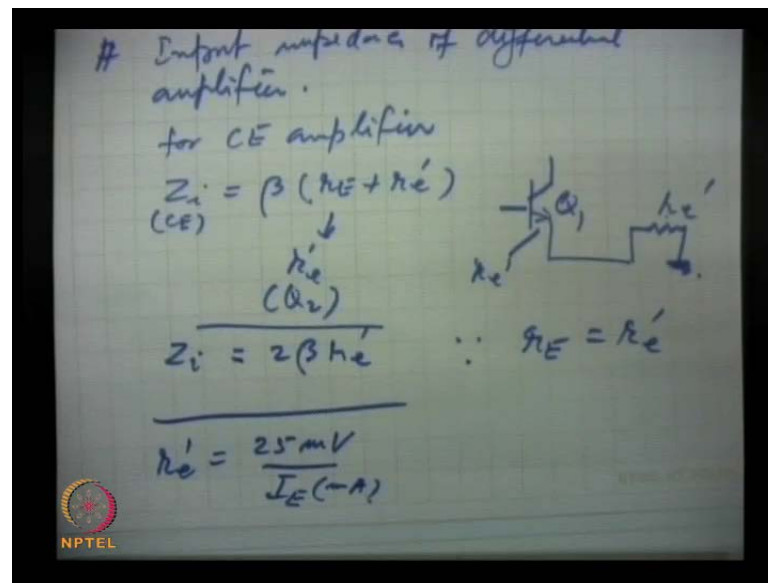


So, input impedance of differential amplifier the differential amplifier is always symmetric is symmetric. So, whether we take we input at the Q 1 or we take at the output which comes out to the same and when we measure it here say at Q 1. This is the C amplifier and for ac amplifier for CE amplifier common emitter amplifier the input impedance for CE amplifier from the analysis the small signal analysis of bi polo transistors we have said that this is beta in the current game into r E effective resistance as seen by the emitter plus r e prime. And this r E is also r e prime was just I take this figure again here this is from Q 2 r e prime. So, this will we seen and this itself has a resistance r e prime this r e prime appearing, because of the dynamic emitter resistance of Q 1 but this is seen because the other will also connected and this is this current source constant current source is open.

So, this is non existence for ac so this is the part and so this r E is also r e prime because of transistor Q 2 and this revolt we are not driving this we have done you just look back to the analysis of a b j t small signal amplifier. So, Z i is equal to 2 beta r e prime because r E is r e prime two. So, this becomes r e prime r e prime 2 r e prime so this is the input impedance in normal is not signal amplifiers like having one input like CB CE. So, the CE amplifier this r e prime was 25 volts but when we multiply with beta that comes out to be it is high voltage of 1 or 2 chromes. In this case, because this depends r e prime if you remember the dynamic emitter resistance of the transistor by definition is 25 mille volts by I E in mille amperes then it depends on current and in differential amplifiers this

current is very small and hence r_e is a very high r_E if it is 1 kilo ohms for example, r_E is 1 kilo ohms then this will be depending on the value of beta several 100 ohms are or even 1000 kilo ohms. So, very high input impedance differential amplifiers have so this was about the input impedance.

(Refer Slide Time: 32:03)

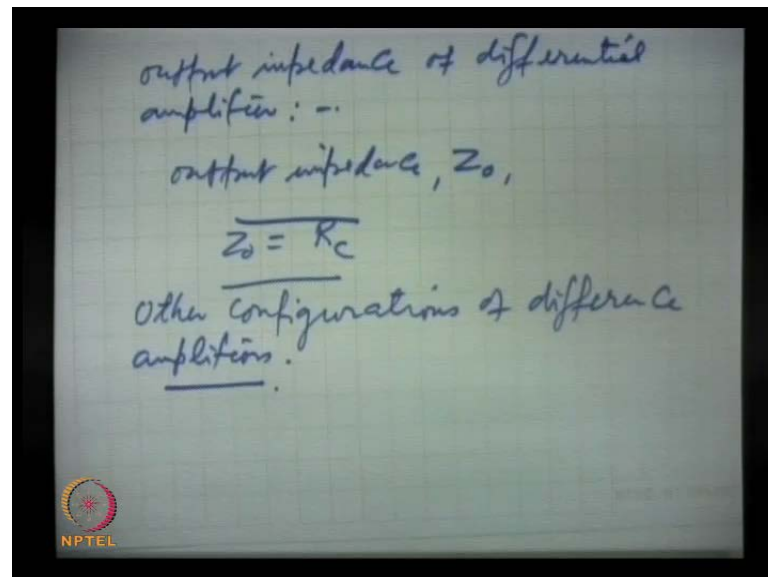


Then the output impedance **output impedance** of differential amplifiers. The output impedance if we look at the diagram and this is grounded then between this and ground what is the impedance which we will be either we measure here or we measure here we are going to get R_C . I repeat between the collector and the ground the impedance which we are going to have output impedance will be equal to R_C whether we measure for Q_1 or Q_2 therefore, output impedance Z_o this is equal to R_C **$R_C R_C$** . Whatever if it is 500 ohms or 1 kilo ohm whatever it is that will be the output impedance. So, the three most important parameters of ac analysis for any amplifier the gain and the input impedance and output impedance that completes the ac analysis of the differential amplifier. This was the general analysis and by general we mean for the differential amplifier when we take output from the two collectors that means for balanced output differential amplifiers dual input balanced output that is the most widely used configuration of the differential amplifier and for that we presented the analysis.

That dc analysis is same for all other possibilities also ac will slightly differ because from whether we are taking output from two collectors or from collector c_2 with respect

to ground that will change the gain and so where that the part is slightly different. So, having done the analysis for the dual input and balanced output differential amplifier we can briefly take other configuration some are not used actually but for the sack of argument and for the sack of logic they are there but others are used. So, what are these and how we can infer the results because input impedance will be the same whatever is the configuration whether single ended output or double ended output input impedance does not depend on that. So, input impedance will not be effective only output impedance will effect will be effective.

Now, the other configurations we take other configurations of differential amplifiers. The next one we take is this dual inputs un balanced output that means, single ended output we take output from c 2 with respect to ground this is sometimes used on some special conditions situations are there we are this configuration proves useful and is used.


(Refer Slide Time: 36:27)

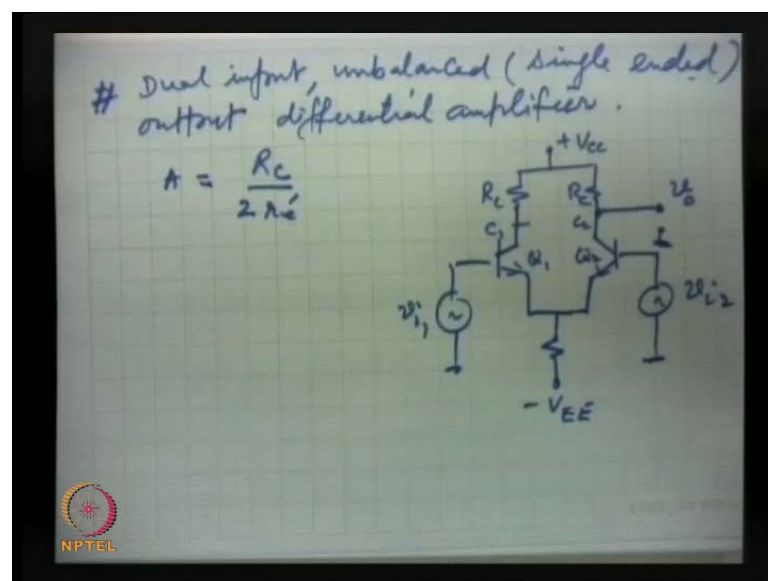

So, this is dual input and unbalanced **unbalanced** that is single ended output differential amplifier. This is dual input unbalanced that is single ended output differential amplifier what we are saying is this we are taking output here this is v out with respect to ground we are applying two inputs and we are taking in the previous case balanced output we are taking output at the two collectors C 1 and C 2. Now, only single ended single ended unbalanced so from collector C 2 with respect to ground in this case only one point is to be remember that let as look at the signal the signal will be amplified it will be


amplification factor will be half of the previous case because here for example, this case was amplified here also and it goes it is amplified here also and similarly, the other one but here this gain a will be equal to $R_C / 2r_e$ because the signals will be amplified what we have now using is only half the capability of the differential amplifier.

(Refer Slide Time: 39:27)

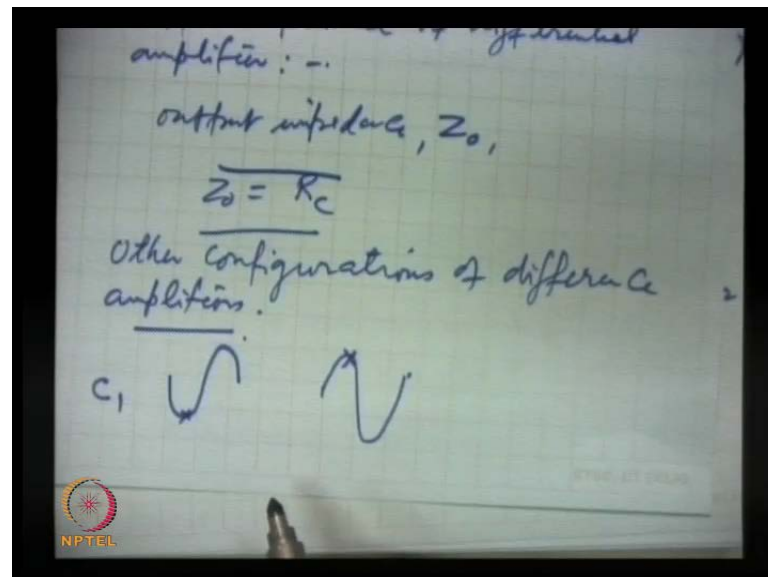


I just make this point clear for example, when both signals were there the output at the Q1 collector was like this was from the collector C1 and the collector of C2 that was that that was like this now if we measure this with respect to ground this will be the gain this two are identical as far as the magnitude is concern, but when this point will be measured this is doubled we explain this that this will come double.

(Refer Slide Time: 40:10)

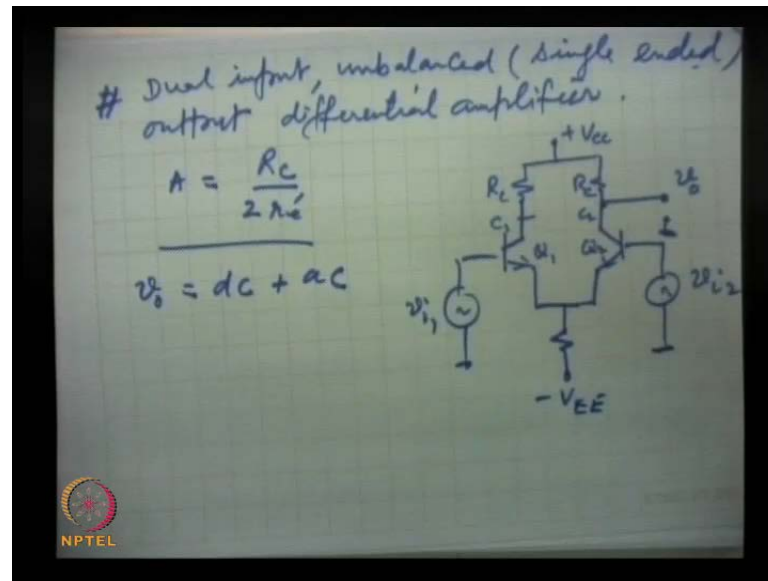


So, in this case when we are taking output with respect to ground that gain will be half. Another important point that because, of the symmetry of the differential amplifier that dc parts were absent because they were equivalent they were they will be cancelled in the output when we take output from two collectors that means, in the case of balanced output the dc parts was absent. Now, the dc part was absent now this dc will also with here so output will contain dc plus ac signal dc voltage will also begin. So, if this configuration is to be used then at some stage you will have to take care because this will change the dc level of the signal so there are circuits which take care of dc level and amplifiers so that is to be used. And as I said input impedance of this amplifier will be the same as in the previous case because input impedance does not depend how we take the output.

(Refer Slide Time: 41:30)

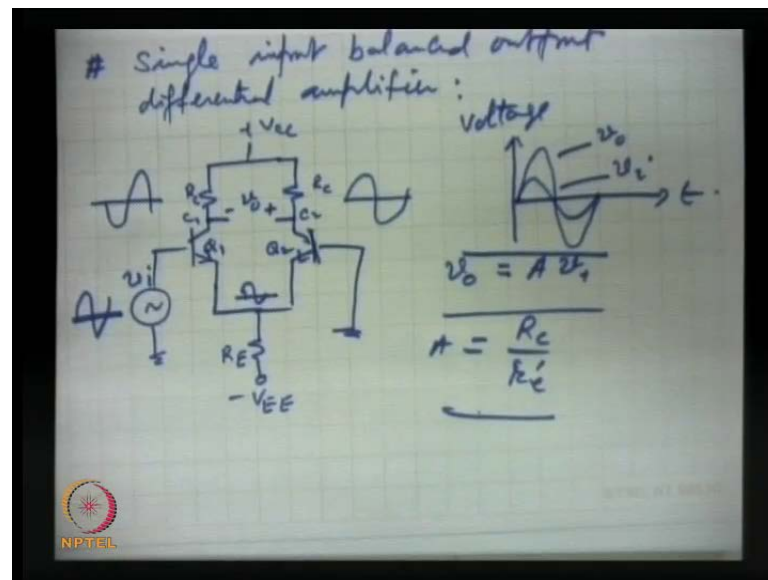

Then the other configuration is single input balanced output single input balanced output differential amplifier this is I draw the figure only one input source is their this is grounded and this is active and output is taken from two collectors C 1 of Q 1 and C 2 of Q 2. So, here this is output now if this signal we take then we remember that this will appear here as inverted but here, it will appear as like this and here. So, when we take the balanced output the voltage is input and output this is in phase with this input. So, this is the voltage time and this is for v_i this v_i and output is in phase with it this is v_o . So, we will get the output and input like that and v_o will be equal to $A v_i$ here A is R_C by $r_{e'}$ as in the first case we studied.


(Refer Slide Time: 44:19)

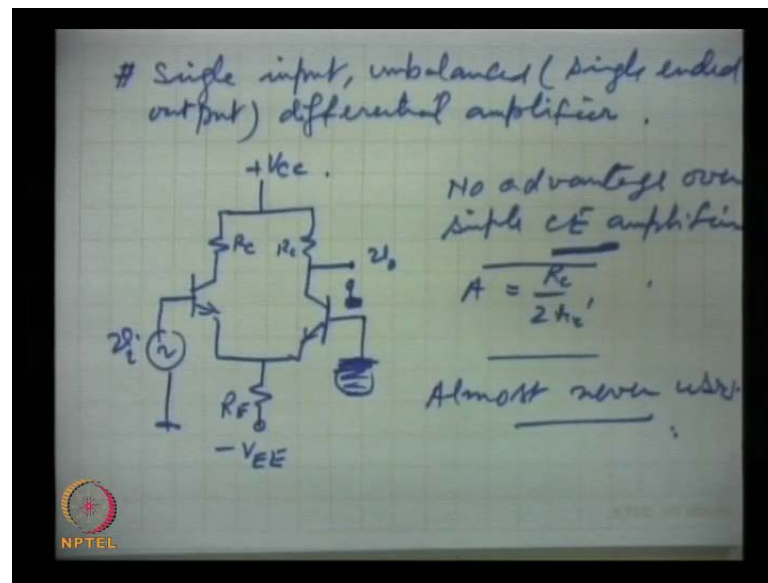

And the last one which is not used actually that is single input unbalanced output single input unbalanced that is single ended output, differential amplifier **differential amplifier** and this is the configuration which show we are talking this is the input signal and output this is grounded and output is taken from here v_o with respect to ground this is the single ended unbalanced output. So, here the gain will be half of the first case plus important feature is that this does not offer any advantage over simple no advantage over simple CE amplifier but a disadvantage is this makes use of much more components large number of components has compare to simple CE amplifier. So this is almost never used there is no advantages in using this the so this is not used here gain will be half of the previous case when we take unbalanced.

So, A will be R_C by half $r_{e'}$ so almost never used, so this were the different configuration which we had said earlier that four possibilities exist and these are the four different differential amplifiers. Now, all through this analysis we have taken b j t differential amplifiers but instead of a b j t we can use a FET JFET or MOSFET and we can found a differential amplifier.


(Refer Slide Time: 47:26)

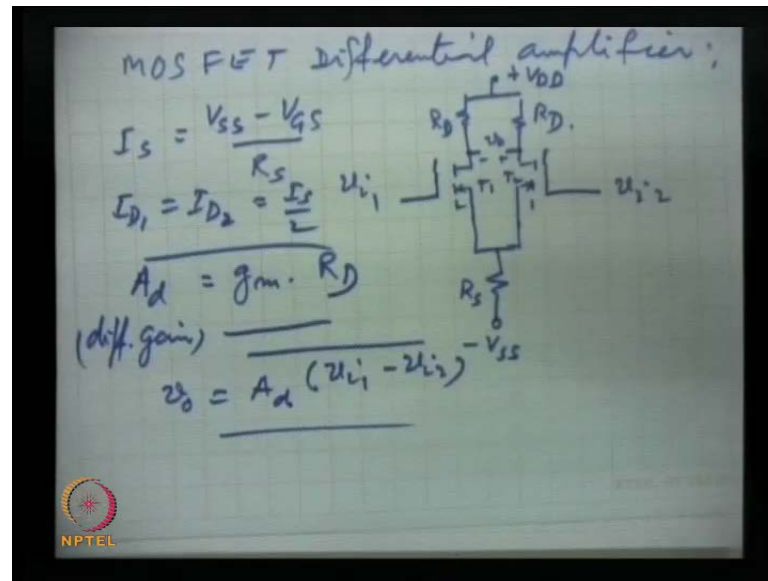

For example, the MOSFET differential amplifier the analysis which we have done they are with slight modification for example, gain will depend on not on beta, but you remember that trans conductance that those terms have to use otherwise this same. So, very briefly I take this here this is the source resistance and these are the two MOSFETS. This is one input this is the another input and we connect this is V_{DD} this is R_D drain resistance and the output can be taken from two drains this is v_o . So, these are the two MOSFETS T_1 and T_2 and they can also form a differential amplifier this is one transistor MOSFET this is another MOSFET and it can be shown actually that the source current R_S is V_{SS} this battery minus V_{GS} by R_S and drain current in one as the same as drain current in two and this will be half of I_S .

So, is by 2 and differential gain **differential gain** in this case this will be g_m into R_D this also for a MOSFET we have derive this relation so this the voltage gain. And v_o will be A_d into v_{i1} minus v_{i2} as usual so this is the differential amplifier. So, differential amplifiers are common and MOSFETS also when very high impedance input impedance **input impedance** in are required are rather is still higher then MOSFETS are used and this may be the requirement in several instrument and instrument fabrication so these differential amplifiers are used.


(Refer Slide Time: 50:57)

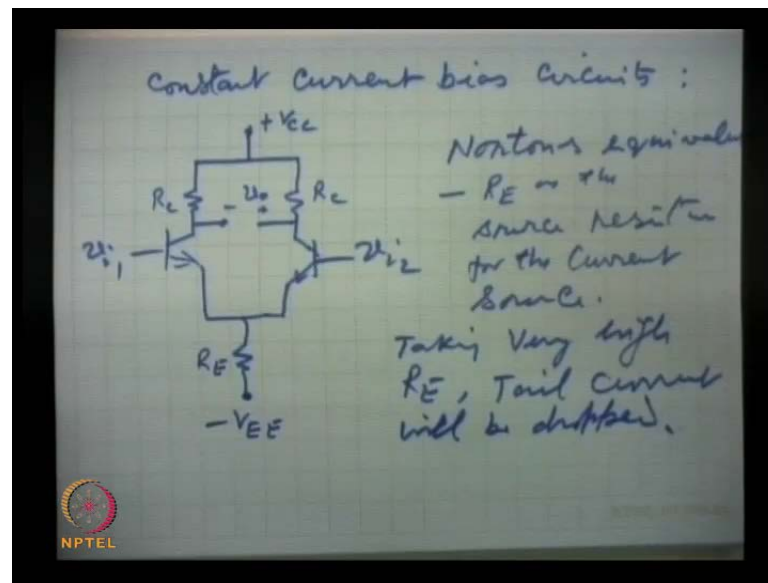

Now, we will talk about the constant current source constant current bias circuits **constant current bias circuits**. In the conventional design which we have been taken as the basics basic differential amplifier this constant current source this resistance R_E and this voltage this forms the constant current. And remember we have said we have made a statement several times v_{i1} v_{i2} we made a statement and in the hole ac analysis we have taken this as a constant current source. Now, if we draw the Norton's equivalent **Norton's equivalent** of this circuit then R_E then for that current source Norton's equivalent will have R_E as the source resistance **source resistance** for the current source. For a current source the source resistance must be very high ideally infinite.

You know this was a voltage source a voltage source constant voltage source should have a low resistance, while a current source should have the and we have neglect that this R_E sets at several places but a current source should have very high resistance but in this case R_E cannot be very high because, if R_E is very high that will reduce the tail current taking very high value of R_E the tail current will be dropped drastically. So, we cannot use very high value of R_E so but a good current source constant current source should have a higher resistance. So, better circuits at this are replaced by a transistor and a constant current source can be fabricated by using a transistor a b j t.

(Refer Slide Time: 54:23)

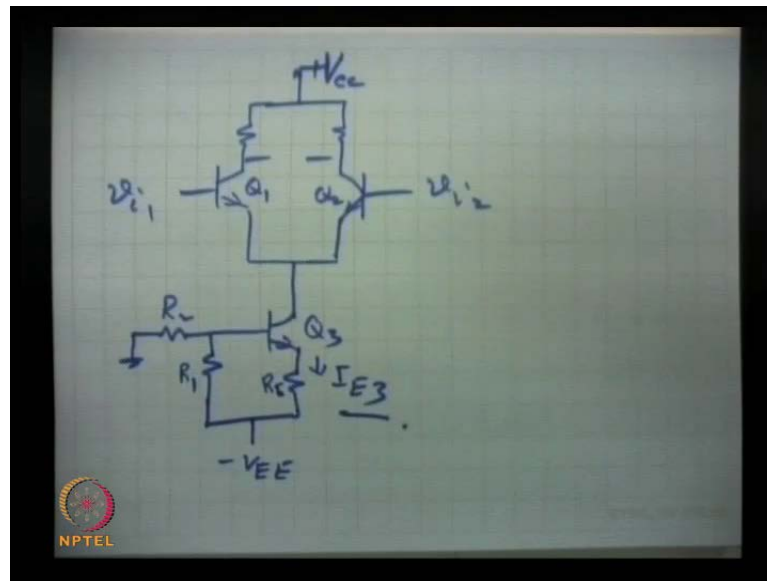

So, what will be the circuit that is this; because the reverse bias collector has a much higher resistance than simple resistance R_E, so this acts as a transistor Q₃, Q₃, this is Q₁, Q₂, this is v_{i1}, v_{i2} rest is same as we have discussed. This circuit is taken, R_E and the current I_{E3} flows through it. What we have done? We have replaced the simple arrangement of that resistance R_E, and this battery, because this does not fall a high quality constant current source. So, this we have replaced by a transistor. The transistor collector, which is reverse bias and that **that** exhibits in much higher impedance as compared to simple R_E. So this x has the better constant current source, very widely used, because this is essential, this point was essential that the constant current source is a providing a constant current to the differential amplifier. And this can be analyzed in a simple manner; we will be talking about that. And this can further be improved; this resistance R₁ can be replaced with two diodes have an identical characteristics as this emitter base junction. So, these are the points, which we will be discussing, and then we will move further.