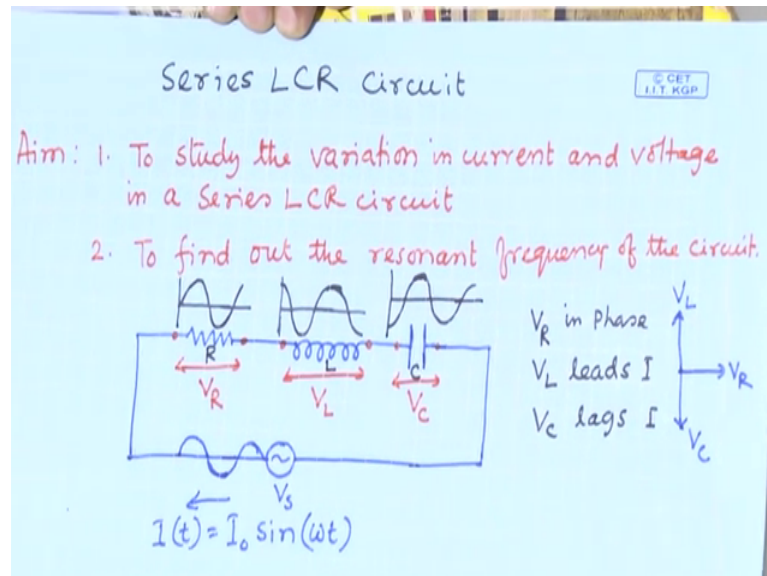


Experimental Physics I
Prof. Amal Kumar Das
Department of Physics
Indian Institute of Technology, Kharagpur

Lecture - 48

To study the variation in current and voltage in a series LCR circuit

(Refer Slide Time: 00:30)



So, today we will perform experiment on series LCR circuit. So, series LCR circuit, you can see here. So, this R , resistance R , inductance L and capacitance C . So, they are connected in a series with this power supply, this is basically AC power supply ok. So, from here this current, we will get in this circuit, because this voltage is this basically AC voltage. So, current you will get of same frequency. This current will vary in this circuit, this I is equal to $I_0 \sin \omega t$ right.


So, what we will study in this experiment is basically the variation of current and voltage in this is LCR series LCR circuit as well as this is the this circuit is basically is it call this tuning circuit. So, this circuit is used to tune is to used to tune; tune of what. So, basically if you tune, if you just vary the frequency this current, you can maximize the current in the circuit ok, so that is why in earlier days in radio (Refer Time: 02:04) to increase the volume or to just find out the channels, so this whatever this varied, so that is we vary the basically frequency ok.

For a particular frequency, then it when it matches with the signal frequency, then there will be resonance and for that maximum current flows in the circuit means, we will get the strong signal ok. So, here if current flows in this circuit, then you can what we can do, we can measure the voltage across the resistance, so this V_R 's, we can measure the voltage across the this inductor, so that is V_L and we can measure the voltage across the capacitor, so that is V_C .

And you can basically if you plot this voltage for say that this V_R , V_L , V_C , then what you will get? So, you will see this V_R is in phase with current. V_L you will see this V_L leads I , this means its phase is basically 90 degree phase this V_L ahead 90 degree with respect to the current. And V_C lags this lags with phase 90 degree. So, phase difference between this V_L and V_C basically 180 in opposite direction.

So, you can draw basically phase diagram and from here so now voltage are different across the; across the; across the resistance, inductor and capacitance. So, this is fine resistance. So, this has also it has resistance. So, resistance is we tell as X_L , it depends on frequency its a ωL . X_L equal to ωL , ω is $2\pi f$, f is frequency. Similarly, $1/\omega C$ that is X_C , ω again $2\pi f$ right. So, $1/2\pi f C$ that will be the X_C that we tell the capacitive reactance X_C , inductive resistance X_L and this is resistive resistance.

(Refer Slide Time: 05:08)

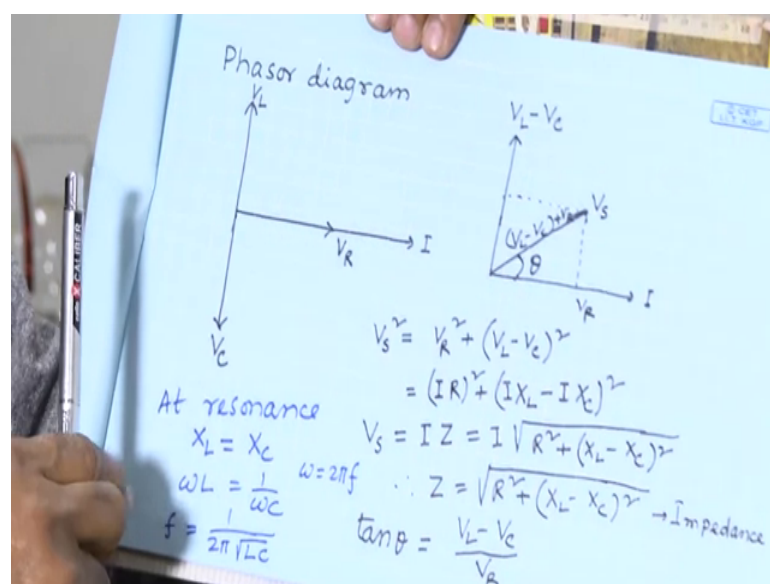

So, what will be the total resistance of this circuit that is called impedance that impedance one can find out impedance of the circuit. So, if you measure the; if you measure the V_L , V_R , V_C as a function of current if you vary current, then if you measure this three and if you plot, then so you will get this type of phasor diagram; you will get this type of phasor diagram.

So, actually we are not going to do that one. But, for calculation if you use this phasor diagram, so then this here so just you can modify this plot, so here V_L and V_C is a 180 phase difference. So, basically V_L minus V_C can plot V_L minus V_C , so this lie in the opposite direction, so V_L minus V_C will be this if so and V_R is as it is, then this from this is a phasor diagram vector diagram.

So, this from vector addition basically, you will get; you will get if you add this plus this, so resultant one you will get this line. So, this line will be V_L minus V_C , this one plus V_R , so this is V_R and this is V_L minus V_C . So, this will be (Refer Time: 06:44) this. And this so this, this, this, this, this, this, will be equal to the of course the source voltage source voltage and the angle between this with respect to this I , this angle is called this phase angle ok.

So, in principle you can find out from this triangle from this triangle, so V_S so this is basically V_S right, resultant on V_S so V_S square equal to will be equal to the V_R square plus V_L minus V_C whole square right. So, V_R is I into R square and V_L is $I X_L$; X_L as I told is reactance is a resistance inductive resistance is called reactance, so $I L$ minus V_C $I X_C$ square ok.

So, V so if total resistance in this circuit that is called impedance if it is Z and current flowing in the circuit if it is I , so V_S equal to $I Z$. Z is impedance equivalent to resistance in the circuit, so that will be equal to I , then from here you are getting basically I square, so it will be I , then square root of R square plus X_L minus X_C whole square right. So, comparing this you can write that impedance is equal to square root of R square plus X_L minus X_C whole square. So, this is called impedance this is called impedance.

And corresponding this phase that is theta will be equal to tan inverse, from here you can see tan theta equal to this by this, so V_L minus V_C by V_R ok. So, from here, you can get this angle theta, so that is called phase. So, resultant whatever this your this you will

get, so that we have phase. So, these are individual phase, it is in phase V_R is in phase V_L is leading lagging.

So, for LCR circuit series LCR circuit, so what will be the resultant, this that is basically this is amplitude and this is the angle. So, this θ one we can find out. So, if we measure V_L , V_C , V_R ; V_L , V_C , V_R , you can find out θ . And now remember this and you can find out also impedance, we can find out also impedance right, you can find out also impedance.

So, basically X_L you will get; X_L you will get how will get X_L ? If you know V_L and I , so from there you will get X_L . Similarly, V_C and I , then you will get X_C right. So, if you measure V_L , V_C and V_R , then you will; you will; you will be able to calculate the impedance also the phase. And these for a particular frequency, these for a particular frequency ok. So, current versus voltage or voltage versus current, you can study. And from there you can find out the impedance or reactance and their phase ok. But, our main interest for this experiment is to find out the resonance frequency.

Now, if you vary the resonance, if you vary the sorry if you vary the frequency, then what will happen? If you vary the frequency, then this impedance changes you know impedance changes impedance changes so, your current also will change in the circuit for a particular V_S source voltage. So, at which frequency; at which frequency, this current will be maximum that is what our interest and that is called the basically resonance and that frequency is called resonance frequency.

So, we will find out the resonance frequency for this LCR circuit ok. For that what we have to do, I have to measure current; I have to measure current as a function of frequency, then I will plot current versus frequency. And then you will see you will you will get this type of curves, so at a particular frequency, you will get maximum current, so that peak you have to find out. And that actually that corresponding that peak that you will get the frequency.

And that frequency also you can calculate theoretically, because at resonance where you will get maximum, so when this impedance will be minimum ok. So, impedance will be minimum when X_L equal to X_C right X_L equal to X_C , so that is the condition of resonance. So, at resonance X_L equal to X_C . So, this is ωL and this $1/C$. So, basically if you put $2\pi f$, so f is equal to $1/2\pi \sqrt{LC}$ ok.

If you know the value of L , if you know the value of C , then you can calculate f . And experimentally you can measure measures f , you will find out this f from this curve, I versus f frequency, so that peak value what about the frequency for peak value, so that will be the basically your resonance frequency, then one you can compare with this frequency. Also yes as I told for a particular a particular frequency, you can measure the impedance and you can measure the individual reactance. So, basically in this experiment, I have to measure I varying the frequency f . This is main part of this experiment.

Another part of the experiment is basically you measure V_R , V_L , V_C for a particular frequency varying the current. So, V_L versus I , V_R versus I , V_C versus I that you can plot for a particular frequency. And for that frequency, what will be the X_L and X_C or R resistance R that you can find out from the slope or it will be straight line from the slope of that curve that part I will not show here, only I will show you, this resonance in this curve ok.

(Refer Slide Time: 14:28)



So, let us go to our setup. So, this is the experiment experimental setup for series LCR circuit. So, this is obviously, you are saying this is L inductor right, this is inductor and its value is written here its written here 9 milli-henry. So, you should note down this value 9 milli henry ok.

Then this is the here a small one that is the basically capacitor this capacitors, so also you can note down this value of the capacitor its written here, I think yes, I cannot see, but anyway I will not disturb it, but its written here. So, this values I guess what is the value again, this capacitor value here we have taken I will tell you, so that you should note down always you should note down this values, this capacitor value 4.7 microfarad. This is the this capacitor; this capacitance is 4.7 microfarad that you should note down.

And this is the resistance and this resistance is 2 ohm ok. So, I have inductance, so that is 9 milli henry. I have capacitance is a 4.7 micro farad and this resistance it is of 2 ohm right. Now, I have connected them in series you see just check it, so to check it series with respect to what series with respect to the power supply right.

So, if you start of one end of the this is the power supply AC power supply ok, here you can vary the amplitude as means voltage as well as; as well as you vary the amplitude you can vary the amplitude as well as frequency ok. So, this option is there. So, AC source, so this so here so this the power supply this AC battery ok.

So, so start from one electrode, then it is connected to the one end of the inductor, and then other end of the inductor is connected, we have used bread board you know we have used bread board, so it is connected with one leg of the; leg of the capacitor ok. So, then through capacitor another leg is connected to the resistance here. And then another end of this resistance is connected to the another electrode of the power supply ok. So, these three are in series. So, we have to check this circuit or you have to made yourself, I can open and just connect it by to save time that I am not going to do it, but I showed you this connection ok.

Now, this is AC ammeter this AC voltmeter yes. So, this is this will be used for measuring the voltage of what measuring the V_R , V_L and V_C right. So, this actually two wires is coming from here ok, so this is the two say so just this is the; this is the voltmeter AC voltmeter, it is giving you the rms value; rms value V_{rms} ok.

So, just if I want to measure the voltage across the; across the resistance, then this is V_R , so I have to connect here; I have to connect here ok. So, if current flows AC current flows through the circuit, the current is same in the circuit. So, if you measure current at any point ok, so either across this; across this resistance, if you measure voltage across

the resistance, inductance or inductance or capacitance ok, so that voltage the reading you will get from here ok.

Now, I need to know the current in the circuits. So, these if I just take the voltage across the resistance and resistance value is known to me, so this resistance value here this is 2 R equal to 2. So, this whatever reading here, I will voltage divide by V_R divided by R , so that will be the current. And this current is same for this for the circuit.

So, this current is passing through inductor, passing through the capacitor, so and why we are taking this voltage across this resistance, because this current whatever we will get from here. So, this is this voltage reading will vary, if I change the frequency, because that is for the frequencies X_L and X_C that will vary, but this R will not vary ok. So, R all the time it is 2, so that is why for measuring current, actually we will measure the voltage across this V_R and just divide by 2 that will give me current.

If I measure the voltage across the X , across this L and C actually this X_L and X_C will vary with the frequency. So, all the time one has to find out the reactance of reactance X_L and X_C and so that will be complicated. So, for knowing the current, we will measure the voltage across this resistance. And resistance R is known to us, it is a equal 2. So, from there I will get the current, so that is I_{rms} value I will get ok.

So, now let us so now if you want to measure the voltage V_R , so you have to connect here you have to connect here this voltmeter or if you want to measure the; measure the; measure the of voltage across the capacitor, then these two I will connect here; these two I will connect here ok, because this is across the; across the capacitor ok.

And here also if you want to measure the voltage across the this inductor, so this I will connect this ammeter voltmeter with this ok. So, here you can study; here you can study the variation of; variation of V_L as a function of current, if you vary the current; if you vary the current ok, so then what will be the variation of V_L or what will be the variation of V_C or what will be the variation of V_R as a function of current that you can measure ok, so that would be the one experiment that has to be done for a particular frequency.

So, we will fix frequency; here say frequency is 100 Hertz ok. So, we will fixed frequency, then I will go to; I will go to the amplitude. Now, here amplitude is 5 volt, this is now remember this 5 volt, it is showing this peak to peak value. So, AC voltage you

know this the ok, so in positive side one peak and negative side one peak. So, this peak to peak value, so that is showing this is 5 volt.

So, now but we have to take rms value, of course this I do not have interest for this one, because I do not need that one. But, you should know this rms value of this one is basically this peak to peak value divided by $2\sqrt{2}$ ok. So, whatever value here, so divide by $2\sqrt{2}$ to that is actually rms value of the voltage, so that voltage. Now, what I will do, I will measure V_R , V_C , V_L ok. So, either you need 3 voltmeter or 1 voltmeter, you can just one after another, you have to you have to do the experiment.

So, now I will vary; now I will vary the amplitude this amplitude means voltage peak to peak value. And for each voltage, so current will vary in the circuit and corresponding voltage drop, I will measure for this three ok. And if I measure automatically current I will get; automatically current I will get, just whatever V_R I will, so V_R divided by this two that will be the current ok.

So, for a particular current, I will measure V_L , V_C and V_R . So, then I will change the change the voltage V_S source voltage and again I will repeat the experiment. So, I can connect current versus V_L , V_C and V_R . Now, if you plot them; if you plot them V_L versus I , V_C versus I , then what you will get? You will get basically straight line. And from the slope, you will get basically X_L and X_C .

And frequency is known to you I have set at 100 Hertz see frequency is known to you, say X_L equal to ωL $2\pi f L$ ok, so f is known. And from there basically you can find out L . Similarly, you can find out C ; of course, R is known to us as I told 2.

So, in this way we can measure the capacitance and inductance also right. So, this part I will not show you, but my interest is to show you the resonance. So, for resonance what I have to do? So, for resonance I have to actually I have to measure the current. So, I will measure the voltage across this resistance, I will measure V_R . If I measure V_R , here I will get V_R , so I will divide by these two, you will be it will be the current ok.

So, now this current I will so current how current varies in this circuit with frequency that is what I want to do experiment. So, here this is a 5 volt that I will keep fixed. Now, I will go to the frequency; I will go to the frequency; I will go to the frequency, (Refer

Time: 26:57), then I will start this experiment from 100 Hertz frequent. So, I will note down this frequency is 100 Hertz ok.

And corresponding what is the V R what is the V R? So, I have to connect it with a V R, here across this ok. So, I have connected; I have connected in electrical circuit always you have to see this, there should not be any loose contact yes is the connected ok. So, I have to note that this is; this is let me put in ok, this is a 7 milli volt, this is 7 milli volt, so, for frequency 100 Hertz.

So, you have to make table this frequency versus V R versus V R and resistance is 2 so this basically V R by R that will be I. So, frequency versus current that you have to make table. So, I will note down; I will note down this for 100 Hertz, this is 7.1 millivolt. And then I will change to 200; I will change to 200 110 120, so I will change to now this frequency is 200. Then I will take reading now, it is 14.7 I will note down this reading.

Then I will go for 300 and then it is 330 ok. Now, it is 300, this reading is 300 that is 23.9 milli volt ok. So, this way I will continue; I will continue to 400, 500, 600 ok. So, now I am it is 600 ok, so 87.3 reading is 87.3. Then I think I am close to the resonance, so I will increase the range of the voltage I kept it at two volt range ok. So, it is in volt range we say 88 volt ok. So, then I will change; I will change I am changing its 670, 680, you see this now it is increasing very fast, this current is increasing very fast.

For slight change your frequency, now 720, 730, it is 200 200, 740 Hertz 216 millivolt, then 750, 236 7 you see earlier with respect to 100 variation of Hertz, whatever change now with respect. Here now with 10 variation of frequency this change is similar. So, 760 770 780 790 you see this 810. So, it will come around 800. Since, I have done this experiment earlier so its the near out 300 near out here 290, 90 290, 292, so at 790, it is 290 at 780 at 780 to 87, so its decreasing.

So, if I go increase it 800, it is 287 or 290 around. So, now 810, now started to decrease 820 it now decreasing. Now, I am increasing 830, 840, 860, so its decreasing know. So, peak so we saw that peak is around 800 Hertz the frequency. When it is 800 hertz is a maximum, it is the 292 millivolt. Then below this, lower side of this frequency, its decreasing. And higher side of the frequency, it is increasing. The also this current is decreasing. This voltage is decreasing means this is the volt, so divided by 2 that is the current.

So, this you have to take this data and then plot it. And then you will see the peak, and then corresponding what is the frequency of that peak that is the that is your resonance frequency. Now, in resonance condition this X_L equal to X_C that is the condition right. So, X_L are in reactance, so I into to X_L is the V_L , I into X_C is the V_C ok. So, X_L equal to X_C means V_L equal to V_C . So, at resonance condition V_L equal to V_C it has to be, so that I want to show you ok.

So, let me go to the resonance condition at 800 Hertz at 800 Hertz ok. So, this is its a change earlier it was 292, but here now its the 280, 85, 86 ok. We have to give time to stabilize it. So, sometimes is reading changes because of heating effect if you pass current for longer time, so no it is a it has come nicely 292 ok.

So, now this is the V_R . Now, what is the; what is the V_C and V_L that I want to measure. So, I will disconnect from here; I will disconnect from here, let me connect here. So, this is one end of the capacitor, this is the other end of the capacitor. And I want to measure, I have to go to the what happens. So, you can see this it is around 9 is the it is in volt it is a coming sorry, we should not disturb the circuit, then it is coming around say 10 volt 10.2 volt ok, so its a in its a in volt range ok. So, its the 10.22 volt. So, this V_C is 10.22 volt at resonance condition.

So, now let me measure the V_L , let me measure the V_L and check it. So, I want to measure V_L , so I have to connect with this ok, but here I will feel difficulties to connect probably ok. Let me just hold it; let me just hold it, but it should be it is a small voltage, so it should not be problem, if I hold with hand.

So, you see that V_C was, but it should not so it is 9.22. Earlier it was 10.22, it is 10.22, but I should connect properly, because some resistance is coming in probably I should here, now it is a 9.34. Anyway, so 10.22 10 volt, and this is 9.3 volt; 9.3 volt. So, it may not be these resonances perfectly at this frequency, so it can be probably 800 something ok, 805 or 795 so one has to tune.

And you have to; you have to, but I could show you properly, but unfortunately its an no my hand is touch here 9.44 and 10.22 is very close. So, it has to be equal V_L and V_C has to be equal. So, this difference it may be due to the just my connection, it is a loose connection. It may be for due to that or we have to slightly adjust the frequency, it may

not be 800 exactly maybe 800 3 4 5, because at the peak position this is very sensitive this current is very sensitive.

So, more or less I could show you that this V_L and V_C means, X_L is equal to X_C at the resonance frequency ok. So, for this the experiment about the LCR main interest is to show the resonance and you could show the resonance, and this resonance is frequencies around 800. So, if you plot it and then accurate frequency can find out from the peak of this plot. So, that if I was doing that one, but I do not think this I cannot open that is the problem this ok, so but I say if I want to show you this ok this is very tight ok.

So, yes now its a 9.9 10.2 now it is 9.9, so that is what here this connection is factor ok. So, I think this 9.9, I could show you, but only problem is we have to; we have to do proper connection you have to do proper connection, otherwise yeah let me just leave it here. Yes it is varying, because this connection is not so strong, it is a loose that is a so forget, but this X_L is equal to X_C . So, V_L is equal to V_C . So, more or less that I could show you. And that it will be if exactly equal, when you will be at exact frequency, so one has to tune and find out. So, I will stop here.

Thank you for your attention.