

Course Name: Power Electronics Applications in Power Systems

Course Instructor: Dr. Sanjib Ganguly

**Department of Electronics and Electrical Engineering,
Indian Institute of Technology Guwahati**

Week: 10

Lecture: 01

Power Electronics Applications in Power Systems

Course Instructor: Dr. Sanjib Ganguly
Associate Professor,
Department of Electronics and Electrical Engineering,
IIT Guwahati
(Email: sganguly@iitg.ac.in)

Activate Windows
Go to Settings to activate Windows.

Lec 31: TCSC reactance and harmonics analysis

So welcome again to my course Power Electronics Applications in Power Systems. In last three lectures, I was discussing the basic operation of a series connected power electronic based compensators that is TCSC which is used in power system for various applications or various reasons. So, in this particular lecture also, I will discuss or rather I will finish the discussion on the analysis of TCSC. So, let us proceed. So, in last lecture, I stopped at this point, deriving the expressions for voltage across the capacitor. As you know, the basic schematic diagram of this TCSC is something like this.

We have a fixed capacitor, this fixed capacitor and we have a variable reactor, we call it a TCR, whose reactance should be controlled by the firing angle control of the thyristors. So voltage across capacitor means voltage across this particular series unit and which is of course the voltage across this TCR unit as well. So the expression for voltage across the capacitor we derive. There are two equations when this TCR is conducting the voltage across capacitor is this when TCR is non-conducting that is $I_{TCR} = 0$. So, voltage across the capacitor is that. So, this is voltage across the capacitor that expression is when TCR is conducting and this is the voltage across the capacitor that expression when TCR is non-conducting. So, you can see, if you look at both the equations, this equation as well as this equation, you can see that these are not ideally

sinusoid. So, this would be some kind of distorted sinusoid. So, therefore, some amount of harmonics would be there within the expression. And we will analyze this harmonic as well. So, in this particular lecture, basically, I will discuss TCSC reactance and harmonics. So, the goal of today's lecture is to discuss the TCSC reactants and the harmonics. Now, what do you mean by TCSC reactants? Already I explained one of my previous lectures, when I discussed this basic operating principle of TCSC, that this TCSC reactants is effectively Z-TCSC, which is a parallel combination of this X_c and X_{tc} . Now, it could be positive. When it is positive, then it is inductive. It could be negative as well. When it is negative, it is capacitive mode of operation. So, we have two Vernier control modes, which I already explained. So, for these two Vernier control modes, the TCSC reactants would be in different Or TCSC reactants will have different sign, one is positive when it is operating at inductive vernier control and it is negative when it is operating at capacitive vernier control.

So, these are the two operating modes of TCSC and we will determine the expression of TCSC in particular as a function of this parameter beta. As I explained this beta is the angle of advance, it is an important parameter for TCSC analysis. And this beta can be varied. Now, with the variation of the beta, what would be the impedance or what would be the expression of the impedance of the TCSC that we are trying to determine today. Now, in order to determine that, as I explained, the voltage across this capacitor is non-sinusoidal.

Lec 31: TCSC reactance and harmonics analysis

The fundamental component of the voltage across the capacitor can be obtained as,

$$V_{c1} = \frac{4}{\pi} \int_0^{\pi/2} V_c(t) \sin \omega t d(\omega t)$$

$$= \frac{4}{\pi} \int_0^{\beta} \underbrace{V_c(t) \sin \omega t d(\omega t)}_{\text{TCR is Conducting}} + \frac{4}{\pi} \int_{\beta}^{\pi/2} \underbrace{V_c(t) \sin \omega t d(\omega t)}_{\text{TCR is Non-Conducting}}$$

$$= \frac{4}{\pi} \int_0^{\beta} \left(\frac{I_m X_c}{\lambda^2 - 1} \right) \left[-\sin \omega t + \frac{\lambda \omega \beta}{\cos \lambda \beta} \sin \lambda \omega t \right] \sin \omega t d(\omega t)$$

$$+ \frac{4}{\pi} \int_{\beta}^{\pi/2} \left(V_c' + I_m X_c \{ \sin \omega t - \sin \beta \} \right) \sin \omega t d(\omega t)$$

Please Verify this Solution $\Rightarrow V_{c1} = I_m \left[X_c - \left(\frac{X_c^2}{X_c - X_L} \right) \left(\frac{2\beta + \sin 2\beta}{\pi} \right) + \left(\frac{4 X_c^2}{X_c - X_L} \right) \left(\frac{\cos^2 \beta}{\lambda^2 - 1} \right) \left(\frac{\lambda \tan \lambda \beta - \tan \beta}{\pi} \right) \right]$

So, therefore, we have to find out the fundamental component of the voltage across the capacitor. So, let us find out this. So, the fundamental component of the voltage across the capacitor can be obtained as. This is we can obtain from Fourier series analysis as you

know. So, this is V_c , 1 stands for the fundamental, V_c stands for voltage across the capacitor. So, this is equal to $\frac{4}{\pi} \int_0^{\pi/2} V_c \sin \omega t \, d\omega t$. Now, you know that why we keep this limit 0 to $\pi/2$ because we have some symmetry of this capacitor voltage as well. So, look at this voltage waveform. So, here basically we restrict our limit from this ωt is equal to 0 to ωt is equal to $\pi/2$ for this two limit. Now, within this two limit we have these two different expressions for VCT. As we know that this VCT expression when TCR is non-conducting would be something else and rather than when TCR is conducting.

Now you can see that here TCR will conduct from the time interval 0 to β . So this is the angle β . So up to this, this TCR will conduct. And then in this particular interval that is β to $\pi/2$, TCR will not conduct. So, TCR will be non-conducting. So, therefore, I can write, I can split this interval of this integration into two parts, one is $\frac{4}{\pi} \int_0^{\beta} V_c \sin \omega t \, d\omega t$. Another is $\frac{4}{\pi} \int_{\beta}^{\pi/2} V_c \sin \omega t \, d\omega t$ that is voltage across the capacitor instantaneous voltage, of course, $V_c \sin \omega t$. Now, you understand that in this particular interval, TCR is conducting. In this particular interval, TCR is non-conducting. So, therefore, this VCT expression whichever we will be using in this particular interval that is 0 to β would not be applicable when we use the interval β to $\pi/2$.

So, if I write the actual expressions for VCT for these two intervals, so it will be something like this $\frac{4}{\pi} \int_0^{\beta} V_c \sin \omega t \, d\omega t$. Now, if you go back and see what the expression for VCT was when TCR was conducting, TCR is conducting. So, this is the expression, this is the expression. So, let us copy it and write over here, it will be equal to $\frac{I_m X_c}{\lambda^2 - 1} [\sin \omega t - \sin \beta + \cos \beta] \frac{\lambda \cos \beta}{\cos \lambda \beta} \sin \lambda \omega t$. So, this is the expression for VCT when TCR is conducting if you look at. So, this is what the expression of VCT is when TCR is conducting. So, therefore, we will use it and this would be multiplied with $\sin \omega t \, d\omega t$. So, this is one part of this expression. Another part would be $\frac{4}{\pi} \int_{\beta}^{\pi/2} V_c \sin \omega t \, d\omega t$. Now, in this particular interval, TCR is non-conducting. So, therefore, the expressions for VCT would be what when it was applicable for TCS, TCR is non-conducting, that means this expression, that means this expression. So I will write this directly. So this will be V_c dash. V_c dash is some parameter which is independent of time.

You can look at this expression is time-independent. So this expression is time-invariant. So, therefore, this is something like a constant, you can find this value and put it over here directly. But this part, this part is a part which is time variant at the $\sin \omega t$ component. So, therefore, this plus $I_m X_c \sin \omega t - \sin \beta$ this is the expression or I should use a different parenthesis for this, because already the square parenthesis is used. So, I will use this curly bracket. So, this is the expression for this

VCT when TCR is non-conducting, right? This is already we determined in the last lecture. So, when we put this, then this has to be multiplied with $\sin \omega t$ d ωt , ok. Now, this is a very big integration. I am leaving to you all the learners to do it by yourself. In fact, in my live classes, I usually tell my students to derive it and then I will match this result that I am having with them. Because this is a very long integration, you need to put considerable effort into solving this. Therefore, we will be coming up with an expression which will be also very large. Do not remember this particular equation, there will be no use of it. You have to understand the concept underlying this equation that is all.

I will never ask you to derive this expression in your examination or I will not set any questions regarding this particular explanation which you need to remember. So, there is no need of that, but this underline concept should be understood. Then this is the basic goal of this particular lecture. Now, I have the solution with me, I can directly write over here and I will leave it with you to match the solution with your solution. So, the solution that I have is I_m multiplied by x_c minus x_c square divided by x_c minus x_l like this, 2β plus $\sin 2\beta$ divided by π plus $4x$ square $\times e$ minus x_l multiplied by $\cos$ square β divided by λ square minus 1 multiplied by $\lambda \tan \lambda \beta$ minus $\tan \beta$ divided by π . This is what the expression which you need to verify. Now, I will leave it to you to verify. Please verify this solution. So, I have this solution which I can show to you, but what you need to do is you need to verify it.

It is a very long equation. As far as this power system learners is concerned, because we do not have such a very big equations having so many you know components, so many things within this equation usually in power system. So, therefore, this is relatively a very long equation. You need to carefully verify it, but I think that you should be able to derive it even though you do not remember this, but you should be able to derive this equation whenever is required. So, this is something is the goal of this particular lecture. Now, what is this V_{c1} ? V_{c1} is the fundamental component of the voltage across the capacitor. And what was our goal? Our goal is to find out the TCSC reactance, right? Now, how can we find out this TCSC reactance? We can find out you by taking the ratio of the voltage across the capacitor and this I_m , I_m is the current flowing through this particular line, because we are interested to find out the this impedance of the TCSC. Now, what would be the impedance of the TCSC? Obviously, the impedance of the TCSC would be the voltage across the TCSC and current flowing through the TCSC. So, voltage across the TCSC is V_{c1} , current flowing is basically this I and the maximum value of it is I_m . So, that is why it is this I_m is the I_m is representation of the current that is the peak value of the current flowing through the TCSC and V_{c1} is the representation of the voltage across the TCSC. Their ratio would be of course the representation of the overall impedance of the TCSC.

So, therefore the impedance or one may tell that this is also reactance because both are representing same thing because we are assuming that the TCSC is lossless. So, therefore, the impedance of TCSC is Z_{TCSC} . And, this is, it is found out to be the ratio of this V_c to I_m . And, in, if you look at this expression that we derived right now, this is, the left hand side we have V_c , right hand side we have I_m . So, therefore, this ratio can be easily determined from that particular expression. And, this ratio is the representation of this impedance or reactance of the TCSC.

Now, if you find this and do some further simplification, then the expression we get of Z_{TCSC} as a ratio of X_c . Now, what is X_c ? X_c is the reactance of the fixed capacitor. So, this expression after doing some simplification is coming out to be $1 + \frac{2}{\pi} \lambda^2 \cos^2 \beta$ divided by $\lambda^2 - 1$ multiplied by a bracket $2 \cos \beta \sin \beta$ minus $\tan \beta$ minus $\sin 2\beta$ by 2. Now, what is that ratio? This ratio is the, this is basically representing, this is basically representing ratio TCSC impedance to the reactance of the fixed capacitor or capacitor of TCSC. Now, you know that at this point this TCSC you know schematic diagram is something like that we have a fixed capacitor in parallel to a TCR.

Now, if you consider the reactance of this particular fixed capacitor is X_c and overall impedance of this is Z_{TCSC} . Then the ratio of this Z_{TCSC} to X_c is found out to be this and this we obtain from this previous expression, from this expression after doing some sort of simplification. We converted this X_c in terms of λ and wherever is possible that we convert all this parameter into λ and β . So therefore, this expression if you look at then you can see Z_{TCSC} / X_c ratio is function of λ and β , only function of λ and β . Now what is λ , if I hope that you can remember it appropriately, this λ already we derived in this one of this expression, it is the ratio of the ωR to ω , where ωR is equal to $1 / \sqrt{LC}$, which is resonating frequency. So it is basically representation of that ratio of the ωR to ω that means ωR is what times of this power frequency that is what. So, basically λ is a constant because it is a design parameter. It depends upon this $1 / \sqrt{LC}$ which are fixed. So, λ is constant. Only parameter here is variable is β . So, if we go back and see. So, therefore, λ is design parameter and constant for a particular TCSC. So, therefore, this ratio is variable only with this β . Now, what is β ? β is the angle of advance as I said this is a very important concept and we will derive all this later on parameter in terms of β and the choice of β is important for controlling the TCSC. So, this ratio is an important parameter which can be varied or controlled with the appropriate choice of the β depending upon the requirement.

This is something one needs to understand. Now we will be doing some case study here. What is the case study? First case study is let us consider β is equal to 0. Now what will happen? And second case study is let us consider β is equal to $\pi/2$. Because if

you look back and see the waveforms that I derived, this possible value of this beta can be 0 to pi by 2. When beta is equal to 0, that means TCR is non-conducting. When beta is equal to pi by 2, then that means TCR is fully conducting. So, that means beta is equal to 0 means TCR is non-conducting or TCR is fully off. Now, what mode of operation it is? It is a fixed capacitor mode of operation. It is a fixed capacitor mode of operation because if your TCR is fully off that means this TCSC is nothing but a fixed capacitor. So, overall impedance of the TCSC should be equal to the reactance of the fixed capacitor or impedance of the fixed capacitor.

Lec 31: TCSC reactance and harmonics analysis

The impedance (reactance) of TCSC is

$$Z_{TCSC} = \frac{V_{c1}}{I_m}$$

$$\frac{Z_{TCSC}}{X_c} = 1 + \frac{2}{\pi} \left(\frac{\lambda^2}{\lambda^2 - 1} \right) \left[\frac{2 \cos^2 \beta}{\lambda^2 - 1} (\lambda \tan \lambda \beta - \tan \beta) - \beta - \frac{\sin 2\beta}{2} \right]$$

Ratio of TCSC impedance to the reactance of the fixed capacitor

$$\left(\frac{Z_{TCSC}}{X_c} \right) = f(\lambda, \beta)$$

λ = design parameter and constant for a particular TCSC

Case study:

(i) $\beta = 0$ [TCR is fully off]: Fixed Capacitor mode of operation

$$\frac{Z_{TCSC}}{X_c} = 1 + \frac{2}{\pi} \left(\frac{\lambda^2}{\lambda^2 - 1} \right) \times 0 = 1 \Rightarrow Z_{TCSC} = X_c$$

(ii) $\beta = \frac{\pi}{2}$ [TCR is fully ON]: Inductive mode of operation

$$\frac{Z_{TCSC}}{X_c} = 1 + \frac{2}{\pi} \left(\frac{\lambda^2}{\lambda^2 - 1} \right) \left(-\frac{\pi}{2} \right) = 1 - \frac{\lambda^2}{\lambda^2 - 1} = \frac{\lambda^2 - 1 - \lambda^2}{\lambda^2 - 1} = -\frac{1}{\lambda^2 - 1}$$

$\lambda = 3$ $\frac{Z_{TCSC}}{X_c} = -\frac{1}{9-1} = -\frac{1}{8} = -0.125$

(iii) $\beta = \beta_c$ for which $\frac{Z_{TCSC}}{X_c} \rightarrow \infty$ $\beta_c = \frac{\pi}{2\lambda}$

Does it happen? Let us see. Now, if we put beta is equal to 0, you look at this cos beta will be equal to 1. 10 lambda beta this part would be 0. So, 10 beta will be also 0. So, if 0 multiplied with this would be 0. So, therefore, this would be also 0, this would be also 0. So, inside this bracket whatever term we will be having corresponding to beta is equal to 0 will be 0. So, that means this ratio there Tc Sc by Xc will be equal to 1 plus 2 divided by pi lambda square divided by lambda square minus 1 multiplied by 0, which is equal to 1. So, this gives that ZTCSC is equal to XC, which is the fixed capacitor mode of operation. So, this gives one indication that this expression is correct, but you need to also verify whether it is true or not. Now, the second case study is when beta is equal to pi by 2.

Now, what do you mean by beta is equal to pi by 2? At this case, TCR is fully on. So therefore, what mode of operation it is, if you look back at this waveform, which we had drawn earlier, this is what the, you know, this TCR current for this value of beta. Now, if beta is equal to pi by 2, then this current would be somewhere like this, up to So, I can draw this by some other color, let us say here, when this beta, this will be equal to I TCR,

this would be equal to I TCR of t corresponds to β is equal to $\pi/2$. So, then this would be equal to the I TCR current. So, when it happens that means TCR is fully conducting. So, in that case there would be no harmonics of course, that is one of the advantages. But when it happens then what would be the value of this ZTCSC that is what something important to us. So, this is you know fixed capacitor mode and when TCR is fully conducting we have to find out what mode of operation it is. So, if we put β is equal to $\pi/2$. Then what we will get? You can see this part would be equal to 0 and now $\cos \beta \cos \pi/2$ is what? It is 0.

So, this has to be multiplied with 0 multiplied this entire block. So, this would be 0, this would be 0. So, only this β will remain. So, then this equation according to me will be equal to equal to Z T C S C divided by X C is equal to or I should write it here ZTCSC divided by XC is equal to $1 + 2 \pi \lambda^2 \lambda^2 \sin^2 \beta$ and then within this bracket it will be multiplication with $\pi/2$. Then, what we will get? This $\pi/2$ and this would be cancelled out. So, this will be equal to $1 - \lambda^2$ divided by $\lambda^2 - 1$. So, this is λ^2 minus this, this is minus 1 divided by $\lambda^2 - 1$. So, this ZTCSC and XCSC will be this. Now, what we can interpret from it? Let us consider λ is equal to 3. That means, this ωr is 3 times of the power frequency. So, then this ZTCSC to this XC ratio would be equal to minus 1 upon 3 square, that is 9 minus 1. So, that is minus 1 divided by 8. Now, minus 1 by 8 is a fractional number, my point around 0.125 or something like that.

So, therefore, it is a fractional number, but negative. Now, what this negative sign signify? This negative sign signify that this overall impedance of T c s c would be minus of this x c. Now, x c is a capacitive impedance. So, negative of that would be an inductive mode. So, therefore, this is a inductive mode of operation. This is an inductive mode of operation. Now, there would be another you know value of β which will be also important to us. This β is the value of this β_c which is called the cutoff value of this β for which this ratio that is ZTCSC to XC ratio would be infinite. That is why this resonance will happen. This is also an important case study that we can do. Now, from this, we can find out at what value of this β , this ratio would be infinitely large.

In a practical sense, it cannot be infinite but it can be infinitely large. That means the resonance will happen which makes it this isolated from the system and that means this will create a discontinuity. The placement of this TCSC will cause a discontinuity at the point where it is placed in the transmission line. So, we have also this point is interest to us. Now, in order to find this, what we will do is, we have to do some more derivations. So, let us do some derivation to arrive at the conclusion that what could be the value of β_c to guess at least what could be the value of this β for which this would be equal to infinite. Now, we can see this mode of operation is prohibited and this we have to identify before and we should control or tune the parameter of TCSC such that this situation or this case will never appear. So, therefore, to find this what we can do, let us

do some derivations of ZTCSC to X_c . So, I am just rewriting this expressions once again. So, $1 + 2 \text{ by } \pi \text{ lambda square divided by lambda square minus 1 multiplied by now}$ you can see here we have two terms; one is $\lambda \tan \lambda \beta$; another is $\tan \beta$.

So, what we can write this is $2 \cos^2 \beta \text{ divided by } \lambda^2 \text{ minus } 1 \lambda \tan \lambda \beta \text{ minus } 2 \cos^2 \beta \text{ divided by } \lambda^2 \text{ minus } 1 \tan \beta$. We did nothing but we just multiplied this multiplier, this multiplier one with this $\lambda \tan \beta$ and another with $\tan \beta$. Now, we write this minus β as it is and minus $\sin^2 \beta \text{ by } 2$ as it is. Now, what we will do? We will go ahead with this derivation once again. So, this will be $\lambda^2 \text{ minus } 1$. Now, this can be written as $2 \cos^2 \beta \lambda \tan \lambda \beta \text{ divided by } \lambda^2 \text{ minus } 1 \text{ minus}$. Now, you can see we can write this $\tan \beta \text{ by } \sin \beta \text{ by } \cos \beta$. So, if we write it, if we just write $\tan \beta \sin \beta \text{ divided by } \cos \beta$, then this $\cos \beta$ and this $1 \cos \beta$ in the numerator will be canceled out. So, in the numerator we will have $2 \cos \beta \sin \beta$ which can be written as $\sin 2 \beta \text{ divided by } \lambda^2 \text{ minus } 1 \text{ minus } \beta \text{ minus } \sin 2 \beta \text{ by } 2$.

Now, we have two $\sin 2 \beta$ term, one is this, another is this. So, let us aggregate these two. So, $1 + 2 \text{ divided by } \pi \lambda^2 \lambda^2 \text{ minus } 2 \cos^2 \beta \lambda \tan \lambda \beta \text{ divided by } \lambda^2 \text{ minus } 1 \text{ minus}$, if I take $\sin 2 \beta$ common outside a bracket, then here we will have $1 \text{ by } \lambda^2 \text{ minus } 1$, here we have $1 \text{ by } 2$, right. Then minus β we, I am keeping as it is. Now let us write it again $2 \text{ by } \pi \lambda^2 \lambda^2 \text{ minus } 1 \text{ multiplied by I will keep this as it is } 2 \cos^2 \beta \lambda \tan \lambda \beta \lambda^2 \text{ minus } 1 \text{ minus the } \sin 2 \beta \text{ I will write as it is}$. Now, if we just do this addition $1 \text{ upon } \lambda^2 \text{ minus } 1 \text{ plus } 1 \text{ upon } 2$, then it will be equal to $2 \text{ plus } \lambda^2 \text{ minus } 1 \text{ divided by } 2 \lambda^2 \text{ minus } 1 \text{ minus } \beta$.

So, again we write $2 \text{ by } \pi \lambda^2 \text{ divided by } \lambda^2 \text{ minus } 1$, this portion as it is $2 \cos^2 \beta \lambda \tan \lambda \beta \text{ divided by } \lambda^2 \text{ minus } 1 \text{ minus } \sin 2 \beta$ with the multiplication of this will be $\lambda^2 \text{ plus } 1 \text{ divided by if I bring this two outside divided by } \lambda^2 \text{ minus } 1 \text{ minus } \beta$. So, this is the expression I wanted to derive. Now look at this particular expression. Here only parameter is varying, only variable parameter is β . So, in this particular expression, so the only variable in this expression is β . Apart from that, everything is constant. λ is a design parameter, it is constant. All other parameters are constant. So, only parameter which is can be varied is β . Now, what is the range of the β ? β can be varied from 0 to $\pi \text{ by } 2$. β can be varied from 0 to $\pi \text{ by } 2$. Now, as you can already have seen neither β is equal to 0 or β is equal to $\pi \text{ by } 2$, two extreme limits gives the ratio ZTCSC to X_c infinite or infinitely large. Then what would be the value of β for which this would be infinity? If you look at this particular expression, you can see this, if we vary β from 0 to $\pi \text{ by } 2$, this minus β , this component will never be


infinite. There is no chance, it is a parameter. Now, $\sin 2\beta$, so $\sin 2\beta$ cannot be infinite within this range, 0 to $\pi/2$. In fact, $\sin 2\beta$ can never be infinite, so as this $\cos^2 \beta$. So, what parameter can be infinitely large so that this ZTCSC to XC ratio will be infinite. So, if you look at then only this $\tan \lambda \beta$ is a parameter which can be infinite. $\tan \theta$ can be infinite. Under what condition $\tan \theta$ can be infinite? You know when θ is equal to $\pi/2$. Then you know that this $\sin \pi \tan \theta$ when θ is equal to $\pi/2$ that is $\tan \pi/2$ is equal to $\sin \pi/2$ divided by $\cos \pi/2$.

Now $\sin \pi/2$ is equal to 1, $\cos \pi/2$ is equal to 0, so this can be infinite. So therefore, in this particular expression, if this $\lambda \beta$ is equal to $\pi/2$, then what will happen? ZTCSC by XC can be infinity. So, this is an important relation. This is an important relation and therefore, this β_c that is known as this cutoff value of this β , which should never be appeared is equal to $\pi/2$ to λ . This is an indirect way of determining it, but you can mathematically also derive this expression, this β_c is equal to $\pi/2 \lambda$ from this particular expression if you want to solve. Now what we will do next? We got these three important cases that at β is equal to β_c , this is infinity and we find out this β_c is equal to $\pi/2 \lambda$.

So, this what we derive. We know that what will happen β is equal to 0, we also know that what will happen at β is equal to $\pi/2$. Then what we can do is that we can plot this ZTCSC to XC ratio with respect to β . Now, how would be the plot? Let us see. So, let us have this plot of this ratio ZTCSC to XC versus this β . So, one axis I will write this particular ratio that is ZTCSC to XC. It can be positive, it can be negative as well. In another axis, we will keep β . And β can be varying from 0 to let us say $\pi/2$. And this is, suppose this β is equal to β_c for which this resonance will happen. Now, as we know that when this β is equal to 0, then this ratio will be equal to 1. So, this is 1. Let us say this is 2, this is 3, this is 4, and so on. And here also this is minus 1, this is minus 2. This is minus 3, this is minus 4, and so on.

Now at β is equal to 0, this is our operating point. This is what would be that value of this ratio. Then what will happen if you take this particular expression and plot it by using any coding language you know either in MATLAB or any C or C++, then this plot we will see something like this. This plot will be something like this. And as we know that when β is equal to $\pi/2$, this would be negative, but this value would be something close to 0. So, this plot of this side would be something like that. So, the plot of this ZTCSC to Xc which is an important you know parameter would be something like this and when β is equal to β_c their value will be infinitely large. So, that is why we keep it as a discontinuity there. So, this plot is also important for the application of TCSC in particular for controlling the TCSC parameters, so that our operation should be within this you know feasible range of these characteristics. Now the question is, we have two

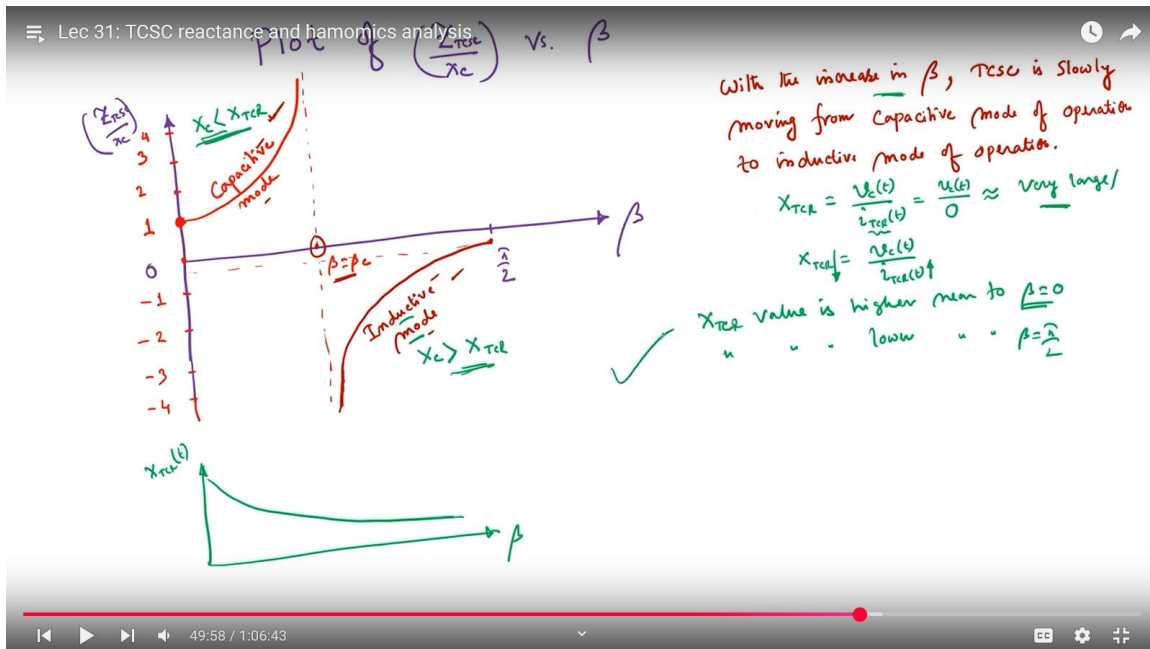plots, one is this red, another is this. Which one is, what mode of operation? Now we can see that in this particular mode of operation, ZTCSC to XC ratio is positive.



That means ZTCSC is having same sign with XC. So therefore, it is a capacitive Vernier mode, capacitive mode of operation. Whereas, in this particular mode, when ZTCSC and XC ratio is negative, that means, the sign of this impedance, overall impedance of the TCSC is negative of the reactance of the fixed capacitor, which is eventually an inductive, you know, reactance. So, therefore, this would be inductive mode of operation. So, this is inductive mode of operation. So, in this Vernier control mode of operation of TCSC either the operation should be here or here. In general it is in capacitive mode. But this point has to be avoided. So, you should have a sufficient you know margin to avoid this state, where this ratio is infinite and this may cause a discontinuity in the transmission line, which is not acceptable at all. So, this is something I want to tell. In fact, what is actually happening over here is that, with the change, with the increase in this beta, what is actually happening is this ZTCSC is slowly moving from capacitive mode of operation to inductive mode of operation or inductive Vernier control mode of operation.

I am just writing in a short inductive mode of operation. Now, why it is actually happening if you look at this waveform once again which I have drawn. At the very beginning when I started the analysis, when beta is equal to 0 means, what does it mean actually? This TCR is non-conducting or TCR is fully off. When TCR is fully off, it is capacitive mode. Now, when TCR is slowly building its current like this, slowly building its current, then what is actually happening when this TCR current is 0, then the net reactance of the TCR is the voltage across TCR which is the voltage across this capacitor

that is V_c divided by the current that is flowing through the TCR that is I_{TCR} . That ratio would be infinitely large when it is operating, β is operating near to 0. And therefore, in this particular, this interval when β is very near to 0 and it is operating in capacitor mode.

So, basically what is actually happening is, since this impedance or reactance of this TCR is, because you can see as I show, show you that X_{TCR} is basically equal to this voltage that is V_{CT} divided by I_{TCR} . Now, when I_{TCR} is close to 0, then this will become very large, very large or infinitely large, whatever the value of V_{CT} might be or infinitely large. Now, when you move this value of the I_{TCR} from 0 to $M1$ value, still this X_{TCR} is usually large. So, therefore, in this particular mode, X_c is lower than X_{TCR} , this condition is getting satisfied and that is why, you know, the capacitive mode of operation is taking place. Whereas, if we keep on this increase in the value of β , then this x_{TCR} , which is the ratio of v_{CT} divided by i_{TCR} , when i_{TCR} is sufficiently large, then x_{TCR} would be lower.

So, therefore, this will be the case when x_c is greater than this x_{TCR} . That is why it is operating in the inductive mode of operation. So, at this happens, so this x_{TCR} value is higher than higher near to β is equal to 0, what I have shown over here, and x_{TCR} value is lower to β is equal to $\pi/2$, which is happening over here. And that makes these two conditions satisfied, which I discussed long time before, when I started this discussion on TCSC. And that is why it is actually happening. Now, so therefore, with the increase of this β , TCS is slowly moving capacitive mode, because actually this TCR reactance, if you plot this TCR reactance, it is getting reduced.

So, if this, if you plot this TCR reactance, X_{TCR} of t with respect to this β , then what we will see, its value is getting reduced. So, that is what is actually happening and this is what the reason is and that is why these two modes of operation is taking place. Now, next if you remember I explained that this when I discussed this waveform I said that this V_{CT} will not be sinusoidal, TCSC it will be only sinusoidal when TCSC operation at fixed capacitor mode. Then the question would be how would be the characteristics of V_{CT} or how would be the waveforms of V_{CT} . So, that is also an important to us. So, this you can eventually verify by taking an example. So, what I can show over here is that V_{CT} waveforms for capacitive and inductive mode of operations. Now, how would be, let us see. So, let us start with this inductive mode of operation. So, what is actually happening in the inductive mode of operation or let us start with this capacitive mode of operation.

So, in capacitive mode of operation, if I draw at this waveform once again. So, suppose Suppose this is our line current is, this is our line current I_t , I of t that is line And, then this for this particular line current as you know when it is operating at this capacitive mode of operation. So, what we know is this would be if we go back and see. Suppose

this is our line current and then this would be our, this green line is showing that this would be our, this ITCRT. So therefore ITCRT would be something like this. I T C R T will be something like this. This is minus beta, this is beta. So, this would be something like this. So, therefore, what would be the net, this current, as we know, if we just draw this, this schematic diagram of this, this is our fixed capacitor, that is the voltage across this is $V_c t$, and this is our, this T c r unit, it is drawing a current, which is equal to I T c r t And, this is basically this I of t. Now, this the difference of this I of t, I of t minus this I TCR t is basically representation of current flowing through the capacitor. Now, how would be the you know this difference that you can see over here, if you have if you take the difference of this, then this would be something like this. Up to this it will be like this, then it would be something like this and then again this would be something like this. So, this green curve is basically representation of current flowing through the capacitor. And integration of this will representation of the voltage across the capacitor which would be you know that there would be a phase displacement of this π by 2, but if you look back I already explained this, but this characteristics would be almost similar to this the current flowing through the capacitor. So, it will be having a phase displacement of this π by 2. So therefore, so this is π by 2. So therefore, this capacitor current, capacitor voltage will be something like this. It will be like this. Similarly, it will be like this. So this is what would be the capacitor voltage or V_c of t.

Now, similarly, this will happen for the capacitive mode of operation. This is for the capacitive mode of TCSC operation. Now, similarly, we can also draw similar characteristics for inductive mode of operation, and similar waveforms. So, suppose this is what this line current that is I of t. Now, we know that we already explained at the very beginning, if you can remember that, for the inductive mode of operation, the direction of the line current and the direction of this TCR current would be different than this capacitive mode of operation.

Therefore, this current would be something like this, ITCR will be something like this. This will be ITCR or actually, I should draw it in a bigger way because here now ITCR will be the considerably higher magnitude, and there will be again this ITCR, this will be again ITCR. So, therefore, the net current, the difference of IT and ITCR which will be the current flowing through the capacitor would be something like this. it would be something it will be follow like this profile and then it will getting be reduced like this then it will have the same profile like this then it will follow this again then it will be again reduced it will be something like this. And accordingly this voltage across this capacitor or $V_c t$ will be something like this, it will follow it will there it will be. So, I although I have not written, but you understand this will be the expression for current flowing through the capacitor. So therefore, the capacitor voltage would be almost similar in nature.

So, it will be something like this or it will be something like that. So, this will be capacitor voltage. So, this will be the actual, you know, waveform for the capacitor voltage, which I told you that I will derive. So, and this would be this, you know, VCT waveform for inductive mode of operation, inductive mode of TCSC operation. Now you can see there is a difference of these waveforms altogether and in between these two different modes of operation of TCS. Now one last thing that I will discuss in this particular lecture before I stop that is the harmonics in TCS. So you know that this harmonic is generated in TCSC because of the TCR operation. So I should write the harmonics in TCSC are generated due to the partial conduction of switches in TCR. This is very important to understand that it is because of because if TCR is responsible for this having harmonics in TCSC because and most importantly if the TCR is operated at partially conducting mode then this harmonics will be generated. But we need to find out this harmonics and we need to find out the mitigations of the harmonic as well.

Lec 31: TCSC reactance and harmonics analysis

Harmonics in TCSC

* Harmonics in TCSC is generated due to partial conduction of switches in TCR

Fundamental TCR current

$$(I_{TCR})_1 = \frac{4}{\pi} \int_0^{\frac{\pi}{2}} i_{TCR}(\omega t) \cos \omega t d(\omega t)$$

$$= \frac{2}{\pi} \left(\frac{\lambda^2}{\lambda^2 - 1} \right) I_m \left[\beta + \sin 2\beta - \frac{\cos \beta}{\omega \lambda \beta} \left\{ \frac{\sin(\lambda+1)\beta}{\lambda+1} + \frac{\sin(\lambda-1)\beta}{\lambda-1} \right\} \right]$$

$\Rightarrow$ Please verify it!

n^{th} Harmonics of TCR current

$$(I_{TCR})_n = \frac{4}{\pi} \int_0^{\frac{\pi}{2}} i_{TCR}(\omega t) \cos n(\omega t) d(\omega t)$$

$$= \frac{2}{\pi} \left(\frac{\lambda^2}{\lambda^2 - 1} \right) I_m \left[\left\{ \frac{\sin(n+1)\beta}{n+1} + \frac{\sin(n-1)\beta}{n-1} \right\} - \frac{\cos \beta}{\omega \lambda \beta} \left\{ \frac{\sin(n+2)\beta}{n+2} + \frac{\sin(n-2)\beta}{n-2} \right\} \right]$$

$n=3, 5, \dots$

But this harmonics will be less as compared to this normal operation of the TCR in shunt. But we need to analyze this harmonic. So, first we need to find out the fundamental TCR current which is I_{TCR} , you can make it 1 to represent it is fundamental, it is equal to $\frac{4}{\pi} \int_0^{\pi/2} I_{TCR} \cos \omega t d\omega t$. So, this is by using this Fourier series expression and you know that I_{TCR} expression already we have drawn, we have derived, this is what the expression for I_{TCR} . So, if I put it over here, then I will come up with the expression for this fundamental TCR current and that expression also you can derive, I ask you to derive and this expression of this is coming out to be $\frac{2}{\pi} \frac{\lambda^2}{\lambda^2 - 1} I_m \left[\beta + \sin 2\beta - \frac{\cos \beta}{\omega \lambda \beta} \left\{ \frac{\sin(\lambda+1)\beta}{\lambda+1} + \frac{\sin(\lambda-1)\beta}{\lambda-1} \right\} \right]$. I am

just writing whatever expressions I got, you also verify it, $\sin \lambda + 1 - \beta$ divided by $\lambda + 1$ plus $\sin \lambda - 1 - \beta$ divided by $\lambda - 1$.

So this expression I got, but please verify it. Similarly, this n-th harmonics of TCR current can be obtained as this I T c r of n-th is equal to $\frac{4}{\pi} \int_0^{\pi/2} I_{TCR} \cos n \omega t \, d\omega t$, which is if you again I will ask you to verify it is coming out to be $\frac{2}{\pi} \frac{\lambda^2 \sin n - 1 - \beta}{\lambda^2 - 1} + \frac{2}{\pi} \frac{\lambda^2 \sin n - 1 - \beta}{\lambda^2 - 1}$. So, let us use some different parenthesis. This is $\frac{-\cos \beta}{\cos \lambda \beta}$ multiplied by $\sin n + \lambda \beta$ divided by $n + \lambda$ plus $\sin n - \lambda \beta$ divided by $n - \lambda$.

Where n is equal to 3, 5, 7 all are harmonics. This is again I will ask you to verify. So, these are the different harmonics that we will have in the TCSC and we cannot do anything else in that we have to bear with this harmonics and but we should analyze it so that we can control this TCSC such that less harmonics would be generated in it. So, that is all about this TCSC analysis and its operation. So, in the next lecture, I will discuss the application of TCSC in power systems. So, till then thank you very much for attending this lecture. So, thank you very much for your attention, we look forward to see you in the next lecture.

❖ TCSC Reactance and Harmonics

As we know, the instantaneous voltage across the capacitor can be written as:

$$v_c(t) = \frac{I_m X_C}{\lambda^2 - 1} \left[-\sin \omega t + \frac{\lambda \cos(\beta)}{\cos(\lambda \beta)} \sin(\lambda \omega t) \right], \quad \omega t \in [-\beta, \beta] \quad \Leftarrow \text{TCR is conducting, } i_{TCR}(t) \neq 0$$

$$v_c(t) = V'_c + I_m X_C [\sin \omega t - \sin \beta] \quad \Leftarrow \text{TCR is non-conducting, } i_{TCR}(t) = 0$$

$$\text{Where, } V'_c = \frac{I_m X_C}{\lambda^2 - 1} [-\sin \beta + \lambda \cos(\beta) \tan(\lambda \beta)] \Leftarrow \text{Time-invariant}$$

The fundamental component of the voltage across the capacitor can be obtained as,

$$\begin{aligned} V_{c1} &= \frac{4}{\pi} \int_0^{\pi/2} v_c(t) \sin \omega t \, d\omega t \\ &= \underbrace{\frac{4}{\pi} \int_0^{\beta} v_c(t) \sin \omega t \, d\omega t}_{\text{TCR is conducting}} + \underbrace{\frac{4}{\pi} \int_{\beta}^{\pi/2} v_c(t) \sin \omega t \, d\omega t}_{\text{TCR is non-conducting}} \end{aligned} \quad (1)$$

$$= \frac{4}{\pi} \int_0^\beta \frac{I_m X_C}{\lambda^2 - 1} \left[-\sin \omega t + \frac{\lambda \cos(\beta)}{\cos(\lambda \beta)} \sin(\lambda \omega t) \right] \sin \omega t \cdot d\omega t + \frac{4}{\pi} \int_\beta^\pi [V'_c + I_m X_C \{ \sin \omega t - \sin \beta \}] \sin \omega t \cdot d\omega t$$

$$\Rightarrow V_{c1} = I_m \left[X_C - \left(\frac{X_C^2}{X_C - X_L} \right) \left(\frac{2\beta + \sin 2\beta}{\pi} \right) + \left(\frac{4X_C^2}{X_C - X_L} \right) \left(\frac{\cos^2 \beta}{\lambda^2 - 1} \right) \left(\frac{\lambda \tan \lambda \beta - \tan \beta}{\pi} \right) \right] \quad (2)$$

The impedance (Reactance) of TCSC is Z_{TCSC}

$$Z_{TCSC} = \frac{V_{c1}}{I_m}$$

$$\begin{aligned} \Rightarrow Z_{TCSC} &= X_C - \left(\frac{X_C^2}{X_C - X_L} \right) \left(\frac{2\beta + \sin 2\beta}{\pi} \right) + \left(\frac{4X_C^2}{X_C - X_L} \right) \left(\frac{\cos^2 \beta}{\lambda^2 - 1} \right) \left(\frac{\lambda \tan \lambda \beta - \tan \beta}{\pi} \right) \\ &= X_C \left[1 - \left(\frac{X_C}{X_C - X_L} \right) \left(\frac{2\beta + \sin 2\beta}{\pi} \right) + \left(\frac{4X_C}{X_C - X_L} \right) \left(\frac{\cos^2 \beta}{\lambda^2 - 1} \right) \left(\frac{\lambda \tan \lambda \beta - \tan \beta}{\pi} \right) \right] \\ &= 1 - \left(\frac{X_C}{X_C - X_L} \right) \left(\frac{2\beta + \sin 2\beta}{\pi} \right) + \left(\frac{4X_C}{X_C - X_L} \right) \left(\frac{\cos^2 \beta}{\lambda^2 - 1} \right) \left(\frac{\lambda \tan \lambda \beta - \tan \beta}{\pi} \right) \\ &= 1 - \left(\frac{\frac{X_C}{X_L}}{\frac{X_C}{X_L} - 1} \right) \left(\frac{2\beta + \sin 2\beta}{\pi} \right) + \left(\frac{\frac{4X_C}{X_L}}{\frac{X_C}{X_L} - 1} \right) \left(\frac{\cos^2 \beta}{\lambda^2 - 1} \right) \left(\frac{\lambda \tan \lambda \beta - \tan \beta}{\pi} \right) \end{aligned}$$

$$\text{Now, } \lambda = \frac{\omega_r}{\omega}, \omega_r = \frac{1}{\sqrt{LC}}$$

$$\Rightarrow \lambda = \frac{1}{\omega \sqrt{LC}} \Rightarrow \lambda^2 \omega^2 LC = 1 \Rightarrow \lambda^2 (\omega L) (\omega C) = 1$$

$$\Rightarrow \lambda^2 (\omega L) = \frac{1}{(\omega C)} \Rightarrow \lambda^2 = \frac{\frac{1}{(\omega C)}}{(\omega L)} \Rightarrow \lambda^2 = \frac{X_C}{X_L}$$

$$\begin{aligned} \Rightarrow Z_{TCSC} &= 1 - \left(\frac{\lambda^2}{\lambda^2 - 1} \right) \left(\frac{2\beta + \sin 2\beta}{\pi} \right) + \left(\frac{4\lambda^2}{\lambda^2 - 1} \right) \left(\frac{\cos^2 \beta}{\lambda^2 - 1} \right) \left(\frac{\lambda \tan \lambda \beta - \tan \beta}{\pi} \right) \\ &= 1 - \left(\frac{2}{\pi} \right) \left(\frac{\lambda^2}{\lambda^2 - 1} \right) \left(\beta + \frac{\sin 2\beta}{2} \right) + \left(\frac{2}{\pi} \right) \left(\frac{\lambda^2}{\lambda^2 - 1} \right) \left(\frac{2\cos^2 \beta}{\lambda^2 - 1} \right) (\lambda \tan \lambda \beta - \tan \beta) \\ &= 1 + \frac{2}{\pi} \left(\frac{\lambda^2}{\lambda^2 - 1} \right) \left[\frac{2\cos^2 \beta}{\lambda^2 - 1} (\lambda \tan \lambda \beta - \tan \beta) - \beta - \frac{\sin 2\beta}{2} \right] \\ \Rightarrow \frac{Z_{TCSC}}{X_C} &= 1 + \frac{2}{\pi} \left(\frac{\lambda^2}{\lambda^2 - 1} \right) \left[\frac{2\cos^2 \beta}{\lambda^2 - 1} (\lambda \tan \lambda \beta - \tan \beta) - \beta - \frac{\sin 2\beta}{2} \right] \quad (3) \\ &\Downarrow \end{aligned}$$

Ratio of TCSC impedance to the reactance of the fixed capacitor.

$$\frac{Z_{TCSC}}{X_C} = f(\lambda, \beta)$$

λ = Design parameter and constant for a particular TCSC

Case study:

(i) $\beta = 0$ [TCR is fully OFF]: Fixed capacitor mode of operation

$$\frac{Z_{TCSC}}{X_C} = 1 + \frac{2}{\pi} \left(\frac{\lambda^2}{\lambda^2 - 1} \right) \times 0 = 1 \Rightarrow Z_{TCSC} = X_C$$

(ii) $\beta = \frac{\pi}{2}$ [TCR is fully ON]: Inductive mode of operation

$$\frac{Z_{TCSC}}{X_C} = 1 + \frac{2}{\pi} \left(\frac{\lambda^2}{\lambda^2 - 1} \right) \left(\frac{-\pi}{2} \right) = 1 - \frac{\lambda^2}{\lambda^2 - 1} = \frac{-1}{\lambda^2 - 1}$$

$$\lambda = 3, \frac{Z_{TCSC}}{X_C} = -\frac{1}{9-1} = \frac{-1}{8} = -0.125$$

(iii) $\beta = \beta_C$ for which $\frac{Z_{TCSC}}{X_C} \rightarrow \infty$

From equation (3) :

$$\begin{aligned} \frac{Z_{TCSC}}{X_C} &= 1 + \frac{2}{\pi} \left(\frac{\lambda^2}{\lambda^2 - 1} \right) \left[\left(\frac{2\cos^2\beta}{\lambda^2 - 1} \right) \lambda \tan\lambda\beta - \left(\frac{2\cos^2\beta}{\lambda^2 - 1} \right) \tan\beta - \beta - \frac{\sin 2\beta}{2} \right] \\ &= 1 + \frac{2}{\pi} \left(\frac{\lambda^2}{\lambda^2 - 1} \right) \left[\left(\frac{2\cos^2\beta}{\lambda^2 - 1} \right) \lambda \tan\lambda\beta - \left(\frac{2\cos^2\beta}{\lambda^2 - 1} \right) \frac{\sin\beta}{\cos\beta} - \beta - \frac{\sin 2\beta}{2} \right] \\ &= 1 + \frac{2}{\pi} \left(\frac{\lambda^2}{\lambda^2 - 1} \right) \left[\frac{2\cos^2\beta \lambda \tan\lambda\beta}{\lambda^2 - 1} - \frac{\sin 2\beta}{\lambda^2 - 1} - \beta - \frac{\sin 2\beta}{2} \right] \\ &= 1 + \frac{2}{\pi} \left(\frac{\lambda^2}{\lambda^2 - 1} \right) \left[\frac{2\cos^2\beta \lambda \tan\lambda\beta}{\lambda^2 - 1} - \sin 2\beta \left\{ \frac{1}{\lambda^2 - 1} + \frac{1}{2} \right\} - \beta \right] \\ &= 1 + \frac{2}{\pi} \left(\frac{\lambda^2}{\lambda^2 - 1} \right) \left[\frac{2\cos^2\beta \lambda \tan\lambda\beta}{\lambda^2 - 1} - \sin 2\beta \left\{ \frac{2 + \lambda^2 - 1}{2(\lambda^2 - 1)} \right\} - \beta \right] \\ &\Rightarrow \frac{Z_{TCSC}}{X_C} = 1 + \frac{2}{\pi} \left(\frac{\lambda^2}{\lambda^2 - 1} \right) \left[\frac{2\cos^2\beta \lambda \tan\lambda\beta}{\lambda^2 - 1} - \frac{\sin 2\beta}{2} \left\{ \frac{\lambda^2 + 1}{(\lambda^2 - 1)} \right\} - \beta \right] \end{aligned} \quad (4)$$

The only variable in the above expression is β and $\beta \in \left[0, \frac{\pi}{2} \right]$

$$\text{if } \left(\lambda\beta = \frac{\pi}{2} \right) \Rightarrow \frac{Z_{TCSC}}{X_C} \approx \infty$$

$$\Rightarrow \beta_C = \frac{\pi}{2\lambda}$$

Plot of $\left(\frac{Z_{TCSC}}{X_C}\right)$ vs β :

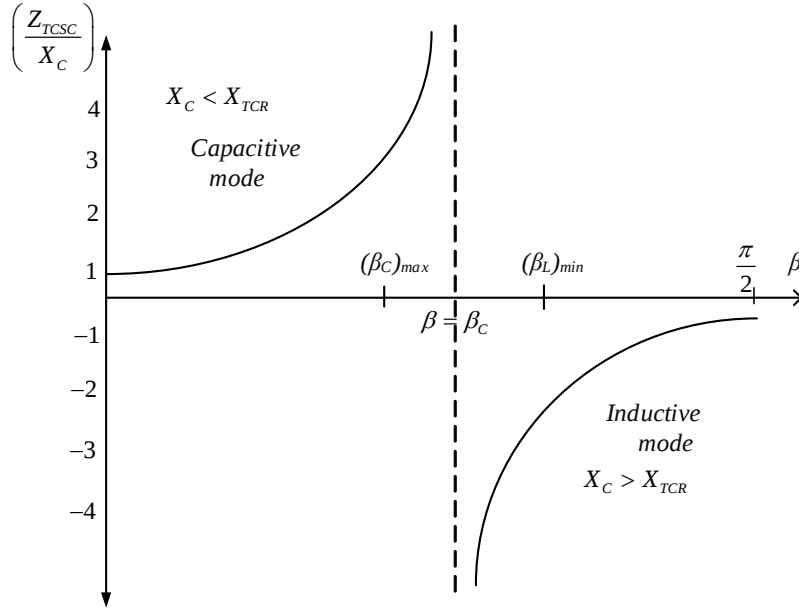


Fig..1 Variation of (X_{TCSC}/X_C) as a function of β

$X_C < X_{TCR}$: Capacitive operation

$X_C > X_{TCR}$: Inductive operation

From Fig.1, it is observed that with the increase in β , TCSC is slowly moving from capacitive Vernier control mode of operation to inductive Vernier control mode of operation.

$$X_{TCR} = \frac{v_c(t)}{i_{TCR}(t)}$$

When, $i_{TCR}(t) \approx 0 \Rightarrow X_{TCR} = \text{Very large value}$

When, $i_{TCR}(t) \uparrow \Rightarrow X_{TCR} \downarrow$

The variation of X_{TCR} with β is shown in Fig.2.

X_{TCR} value is higher near to $\beta = 0$

X_{TCR} value is lower near to $\beta = \frac{\pi}{2}$

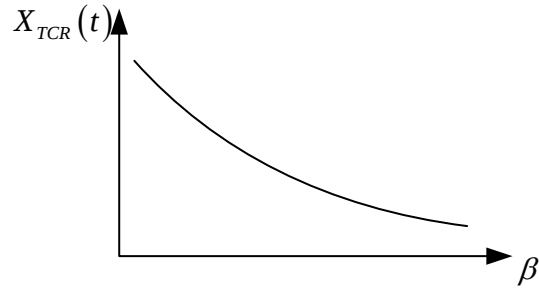


Fig.2. Variation of X_{TCR} with respect to β

$v_c(t)$ waveforms for capacitive and inductive mode of operations:

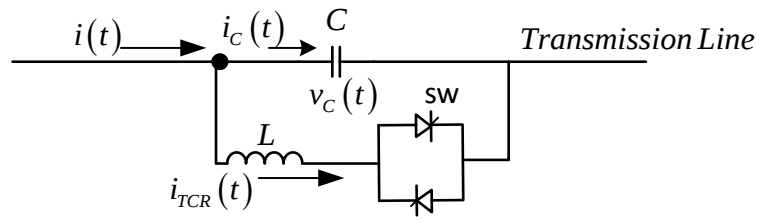


Fig.3. Equivalent circuit diagram of TCSC

From Fig.3, $i(t) - i_{TCR}(t) = i_c(t)$ = Current flowing through the capacitor

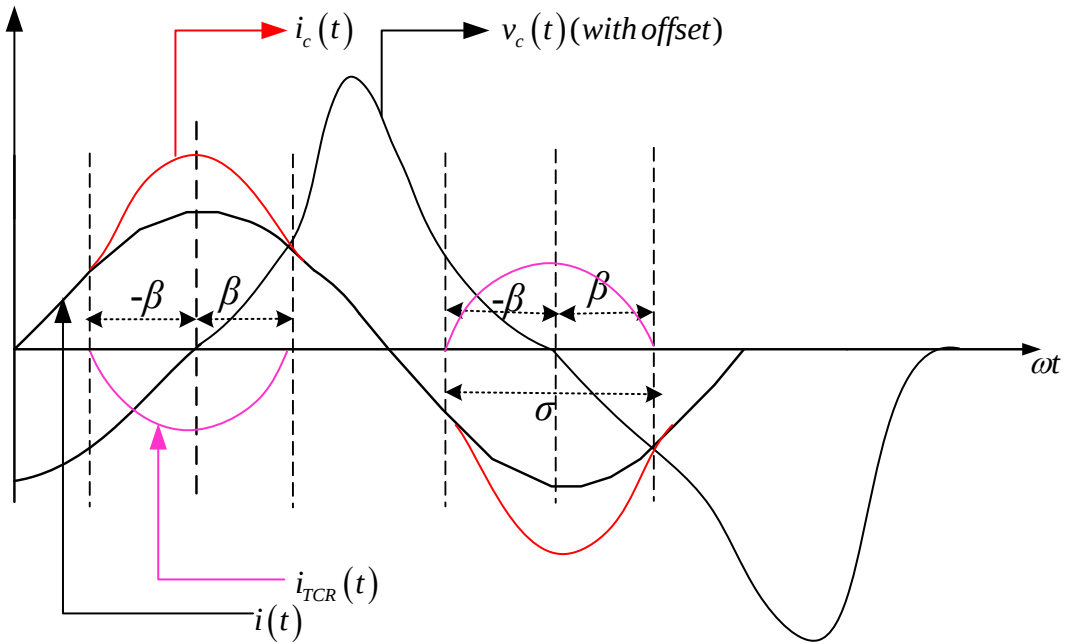


Fig.4. Waveforms of $i_c(t)$, $i_{TCR}(t)$, $v_c(t)$ for capacitive mode of TCSC operation

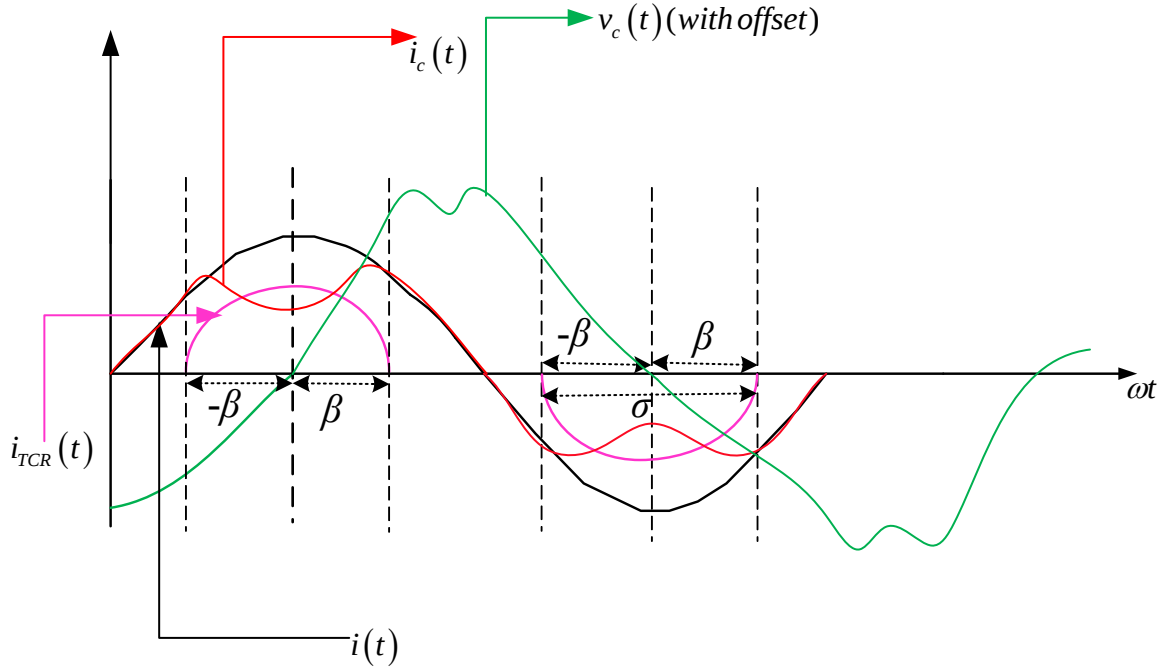


Fig.5. Waveforms of $i_c(t)$, $i_{TCR}(t)$, $v_c(t)$ for inductive mode of TCSC operation

The waveforms of $i_c(t)$, $i_{TCR}(t)$, $v_c(t)$ for capacitive and inductive mode of TCSC operation are shown in Fig.4 and Fig.5 respectively.

Harmonics in TCSC

The harmonics in TCSC is generated due to partial conduction of switches in TCR.

Fundamental TCR current

$$(I_{TCR})_1 = \frac{4}{\pi} \int_0^{\frac{\pi}{2}} i_{TCR}(t) \cos \omega t d(\omega t)$$

$$(I_{TCR})_1 = \frac{2}{\pi} \left(\frac{\lambda^2}{\lambda^2 - 1} \right) I_m \left[\beta + \sin 2\beta - \frac{\cos \beta}{\cos \lambda \beta} \left\{ \frac{\sin(\lambda+1)\beta}{\lambda+1} + \frac{\sin(\lambda-1)\beta}{\lambda-1} \right\} \right] \quad (5)$$

n^{th} harmonics of TCR current

$$(I_{TCR})_n = \frac{4}{\pi} \int_0^{\frac{\pi}{2}} i_{TCR}(t) \cos n(\omega t) d(\omega t)$$

$$(I_{TCR})_1 = \frac{2}{\pi} \left(\frac{\lambda^2}{\lambda^2 - 1} \right) I_m \left[\left\{ \frac{\sin(n+1)\beta}{n+1} + \frac{\sin(n-1)\beta}{n-1} \right\} - \frac{\cos \beta}{\cos \lambda \beta} \left\{ \frac{\sin(n+\lambda)\beta}{n+\lambda} + \frac{\sin(n-\lambda)\beta}{n-\lambda} \right\} \right] \quad (6)$$

$n = 3, 5, 7, \dots$