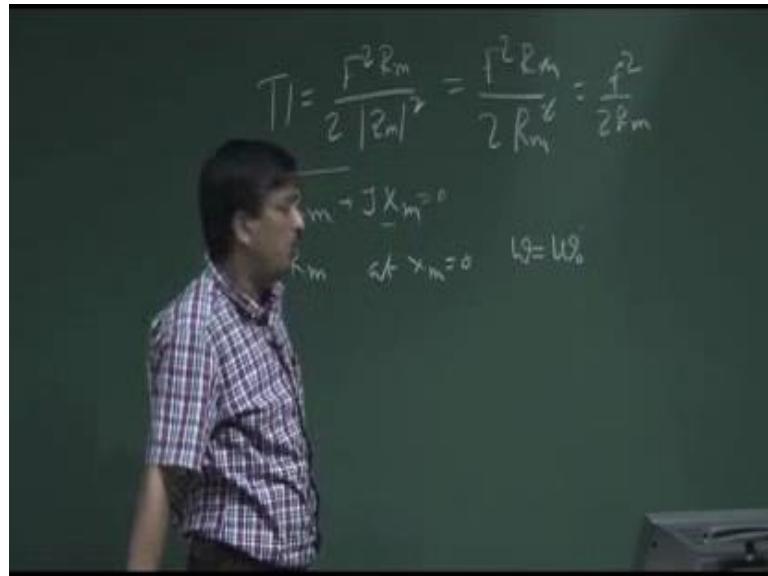


Audio System Engineering
Prof. Shyamal Kumar Das Mandal
Department of Electronics and Communication Engineering
Indian Institute of Technology, Kharagpur

Lecture – 04
Equivalent Electrical Circuits for Oscillators

(Refer Slide Time: 00:29)




Morning, now last class we have said that average power for a forced oscillation we have derived that average power in case of force oscillation is nothing but a F^2 is the applied force divided by R_m – mechanical resistance divided by two mod of Z_m square, which is mechanical impedance. And we said that average power will be maximum when Z_m is minimum. And Z_m is nothing but a R_m plus jX_m , and Z_m will be minimum, if X_m is equal to 0, if X_m is equal to 0, so; that means, Z_m is equal to R_m at X_m is equal to 0. When X_m is equal to 0, the X_m will be zero, if the (Refer Time: 01:12) of the force frequency, if the force oscillation, so the force frequency is equal to the natural resonance frequency of the system, ω is equal to ω_0 .

So, if the natural resonance frequency of the system is ω_0 , and if the applied force is the ω , frequency is ω then X_m will becomes zero, because we have done that in last class we prove that because X_m is nothing but a ωm minus S by ω , you prove that. At ω equal to ω_0 , X_m is equal to 0, so in that case, the maximum power transfer will be happen. Now, if ω is equal to ω_0 , this has a


another name, if ω is equal to ω_0 then the maximum power is nothing but F^2 square by R m into $2 R$ m square, so R m square will be cancel, so F^2 square by $2 R$ m is the maximum power. Now, when the ω , applied force frequency is equal to the natural resonance frequency, we said the mechanical resonance has happened, so that phenomena are called mechanical resonance.

(Refer Slide Time: 02:48)

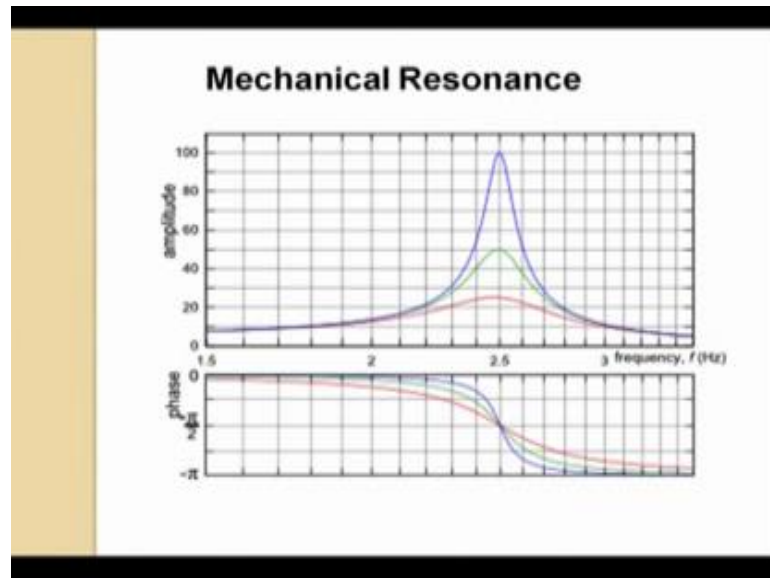

Now, if you see, if I draw, so I said the mechanical resonance maximum power transfer will be happen at ω equal to ω_0 . Now, if I draw the curve maximum power transfer curve, if you see the curve in the power point, what is saying that if I take axis this axis is ω and this axis is the power.

(Refer Slide Time: 02:54)

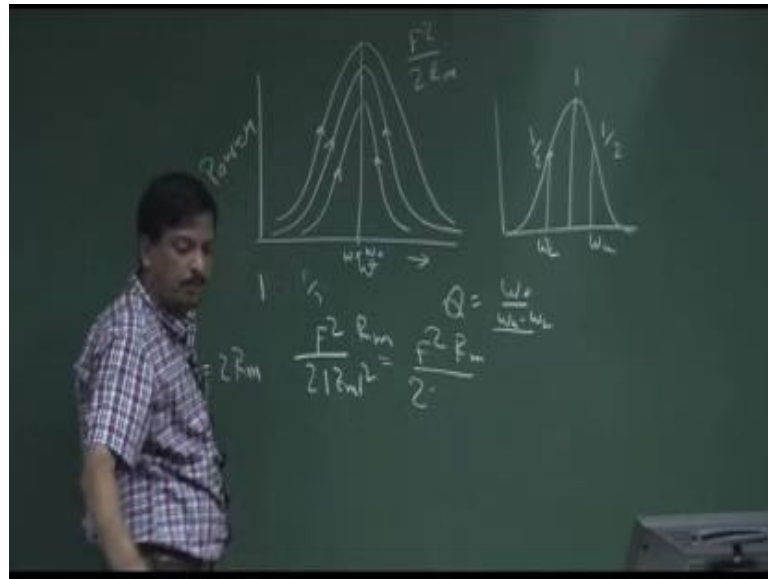


Then I said the maximum power will be happen at omega is equal to omega 0, maximum power transfer value. So, less than omega 0, this kind of curve I will get; so this is called mechanical, this is the power; mechanical resonance curve. So, mechanical resonance curve different kind of resonance curve will be I will get; so the maximum power is F square by 2 R m. Now, how we define this slope of the curve, who define, which parameter define this slope of the curve. So, how to find out those parameter which define the slope of the curve?

Now, you know that from electron is where the electronics background they know that that if I have a this kind of curve, if this is the maximum power then Q dB down, if the power expressing dB then Q dB down is half power frequency, this is called half power frequency. So, if this power is one, this will be half, this will be half that will (Refer Time: 04:28) Q dB down. So, if the lower half power frequency is omega L and upper half power frequency is omega U, upper half power frequency.

Then we know the quality factors of this resonance curve, how steep is the resonance curve is defined as omega 0 divided by omega U minus omega L that is called quality factor; that means, if this bandwidth omega U minus omega L is the bandwidth. If bandwidth is very small then the curve will be steeper; if the bandwidth is very large, curve will be broader, so that is the power transfer curve of the mechanical oscillator. So, the quality factor is depend on omega 0 divided by omega U minus omega L.

Now, how do we get the value of this parameter, ωL and ωU ? Now, think a mechanical system, we said it is half power, so if the if the power is maximum is the one then it is the power is half so what does the power, what is the power equation if average power is F^2 by $2 Z_m^2$ into R_m this is the power equation. Now, if this is the power equation, when it will be half, when the Z_m is equal to at Z_m is equal to $2 Z_m$ the power is if it is twice then the power will be half, if it is twice then the power will be half. So, I said that if Z_m is equal to $2 R_m$ because as the total power is F^2 by $2 R_m$, so this will be half, when Z_m is equal to $2 R_m$. If you put that Z_m is equal to $2 R_m$, you get this equation half of this, half of the total power. Because if it is nothing but a F^2 by R_m divided by 2 into $4 R_m^2$ so half power will be happen.

(Refer Slide Time: 06:45)

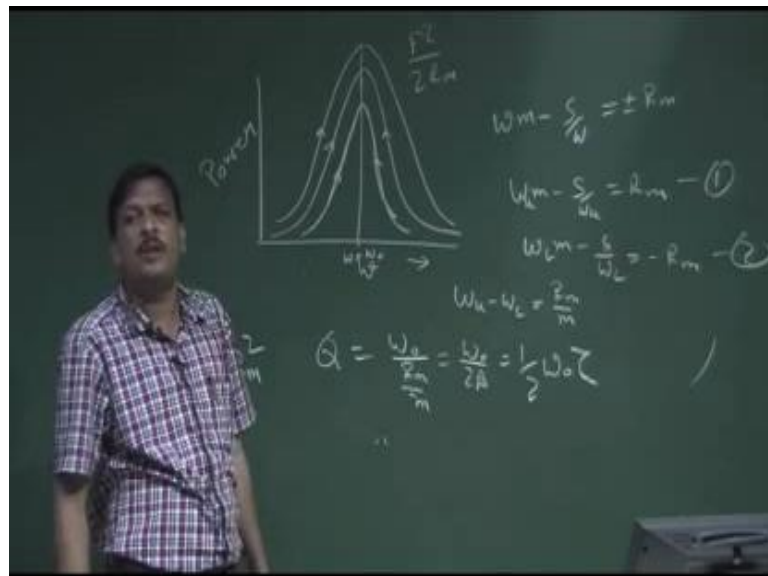


So, if it is up power happen, then I said Z_m^2 will be sorry Z_m^2 will be $2 R_m^2$. So, if it Z_m^2 is equal to $2 R_m^2$, then I said π is equal to F^2 by F^2 into R_m divided by $2 Z_m^2$. So, I said F^2 by R_m into 2 into $2 R_m^2$, so $R_m R_m$ - cancel. It is 1 by 2 into F^2 by $2 R_m$. So, this is half power happen. So, the condition is that if Z_m^2 is equal to $2 R_m^2$, then the half power is happen. So, this is the condition that when half power will be happen, when Z_m^2 is equal to $2 R_m^2$. What is Z_m^2 ? It is nothing but R_m^2 plus X_m^2 , nothing but a Z_m^2 is equal to $2 R_m^2$. Now, then X_m^2 will be what plus minus will be one $R_m R_m^2$, so X_m will be plus minus R_m .

So, if X_m is plus minus R_m that what is X_m . Reactance X_m is nothing but a ωm minus S by ω is equal to plus minus R_m . So, I can say if it Z value is plus minus R_m , so X_m is plus R_m and X_m is equal to minus R_m . So, at upper frequency value will be half – high, lower frequency the value will be low. So, in that case, the ωm minus S by ω thus ω is u S by ω u is equal to plus R_m ; and ωL minus S by ω L equal to minus R_m . Now, if I substitute these two equations in the S , this is the equation number one, equation number two. Just substitute the S , I get ωU minus ωL is equal to R_m by m . So, then quality factor is nothing but a ω_0 divided by R_m by m .

So, steepness of that curve, how narrow is the curve is defined by parameter R_m by m – mechanical resistance divided by the mass of the system. So, quality factor is nothing but a ω_0 divided by R_m by m . So, I can write it is ω_0 divided by two β , because β is equal to R_m by $2m$. Similarly, 1 by β is equal to τ , I can write half $\omega_0 \tau$. So, this is called mechanical resonance.

Now, why it is require? Suppose, I want to design this microphone, if I operate a microphone at resonance frequency, what will happen, the diaphragm will be broke down. So, I have to design that value below the resonance frequency, and I have to know what is the power transfer of that point. So, I have to draw the power curve of the diaphragm. So, I have to know these what is the quality factor of that power curve. So, I can easily calculate the quality factor of the power curve, so that is why this theory has to be known.

(Refer Slide Time: 11:24)

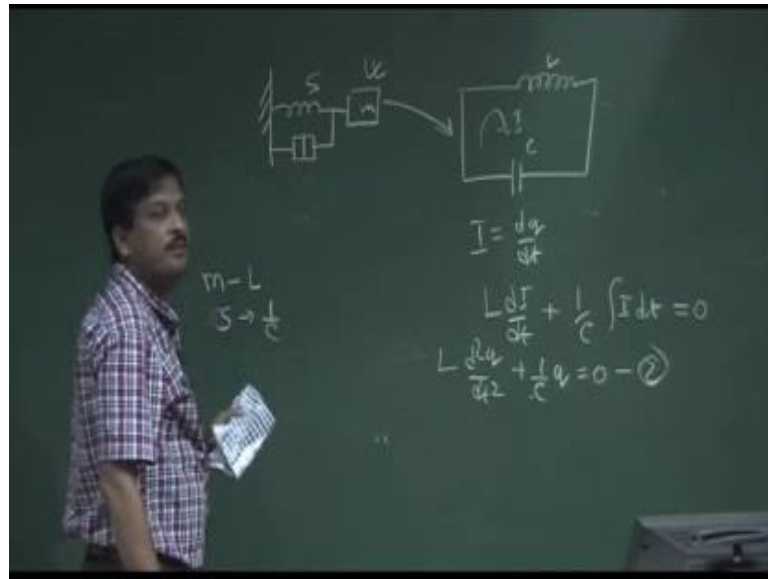

Now, I go for another chapter which is called mechanical to electrical conversion or equivalent circuits; it is not equal, it is equivalent circuits. Can I draw an equivalent electrical system for a mechanical system, yes, it is possible. If I start with the simple oscillator, you know that and mass, the simple oscillator mass and stiffness is S . What is the equation of motion, d^2x by dt square plus Sx is equal to 0.


Similarly, if I draw a simple LC circuits, let us L is inductance, and there is a capacitance, simple L and C circuits. Now, if I say if the current is I varying in this circuit then what is the equation of the charge flow in this circuit? So, what is current, I is nothing but a charge per unit time, so I can write dq by dt . Now, what is the electrical equation of this circuit, total equation, it is nothing but a voltage across the L plus voltage across the C will be equal to 0. So, voltage across the L what is the voltage across the L , $L dI$ by dt plus voltage across the C 1 by C integration of $I dt$ that should be equal to 0. There is no external voltage source, so that is will be equal to 0 that is called Kirchhoff's loop rule.

So, inductance is if there is no variation in the current, inductance across the voltage of the inductance is 0. See if there is variation in the current, then there is voltage across the inductance, capacitance – it store the charges, so it is I integration of $I dt$. Now, you just replace, what is I , dq by dt , so it is nothing but a $L d^2q$ by dt square plus 1 by $C dq$ by dt

integration over the dt, so integration and differentiation will be cancel, so it is nothing but a q equal to 0.

So, if you see this equation, equation number two and equation number one, they are equivalent equation; $m \frac{d^2 x}{dt^2} + S x$ is equal to 0. Here, $L \frac{d^2 q}{dt^2} + \frac{1}{C} q$ is equal to 0. So, I can say the m – mass is analogous to electrical inductance and or stiffness of the spring is analogous to inverse of the electrical capacitance. So, mass is analogous to L and capacitance is inverse of that stiffness or I can say C is 1 by S or S is 1 by C . So, any mechanical circuits if it is given, so if this is the mechanical circuits, I can say the electrical equivalent circuit is this one.

(Refer Slide Time: 15:25)

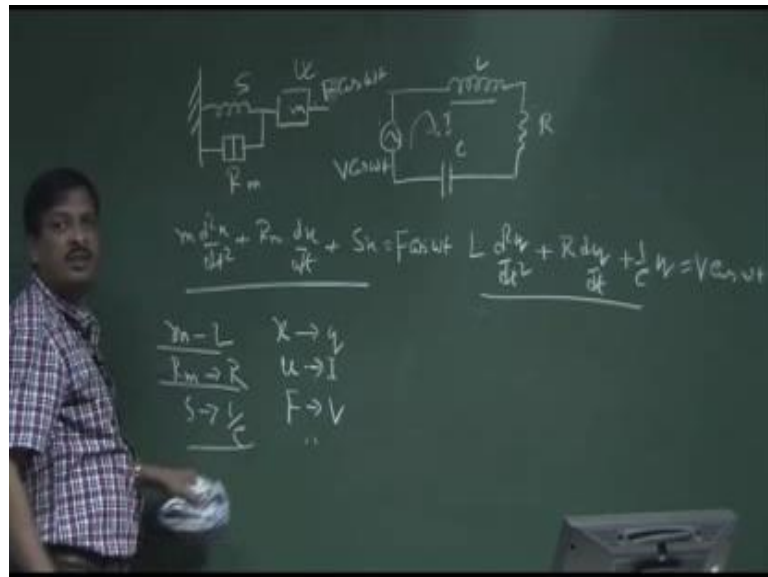


Now, if I add in the mechanical circuit mechanical damping. I just add a mechanical damping in that, which is R_m . Now, if I apply a voltage source F in here, then the equation of motion, if the force is not there then the total equation of motion is $m \frac{d^2 x}{dt^2} + R_m \frac{dx}{dt} + S x$ is equal to 0, equation of the motion. Similarly, just add a resistance here, I add a resistance R in here, electrical resistance, then what is the equation of this electrical circuits, it is nothing but a voltage across the L , which $L \frac{d^2 q}{dt^2} + R \frac{dq}{dt} + \frac{1}{C} q = V \cos wt$ we have already proved plus across the resistance R into I , I means dq dt plus one by C into q is equal to 0.

Now, see this equation and this equation are the identical equation, where m is again equal to L and R_m is equal to R and S is equal to one by C – equivalent to one by C .

And x displacement in case of mechanical system is equivalent to charge in electrical system. Similarly, vertical velocity in mechanical system is equal to nothing but $\frac{dx}{dt}$, so this is equal to $\frac{dq}{dt}$, so it is nothing but a current. Now, if I apply a voltage source here, sinusoidal voltage source here, and here apply a sinusoidal force here, so it is nothing but a sinusoidal voltage source let us $V \cos \omega t$, it is $F \cos \omega t$. So, this is equal to $F \cos \omega t$ and this is equal to $V \cos \omega t$. So, force here, mechanical force is nothing but electrical voltage. So, equivalent electrical circuit for this mechanical circuit is this one. So, I can easily draw any given mechanical circuits, I can easily draw its equivalent electrical circuits.

And I know the equivalence of mass is equal to electrical inductance, equivalence of mechanical resistance, electrical resistance equivalent to stiffness is inverse to the capacitance; x equivalence to q is the charge; u equivalent to I - current, and force is equivalent to voltage. Similarly, Z is nothing but a force by velocity, force by u ; so, in case of electrical, impedance is nothing but a voltage by current, V by I . So, impedance is nothing so mechanical impedance is nothing but equivalent to electrical impedance, so is it know that.

(Refer Slide Time: 18:59)

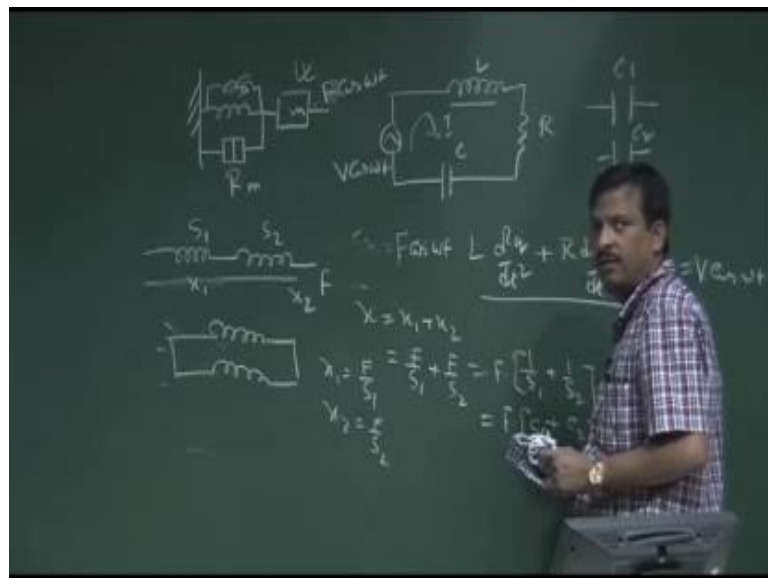


Now, cascading, another point is that suppose I make two spring together above to that or I can replace one single spring by this kind of cascading or I can replace this spring by a parallel cascading. So, this two kind of cascading I can do, two kind of cascading I can

do, one is called parallel cascading, another is called series cascading. Now, in case of series, so a force is apply on spring one let say it is spring two – S 2 and this is spring one. So, force is apply on a spring two and it is extended, displace by x 1 or sorry x 2, let say it is x 2. And S 1 spring displace is x 1. So, total displacement is nothing but a x 1 plus x 2. Now, what is x 1, x 1 is nothing but a force by spring one stiffness; and x 2 is nothing but a force by spring two stiffness x 2.

So, if I put that this is nothing but a F by S 1 plus F by S 2. So, 1 by S 1, 1 by S 2, so it is nothing but a F into 1 by S 1 plus 1 by S 2. Now, if I put in F into C 1 equivalence, 1 by S 1 means C 1 and 1 by S 2 means, so it is nothing but a C 1 plus C 2. So, when it will be C, if I have 2 capacitance, one is C 1 and another is C 2. How it will be connected to get the equivalent capacitance, which is C 1 plus C 2. So, in that case, if it is connected in parallel, what will happen let say the 2 C 1 and C 2 are connected in parallel. What is the equivalent capacitance, C effective is C 1 plus C 2 because impedance is 1 by C 1 it 1 by C 2, so it will be 1 by C 1 by 1 by C 2. So, effective will be C 1 plus C 2. So, in that case, this is equivalent to this one. So, I can say if the two springs are connected in a series that means, it is nothing but a two equivalent circuit will be two electrical capacitance connected in series.

(Refer Slide Time: 22:19)

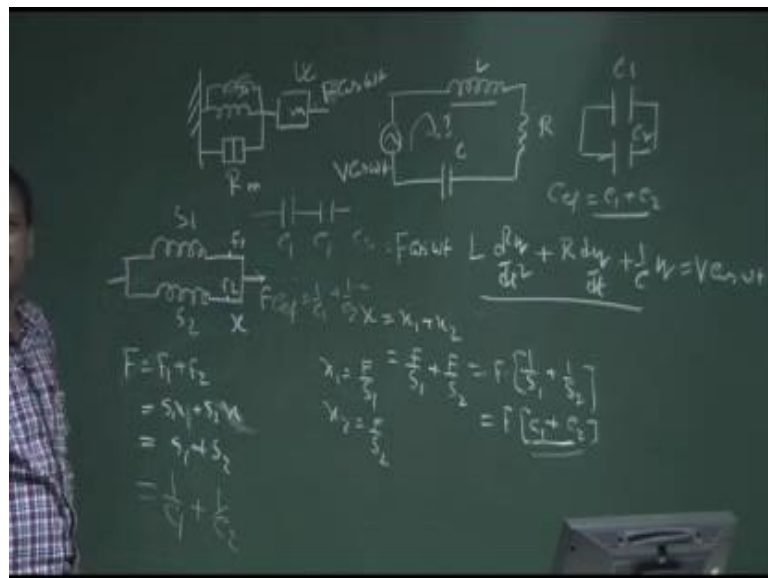

Similarly, if the two springs connected in parallel, this is the one spring and this is another spring connected in parallel. This is S 1; this is S 2; force is applied F. Then what


will happen, in that case, let us F is applied and displacement is x , total displacement is x . So, the total force is acting here is force in here plus force in here. So, if it is F_1 and if it is F_2 , so F is equal to nothing but a F_1 plus F_2 . Now, what is F_1 ? Spring into displacement, so it is nothing but $S_1 x_1$ plus $S_2 x_2$, it is nothing but $S_1 x_1$ sorry displacement is x , so x and x . So, it is nothing but a S_1 plus S_2 ; displacement will be x , so it is nothing but a S_1 plus S_2 . Now, it is equivalent to 1 by C_1 plus 1 by C_2 , because S is 1 by C , so 1 by C_1 plus 1 by C_2 . So, when will be that capacitance 1 by C_1 plus 1 plus C_2 , when they are connected in series? If it is C_1 and C_2 , C effective is 1 plus C_1 plus 1 by C_2 , so when they are connected in series.

(Refer Slide Time: 24:48)



So, if the two springs are parallel, its equivalent circuit is two capacitances are in series which is C_1 and C_2 . So, I can draw easily for any mechanical circuits to its electrical equivalent circuits. So, if I have a mechanical circuit is like this, let us do some exercise for that. Let us I have a mechanical circuit, so there is a mass, spring constant S , mechanical resistance R_m and the force is applied in here. What is an equivalent electrical circuit? Always look for the u , total current in here – u , u is nothing but a current, current accure mass, you have to look out that then though the equivalent circuits. So, I can see one or two exercise from the book, then I solve in here, so that you can easily conversion with that things.

(Refer Slide Time: 26:01)

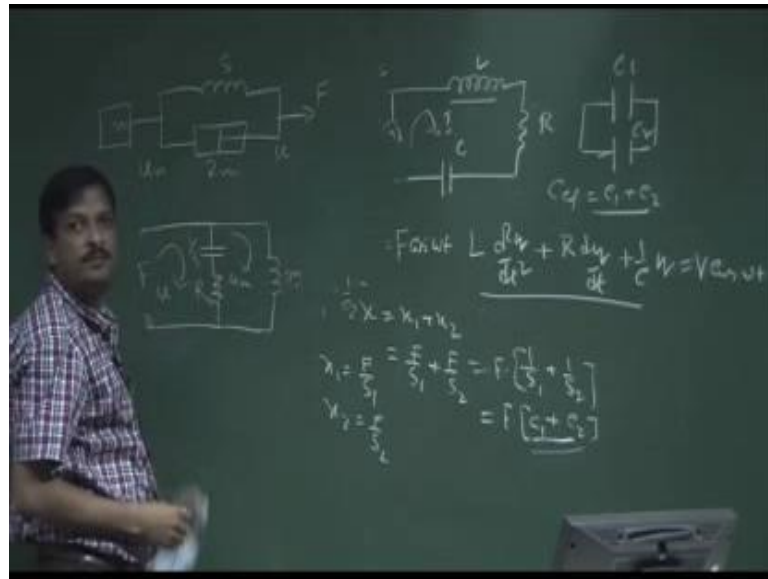

So, this is simple, which I have drawn; all are in series, all will be in series – resistance, capacitance then inductance then the voltage source. Now, instead of that if I give you the circuits' mechanical circuits like that let us m is here and it is connected to a mechanical resistance and a spring S , R_m and a force is applied in here. Then what is the equivalent electrical circuit, if I told you to draw the equivalent electrical circuits, so that means, if the force is applied here, so the velocity in here is u , and velocity in here is u . If I pull this circuit, so velocity on here it is u , and velocity on here is mass velocity, if the mass is acting on the velocity. The mass in motion, if the mass is motion, the motion of the mass is the particle velocity here.

So, now if I said this is my force; these two points I apply this force F between these two points. So, here I will go for a current u , particle velocity u , the current will flow like this way, so which will be expressed to the u , S and R_m . So, what is S - capacitance, what is R_m - resistance, and I have another current is u here. So, u is what is u ; m , L inductance. So, it is 1 by S , it is R_m , it is m , so equivalent electrical circuits. Similarly, suppose, I have circuits - mechanical circuits like this, mass, spring, force – force is applied here. Similarly, I will say this is u , and this is u , so this is the force within the two point force is applied here, so who see the u current, this is the u current spring see the u current; spring is nothing but a capacitance; and u see will by the mass. So, this is m , this is 1 by S .

(Refer Slide Time: 28:27)



Similarly, let us another example, another example is like this. Let us I have a ground, spring, then I have a mass m , this is S . This is S , this is m , and then I have mechanical impedance and I apply a force in here. So, if I see, the two system, let us this is one system and this is another system, so this will be u in here and this system let us u m is here. So, I can let us again you write the force, F then this is the u will be here acquires what resistance, draw. Then I get u m in two circuits, so there will be a capacitance and inductance L or m , 1 by S , R m , here is u will be implying, because this side is grounded so these two is one combined together.

Earlier, we said mass is different because mass is not supported by the ground, this side it is zero, because this is the grounded, so this total circuits is exposed to the u m current, so it is u m and this is u . So, this way you can solve any mechanical circuits into its equivalent electrical circuits. Similarly, if this is very easy to prove that the power average power, total power in the mechanical oscillation, which is e , it is nothing but a potential energy plus kinetic energy, which is same expression will come with the current problem V into I , same expression will come. So, power will also be the same.