

Power System Analysis
Prof. Debapriya Das
Department of Electrical Engineering
Indian Institute of Technology, Kharagpur

Lecture – 45
Three phase fault studies

(Refer Slide Time: 00:23)

Above two assumptions suggest that I_{k1} and I_L have the same phase angle and so I_{k2} and I_L . These lead us to the conclusion that current distribution factors A_{k1} and A_{k2} are real quantities.

Let,

→ $I_{g1} = |I_{g1}| \angle \alpha_1$ and $I_{g2} = |I_{g2}| \angle \alpha_2$.

Substituting I_{g1} and I_{g2} in Eqn.(80), we get,

→ $|I_k|^2 = \left[A_{k1}|I_{g1}| \cos \alpha_1 + A_{k2}|I_{g2}| \cos \alpha_2 \right]^2$
 $+ \left[A_{k1}|I_{g1}| \sin \alpha_1 + A_{k2}|I_{g2}| \sin \alpha_2 \right]^2$

Ok. So, now, So, this here now we assume that let us assume I_{g1} actually magnitude $|I_{g1}|$ its angle is α_1 and I_{g2} actually magnitude $|I_{g2}|$ angle α_2 right.

(Refer Slide Time: 00:40)

(122)

When both the generators are supplying current into the power network as shown in Fig.10, the current in the branch K can be obtained by applying the principle of superposition. Thus, we can write,

→ $I_k = A_{k1}I_{g1} + A_{k2}I_{g2} \dots (80)$

Now we will make certain assumptions:

→ Assumption-1: For all network branches ratio $\frac{X}{R}$ is same.

→ Assumption-2: All the load currents have the same phase angle.

So, what we will do in this equation I am writing one or 2 lines for you, in this equation 80 right in equation 80 you put that one right.

(Refer Slide Time: 00:48)

The image shows a handwritten derivation on a light blue background. The equations are as follows:

$$I_k = A_{k1} \cdot |I_{g1}| \angle \alpha_1 + A_{k2} \cdot |I_{g2}| \angle \alpha_2$$

$$\therefore I_k = A_{k1} \cdot |I_{g1}| (\cos \alpha_1 + j \sin \alpha_1) + A_{k2} \cdot |I_{g2}| (\cos \alpha_2 + j \sin \alpha_2)$$

$$\therefore I_k = \left(A_{k1} |I_{g1}| \cos \alpha_1 + A_{k2} |I_{g2}| \cos \alpha_2 \right) + j \left(A_{k1} |I_{g1}| \sin \alpha_1 + A_{k2} |I_{g2}| \sin \alpha_2 \right)$$

That means your I_k actually, I_k is equal to your $A_{k1} \cdot |I_{g1}| \cos \alpha_1$ right and similarly this one $A_{k2} \cdot |I_{g2}| \cos \alpha_2$ right; that means, this one you can write $A_{k1} \cdot |I_{g1}| \cos \alpha_1$, plus $j \sin \alpha_1$ right.

Then similarly this one A_{k2} then magnitude $|I_{g2}|$ right, in bracket sorry cosine α_2 plus $j \sin \alpha_2$ right so; that means, what? That means, I_k you can what you call you can write you take you are in separate you are you just real and imaginary part make it together, this side first you collect the real one. So, it is $A_{k1} \cdot |I_{g1}| \cos \alpha_1$, plus $A_{k2} \cdot |I_{g2}| \cos \alpha_2$ this is of real part and then imaginary part j it is $A_{k1} \cdot |I_{g1}| \sin \alpha_1$ plus $A_{k2} \cdot |I_{g2}| \sin \alpha_2$ right.

So, what you do, you take the magnitude of these right you take the magnitude of this and then square it. So, if you do so, right I mean after making this just hold on after making this you just take the take the magnitude of this and then you square it. If you do so, you will get magnitude of I_k square is equal to $A_{k1} \cdot |I_{g1}| \cos \alpha_1$ plus $A_{k2} \cdot |I_{g2}| \cos \alpha_2$ whole square right plus $A_{k1} \cdot |I_{g1}| \sin \alpha_1$ plus $A_{k2} \cdot |I_{g2}| \sin \alpha_2$ whole square right.

Then what you do, you expand it right and then your sin square alpha 1 cosine square alpha 1 there should be 1. If you take similarly cos square alpha 2 sin square 1.

(Refer Slide Time: 03:34)

$$\Rightarrow \therefore |I_k|^2 = A_{k1}^2 |I_{g1}|^2 + A_{k2}^2 |I_{g2}|^2 + 2A_{k1}A_{k2}|I_{g1}||I_{g2}|\cos(\alpha_1 - \alpha_2) \dots (81)$$

$$\xrightarrow{\text{But}} |I_{g1}| = \frac{P_1}{\sqrt{3} |V_1| \cos\phi_1} \dots \dots 82(a)$$

$$\xrightarrow{\text{But}} |I_{g2}| = \frac{P_2}{\sqrt{3} |V_2| \cos\phi_2} \dots \dots 82(b)$$

there,
 P_1 and P_2 = Three phase real power injected at Plants 1 & 2.
 $\cos\phi_1$ and $\cos\phi_2$ = Power factors
 V_1 and V_2 = Bus voltage of the plants.

So, these 2 term plus your if the plus it will be 2 into this one, cosine alpha 1 alpha 2 here also 2 into this one sin alpha 1 alpha2. So, all the 4 terms your all the terms will be common, and ultimately it will become cosine alpha 1 minus alpha 2 right.

So, you just expand and simplify this is simple thing; that means, you will get mod I k square is equal to A K 1 square I g 1 square magnitude, again and again I am not telling understandable then plus A K 2 square I g 2, square plus 2, A K 1, A K 2, I g 1, I g 2 it will become cos alpha 1 minus alpha 2 this is equation 81 right.

Now, we know in general P is equal to your power is equal to root 3 vi cos phi therefore, for generator one magnitude I g 1 is equal to P 1 upon root 3 V 1, cosine phi 1 right cos phi and cosine phi 1 or phi 2 are the power factor angle at generating station 1 and 2 respectively. So, that is I g 1 is equal to P 1 upon root 3 V 1 your cosine phi 1, this is equation say 82 a I have given. And among magnitude I g 2 is equal to P 2 upon root 3 magnitude V 2 cosine phi 2 right this is given equation 82 B right; where P 1 and P 2 is equal to 3 phase real power injected at plants one and two right. Cos phi 1 and cos phi 2 is equal to power factors V 1 and V 2 is the bus voltage of the plants right.

(Refer Slide Time: 04:50)

Total real power loss is given by

$$\rightarrow P_{Loss} = \sum_{k=1}^{NBR} 3|I_k|^2 R_k \dots (83)$$

where
 R_k = resistance of branch k .

From Eqs. (83), (82a), (82b) and (81), we get,

$$\rightarrow P_{Loss} = \left(\frac{P_1^2}{|V_1|^2 \cos^2 \phi_1} \right) \sum_{k=1}^{NBR} A_{k1}^2 R_k + \left(\frac{2P_1 P_2 \cos(\alpha_1 - \alpha_2)}{|V_1| |V_2| \cos \phi_1 \cos \phi_2} \right) \sum_{k=1}^{NBR} A_{k1} A_{k2} R_k + \left(\frac{P_2^2}{|V_2|^2 \cos^2 \phi_2} \right) \sum_{k=1}^{NBR} A_{k2}^2 R_k \dots (84)$$

So, the next what we will do this next one is that what is the 3 phase power loss total right. So, in that case the total real power loss is given by k is equal to 1 to NBR . NBR means total number of branches right in the transmission network. So, k is equal to one to number of branches that is why NBR right. Is equal to 3 into magnitude I_k square into R_k it is a 3 phase. So, that is why multiplied by 3 right.

So, this is equation 83; now this I_k square in this I_k square this I_{g1} and I_{g2} you substitute, I have not writing all the step now you have understood everything right. So, this I_{g1} and I_{g2} you substitute here right in this expression I_k square, and then you put it we see root 3 is there if you square it will be 3 here also 3 so that 3 will be canceled actually right. So, you put it here and use this expression and simplify.

If you do so, then you will get R_k is the resistance of the branch k right. If you do so, that is why I am written from equation 83, 82 a, 82 B and 81 you will get right. You will get P_{Loss} is equal to P_1 square divided by V_1 square cos square ϕ_1 the magnitude, but not telling again and again then in bracket sigma k is equal to 1 to NBR , it is A_{k1} square R_k k th term. All the k th your k th coefficient right or this thing you put in the sigma, but other things you take it out plus $2 P_1 P_2 \cos(\alpha_1 - \alpha_2)$ divided by $V_1 V_2 \cos \phi_1 \cos \phi_2$ take it out, k is equal to one to NBR again number of branches A_{k1} into A_{k2} into R_k right plus P_2 square upon V_2 square cos square ϕ_2 your ϕ_2 sigma k is equal to 1 to NBR , then A_{k2} square into R_k this is equation 84; that means,

this equals this I g 1, I g 2 substitute here with that I see I k square whatever will get you put it here then you mix you separate the 3 terms right.

Your one is this due to your this thing you are what you call P 1 square, P 2 square another is a product of P 1 P 2 this way you make it. Here the sigma is there sigma is there sigma is there right.

(Refer Slide Time: 07:21)

Eqn. (84) can also be written as:

$$\rightarrow P_{Loss} = B_{11} P_1^2 + 2 P_1 P_2 B_{12} + B_{22} P_2^2 - \dots (85)$$

where

$$\rightarrow B_{11} = \frac{1}{|V_1|^2 \cos^2 \phi_1} \sum_{k=1}^{NBR} A_{k1}^2 R_k$$

$$\rightarrow B_{12} = \frac{\cos(\alpha_1 - \alpha_2)}{|V_1| |V_2| \cos \phi_1 \cos \phi_2} \sum_{k=1}^{NBR} A_{k1} A_{k2} R_k$$

$$\rightarrow B_{22} = \frac{1}{|V_2|^2 \cos^2 \phi_2} \sum_{k=1}^{NBR} A_{k2}^2 R_k$$

So, this is equation 84; now this equation this 84 equation right it is a equation 84 it can be written as P Loss is equal to your B 11, P 1 square; that means, this term right I will come to that B 11, P 1 square plus 2 P 1, P 2, B 12 plus B 22, P 2 square right.

So, listen one thing that this P 1 square P 2 square actually it is a taken generator one generator 2 no question of slack bus just reached on top you are generating power that pg one pg 2. Actually this P 1 P 2 is nothing, but pg 1 pg 2 right. So, only 2 generating units, but when you will do it in general of course, you have to see that pg 2 pg 3 up to pgm right, but anyway this is actually your P 1 if your what you call in terms of P 1 and P 2 right.

So, this where B 11 as we are taking P 1 square this means; that means, this is P 1 square into B 11, B 1 here actually is equal to 1 upon V 1 square, cos square phi 1 into your k is equal to 1 to NBR A K 1 square Rk; k is equal to 1 to NBR A K 1 square Rk. Similarly B 12 that is it is p it is your what you call this term only right that is equal to cosine alpha 1

minus α_2 divided by your what you call your $V_1, V_2 \cos \phi_1 \cos \phi_2$, because it is product $P_1 P_2$ is there. So, $2 P_1, P_2, V_1^2$ and third term actually B_{22}, P_2^2 square; that means, coefficient of the P_2^2 square. That is your B_{22} is equal to 1 upon $V_2^2 \cos^2 \phi_2$ sigma k is equal to 1 to $NBR, A_k^2 \cos^2 \phi_k$. So, this is actually called B coefficient right.

Now, if you look at the dimension of B coefficient B_{11}, B_{12} look this P Loss when you put in real dimension it is megawatt right, but in this case this P_1^2 square P_1^2 square or P_1, P_2^2 square it is becoming megawatt square right; that means, what will be what will be the dimension of B_{11} it will be megawatt inverse right; that means, a; that means, if whatever suppose it is given 0.2 ; that means, 0.2 megawatt inverse right. So, that is why because it is square it is megawatt square P Loss is megawatt. So, B B B the dimension is megawatt inverse right.

(Refer Slide Time: 09:56)

The terms B_{11}, B_{12} and B_{22} are called loss coefficients or B -coefficients.

In general, Eqn.(84) can be written as:

$$\rightarrow B_{pq} = \frac{\cos(\alpha_p - \alpha_q)}{|V_p||V_q| \cos \phi_p \cos \phi_q} \sum_{k=1}^{NBR} A_{kp} A_{kq} R_k \quad \dots (85)$$

General expression of transmission loss can be given as:

$$\rightarrow P_{Loss} = \sum_{p=1}^m \sum_{q=1}^m P_p B_{pq} P_q \quad \dots (86)$$

So, once this is done then this equation actually we can put in general form; for instead of one and two like the terms B_{11}, B_{12} and B_{22} are call these are loss coefficient or B coefficient right loss coefficient will be data right or B coefficient in general equation 4 forty eighty 4 are can be written as B_{pq} right instead of instead of your B_{11}, B_{12}, B_{22} if we assume p and q , in general it can be written that B_{pq} is equal to cosine alpha p minus alpha q divided by $V_p V_q \cos \phi_p \cos \phi_q$ k is equal to 1 to $NBR A_{kp} A_{kq}, R_k$ this is 85 equation, 85 say right; that means, if you put P is equal to $1, q$ is equal to 1 you


will find this is your $\cos^2 \theta$ right it will be $V^2 \cos^2 \theta$ and it will become your $\cos^2 \theta$ right and automatically you will get this is actually $P = V^2 \cos^2 \theta$ you will get $A^2 \cos^2 \theta$ into your R_k k is equal to 1 to n NBR right.

So, this is from this simple this expression all this B this can be made as a general thing right. So, it is from here you can make it $\cos^2 \theta = \frac{1}{2} [1 + \cos 2\theta]$, $V_p V_q \cos^2 \theta = \frac{1}{2} [V_p V_q + V_p V_q \cos 2\theta]$ and then R_k . From here you can make it B_{pq} and when p is equal to q you can this one you can make it when q is equal to p you can get it. So, all these things we will get it and this one is a quadratic relationship this one right.

So, this one also it can be generalized that P_{loss} is equal to P is equal to 1 to m , q is equal to 1 to m , it can be made $\sum_{p,q} B_{pq} p q$ this is equation 86. So, this loss expression also if you do this you will get p is equal to 1 to m , q is equal and in this case if you make m is equal to 2 then you will get this expression. We had 2 is there because this term will be repeated right this term will be repeated because B_{12} is equal to say B_{21} one this term will be repeated that is why 2 is here. So, ultimately if we expand this there will be 4 terms for m is equal to 2 . So, what, but 2 terms will be common summation will be $2 P_{12} + 2 B_{12}$.

So, this term that is why when we are when we took your what you call that loss formula we took $\sum_{i,j} p_i b_{ij} p_j$. So, this is the $\sum_{i,j} p_i b_{ij} p_j$ right this loss formula. So, this is actually quadratic equation, this is actually this equation is 86. Now economic load dispatch and loss formula whatever we have done this topic all the theory as concern some examples are given, all together I think before 8 examples are shown on this right. Your object will be not to practice as far as classroom is concerned very big formulas and other things right, and simple example right and meaningful example right a something something will be you can solve right. Take a any book and you will find this small thing only thing is that see that do not make any calculation error right I mean when you are using calculator. So, do not use do not make any mistake right these are the thing.

(Refer Slide Time: 13:15)

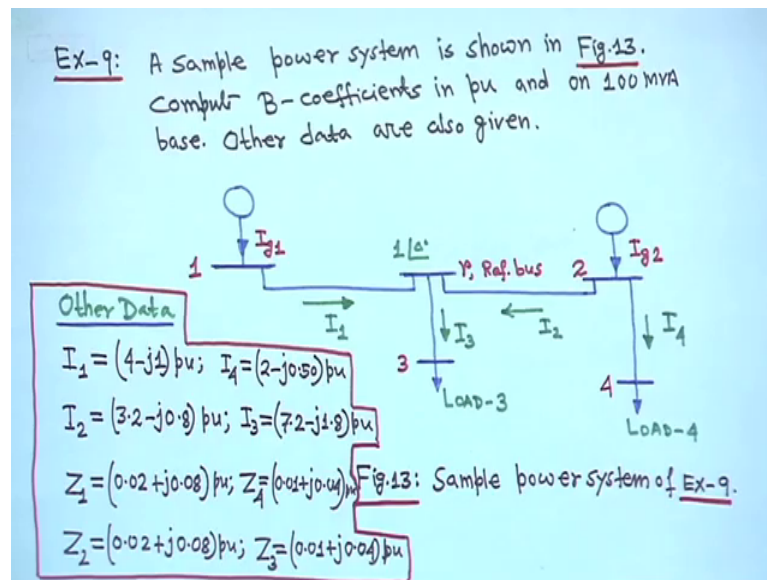

Now, next we will take 1 or 2 example on it right. So, here this example is taken like this here what we will do that a coefficient one part I will do it for you, other part I will give the answer, but you will do for yourself right. So, a sample power system is shown in figure 13, this is actually figure 13 right and your B coefficient come you have to compute B coefficient in per unit and on 100 MVA base, other data are also given. So, this is that network is given, and in this network this is one this bus actually has taken as say for example, reference bus. This voltage is given one angle 0 right and this is bus one current from this generator is I_{g1} , and this is bus 2 current from this generator is I_{g2} right and this is and bus 3 and bus 4 they are load bus.

So, here that current is going through this load is I_3 , and this is going to I_4 is going to the load 4 right. So, now some data you need some data. So, this is 1 2 3 4 there are 4 branches, and current direction is shown I_1 its. So, going like this say I_2 going like this, this is I_3 right and this is this I_4 is going to this load right. So, in that can this voltage is a reference bus voltage one angle 0. Now I_1 is given say $4 - j1$, this I_1 is given $4 - j1$ per unit. I_4 is I_2 is also given $3.2 - j0.8$. So, this I_2 direction is shown it is given $3.2 - j0.8$ right.

Then I_4 is also given this is I_4 , $2 - j0.5$ per unit, and I_3 this is I_3 is given $7.2 - j1.8$ per unit these are given right. Now Z_1, Z_2, Z_3, Z_4 this is branch 1, branch 2, branch 3, branch 4. So, Z_1 is given $0.02 + j0.08$, and Z_2 is $0.02 + j$

0.08, Z 4, Z 3 is given 0.01 plus j 0.04 and Z 4 is 0.01 plus j 0.04 these all are given this data are given.

Now, we have to find out this B coefficient for this example right. So, what we will do first you this is that 2 loads are there this is load 3 and load 4 which is it and that is at bus 3 and bus 4. So, let me I 3 and I 4 is the total load current, because these 2 I 3 and I 4 going to the load right.

(Refer Slide Time: 15:57)

(130)

Soln.
 Total load current,

$$I_L = I_3 + I_4 = (7.2 - j1.8) + (2 - j0.50) = \underline{(9.2 - j2.3)} \text{ pu}$$
 Now imagine plant 2 is off (Fig. 14)

Fig. 14:

That means your total load current right is equal to I_L is equal to I_3 plus I_4 , I_3 is 7.2 minus j 1.8, plus it is 2 minus j 0.50 is equal to 9.2 minus j 2 0.3 per unit is a total load current.

Now, the way we have derived this thing a formula same way we will do it now imagine plant 2 is off; that means, this generator 2 is not there it is off right this is figure 14, I have written here figure. As soon as the generator 2 is off look at that that the direction of the current will change because from this generator only current will flow this and this will going to the load. So, this is off this is off. So, direction of the current will change right that is why that this direction of the current is change.

So, this is all this is off; that means, I_2 actually is equal to I_4 right. So, if it is so, then this at this point we apply Kirchoff's first law right so; that means, your I_1 is equal to I

2 plus I 3 plus I 2 and here, it is I 2 is equal to I 4 because same current is going here this is off right.

(Refer Slide Time: 17:12)


Note that direction of current in branch-2 has changed. Now,

$$I_1 = I_3 + I_2 = I_3 + I_4 = I_L = \underline{(9.2 - j2.3) \text{ pu}}$$

$$I_2 = I_4 = \underline{(2 - j0.5) \text{ pu}}$$

Using Eqn(78)

$$A_{11} = \frac{I_1}{I_L} = \frac{I_L}{I_L} = \underline{1.0}$$

$$A_{21} = \frac{-I_2}{I_L} = \frac{-(2 - j0.5)}{(9.2 - j2.3)} = \underline{-0.2174}$$


That means; that means, your I 1 is equal to you apply Kirchhoff's first law here I 1 is equal to I 3 plus I 2 that is I 3 plus I 2 is equal to actually I 3 plus I 4, because I 2 is equal to I 4, I have written here I 2 is equal to I 4 right. So, is equal to your total load current I_L, because this is the I 3 and I 4 the total load current is equal to 9.2 minus j 2.3 per unit right and I 2 is equal to I 4. So, I 2 is equal to I 4 is equal to 2 minus j point 50 because I 4 is equal to 2 minus j point 50 right. So, all these currents we have got.

Now, using equation 78 A 11 right if you go to equation let me find out right just hold on anyway, it has been mixed up I am telling you that A 11 actually is equal to I k 1 upon the total load current right. So, this equals if you use 78, A 1 is A K 1 your I k I k 1 upon I_L right. So, in that case k is equal to one the first branch. So, I 1 upon I_L its equal to I_L upon I_L, because I 1 is equal to I_L because I 1 is equal to just now I have told you that your where it has gone again right this this is I_L total load current right and I 1 is equal to actually I 2 this I 3 plus I 2 is equal to I 3 plus I_L, this is I 1 this I 1 is equal to actually I_L, because I 1 is equal to I 3 plus I 2 is equal to I 3 plus I 4 right.

So, here it is. So, I 1 is equal to I_L right; that means, A 11 will be I 1 upon I_L that is one similarly A21 that here that direction and the original diagram direction was this way I 2 this way I 2, but as soon as this is off direction has changed. So, minus sign will be there

right because this is off direction of I 2 is change from the original one, that is why a minus sign is there right and A21 will be minus I 2 upon IL, that is minus 2 minus j point 5 upon 9.2 minus j 2.3 that will become actually minus 0.2174 right that is your what you call your A21 right.

Then from the branch 3 it is simple actually, but the numerator denominator denominator you always IL. So, A31 will be I 3 upon IL. So, I 3 you know 7.2 minus j 1.8 divided by 9.2 minus j 2 point. that is coming 0.7826 right. Similarly for branch 4 I 4 1 is equal to I 4 upon IL right. So, it is 2 minus j 0.5, divided by 9.2 minus j 2.3 that is 0.2174 right.

Similarly, the plant one is off I mean this one this one you will do of your own this plant one is off right as soon as plant one is off right; that means, no current will come from generator. So, I 1 will become 0, right and plant 2 is this. So, this current direction all other will remain same, but this one I 1 will become 0, that is why A12 is 0 rest I have computed.

(Refer Slide Time: 19:49)

$$\rightarrow A_{31} = \frac{I_3}{I_L} = \frac{(7.2 - j1.8)}{(9.2 - j2.3)} = \underline{0.7826}$$

$$\rightarrow A_{41} = \frac{I_4}{I_L} = \frac{(2 - j0.5)}{(9.2 - j2.3)} = \underline{0.2174}$$

Similarly, if plant-1 is off, using eqn.(79), we have

- $\rightarrow A_{12} = 0.0$
- $\rightarrow A_{22} = 0.7826$
- $\rightarrow A_{32} = 0.7826$
- $\rightarrow A_{42} = 0.2174$

So, accordingly you can easily compute this right following the same procedure right.

So, I am giving you the final one A 21 is equal to 0.7826, A32 is equal to 07826 and A 42 is equal to 0.2174 right. So, once; that means, all the a coefficient are computed.

(Refer Slide Time: 21:10)

Now

$$V_1 = V_r + I_1 Z_1 = 1 \angle 0^\circ + (4-j1)(0.02+j0.08)$$

$$\rightarrow \therefore V_1 = \underline{1.198 \angle 14.5^\circ}, \quad \underline{\delta_1 = 14.5^\circ}$$

$$V_2 = V_r + I_2 Z_2 = 1 \angle 0^\circ + (3.2-j0.8)(0.02+j0.08)$$

$$\rightarrow \therefore V_2 = \underline{1.153 \angle 12^\circ}, \quad \underline{\delta_2 = 12^\circ}$$


$$\rightarrow I_{g1} = (4-j1) = 4.123 \angle -14^\circ; \quad \therefore \delta_1 = -14^\circ$$

$$\rightarrow I_{g2} = I_2 + I_4 = (3.2-j0.8) + (2-j0.5) = (5.2-j1.3)$$

Now again we will come back to that diagram just hold on this diagram right. So, in that in this diagram if this is the reference voltage right and all the branch impedance Z_1 Z_2 Z_3 Z_4 all are given all data are given here, all data are given here; that means, V_1 is equal to you can write V_r plus $I_1 Z_1$ right. So, V_1 is equal to your V_r this is a reference voltage V_r one angle 0° right. So, it is actually it is V_r right this is V_r .

So, V_r , V_1 is equal to V_r plus $I_1 Z_1$. So, V_r is one angle 0° , I_1 is known and Z_1 is also known everything is known. So, you will get V_1 is equal to 1.198 angle 14.5 degree; that means, delta one is equal to 14.5 degree that is the v your what you call at bus one the voltage angle is 14.5 degree. Similarly V_2 is equal to V_r plus $I_2 Z_2$ right. So, V_r is one angle 0° and I_2 is equal to 3.2 minus j 0.8 and this is Z_2 0.02 plus j 0.08 then we V_2 is 1.153 angle, 12 degree then we delta 2 is equal to 12 degree right.

(Refer Slide Time: 22:35)

$$\begin{aligned} & \rightarrow \therefore V_1 = \underline{1.198} \angle 14.5^\circ, \quad \underline{\delta_1 = 14.5^\circ} \\ & V_2 = V_\gamma + I_2 Z_2 = 1 \angle 0^\circ + (3.2 - j0.8)(0.02 + j0.08) \\ & \rightarrow \therefore V_2 = \underline{1.153} \angle 12^\circ, \quad \underline{\delta_2 = 12^\circ} \\ & \rightarrow I_{g1} = (4 - j1) = 4.123 \angle -14^\circ; \therefore \underline{\alpha_1 = -14^\circ} \\ & \rightarrow I_{g2} = I_2 + I_4 = (3.2 - j0.8) + (2 - j0.5) = (5.2 - j1.3) \\ & \quad = \underline{5.36} \angle -14^\circ; \therefore \underline{\alpha_2 = -14^\circ} \end{aligned}$$


That means your general current I_{g1} is given, this generator current your I_1 is actually I_{g1} is equal to I_1 right and I_1 data is given $4 - j1$ this is given; that means, your I_{g1} is equal to $4 - j1$ that is 4.123 angle minus 14 degree. So, α_1 is equal to minus 14 degree; that means, that current angle generator one current angle is minus 14 degree, and I_{g2} is equal to $I_2 + I_4$ because this is I_{g2} at this point you apply Kirchhoff's first law at this bus. So, I_{g2} is equal to $I_2 + I_4$ right therefore, this I_{g2} is equal to $I_2 + I_4$. So, I_2 is given I_2 is given I_4 is also given.

So, you put it here $I_2 + I_4$ $3.2 - j0.8$, plus $2 - j0.5$ that actually coming a 5.36 angle minus 14 degree, then α_2 that is the angle of the a current of generator 2 is minus 14 degree right.

(Refer Slide Time: 23:44)


(34)

$$\therefore \cos(\alpha_1 - \alpha_2) = \cos 0^\circ = 1.0$$

Generating station power factors are:

$$\cos \phi_1 = \cos(14.5^\circ + 14^\circ) = 0.8788$$
$$\cos \phi_2 = \cos(12^\circ + 14^\circ) = 0.8988$$

Loss coefficients are: (Eqn. 85)

$$B_{pq} = \frac{\cos(\alpha_p - \alpha_q)}{|V_p||V_q| \cos \phi_p \cos \phi_q} \sum_{k=1}^{NBR} A_{kp} A_{kq} R_k$$


So, once you have got this then this thing your cosine alpha 1 minus alpha 2 is equal to one right because both alpha 1 and alpha 2 just both alpha 1 and alpha 2 they are same 14 minus 14 degree minus 14 degree. So, alpha 1 minus alpha 2 is 0. So, it is cos 0 is equal to 1 right and generating station power factor that is cosine of 14.5 plus 14 degrees.


So, take for example, V 1 it is 14.5 degree and if you take the current I g 1 right your I g 1 is minus 14 degree.

(Refer Slide Time: 24:27)

Generating station power factors are:

$$\cos \phi_1 = \cos(14.5^\circ + 14^\circ) = 0.8788$$
$$\cos \phi_2 = \cos(12^\circ + 14^\circ) = 0.8988$$

Loss coefficients are: (Eqn. 85)

$$B_{pq} = \frac{\cos(\alpha_p - \alpha_q)}{|V_p||V_q| \cos \phi_p \cos \phi_q} \sum_{k=1}^{NBR} A_{kp} A_{kq} R_k$$


So, from a reference line right it is something like this your I have told you earlier also. So, if you this is a reference line right. So, this is your voltage angle this is your V 1 these angle is actually 14.5 degree, and the current is this side lagging actually from the reference if you take this is I g 1 right and it is a angle is your 14 degree it is lagging.

So, angle between this voltage V 1 and the current I g 1, this 14.5 plus 14 degree right; that means, this your this your where it has gone here right; that means, it is cos phi 1 it cos 14.5 plus 14 degree is equal to 0.8788 similarly for generator 2 same thing it is cosine 12 degree plus 14 degree that is 0.8988 degree sorry 0.8988 sorry right.

So, now loss coefficient equation 85 right this is the general formula Bp q is equal to cos alpha p minus alpha q upon Vp Vq magnitude of course, right cos phi p cos phi q sigma k is equal to 1 to NBR, Akp a Akq into Rk right now here total number of branch for this network is 4 we have total 1 2 3 4, 4 branches are there; that means, your NBR is equal to 4 the total number of branch right. So, now your NBR is equal to 4 and say P and p is equal to q is equal to one then you find out B 11.

(Refer Slide Time: 26:05)

(13)

$$NBR = 4, \quad p = q = 1$$

$$\rightarrow B_{11} = \frac{\sum_{k=1}^4 A_{k1}^2 R_k}{|V_1|^2 (\cos \phi_1)^2} = \frac{R_1 A_{11}^2 + R_2 A_{21}^2 + R_3 A_{31}^2 + R_4 A_{41}^2}{(|V_1| \cos \phi_1)^2}$$

$$\rightarrow B_{11} = \frac{0.02 \times (1)^2 + 0.02 \times (-0.2174)^2 + 0.02 \times (0.7824)^2 + (0.00) \times (0.224)^2}{(1.198 \times 0.8788)^2}$$

$$\therefore B_{11} = 0.02485 \text{ pu.}$$

Similarly, when $p = q = 2$

So, k is equal to 1 to 4 A K 1 square into Rk divided by V 1 square cos square phi 1 right is equal to we expand this term R 1 A 11 square plus R 2 A 21 square, R 3 A 31 square plus R 4 A 41 square all the branch resistance you know because impedance is given. So, real part is R right.

So, it is $V^2 \cos^2 \phi_1$. So, $V^2 \cos^2 \phi$ whole square right. So, put all these values because now all a coefficient known R_1 is known, $\cos \phi_1$ is known V_1 is known everything is known just you substitute you will get B_{11} is equal to 0.02485 per unit. Similarly when p is equal to q is equal to 2 right when p is equal to q is equal to 2 you will get B_{22} is equal to k is equal to one to 4, $A_k^2 R_k$ divided by $V^2 \cos^2 \phi$. So, writing as a whole square right.

(Refer Slide Time: 26:58)

$$\begin{aligned} \rightarrow B_{22} &= \frac{\sum_{k=1}^4 A_{k2}^2 R_k}{(V_2 \cos \phi_2)^2} \\ \rightarrow \therefore B_{22} &= \frac{R_1 A_{12}^2 + R_2 A_{22}^2 + R_3 A_{32}^2 + R_4 A_{42}^2}{(V_2 \cos \phi_2)^2} \\ \rightarrow \therefore B_{22} &= \frac{0.02 \times (0)^2 + 0.02 \times (0.7826)^2 + 0.01 \times (0.7826)^2 + 0.01 \times (0.2174)^2}{(1.153 \times 0.8988)^2} \\ \rightarrow \therefore B_{22} &= \underline{0.01755 \text{ pu.}} \end{aligned}$$

So, that means, you expand this and all the values are known to you, you substitute all these values you substitute all have been done listen all this all this calculations done by me only. So, if I that this every lecture I repeat this once or twice if you find any calculation or anything I will appreciate if you can mail me that where is the error then if any calculation error, then I can rectify myself I can correct this right. So, this B_{22} will be 0.01755 right for.

Thank you for B_{12} we will come again.