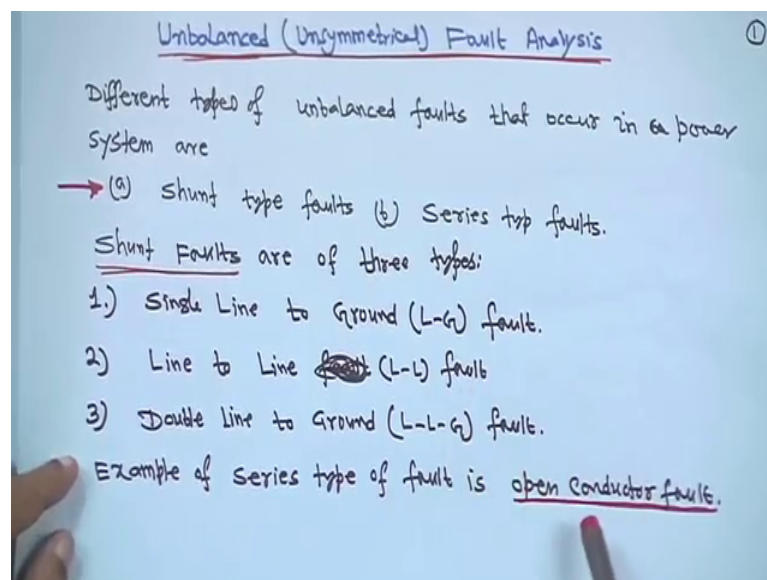


Power System Analysis
Prof. Debapriya Das
Department of Electrical Engineering
Indian Institute of Technology, Kharagpur

Lecture - 53
Symmetrical Components (Contd.)

In the previous class we ended with that unbalanced or unsymmetrical fault analysis. So, different types of unbalanced fault that occur in a power system is one is called shunt type fault another series type of faults. So, shunt faults are of you know three types: that is single line to ground fault that is we call L-G fault, then line to line fault we call L-L fault.

(Refer Slide Time: 00:47)




And double line to ground fault that is L-L-G fault. So, these are the fault very common in transmission system, but I mean it is not like that simultaneously if fault occurs in one phase say line to ground fault another two phase is line to line fault. These kinds of occurrence are very rare, but this three are very common. And the example of series type of fault is that open conductor that is open conductor fault. For example one phase suppose one conductor has broken or may be two conductors broken, but this are very rare faults but still will see, will go for this kind of analysis.

So, already we have studied the symmetrical component and positive negative and zero sequence components. And in to that most important is that zero sequence network for

the fault studies that is more important. So, first what you will do; will study that your line to ground fault that is your L-G fault.

(Refer Slide Time: 01:51)

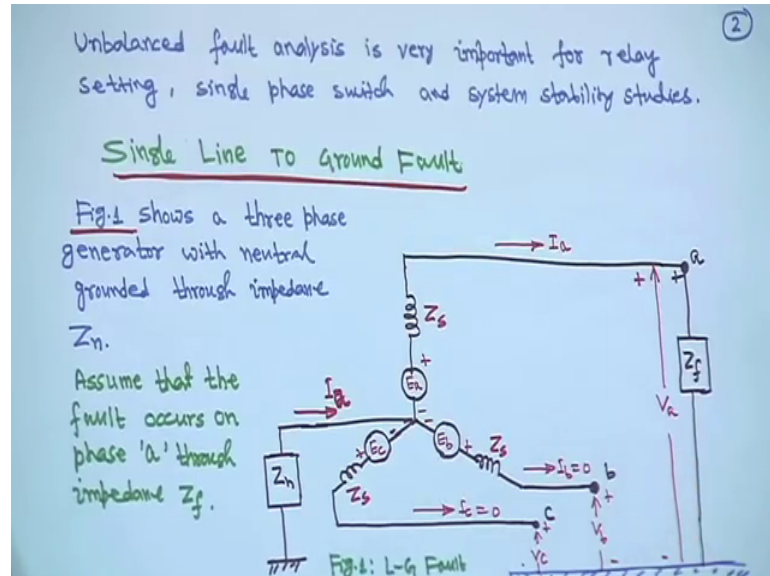

For example: suppose that your single line to ground fault. So, suppose this is figure one suppose at phase a that there is a single line to ground fault right. Therefore, your phase b and c the bound I mean that is the boundary condition right that is I_b will be 0 and I_c also will be 0, because we assume in that fault has occurred this thing. So, figure this one is shows a three phase generator with neutral grounded through impedance Z_n , then neutral is grounded. And we are assuming that fault occurs at phase a through impedance Z_f . So, fault impedance is there so it is your Z_f . That means, this V_a is equal to actually this your I_a into Z_f . And your this thing that current through phase b and phase c it is 0; I_b is equal to 0 I_c is equal to also 0 because fault has occurred here.

(Refer Slide Time: 02:59)

Also assuming that the generator is initially on no load ⁽³⁾
and the boundary conditions at the fault point are:

$$I_b = 0 \quad \dots (1)$$
$$I_c = 0 \quad \dots (2)$$
$$V_a = Z_f I_a \quad \dots (3)$$

The symmetrical components of the fault currents are:

$$\begin{bmatrix} I_{a1} \\ I_{a2} \\ I_{a0} \end{bmatrix} = \frac{1}{3} \begin{bmatrix} 1 & \rho & \rho^2 \\ 1 & \rho^2 & \rho \\ 1 & 1 & 1 \end{bmatrix} \begin{bmatrix} I_a \\ 0 \\ 0 \end{bmatrix}$$
$$\therefore I_{a1} = I_{a2} = I_{a0} = \frac{1}{3} I_a \quad \dots (4)$$

So, in this case assuming that we have we will make some assumption that generator is initially on no load and the boundary conditions of the fault point are that I_b is equal to 0 and I_c also is equal to 0, because fault has occurred in phase a. And V_a is equal to $Z_f I_a$. So, this is the fault current this I_a is going through the fault, so V_a is equal to $Z_f I_a$.

So, the symmetrical component of the fault currents are we know this from our symmetrical component analysis, we know this that I_{a1} is equal to I_{a2} is equal to I_{a0} is equal to one-third $1 \beta \beta^2$, $1 \beta^2 \beta$ and $1 \ 1 \ 1$: this is I_a , I_b is equal to 0, I_c is equal to 1.

Therefore this I_{a1} is equal to I_{a2} is equal to I_{a0} is equal to one-third I_a , you will find I_{a1} also one-third I_a , I_{a2} also one-third I_a , and I_{a0} also one-third I_a . That means, I_{a1} is equal to I_{a2} is equal to I_{a0} all are equal that is one-third of the I_a . This is $I_b = 0$ is you a marked equation 1, $I_c = 0$ we have marked equation 2 and V_a is equal to $Z_f I_a$ we have marked equation 3. And if you express equation 3 that equation 3 that V_a is equal to actually.

(Refer Slide Time: 04:29)

Expressing eqn. (3) in terms of symmetrical components, we get, ⁽¹⁾

$$V_{a1} + V_{a2} + V_{a0} = Z_f I_a = 3Z_f I_{a1} \dots (5) \quad [\because I_a = 3I_{a1}]$$

→ As per eqns (4) and (5), positive, negative and zero sequence currents are equal and the sum of sequence voltages equals $3Z_f I_{a1}$.

→ These equations suggest a series connection of ~~sequence~~ sequence networks through an impedance $3Z_f$.

In many practical applications, the positive and negative sequence impedances are found to be equal, if the generator is solidly grounded $Z_n = 0$ and for bolted faults $Z_f = 0$.

Fig. 2 shows the equivalent circuit connection.


V_a is equal to V_{a1} plus V_{a2} plus V_{a0} . So V_a is equal to Z_f in to I_a and is equal to Z_f in to I_a , but your I_a is equal to your $3I_{a1}$, because here you know I_{a1} is equal to I_{a2} is equal to I_{a0} one-third I_a . So, I_a is equal to 3 into I_{a1} . So, here we are putting $3Z_f I_{a1}$. In bracket I have write in I_a is equal to $3I_{a1}$. That means, as per equation 4 and 5 then if you come to this equation 4 that all I_{a1} I_{a2} I_{a0} I, I mean they are all equal is equal to one-third I . Its close actually, it is a series connection of the positive negative and zero sequence network, because all component positive negative and zero sequence components they are same and they are equal to one-third I_a .

That means, an equation and this equation 5 V_{a1} plus V_{a2} plus V_{a0} that is $3Z_f$ in to I_{a1} . That means, this positive negative and zero sequence currents are equal and the sum of the sequence voltages is equal to $3Z_f I_{a1}$.

So, these equations suggest particularly this one equation 4, because all your sequence currents are equal. Therefore, the these equations suggest a series connection of sequence network; twice I have written sequence, sequence network through an impedance $3Z_f$; because it is $3Z_f$, this is $3Z_f$ in to I_{a1} . In many practical applications the positive and negative sequence impedances are found to be equal. That also we have discussed before. If the generator is solidly grounded then Z_n is equal to 0. That means, in this thing if your generator is solidly grounded then this Z_n will be 0. And for bolted faults that Z_f will be 0.

That means, figure two shows the equivalent circuit connection. So, how we have made this connection? I mean you will make it like this that first what we will do it is a series connection.

(Refer Slide Time: 06:54)

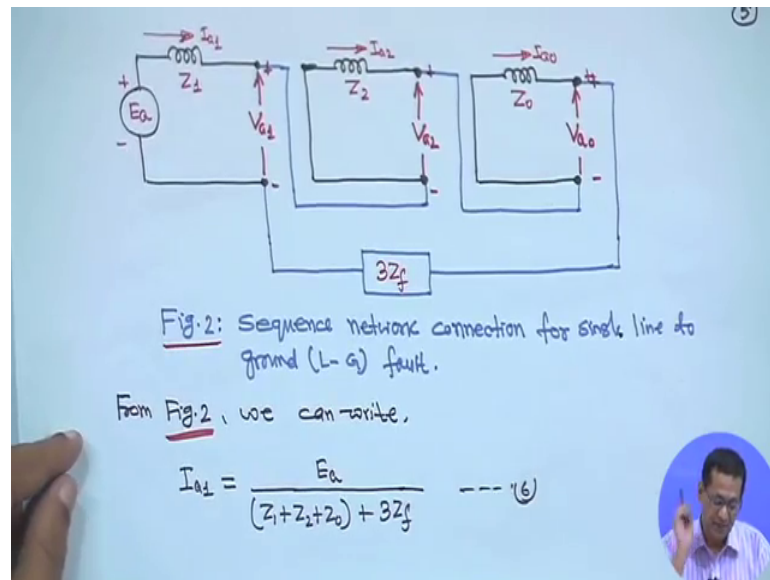

So, first the black ink I have made it, this is your positive sequence. First you make this is your positive sequence network, so E_a will be there plus minus this is Z_1 positive sequence impedance and current is I_{a1} . Next that black one there is other two there will be no voltage source, so this is Z_2 and this voltage is V_{a2} . And for zero sequence this is Z_0 current is I_{a0} and this is your V_a .

Now as it will be series connection and all I_{a1} I_{a2} and I_{a0} currents are same, is equal to one-third I_a all currents as same so this series connection this is plus this blue one plus will be connected to the minus. Similarly here from negative sequence that from the plus terminal it will be connect to the minus and finally from zero sequence plus will be connected to the minus through $3Z_f$, because your V_{a1} plus V_{a2} plus V_{a0} is equal to $3Z_f$.

So, in this case you can see that this I_{a1} I_{a2} I_{a0} all are same, because this current is flowing like this, flowing like this, flowing like this, and flowing like this and returning to that here. And this is actually sequence connection for single line to ground fault. And if you apply what you call that KVL thing then will find I mean will come to that. So, V_{a1} plus V_{a2} plus your V_{a0} that will be equal to your $3Z_f$ in to I_{a0} because all are

same actually I_{a1} I_{a2} I_{a0} all three are equal is equal to one-third I_a . So, in this case now from this figure we can write that I_{a1} is equal to this is the voltage a divided by your Z_1 plus Z_2 plus Z_0 and plus $3Z_f$, because it is a series circuit. If I make this one as something like this, it is a series circuit this is your Z_1 , this is Z_2 , this is Z_0 , and this is say your $3Z_f$ and this is your voltage E_a , this is Z_1 , this is Z_2 , this is Z_0 , and this is $3Z_f$. And current is here your I_{a1} is equal to I_{a2} is equal to I_{a0} .

So, that is why as all three as same you are writing that I_{a1} is equal to E_a up on Z_1 plus Z_2 plus Z_0 plus $3Z_f$. So, this is that simple one. So, fault current I_a then is given by because this is I_{a1} , therefore fault current is then given by I_a is equal to $3I_{a1}$. So, I_{a1} is equal to this 3 in to then I_{a1} you substitute here. This is equation 7. Now under L-G fault condition the voltage of the line b to ground.

Now V_b is equal to underline to ground fault we know this expression $\beta^2 V_{a1}$ plus βV_{a2} plus V_{a0} you know β is equal to e to the power $j120$ degree. That we have seen also. Therefore, that V_{a1} from this diagram, from this positive sequence diagram $Z_1 I_{a1}$ I am just telling for my this thing. From this diagram $Z_1 I_{a1}$ plus V_{a1} minus E_a is equal to 0 . So, I am writing $Z_1 I_{a1}$ plus V_{a1} minus E_a is equal to 0 here.

That means, V_{a1} is equal to E_a minus $Z_1 I_{a1}$. So, here we are substituting V_{a1} instead of V_{a1} you are like β^2 in to E_a minus $Z_1 I_{a1}$. Now plus β now V_{a2} now in the negative sequence you apply again in this network KVL. So, it will be $Z_2 I_{a2}$ plus V_{a2} is equal to 0 . So, $Z_2 I_{a2}$ plus V_{a2} is equal to 0 . So, V_{a2} is equal to minus $Z_2 I_{a2}$.

Similarly, in the zero sequence network $Z_0 I_{a0}$ plus V_{a0} is equal to 0 , therefore V_{a0} will be minus $Z_0 I_{a0}$. So, here I am writing V_{a0} is equal to minus $Z_0 I_{a0}$. So, here in the expression of V_{a1} we are substituting E_a minus $Z_1 I_{a1}$ in to β^2 , then plus β in to that V_{a2} is equal to minus $Z_2 I_{a2}$ plus this minus $Z_0 I_{a0}$. Or V_b is equal to we can write that I_{a1} is equal to I_{a2} is equal to I_{a0} is equal to I_a by 3 we know that. So, it will be E_a minus Z_1 in to I_a by 3 plus β in to minus Z_2 ; instead of I_{a2} you write I_a by 3 plus minus $Z_0 I_{a0}$ is equal to I_a by 3 . This is equation 8.

Now from this equation 7 we are writing from equation 8 and 7, so from this equation what you will do you will this I_a is equal to this expression $3E_a$ up on Z_1 plus Z_2 plus Z_0 plus $3Z_f$ this I_a you put it here you put in this equation 8; you put in equation 8 and you please simplify such that I am giving you the final expression.

(Refer Slide Time: 12:22)

⑦

$$V_b = E_a \cdot \frac{[3\beta^2 Z_f + Z_2(\beta^2 - \beta) + Z_0(\beta - 1)]}{(Z_1 + Z_2 + Z_0) + 3Z_f} \dots (9)$$

Similarly,

$$V_c = \beta V_{a1} + \beta^2 V_{a2} + V_{a0}$$

$$\therefore V_c = \beta \left(E_a - Z_1 \frac{I_a}{3} \right) + \beta^2 \left(-Z_2 \frac{I_a}{3} \right) + \left(-Z_0 \frac{I_a}{3} \right) \dots (10)$$

Using eqn. (7) and (10), we get,


$$\therefore V_c = E_a \frac{[3\beta Z_f + Z_2(\beta - \beta^2) + Z_0(\beta - 1)]}{(Z_1 + Z_2 + Z_0) + 3Z_f} \dots (11)$$

If you simplify you will get V_b is equal to E_a into $3\beta^2 Z_f$ plus Z_2 in to $\beta^2 - \beta$ plus $Z_0(\beta - 1)$ divided by $Z_1 + Z_2 + Z_0 + 3Z_f$. This is equation 9. Similarly if you do in similar fashion for phase voltage your V_c then V_c will be βV_{a1} plus $\beta^2 V_{a2}$ plus V_{a0} . Then again same as before substitute V_{a1} is equal to $E_a - Z_1 \frac{I_a}{3}$ because I_{a1} is equal to $I_a/3$. Similarly plus β^2 minus Z_2 in to I_{a2} I_{a2} is equal to $I_a/3$ plus in bracket minus Z_0 in to $I_a/3$; I_{a0} is equal to $I_a/3$ So, equation 10.

Here also you substitute expression of I_a from your equation 7. If you substitute expression of I and simplify then you will get V_c is equal to E_a into $3\beta Z_f$ plus Z_2 in to $\beta - \beta^2$ plus $Z_0(\beta - 1)$ divided by $Z_1 + Z_2 + Z_0 + 3Z_f$. And if fault impedance is 0 then this term will be drop and this term will be dropped. From this equation 11, similarly fault impedance is 0 then from this equation also this term will be dropped if Z_f is equal to 0 this will be dropped.

So, that is for your single line to ground fault, these are the expression.

(Refer Slide Time: 14:03)

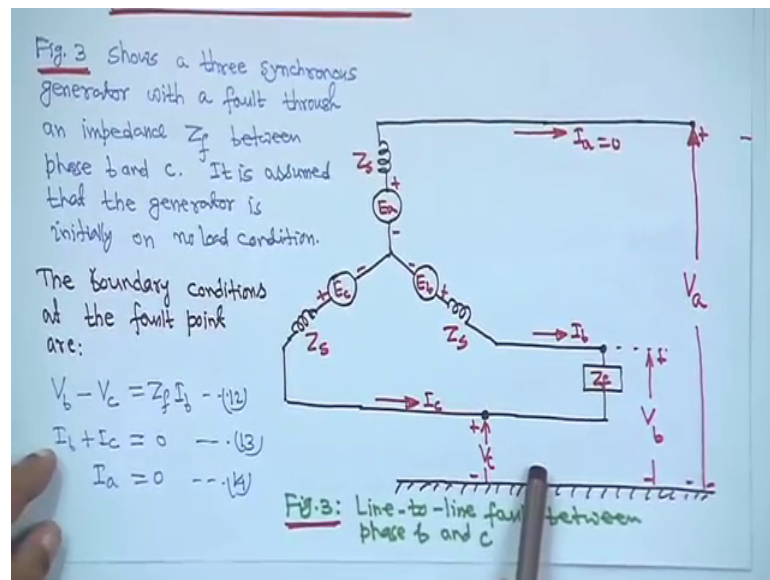

Similarly, now let us consider line to line fault that is L-L fault. So, line to line fault. So, suppose in phase b and c we are assuming there is a line to line fault. So, figure 3 actually this is figure 3; it shows a three synchronous generator with a fault through an impedance Z_f . So, there is a fault, line to line through an impedance Z_f when Z_f is there, if it is not there it will be your Z_f will be 0. So, between phase b and c it is assumed that the generator is initially on no load condition.

Now the boundary condition at the fault point are, so fault this is a line to line fault through impedance Z_f that means, I_a will be equal to 0. And second thing is that V_b this is ground as reference. So, $V_b - V_c$ this what you call we can say this is $Z_f I_b$ in to I_b , but question is that this is I_c this is I_b ; that means, $I_b + I_c$ if you is equal to 0. Because I_c we have taken this direction, I_b this direction at point that is basically it is going I_b flowing this direction, this is this direction so opposite direction, so $I_b + I_c$ is equal to 0.

And $V_b - V_c$ it will be $Z_f I_b$, because if you apply your KVL like your this way, so it will be your $V_b - V_c$ is equal to; that means I mean in this way we put I_b in to Z_f plus $V_c - V_b$ is equal to 0. Therefore, $V_b - V_c$ is equal to I_b in to Z_f . That means, $I_b + I_c$ is equal to 0 this is another condition and I_a is equal to 0. This are all the you call sometimes boundary condition at what you call fault point. That means, now with this with this fault condition will try to find out other things.

(Refer Slide Time: 16:11)

The Symmetrical components of the fault currents are:

$$\begin{bmatrix} I_{a1} \\ I_{a2} \\ I_{a0} \end{bmatrix} = \frac{1}{3} \begin{bmatrix} 1 & \beta & \beta^2 \\ 1 & \beta^2 & \beta \\ 1 & 1 & 1 \end{bmatrix} \begin{bmatrix} I_a \\ I_b \\ I_c \end{bmatrix} \dots (15)$$

Substituting $I_a = 0$, $I_c = -I_b$ in eqn(15), we get

$$\begin{bmatrix} I_{a1} \\ I_{a2} \\ I_{a0} \end{bmatrix} = \frac{1}{3} \begin{bmatrix} 1 & \beta & \beta^2 \\ 1 & \beta^2 & \beta \\ 1 & 1 & 1 \end{bmatrix} \begin{bmatrix} 0 \\ I_b \\ -I_b \end{bmatrix} \dots (16)$$

From which we get,

$$I_{a2} = -I_{a1} \dots (17)$$

$$I_{a0} = 0 \dots (18)$$

$$I_{a1} = \frac{1}{3}(\beta - \beta^2)I_b$$

$$I_{a2} = \frac{1}{3}(\beta^2 - \beta)I_b$$

$$\therefore I_{a2} = -\frac{1}{3}(\beta - \beta^2) = -I_{a1}$$

So, the symmetrical components of the fault currents are: that means, we know this I_{a1} I_{a2} I_{a0} is equal to one-third $1 \beta \beta^2$, $1 \beta^2 \beta$ and $1 1 1$, this is $I_a I_b I_c$. So, this is actually rewriting this equation from the previous topic your symmetrical component.

Now I_a is equal to 0 and I_c is equal to minus I_b , this are the boundary condition for your line to line fault through impedance Z_f . So, if you put this we are putting I_a is equal to 0, I_b will remain as I_b and I_c is equal to minus I_b . So, this is actually minus I_b . From which you will get that I_{a2} is equal to minus I_{a1} , I mean from this equation another will get I_{a0} is equal to 0 that means no zero sequence current. So, if you take I_{a1} here, I have written here that I_{a1} is equal to from here one-third your β minus β^2 I_b , and I_{a2} is equal to from this equation only one-third β^2 minus β I_b .

That means I_{a2} is equal to minus one third β minus β^2 is equal to then minus I_{a1} . That is why we are writing from this I_{a2} is equal to minus I_{a1} and I_{a0} is equal to 0. So, that is line to line fault there is no zero sequence current. And I when I_{a2} is equal to minus I_{a1} I mean it is just in opposition. So, will see later all this.

(Refer Slide Time: 17:52)

The symmetrical components of voltages under fault are:

$$\begin{bmatrix} V_{a1} \\ V_{a2} \\ V_{a0} \end{bmatrix} = \frac{1}{3} \begin{bmatrix} 1 & \beta & \beta^2 \\ 1 & \beta^2 & \beta \\ 1 & 1 & 1 \end{bmatrix} \begin{bmatrix} V_a \\ V_b \\ V_c \end{bmatrix} \dots (19)$$

Substituting $V_c = V_b - Z_f I_b$ in eqn(19), we get.

$$\begin{bmatrix} V_{a1} \\ V_{a2} \\ V_{a0} \end{bmatrix} = \frac{1}{3} \begin{bmatrix} 1 & \beta & \beta^2 \\ 1 & \beta^2 & \beta \\ 1 & 1 & 1 \end{bmatrix} \begin{bmatrix} V_a \\ V_b \\ V_b - Z_f I_b \end{bmatrix} \dots (20)$$

With this the symmetrical component of the, your what you call symmetrical component of the voltages under fault are that V_{a1} V_{a2} V_{a0} we know this repeating from the symmetrical component only that one-third 1 1 1, beta beta square 1, beta square beta 1, V_a V_b V_c . Now we know V_c is equal to from this equation 12 V_c is equal to V_b minus $Z_f I_b$. So, this V_b minus $Z_f I_b$ will be there, but this V_c is equal to V_b minus $Z_f I_b$ we are substituting in equation 19. So, here it is V_b minus $Z_f I_b$. This is equation 20.

(Refer Slide Time: 18:56)

From eqn(20), we get,

$$3V_{a1} = V_a + (\beta + \beta^2)V_b - \beta^2 Z_f I_b \dots (21)$$

$$3V_{a2} = V_a + (\beta + \beta^2)V_b - \beta Z_f I_b \dots (22)$$

Subtracting eqn(22) from eqn(21), we get,

$$3(V_{a1} - V_{a2}) = (\beta - \beta^2) Z_f I_b \dots (23)$$

$$\therefore 3(V_{a1} - V_{a2}) = j\sqrt{3} Z_f I_b \dots (24)$$

~~Handwritten scribbles and a boxed formula $\beta - \beta^2 = j\sqrt{3}$ are visible at the bottom of the slide.~~

Now from equation 20, what you will get you make a first V_{a1} I mean this one V_{a1} if you make it will be one-third of everything, so cross multiplication I am writing $3V_{a1}$ is equal to $V_a + \beta + \beta^2 V_b - \beta^2 Z_f I_b$. That means, from this equation you can write V_{a1} actually one-third in to $V_a + \beta V_b + \beta^2$ in to $V_b - Z_f I_b$. If you simplify and cross multiply by 3 this side then actually you will get $3V_{a1}$ is equal to $V_a + \beta + \beta^2 V_b - \beta^2 Z_f I_b$. This is actually from this one, just you write one line, I am not writing understandable very simple thing.

Similarly $3V_{a2}$: similarly we are making it that this V_{a2} is equal to one-third of this, so $3V_{a2}$ from this equation will become $V_a + \beta + \beta^2 V_b - \beta^2 Z_f I_b$, this is equation 22. Now subtracting equation 22 this one you subtract from this equation 21 you subtract. If you do so you will get $3V_{a1} - 3V_{a2}$ is equal to $V_a - V_a + \beta - \beta + \beta^2 V_b - \beta^2 V_b - \beta^2 Z_f I_b + \beta^2 Z_f I_b$. This is equation 23. If you subtract V_a will be cancel, even $\beta + \beta^2$, $\beta + \beta^2 V_b$ also will be cancel ultimately it will remain $\beta^2 Z_f I_b - \beta^2 Z_f I_b$. This is equation 23.

Look we are not doing anything on your what you call on V_{a0} . The reason is very simple that initially we have seen that zero sequence current I_{a0} is equal to 1. That means, in that equivalent circuit that zero sequence network will not appear for line to line fault, because I_{a0} is equal to 0 will come to that. That means this $\beta - \beta^2$ if you please simplify β is equal to e^{j120° , so $\beta - \beta^2$ actually it will become j in to $\sqrt{3}$. That means, this $\beta - \beta^2$ we are putting here j in to $\sqrt{3}$ into $Z_f I_b$.

Therefore, from equation 16, again I have to just hold on again I have to go back to equation 16. From equation your 16 this one we can write that one-third $\beta - \beta^2 I_b$ minus $\beta^2 I_b$; that means, from this equation 16 I_{a1} is equal to one-third $1 - 0$ then $\beta - \beta^2 I_b$ minus $\beta^2 I_b$. So, that is why from equation 16 we are writing that I_{a1} is equal to one-third then $\beta - \beta^2 I_b$ minus $\beta^2 I_b$ is equal to one-third $\beta - \beta^2$ in to I_b .

So, I_{a1} is equal to one-third and $\beta - \beta^2$ is equal to j in to $\sqrt{3}$; I gave you that $\beta - \beta^2$ is equal to j in to $\sqrt{3}$. So, here if $\beta - \beta^2$ is equal to you put here j in to $\sqrt{3}$. So, I_{a1} is equal to one-third in to $j\sqrt{3}$


into I_b is equal to j by $\sqrt{3} I_a$. That means, I_b is equal to $\sqrt{3}$ up on $j I_a$ numerator and denominator multiply by j , so it will be j^2 square minus 1 so it will be I_b is equal to minus $j \sqrt{3}$ into I_a . This is equation 25.

Now using equation 24 and your 25; that means in this equation that equation 24 in this equation you put the expression of I_b from equation 25. So, in this equation you put I_b is equal to minus $j \sqrt{3}$ into I_a ; that is why using equation 24 and 25 we get you if you put in this equation V_a is equal to your minus $j \sqrt{3} I_a$ then you will get $V_a - V_b$ is equal to Z_f in to I_a . This is equation 26.

So, equation 17 and 26, so I have to come back to equation 17; this equation 17; that means, $I_a = -I_b$ this equation 17. Even 18 also it suggest because $I_0 = 0$ means zero sequence network will not come up here because I_0 is equal to 0. So, from equation 17 and from equation 26 that means, this equation, can be represented by connecting the positive and your negative sequence networks in opposition and the equivalent circuit is shown- I will show you.

So, from this equation only you have to judge that how this network will be connected. So, if you so, look how we can make it.

(Refer Slide Time: 24:02)

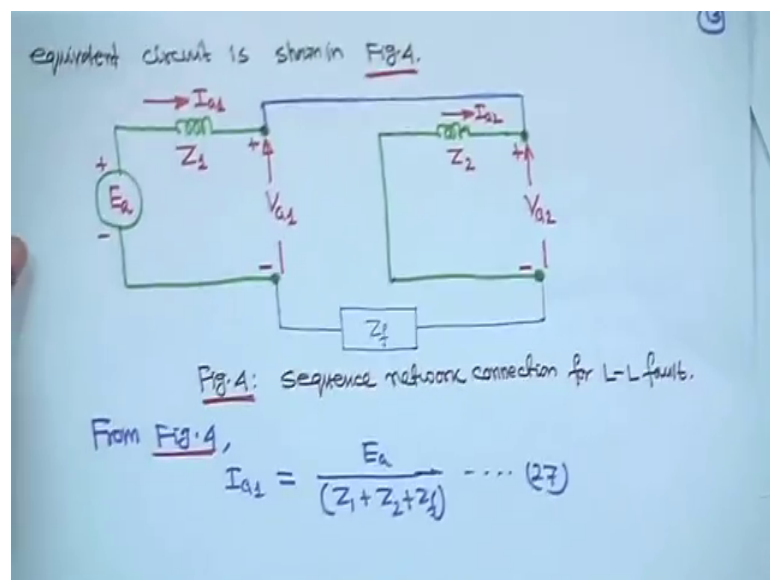

That in this case, this is our green color, this is our positive sequence network this is our negative sequence network, but we know your I_a2 is equal to your minus I_a1 . That

means, I_{a1} is equal to minus I_{a2} other way I_{a2} is equal to minus I_{a1} ; that means, I_{a1} is equal to minus I_{a2} , that means there is no opposition. That means, this is plus minus V_{a1} , plus minus it is V_{a2} negative sequence. So, as there in opposition plus will be connected to the plus.

And similarly minus is connected to the minus. And from this equation if you apply KVL then you will see V_{a1} minus V_{a2} is equal to this condition, Z_f in to I_{a1} . So, this is your V_{a1} this is your V_{a2} . Apply now KVL here then it will be like this plus your, if you come like this then plus your V_{a2} . Then this current is your what you call if you take this way I_{a1} then it will be I_{a1} Z_f that is actually nothing but minus I_{a2} right minus V_{a1} is equal to 1. That means, you will get V_{a1} minus V_{a2} is equal to $Z_f I_{a1}$.

And if I make it for you just this thing; if you make it like this. So, this is V_{a2} , so it is plus so it is V_{a2} right then this I_{a1} current let us take suppose this I_{a1} movingly of course, I_{a1} is equal to minus I_{a2} , but will consider this I_{a1} only moving like this, so it is your I_{a1} Z_f and then minus V_{a1} is equal to 0. That means, V_{a1} minus V_{a2} is equal to $I_{a1} Z_f$.

So, that is why this equation V_{a1} minus V_{a2} ; this two suggest actually current direction that it will be opposition. And zero sequence network will not come because I have shown you that I_{a0} is equal to 1. So, this is that your line to line fault that equivalent circuit connection positive sequence and negative sequence. Through that impedance of course is there.

Now from this figure you can write I_{a1} is equal to E_{a1} up on Z_1 plus Z_2 plus Z_f . I mean this direction if you take and apply your KVL like this then you will get I_{a1} is equal to E_{a1} up on Z_1 plus Z_2 plus Z_f . So, this is equation 27. And as it is line to line fault at the beginning we have seen that I_b is equal to your minus I_c .

(Refer Slide Time: 26:41)

(14)

Also

$$I_b = -I_c = \frac{-j\sqrt{3} E_a}{(Z_1 + Z_2 + Z_f)} \quad \dots (28)$$

Double-Line to Ground Fault.

Fig 5 shows a double line to ground fault.

The boundary conditions of the fault point are:


$$I_a = 0 \quad \dots (29)$$

$$\therefore I_{a1} + I_{a2} + I_{a0} = 0 \quad \dots (30)$$

I_b is equal to your minus I_c it can be made minus $j\sqrt{3} E_a$ divided by Z_1 plus Z_2 plus Z_f . So, this is the expression of because I_{a1} is equal to your E_a up on Z_1 plus Z_2 plus Z_f and I_b this one, I_b expression is this one minus $j\sqrt{3} I_{a1}$. So, this I_{a1} you substitute in equation 25 I have not written here. So, in this expression you know I_b is equal to minus I_c that directly I am writing I_b is equal to minus I_c is equal to, but I_b is equal to minus $j\sqrt{3}$ into I_{a1} . So, this I_{a1} you directly substitute. Then you will get this I_{a1} then you will get I_b is equal to minus I_c is equal to minus $j\sqrt{3} E_a$ divided by Z_1 plus Z_2 plus Z_f this is equation 28. So, this is actually your line to line fault.

Now next one is that double line to ground fault

(Refer Slide Time: 27:51)

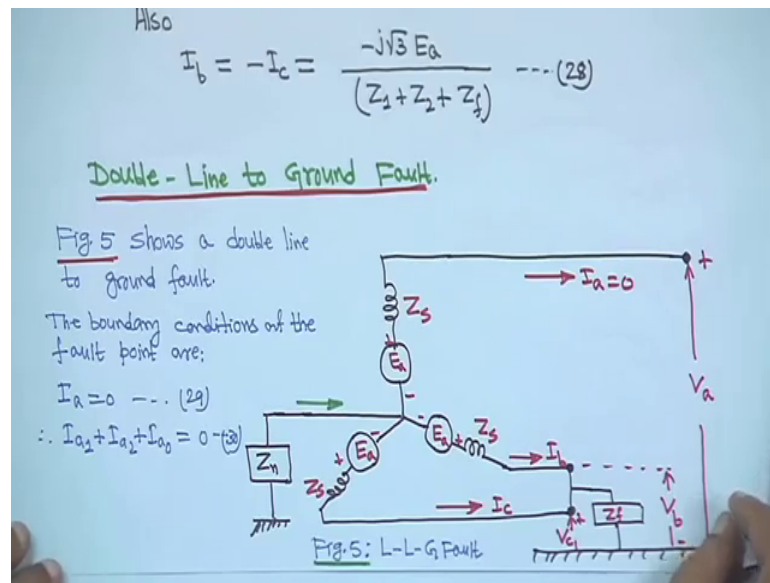


That is L-L-G fault. For example: suppose this two line your first let me tell you this is figure 5 this is double line to ground fault, we call L-L-G fault. So, figure 5 shows a double line to ground fault that is this phase b and phase c this two are short circuited then it is your double line to ground fault and from one fault impedance Z_f is here. So, in this case that I_a is equal to 0 because it is double line to ground fault I_a is equal to 0.

That means if I_a is equal to 0 means $I_{a1} + I_{a2} + I_{a0}$ is equal to 0, I_a is equal to $I_{a1} + I_{a2} + I_{a0}$ is equal to this thing 0, then V_b is equal to your what you call V_c V_b is equal to this total current this is this current is I_b , this current is I_b this is I_c . So, in the fault current is going $I_b + I_c$, I have not written here but this current is I_c this is I_b . So, in this case that current is $I_b + I_c$ this is the current going to a fault say during fault. That means, you can write and this two point are short circuited these two point actually together. Just here I have made it separately for your understanding this two point are short circuited together.

That means, V_b is equal to your V_c then before showing you then V_b will be is equal to V_c will be is equal to your what you call Z_f . The idea is something like this just two points that b and c phases are short circuited.

(Refer Slide Time: 29:32)

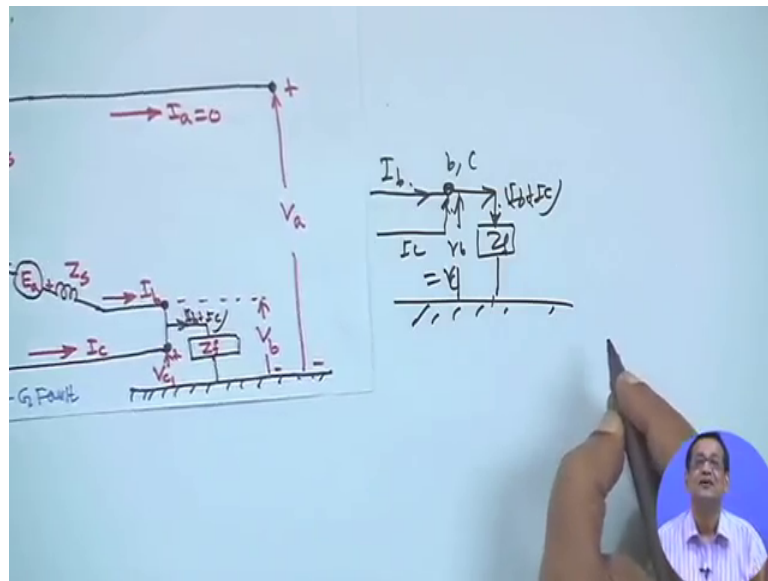

That means this is your b and c short, this is a common point right b and c together short circuited. So, in this case current is coming from your this thing for phase b I and from c it is your I c I b and I c and this is your what you call this is your fault impedance Z f right and this is this is ground. So current here, current actually going through this I b plus I c. As this two points are common, so b v and b c both are same this is b v this two point are common is equal to b c. Therefore, b v is equal to b c is equal to Z f in to I b plus I c because this two points are common.

So, in that case; I hope this simple thing I hope you are understood. So, in that case your we can say that b v is equal to b c is equal to I b plus I c in to Z f is equal to 3 Z f in to I a0 this is equation 31.

Thank you, again we will be back.