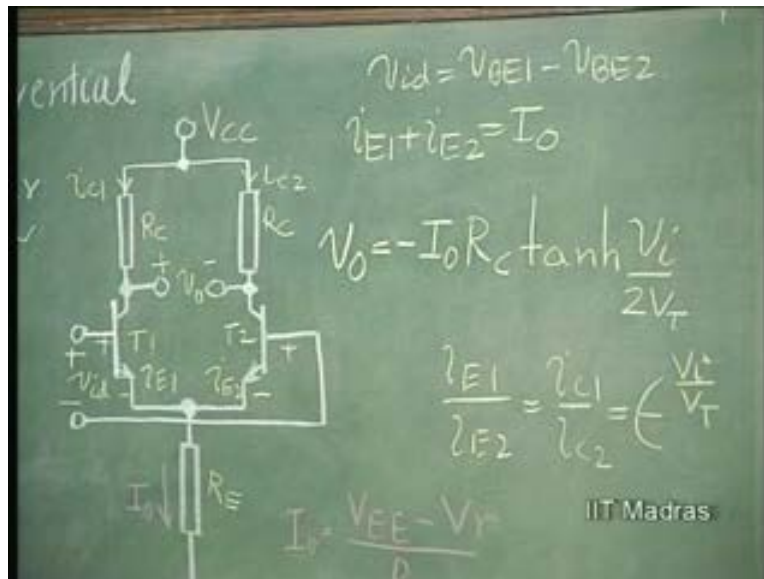


Electronics for Analog Signal Processing - I
Prof. K. Radhakrishna Rao
Department of Electrical Engineering
Indian Institute of Technology – Madras

Lecture - 33
BJT Differential Amplifiers


Continuing our discussion about differential amplifier, we saw in yesterday's lecture how V_{id} is V_{BE1} minus V_{BE2} ; and i_{E1} minus, i_{E1} plus i_{E2} is I_{naught} at all times.

(Refer Slide Time: 02:00)



And then we saw that i_{E1} by i_{E2} ratio is exponent V_i by V_T , from which we derived V_{naught} as equal to minus $I_{naught} R_C \tan$ hyperbolic V_i by $2 V_T$, I_{naught} being equal to V_{EE} minus V_{Gamma} by R_E . Then we said we will plot this; and this plot tells us that for V_i negative, output is going to be positive; V_i negative... This is going to be minus 1 and there is minus 1 here; so, it is positive $I_{naught} R_C$.


(Refer Slide Time: 02:33)

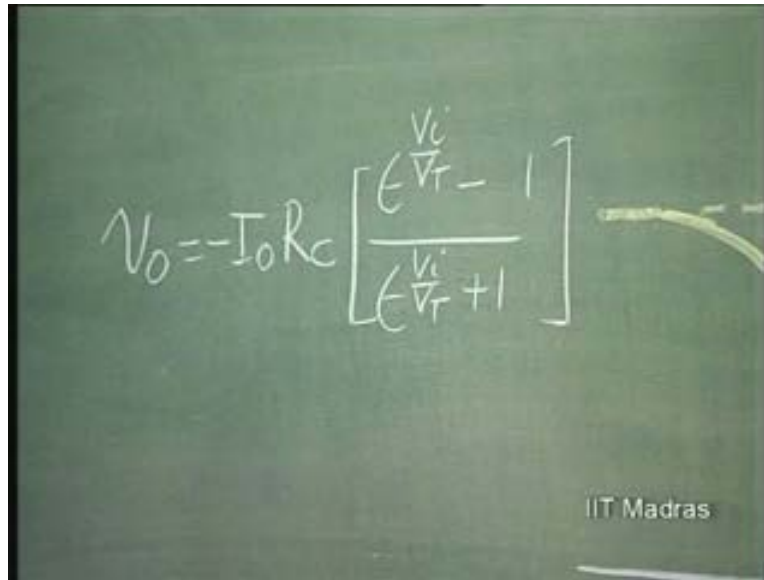
$$V_o = -I_o R_c \left[\frac{e^{\frac{V_i}{V_T}} - 1}{e^{\frac{V_i}{V_T}} + 1} \right]$$

V_i large positive; this one will become negligible; and this will go to 1. So, this actually switches between plus 1 and minus 1. This is the characteristic of hyperbolic tan function; and this goes from $I_o R_c$ to minus $I_o R_c$; and that is the output swing of a differential amplifier.

Now, let us see how this is equal to minus $I_o R_c$; and if e to power x , you expand it as when x is small; that means for V_i by V_T , much less than 1. You can say that this is $1 + x + \frac{x^2}{2!} + \dots$ So, you can see that out of this, if you just put it as $1 + x$, ignore the higher order terms; then, this is minus 1 and this is plus 2; because again, compared to 2, V_i by V_T is negligible.

(Refer Slide Time: 03:59)

 

So, even V_i by V_T is neglected there; whereas here, this one gets cancelled with this one. So, V_i by V_T becomes dominant factor. So, you cannot neglect it. So, this becomes, minus $I_o R_c$ into V_i divided by $2 V_T$ which is nothing but...if you look at it, minus g_m into R_c , because g_m is $I_E Q$ by V_T . $I_E Q$ is I_o by 2 for each transistor. So, g_m is equal to $I_E Q$ by V_T . This is I_o by 2 for this differential amplifier.

(Refer Slide Time: 05:01)

The image shows a chalkboard with the following handwritten equations and notes:

$$v_o \approx -I_0 R_c \left[1 + \frac{v_i}{V_T} - 1 \right]$$

$$= -\frac{I_0 R_c}{2 V_T} v_i$$

$$= -g_m R_c v_i$$

Notes on the board include:

- $\frac{v_i}{V_T} \ll 1$
- $g_m = \frac{I_{E_{eq}}}{V_T} = \frac{I_0}{2 V_T}$
- $-I_0 R_c$
- IIT Madras

So, we know that this is I_0 by $2 V_T$. That is g_m ((the ...Refer Slide Time 5:05)). This is what we had earlier surmised from small signal equivalent. That means small signal here means V_i is again, much less than V_T . So, V_i is much less than V_T ; same thing that we had used earlier for common emitter amplifier. So now, this defines what is meant by small signal in the case of differential amplifier.

Now, what is a hyperbolic tan function, really speaking? Hyperbolic tan V_i by $2 V_T$ can also be expanded as what? Can you from this, conclude what it is? Hyperbolic sine function by hyperbolic cos function. So, if that is the case, what is hyperbolic tan function, strictly speaking? It is true that we will have minus $I_0 R_c$ into V_i by V_T as one term, first term; V_i by $2 V_T$. So, V_i by $2 V_T$ means tan hyperbolic x , is x ; Then, what else?

(Refer Slide Time: 06:35)

$$V_{id} = V_{BE1} - V_{BE2}$$
$$I_{E1} + I_{E2} = I_O$$
$$V_O = -I_O R_C \tanh \frac{V_i}{2V_T}$$

The next term is not squared but cubic. In the hyperbolic tan function, you will not have the square function coming into picture. Why? This is because they get cancelled with one another.


These square functions, V_i by V_T whole square and V_i by V_T to the power 4, all these things; and then you get cubic and fifth order, like that; it is an odd function. So, you will see that, as far as the differential amplifier is concerned, the nonlinearities will be less than the nonlinearities in common emitter amplifier, where you have what? What kind of nonlinearity? - exponential nonlinearity. That means e to power x is: $1 + x + x^2/2$ factorial, so on... So, all the terms are existing. So, after x , you have x^2 by factorial 2.

Here, after x , you have x^3 by factorial 3; and therefore, obviously, the extent of distortion here is much less than that in the common emitter; and it will give the same small signal gain, input impedance, etcetera, but distortion is less. Is it clear?

Now, we will illustrate it later by an example. However, here we can see that tan hyperbolic nonlinearity results in only what kind of harmonics at the output? Only odd

harmonics existing at the output, if I apply a sine wave; whereas, in the case of a common emitter amplifier, all harmonics are invariably present. That can be seen. How is it obvious for us here? Now for...if it is fundamental that is applied, you have for the fundamental, a phase shift of 180 degree here; and no phase shift between this and this.


(Refer Slide Time: 09:22)

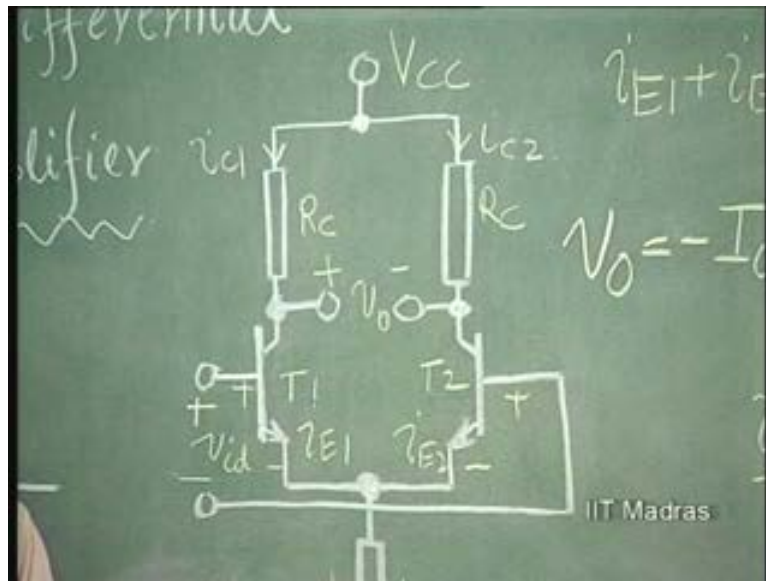

And for the, let us say, since it is a function where the square law gets eliminated, because of the difference, the...how it happens is, because of the difference, there is no phase shift between the even functions and they get cancelled with one another; and only the odd functions remain.


Now, that is illustrated very clearly by this hyperbolic tan non-linearity. Now, this slope here - this is nothing but ΔV naught by ΔV i,...

(Refer Slide Time: 10:23)

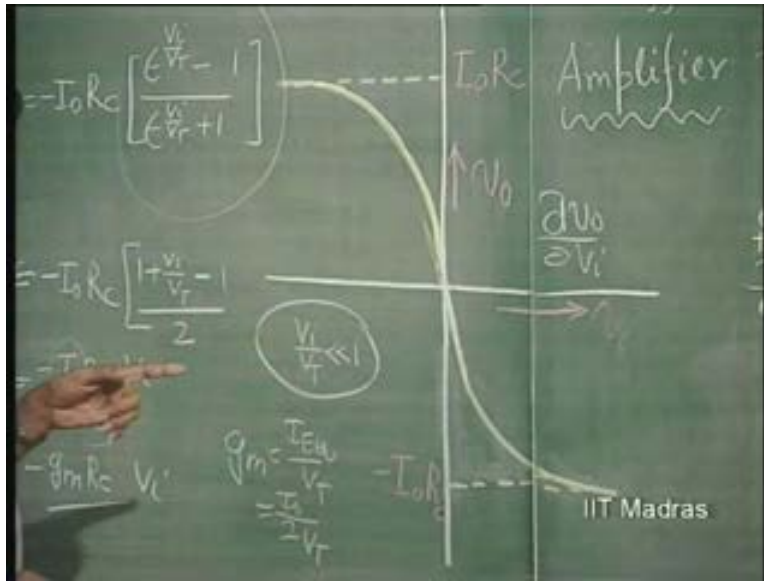

... is nothing but this.


(Refer Slide Time: 10:27)

 

It is going to be...if you do that, please do the differentiation of this from...using the hyperbolic tan function and show that ΔV_o by ΔV_i is nothing but the gain; is the same as minus $I_o R_c$ by $2 V_T$ into V_i .

It is the slope; that we have illustrated here by making approximation. You can do that mathematically by finding ΔV_o by ΔV_i , ΔV_o by ΔV_i as $\frac{-I_o R_C}{2V_T}$, from this.

(Refer Slide Time: 11:18)

 


Now, the negative sign is also indicated by the negative slope here; and the slope will keep on decreasing. That means, if there is an offset in this differential amplifier, the gain is going to be less. Small signal is going to be... small signal gain is going to be less; and not only that, this swing also is going to be less, if there is an offset, if the operating point is not this.

What is an offset? Even when V_{id} is zero, this voltage is not zero. Why is it going to happen? Simply because, these two transistors are not so matched. I_E of this transistor is not same as I_E of this transistor; in which case, even when this is zero, then these two currents will be what? – different, even though the base to emitter voltages are the same.

So, the output will be having an offset. Now, I would like you to understand something about the offset now. What is the offset? Offset, output offset is that voltage that appears when the input is zero.

(Refer Slide Time: 12:40)

 

Output offset is that voltage that appears at the output when the input is zero. So, we have what is called output offset. Why does it happen that there is an offset? That is because the transistors may not be, that is, $I_{E1} \neq I_{E2}$. Transistor 1, T1, is having I_{E1} and transistor T2 is having I_{E2} as its reverse saturation current. Then, what will be i_{E1} ? $i_{E1} = I_{E1} \exp(V_{BE1}/V_T)$. i_{E2} is equal to $I_{E2} \exp(V_{BE2}/V_T)$.

(Refer Slide Time: 13:56)

Transistor mismatch

$$T_1 \quad I_{E01} \quad \lambda_{E1} = I_{E01} \left(\frac{V_{BE1}}{V_T} \right) \left(\frac{1}{\beta} \right)$$

$$T_2 \quad I_{E02} \quad \lambda_{E2} = I_{E02} \left(\frac{V_{BE2}}{V_T} \right) \left(\frac{1}{\beta} \right)$$

IIT Madras

So, what will be the ratio of the currents when the input is zero? If V_{id} is equal to zero, then V_{BE1} is equal to V_{BE2} . Is this clear? If V_{id} is zero, V_{BE1} is equal to V_{BE2} . If this is a shorted, this voltage is always same as this voltage.

(Refer Slide Time: 14:29)

$$T_1 \quad I_{E01} \quad \lambda_{E1} = I_{E01} \left(\frac{V_{BE1}}{V_T} \right) \left(\frac{1}{\beta} \right) = -I_0 R$$

$$T_2 \quad I_{E02} \quad \lambda_{E2} = I_{E02} \left(\frac{V_{BE2}}{V_T} \right) \left(\frac{1}{\beta} \right) = -\frac{I_0 R}{2}$$


If $V_{id} = 0$
 $V_{BE1} = V_{BE2}$

$$= -g_m R$$

IIT Madras


Then, V_{BE1} is same as V_{BE2} . Therefore, i_{E1} by i_{E2} is not equal to 1. You take the ratio. It is I_{E1} by I_{E2} .

(Refer Slide Time: 14:56)

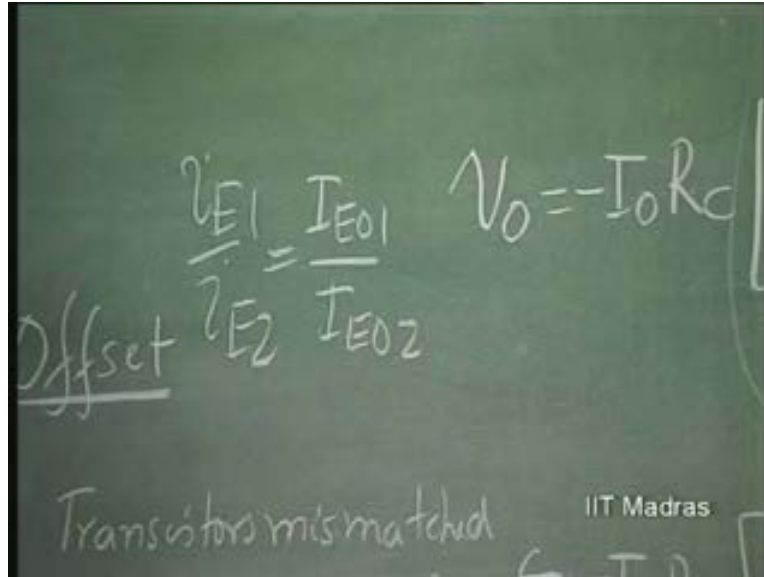

Is this clear? It is understood or not? And $i_{E1} - i_{E2}$ by $i_{E1} + i_{E2}$ equals this ratio; $I_{E1} - I_{E2}$ by $I_{E1} + I_{E2}$.

(Refer Slide Time: 15:34)

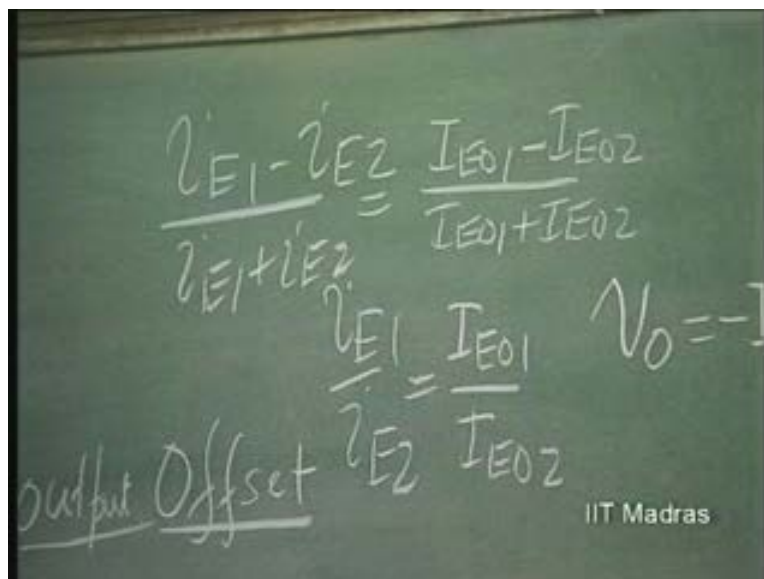

What is this? I_{E1} plus I_{E2} . That is always equal to I_{E0} and I_{E1} minus I_{E2} is equal to i_{c1} minus i_{c2} by Alpha. i_{c1} minus i_{c2} by Alpha.

(Refer Slide Time: 16:18)

$$\frac{(v_{c1} - v_{c2}) R_C}{\alpha I_0} = \frac{(I_{E01} - I_{E02}) R_C}{I_{E01} + I_{E02}}$$

$$v_{E1} = \frac{I_{E01}}{\alpha} \quad v_0 = -I_0 R_C$$

$$v_{E2} = \frac{I_{E02}}{\alpha}$$

Output Offset

IIT Madras

i_{c1} minus i_{c2} into R_C is equal to minus V_{naught} ; that we had already written earlier. i_{c1} minus i_{c2} into R_C is equal to minus V_{naught} and therefore V_{naught} ...now this offset, this is what is called the offset voltage, output offset voltage; equal to minus Alpha $I_{naught} R_C$ into $I_{E_{naught1}}$ minus $I_{E_{naught2}}$ by $I_{E_{naught1}}$ plus $I_{E_{naught2}}$.

(Refer Slide Time: 17:42)

$$V_{o \text{ offset}} = -\alpha I_C R_C \frac{I_{E01} - I_{E02}}{I_{E01} + I_{E02}}$$

So, if you know the extent of mismatch of I E naughts; I E naught 1 minus I E naught 2 is the mismatch; I E naught 1 plus I E naught 2; then, you know the output offset as minus Alpha I naught R C into this mismatch factor. So, this is an important aspect of output offset. So, if there is a mismatch you can tell based on the extent of mismatch what the output offset is going to be; and our effort should be to make I E naught 1 as close to I E naught 2 as possible so that this V naught offset is always close to zero.

So, if it is close to zero, fine. We get the maximum gain which we intend to have; but otherwise, the gain will keep decreasing depending upon the offset. Therefore, the offset itself is not a serious problem. It can be compensated. It is a constant voltage. If it is a constant voltage, it does not vary with time; then it is not a problem.


Unfortunately, it is a D C which drifts with time. This is what I have told you. So, it keeps changing with respect to time because of dependence of I E naught 1 and I E naught 2 with respect to temperature; and they may not track exactly. And therefore, this fact that these vary with respect to temperature causes the output voltage to drip with respect to time.

So, even when the input signal is not there, it is indicating an output signal which is time dependent. This is adding to the noise; this itself is now generating some amount of noise. Particularly, this is of great nuisance in the case of low frequency amplifier where the signal also changes very slowly with respect to time. We cannot separate out this from the signal.

So, it interferes with the signal. Therefore, in a good amplifier, we must make this as close to zero as possible. Not only that, then it should not further drift with respect to time. These are two important things. Now that we know the origin of this offset, with...it will be clear for us how to compensate for this offset also, so that, if that it is not zero, how to make it equal to zero.

Now therefore, input offset definition is... This is output offset. Is this clear? When the input is zero, what the output is? This is called output offset. Input offset, we will now talk about. Input offset is that voltage that has to be applied to the input in order to make the output go to zero, input offset. These are all important parameters associated with the differential amplifier. The input offset is that voltage that we have to apply at the input in order to make output offset, output voltage go to zero. Is the definition clear?


(Refer Slide Time: 20:46)

 

Now, how do we find out input offset? It is very clear. Input offset is that V_{id} that I have to apply so that exponent V_{id} by V_T , this becomes equal to what? - this becomes equal to... What is this normally? I_{E1} by I_{E2} equals I_{C1} by I_{C2} ; that is what we have put.


In order to make the output offset zero, I have to have I_{E1} equal to I_{E2} ; I_{C1} equal to I_{C2} ; that means this should go to 1. So, that means V_{id} for that...this should go to 1.

(Refer Slide Time: 21:42)

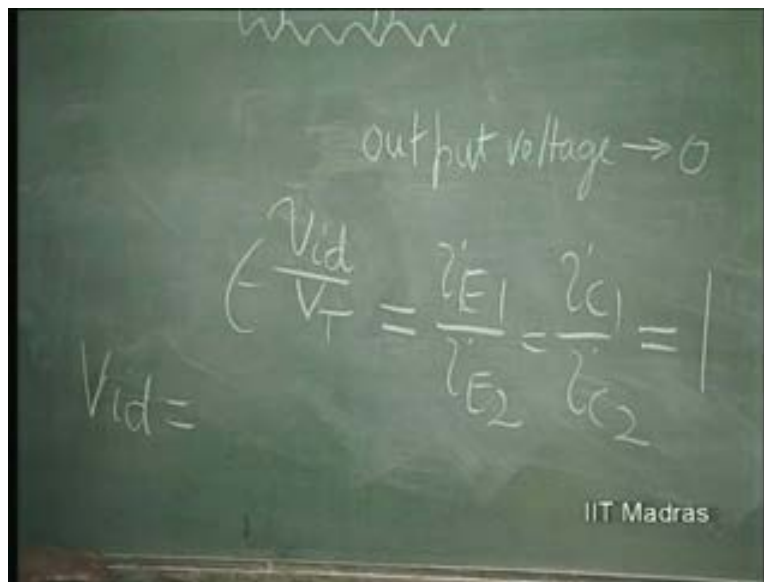


So what is that? This is equal to I_{E1} is I_{E2} naught 1 into exponent, what? - V_{id} , V_{BE1} by V_T ; and this is I_{E2} exponent V_{BE2} by V_T . Is this clear?

(Refer Slide Time: 22:15)

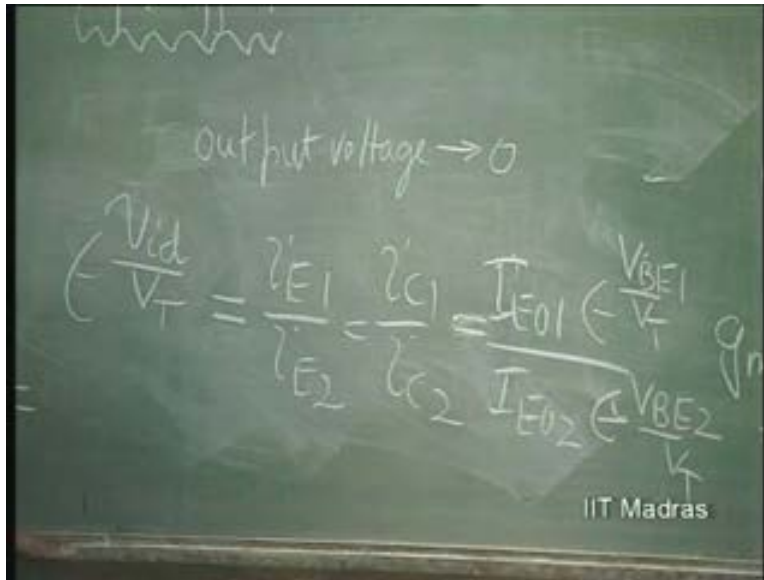

Strictly speaking, when I E naughts were matched, this was going to, what? – one, this was becoming equal to exponent V i d by V T. Is this clear or not? This was equal to I E 1 by I E 2.


(Refer Slide Time: 22:42)

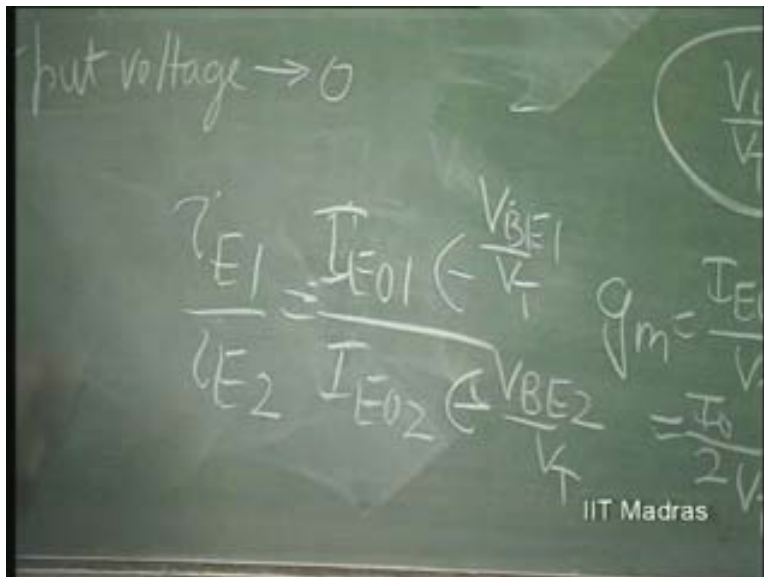

I E 1 or I E naught 1 exponent V B E 1 by V T; I E 2 is equal to I E naught 2 exponent V B E 2 by V T; I E naught 1, when it was equal to I E naught 2, this was going to exponent

V_{id} by V_T . And, this should then become equal to 1. So, in this case, this is 1, when I_{E1} is not equal to I_{E2} .


(Refer Slide Time: 23:08)

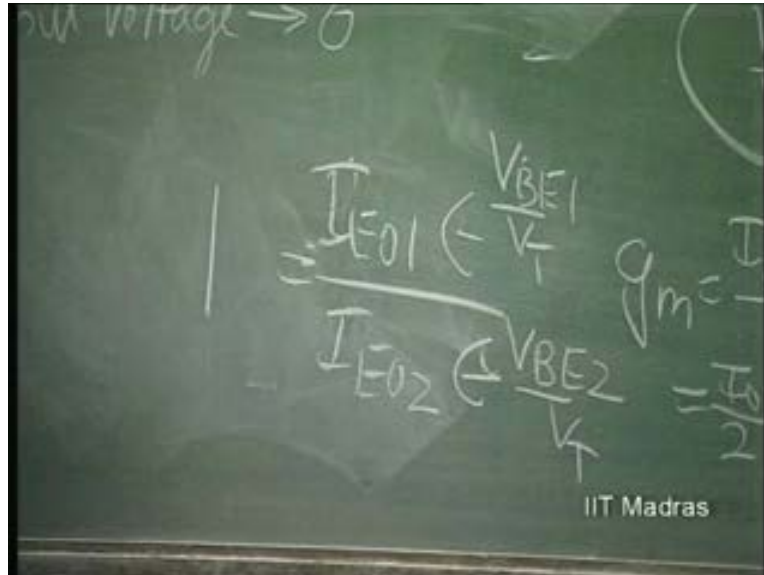

If I_{E1} is equal to I_{E2} , then we will get exponent V_{id} by V_T equal to 1 or V_{id} equal to zero. That is the input offset. If I_{E1} is not equal to I_{E2} , then, even when I_{E1} by I_{E2} is equal to 1, exponent V_{id} by V_T is equal to I_{E2} by I_{E1} .

Earlier, it was equal to 1. And therefore V_{id} was equal to zero. Now obviously, V_{id} is equal to the offset voltage. So, this is equal to $V_T \log i_{E1}$ by i_{E2} . So, this is an important thing.


(Refer Slide Time: 24:10)

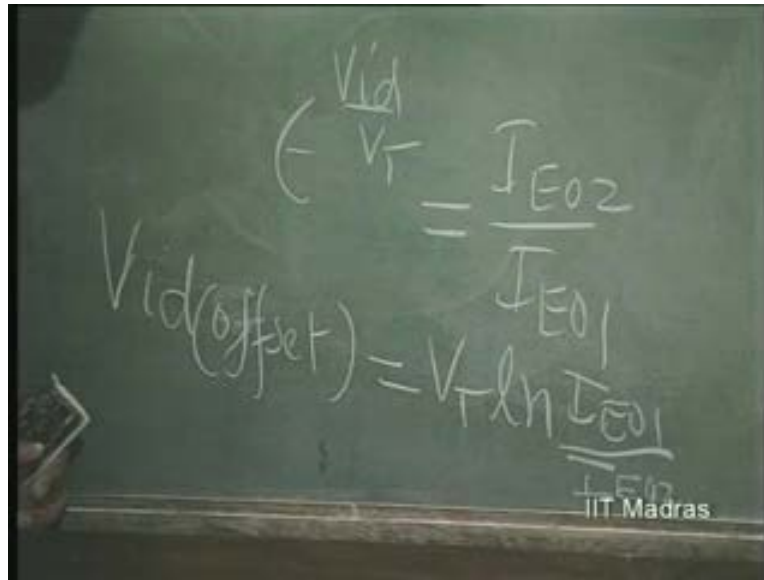

The image shows a chalkboard with handwritten mathematical equations. At the top, the expression $\left(-\frac{V_{id}}{V_T} = \frac{I_{E02}}{I_{E01}} \right)$ is written. Below it, the equation $V_{id}(\text{offset}) = V_T \ln \frac{I_{E01}}{I_{E02}}$ is written. In the bottom right corner, the text "IIT Madras" is visible.

Input offset is equal to $V_T \ln \frac{I_{E01}}{I_{E02}}$. So, it may be positive or negative depending upon whether I_{E01} is greater than I_{E02} or I_{E01} is less than I_{E02} .

(Refer Slide Time: 24:46)

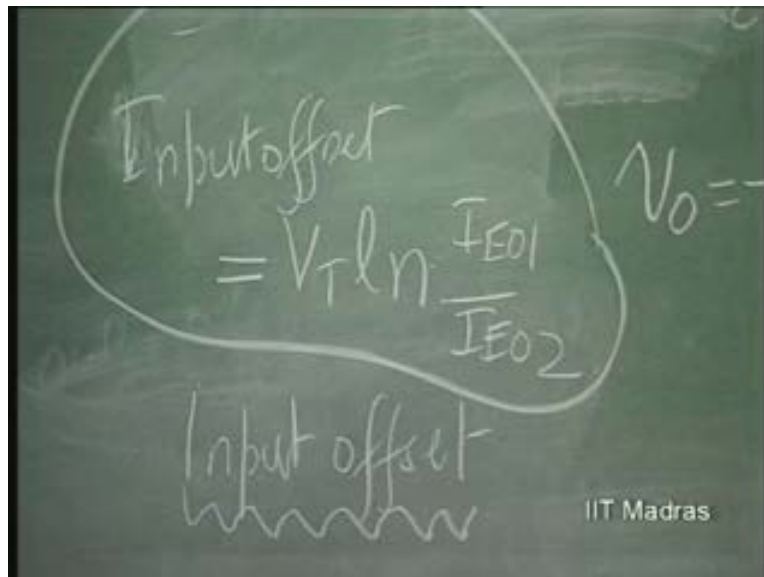

The image shows a chalkboard with handwritten text. The phrase "Input offset" is written and circled in white. Below it, the equation $= V_T \ln \frac{I_{E01}}{I_{E02}}$ is written. To the right of the circle, the text $V_0 = -$ is written. Below the circle, the phrase "Input offset" is written again with a wavy underline. In the bottom right corner, the text "IIT Madras" is visible.

The order of this is typically about a few millivolts, say 1 to 2 millivolts typically; because this is about 25 millivolts; and I_{E01} by I_{E02} is practically close

to 1. That means log of 1 is pretty close to zero, I E naught 2. So, the offset voltage is minus V T log. That only changes the sign.

(Refer Slide Time: 25:23)

$$\left(- \frac{V_{id}}{V_T} = \frac{I_{E02}}{I_{E01}} \right)$$

$$V_{id}(\text{offset}) = -V_T \ln \frac{I_{E01}}{I_{E02}}$$


IIT Madras

So, the sign can be positive or negative; that is of no consequence, depending upon whether I_{E01} is greater than I_{E02} or I_{E01} is less than I_{E02} , because we have not said which is really the input offset. So, it can be plus minus $V_T \log I_{E01}$ by I_{E02} . So, typical value for BJT is, this input offset is, 1 to 2 millivolts. Therefore, you must always know this; that a single stage circuit like this with one pair of transistors will result in something like an offset of 1 to 2 millivolts.

If you put Darlington pair here... Darlington pair means, actually, to connect a transistor like this and another transistor like this, in order to artificially boost up the Beta of the transistor.


Now, there are two pairs coming into picture. The uncertainty will be doubled. So, it will be 2 to 4 millivolts. So, using more pairs of transistors will result in more input offset even though you might put this, in order to improve the beta of the transistor. You will degrade the transistor differential amplifier in terms of its input offset.

(Refer Slide Time: 27:17)

 

So, the best for lowest input offset is a single pair; not these modifications. Never modify this. The best thing is just a single pair, if you are interested in maintaining minimum offset.

(Refer Slide Time: 27:34)

 


Such is the case with amplifiers, particularly usable for very low frequency, where this offset has to be kept at a low value in order to prevent the output from drifting.

We have seen that the current ratio i_{E1} by i_{E2} is same as i_{C1} by i_{C2} ; is equal to exponent V_{id} by V_T , if the two transistors are matched. Otherwise, of course, it is going to be I_{E1} by I_{E2} into exponent V_{id} by V_T and from which we could get the input offset, etcetera.

Now, let us discuss once again about how this V_{id} can swing this current; portion of this current is going to flow through this. Initially, this will be I_{E1} by 2; this will be I_{E2} by 2, when V_{id} is zero, if the two transistors are matched.

(Refer Slide Time: 28:42)

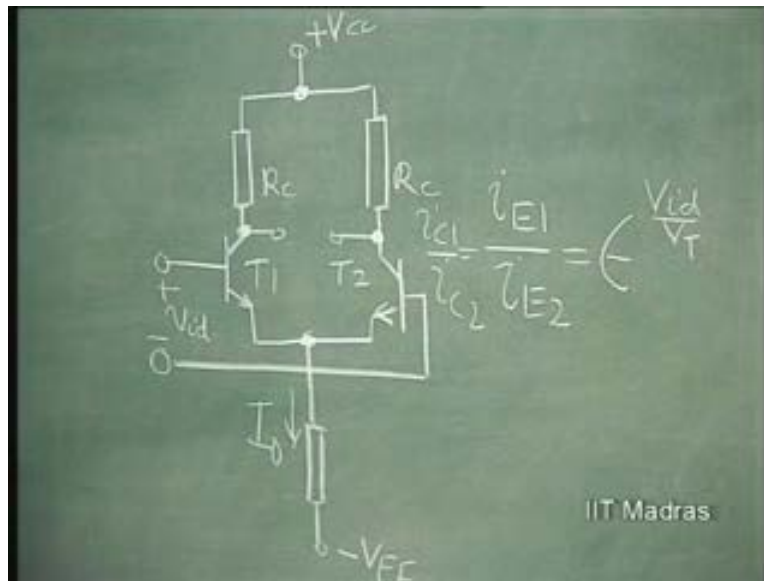

Now, let us apply V_{id} . The current ratio is going to be varying according to this. If V_{id} is zero, this will be 1; and I_{E1} is equal to I_{E2} equal to I_{E1} by 2. Now, by therefore applying V_{id} , I can make the current I_{E1} much greater than I_{E2} , this current will...can keep on increasing; this current will keep on decreasing. Ultimately, what happens?


This transistor will have the total current I_{E1} and this will have zero. That is the limit. This is off. T_2 is off. T_1 is fully drawing the current. At that point of time, this voltage is going to be V_{CC} minus $I_{E1} R_C$. This will be V_{CC} , because there is no

current here. Therefore, this output voltage will be V_{CC} minus $I_{C1} R_C$ minus V_{CE1} and therefore it is V_{CC} minus $I_{C1} R_C$. When V_{id} is a large positive, output voltage will go towards V_{CC} minus $I_{C1} R_C$.

Then, I make V_{id} now negative. This current will increase; this current will decrease as determined by this ratio. And this will keep on increasing, if I make it more and more negative; and ultimately T_1 will go to off state and T_2 will take the complete current and this voltage will be V_{CC} minus $I_{C2} R_C$ and this will be V_{CC} and V_{CE2} will be $I_{C2} R_C$.


This is called current switching. What has taken place now by applying a V_{id} of positive polarity and going to negative polarity, as far as V_{id} is concerned; the current here has totally switched from this transistor to this transistor. This is called current switching and any logic circuit using this for driving the transistors of this logic circuit is called current mode logic circuit.

(Refer Slide Time: 31:30)

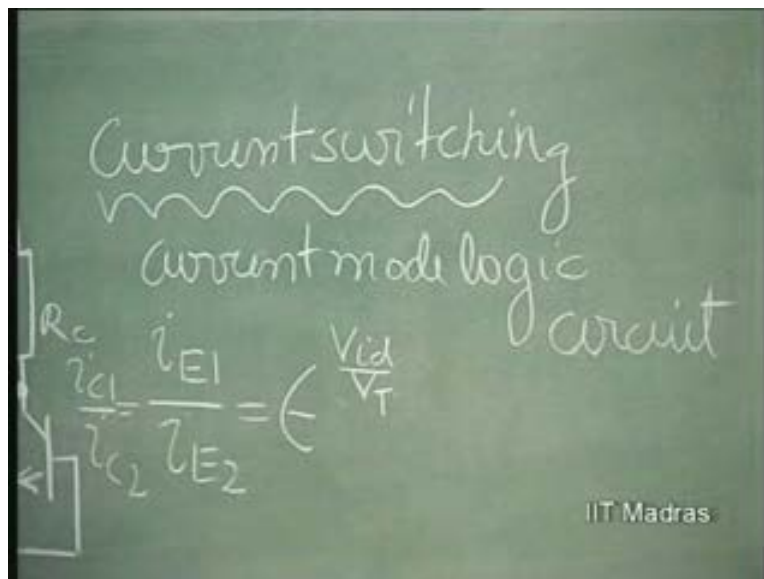


So, a differential amplifier is belonging to a family of logic circuits called current mode logic circuit; or, it is in this particular case popularly called emitter coupled. Emitter is coupling this transistor. It is coupled at the emitters to a common point. So, this is called Emitter Coupled Logic or popularly, E C L; or, Current Mode Logic, E C L or C M L, current mode logic.

(Refer Slide Time: 32:18)

 

This by nature, because only the current is switched from this to this; by nature, is the fastest known logic family resulting in... Any computer designed using this logic family will be the fastest computer run. As far as transistors are concerned, any computer using such logic family is going to be the fastest logic family computer; and therefore fastest computer.

(Refer Slide Time: 32:42)

 

Why is it fastest compared to other logic families? When the current is completely switched to this, the potential here is $V_{CC} - I_{\text{sat}} R_C$. At that point of time, T1 should not go to saturation. That means there should be enough collector to base potential, which is positive in this case, in order to retain T1 in active region. This is an important aspect.

If...when this current is completely switched over to this, this transistor goes to saturation. Everything is lost. It has to come out of saturation before it can really respond to the input signal that is causing a certain amount of delay. All your TTL circuits got into the problem of low speed only because they were going into saturation. Then came about what is called Schottky TTL where VCB was forced to be retained close to zero, preventing such transistors from going to saturation.

They were faster than the ordinary TTL. However ECL, by nature, is the fastest without the requirement of introducing Schottky barrier transistor junction diodes; so, between collector and base... So, this is the fastest logic family here. We have the current switching taking place and the logic level in this particular case is going from V_{CC} .

You consider one side; V_{CC} to $V_{CC} - I_{naught} R_C$. On the other side also, V_C minus $I_{naught} R_C$ to V_{CC} .

Or, if you take the differential, it will go from I_{naught} , minus $I_{naught} R_C$, to plus $I_{naught} R_C$. However, if you connect an identical differential amplifier as its output, this is again connected. Normally, that is the state of most of the logic circuit. This logic circuit will be further connected to another logic circuit; so, the extent of voltage variation will get limited, just like this happening at the input.

At the input, we need only a change in voltage of the order of few tens of millivolts to switch the current from one transistor to other. Let us investigate this. How much voltage is needed at the input in order to switch the current totally from one transistor to other? This is an important aspect of finding out the drive requirement for such logic families.

So, the question is what is the V_{id} required to take the current from one transistor to the other and vice versa? Now, if you see the relationship, it is exponential. That means, when V_{id} is plus infinity, and V_{id} is equal to minus infinity only, this takes place. But in all such situations, we say that the current is completely switched over to this transistor, when this transistor gets 90 percent of the total current; this transistor has 10 percent of the total current. Is it clear?

This is always the case in making a measure of what kind of voltage you require for such drive. So, I want this transistor to get 90 percent; this transistor to get 10 percent. That will be 1 voltage; the other voltage will be... When this is 10 percent and that is 90 percent.

Let us therefore call V_{id1} as that voltage where exponent V_{id1} by V_T is equal to... I_{E1} is 90 percent and I_{E2} is 10 percent of I_{naught} . Is this clear? This is 1; then exponent V_{id} by $2 V_T$ corresponds to this 10 and this 90.

(Refer Slide Time: 37:52)

Chalkboard content:

$$\epsilon^{-\frac{V_{id1}}{V_T}} = \frac{90}{10}$$
$$\epsilon^{-\frac{V_{id2}}{V_T}} = \frac{10}{90}$$

Know
logic
famil

IIT Madras

And, what do we need? We need $V_{id1} - V_{id2}$. What is the extent of variation in this, which will cause this switching from one transistor to other and vice versa? So, you divide this one by other; you get exponent $V_{id1} - V_{id2}$ by V_T equal to... How much is it? This is 9 and this is 1 by 9. Dividing one by the other, we will get it as 81, clear?

(Refer Slide Time: 38:31)


Chalkboard content:

$$\epsilon^{\frac{V_{id1} - V_{id2}}{V_T}} = 81$$

IIT Madras

And therefore, $V_{id1} - V_{id2}$ is equal to $V_T \log$, natural log of 81. V_T , please remember, natural log of 81. So, that comes out to be, how much? 114 millivolts. This is an important conclusion. The voltage swing that is required to switch the transistor from one to the other and vice versa is only about 114 volts, millivolts.

(Refer Slide Time: 39:08)

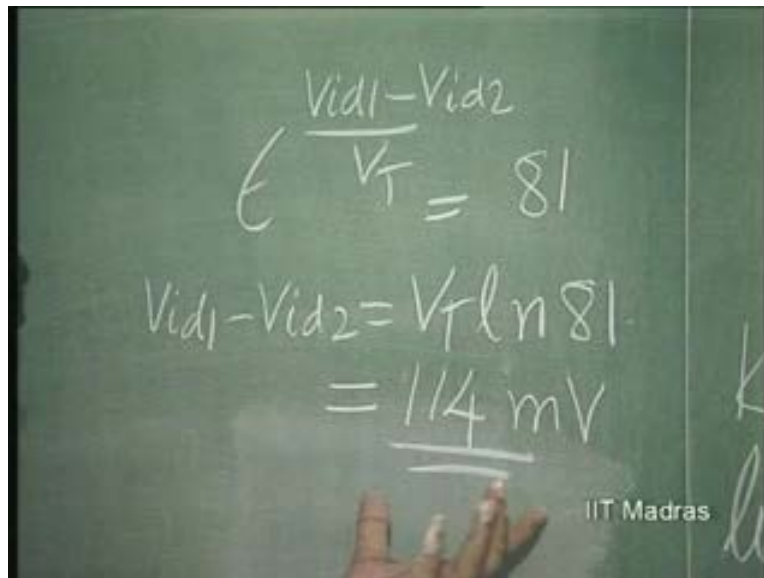
$$e^{\frac{V_{id1} - V_{id2}}{V_T}} = 81$$
$$V_{id1} - V_{id2} = V_T \ln 81$$
$$= \underline{114 \text{ mV}}$$

Please remember this always; and how it can be derived. So, the...in the case of emitter coupled logic, you will see that the logic level, for zero to logic level to 1, should only swing from one value to other by an extent of 114 millivolts. Unlike in the case of T T L, etcetera, where the swing is about 5 volts, this is the kind of thing.

Next problem. We will come back to our analog circuitry now. We would like to know what is meant by distortion; what should be the small signal; what is the quantitative measure of the small signal in order to maintain distortion at a certain level. This, we did in the case of BJT tran... common emitter configuration as well. What will ... should be the magnitude of V_{id} , if it is a sinusoid that I should apply here in order to retain distortion at the output lower than a specific value; and this will also facilitate comparing this with that of common emitter amplifier.

So, we have seen that this V_{id} is equal to $I_{naught} R C$. That is, minus, tan hyperbolic V_{id} by $2 V_T$. Now, we are taking V_{id} as equal to... What is it? $V_p \sin \omega t$. I am applying a sine wave as the input. So, as far as the x factor is concerned, we know that this is straight away coming as V_{id} by $2 V_T$.

(Refer Slide Time: 43:40)

The image shows a chalkboard with the following handwritten equations:

$$V_{id} = V_p \sin \omega t$$

$$= - \left(\frac{V_{id}}{2V_T} - \frac{\left(\frac{V_{id}}{2V_T}\right)^3}{3} \right) I_0 R_C$$

$$= - \left[\frac{V_p \sin \omega t}{2V_T} - \frac{(V_p \sin \omega t)^3}{24V_T^3} \right] I_0 R_C$$

IIT Madras

This tan hyperbolic V_{id} by $2 V_T$ can expand as...this, if it is x, it is x minus x cube by 3. That means V_{id} by $2 V_T$ minus x cube, V_{id} by $2 V_T$ whole cube by 3 and so on... The other factors are going to be ignored. So, if we now consider $V_p \sin \omega t$ as V_{id} equals $V_p \sin \omega t$, this whole thing into $I_{naught} R C$ with a minus sign is the output. If V_{id} is $V_p \sin \omega t$, this is going to be minus $V_p \sin \omega t$ divided by $2 V_T$ minus $V_p \sin \omega t$ whole cube. That is V_{id} . This will be $8 V_T$ cube. Therefore, this will be $24 V_T$ cube. This into $I_{naught} R C$.

Now, as far as the gain is concerned, we can see that $I_{naught} R C$ divided by $2 V_T$... So, output will be corresponding to $V_p \sin \omega t$ into $I_{naught} R C$ divided by $2 V_T$, with a minus sign. What does it indicate? This is the gain; this was the original signal and there is an inversion; there is a phase inversion. This is nothing but...this whole thing is nothing but g_m of the differential amplifier; g_m into $R C$. Each transistor is operating at

I naught by 2; and therefore, that I divided by V_T is the g_m . Thus, g_m into R_C . So, this is g_m into R_C ; minus g_m into R_C into $V_p \sin \omega t$. This is actually the wanted input.

(Refer Slide Time: 44:30)

The image shows a chalkboard with the following handwritten derivation:

$$- \frac{I_0 R_C - V_p \sin \omega t}{2 V_T} = V_{id}$$

$$- \frac{g_m R_C V_p \sin \omega t}{2 V_T}$$

The chalkboard also features the text "IIT Madras" in the bottom right corner.

This factor is going to cause certain amount of distortion in the signal, because apart from $\sin \omega t$ component, we will have other components also coming into picture. So, this $V_p \sin \omega t$ whole cube could be expanded as...that is equal to $V_p^3 \sin^3 \omega t$ minus $\sin^3 \omega t$ by 4. That is, $\sin^3 \omega t$.

So, that divided by $24 V_T^3$ is what is going to remain of this. So, this factor, therefore is going to contribute to certain amount of distortion because of the third harmonic. So the third harmonic distortion is going to arise here. Now, let us compare it with the fundamental; the fundamental component was V_p by $2 V_T$, peak value; V_p by $2 V_T$. This is the fundamental component.

As against that, we have this; which is going to be the amplitude of the harmonic; which is going to be, let us say, V_p^3 by $96 V_T^3$. So, we have this equal to V_p^2 by V_T^2 into 48. So, this is the ratio of the third harmonic to the fundamental. This

is also going to be the ratio of the... I mean percentage distortion. If you multiply it by 100, this will give you the percentage distortion.

(Refer Slide Time: 46:42)

$$\begin{aligned}
 & \frac{V_b^3 (3 \sin \omega t - \sin 3 \omega t)}{4 \times 24 V_T^3} \\
 & \frac{V_b^3 / 96 V_T^3}{\frac{V_b}{2 V_T}} = \frac{V_b^2}{V_T^2} \frac{1}{48} \\
 & I_0 R_C
 \end{aligned}$$

IIT Madras


So, this will give you an idea as how to control the percentage distortion in your differential amplifier. This, if it has to be 1 percent, then this factor should be less than point 01. Now, that is how you have to control the differential signal amplitude.

Now, we have another aspect of the amplifier to be taken care of in the differential amplifier. If this is operating at a current of I_{naught} apart from the differential signal, you have a common mode signal which is coming into picture, $V_{c i}$.

So, if there is no differential signal, only common mode signal is present, how do we now fix up the sort of signal limitation at the input? If this is $R C$, this is also $R C$. This is $V C C$. Then, the current in this will be $I_{naught} / 2$; $I_{naught} / 2$. And, since the common mode signal is not going to cause any change in this current...so, this common mode signal, when it is increasing, the reverse bias voltage applied to the transistor will keep decreasing.

So, this can go on up to $V_{CC} - I_{CQ} R_C$; at this voltage is going to remain almost constant at $V_{CC} - I_{CQ} R_C$. So, this cannot rise above that; particularly, if such an amplifier is the input stage of an op amp or something like that. If the common mode voltage changes above this, this transistor will lose its active nature and it will come to saturation and the polarity is going to change from negative; that is, feedback is going to change from negative to positive; and that will cause what is called as this instability, signal dependent instability.

(Refer Slide Time: 49:36)

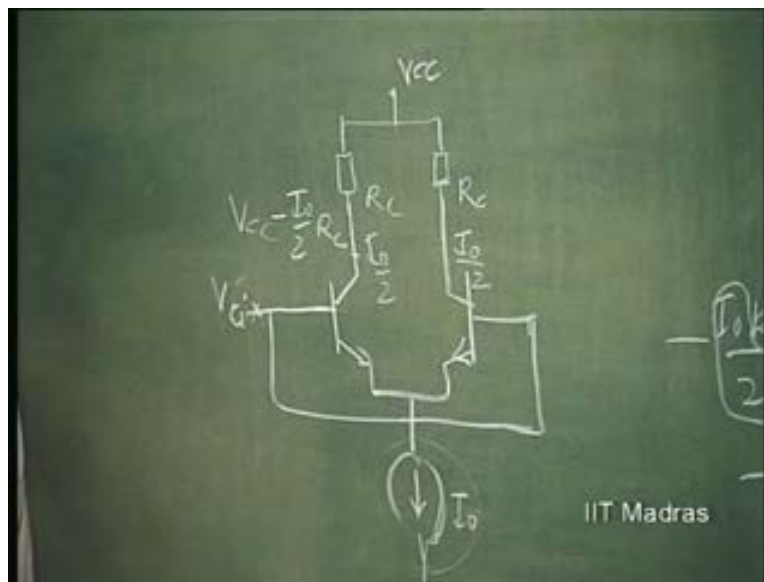

So, this kind of thing can be prevented if you take care to see that this common mode voltage does not exceed this here. On the other side, this voltage can go down and this voltage will follow this. $V_{CC} - V_{\gamma}$ will be the voltage here. And at that time, this current source should remain still active. So, that is the condition. So, there is a limit on $V_{CC} \max$ as well as $V_{CC} \min$, as far as the input stage is concerned.