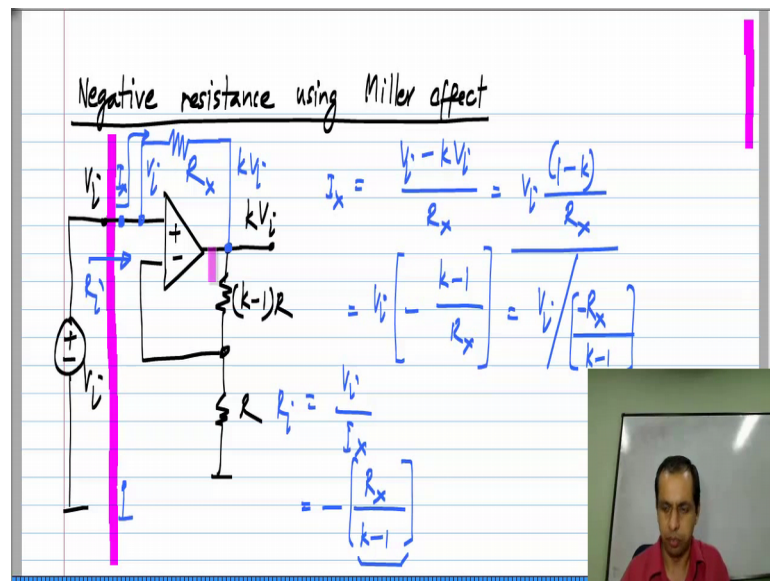


Basic Electrical Circuits
Dr Nagendra Krishnapura
Department of Electrical Engineering
Indian Institute of Technology Madras

Lecture – 110

In this lesson we look at another example circuit, which is to synthesize a negative resistance using an op amp.

(Refer Slide Time: 00:09)



I will say negative resistance using Miller effect; I will explain what that is. Let us consider a non inverting amplifier, if the input is V_i the output will be kV_i , because of this resistance ratio. It is 1 plus the upper resistance divided by the lower resistance. Now, of course in this condition no current flows into the op amp. So, the input resistance of this circuit is infinity, let me show the voltage source explicitly and let us say, I connect a resistance R_x between the input and output.


Then, I will evaluate the resistance of this part of the circuit that is to the right of this line between these terminals here and ground and we know how to evaluate the resistance of any linear circuit. We apply a test voltage, find the current that is flowing in, divide the voltage by the current to obtain the resistance. Now, the only current here is flowing through R_x , this node is at V_i , this node is at kV_i . So, this current I_x is V_i minus kV_i divided by R_x , which is V_i times 1 minus k divided by R_x .

Now, you can see that this I_x will actually be negative, because this k will be greater

than 1. We will assume that k is more than 1, because we are making an amplifier of gain k , k is at least 1 and in this case we will choose k to be more than 1, so that this k minus 1 is a positive number. So, this I_x in this direction will be actually negative, so the current in this direction I_x is V_i times minus k minus 1 by R_x , which is V_i divided by R_x by k minus 1 with a negative sign.

So, the resistance looking in here R_i which is V_i by I_x is nothing but, minus R_x divided by k minus 1. So, this k minus 1 is a positive number and R_x is of course, positive, it is a physical resistor. So, the input resistance of this circuit is negative.

(Refer Slide Time: 03:54)

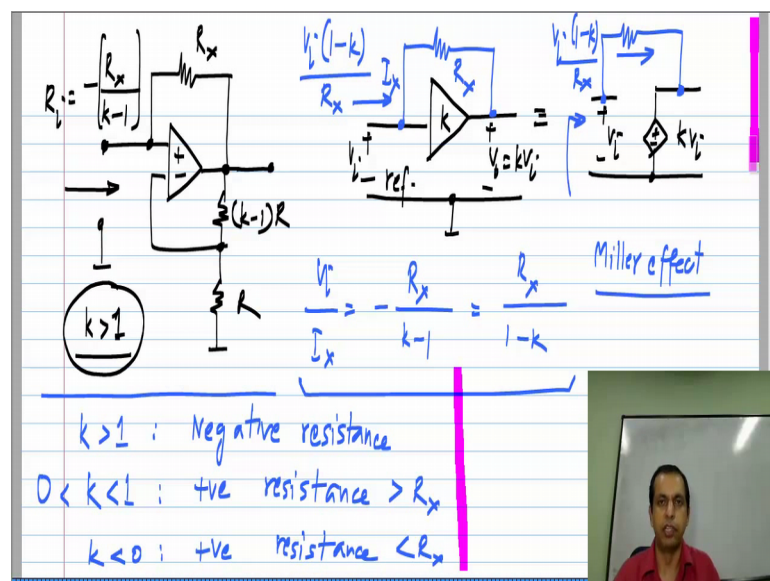

So, if you wanted to synthesize a negative resistance, this is how we do it. This is an amplifier of gain k and I connect some R_x , then between this point and ground I see a resistance, which is minus R_x divided by k minus 1 and in this circuit of course, k is more than 1. Now, this is quite easy and it turns out, this is a specific case of what is known as Miller Effect. If you have an amplifier of gain k , I use this symbol to mean this circuit. Let say ground is the reference terminal and this is V_i , this is v naught equals k V_i . This is nothing but, a voltage control voltage source of gain k , so if this is V_i , this will be k times V_i .

If you connect a resistance between the input and the output of the amplifier R_x , let us assume that no current flows in here, like the here it is an open circuit no current flows in there and the amount of current that flows in there would be V_i times 1 minus k divided by R_x , exactly what I evaluated for the other circuit. If you apply V_i here, the amount of

current that flows in there is V_i times $1 - k$ divided by R_x , this comes from simple ohms law.

So, the looking in resistance which is V_i divided by I_x , let me this I_x is the same formula as before. It is $-R_x$ divided by $k - 1$ or R_x divided by $1 - k$. So, by connecting a resistance between the input and the output of the amplifier, you have an input resistance which depends on the gain of the amplifier and this is in general known as miller effect and also depending on the gain value, there are a few possibilities.

If k is more than 1, we see a negative resistance at the input and if k is between 0 and 1, we see a positive resistance which is more than R_x more than the resistor that you have in the circuit. And if k is smaller than 0, that is if k is negative then we have a positive resistance that is smaller than R_x . You can make a large resistance look like a small resistance by connecting it across an amplifier, whose gain is negative. So, this is known as miller effect and it manifest itself in some circuits and this is how you calculate the input resistance.

The main point is that, the input resistance is determined by the gain of the amplifier. So, you can think of many possibilities, such as if you have an electronically varying gain you could also have an electrically varying resistance and so on and of course, the additional application is, what I already showed you how to make a negative resistance. It can also be used for realizing a very small resistance and so on.