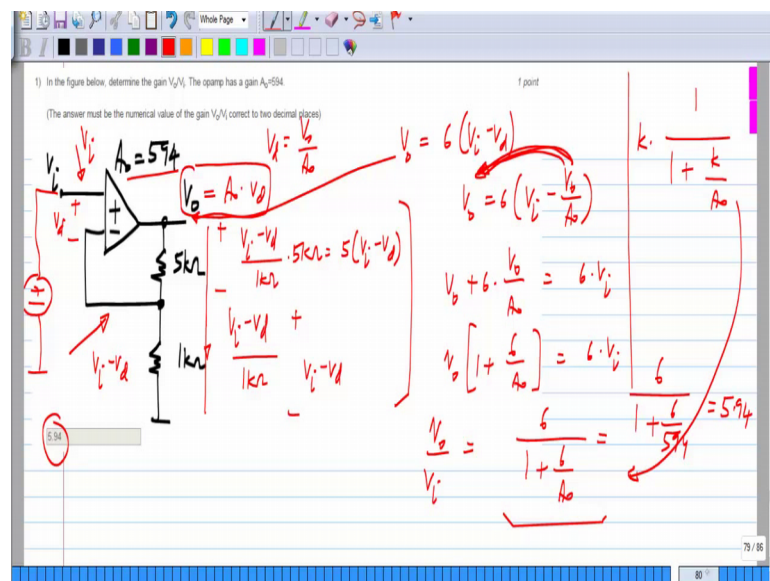


Basic Electrical Circuits
Dr Nagendra Krishnapura
Department of Electrical Engineering
Indian Institute of Technology Madras

Lecture - 114

Now, we will discuss the solution to the assignment for the 8'th week on op amp and negative feedback.

(Refer Slide Time: 00:13)



The first question there is a non inverting amplifier with an op amp which has a finite gain which is given 594 and what your asked for is V_o by V_i . Now, what does this A_0 equals 594 mean, it means that the output voltage V_o of the op amp with respect to ground equals A_0 times the difference voltage V_d . So, now, we know that the voltage at this point, the voltage here is the applied voltage V_i again with respect to ground by now all of you are familiar with this notation.

If V_i is written at a particular node, it means that the voltage between that node and ground is V_i , the voltage here would be $V_i - V_d$ and the current here is $V_i - V_d$ divided by 1 kilo ohm and the same current flows there. So, the voltage across this 5 kilo ohm resistor is $V_i - V_d$ divided by 1 kilo ohm times 5 kilo ohms or 5 times $V_i - V_d$ and the voltage here across the 1 kilo ohm resistor is just $V_i - V_d$. So, this voltage here V_o equals 6 times $V_i - V_d$ that is the sum of these two

voltage drops and we know that we note is V_d in other words V_d is V_{naught} by A_{naught} .

So, V_{naught} equals 6 times V_i minus V_{naught} by A_{naught} which can be rewritten as taking this to this side we can write V_{naught} plus 6 times V_{naught} by A_{naught} is 6 times V_i . So, V_{naught} times 1 plus 6 by A_{naught} equals 6 times V_i in other words V_{naught} by V_i equals 6 divided by 1 plus 6 by A_{naught} by the way you probably remember the formula from the lecture that if you have a non inverting amplifier with a desired gain k the actual gain when the op amps gain is finite would be k times 1 by 1 plus k by A_{naught} that is exactly what we have got.

But, I just showed you the analysis from first principles which you should be able to carry out even if you do not remember any of the results. So, this in our case turns out to be 6 divided by 1 plus 6 divided by 594 and if you calculate this it turns out to be exactly 5.94 that is the answer.

(Refer Slide Time: 03:24)

2) In the figure below, determine the negative terminal of the opamp such that the opamp is in negative feedback. (Indicate the negative terminal as A or B)

Handwritten analysis:

$$V_A = V_{res} \cdot \frac{2k\Omega}{2k\Omega + 10k\Omega} = V_{res} \cdot \frac{1}{6}$$

$$V_B = V_A - V_B = V_{res} \left(\frac{1}{6} - \frac{1}{5} \right)$$

$$= V_{res} \left(-\frac{1}{30} \right)$$

Since V_B is negative, terminal B is the negative terminal.

Final answer: $V_A = V_B$, A: +, B: -

Now, in the next question you asked to find the negative terminal of the op amp. So, that the op amp is in negative feedback. So, the first step is there is a independent voltage source here which you can null and set to ground then you remove the op amp. So, that is I will draw the circuit again here the independent voltage sources here and I have grounded that this is 2 kilo ohm, 10 kilo ohm, 1 kilo ohm and 4 kilo ohm A and B and here I have the voltage $V_A B$.

So, the procedure for finding the sign is straight forward I remove the op amp I apply a test voltage here and find the voltage $V_A - B$ and this is pretty straight forward, because we just have two different voltage dividers. So, if I call this V_A and call this V_B in this particular case V_A and V_B can be found out independently. So, V test goes through this voltage divider and you get V_A , so V_A will be V test times voltage divider formed by 2 kilo ohms and 10 kilo ohm which is 2 kilo ohms by 2 kilo ohms plus 10 kilo ohm which is V test times $1/6$ this V_B here we have V test times voltage divider formed by 1 and 4 kilo ohms. So, 1 kilo ohm by 1 kilo ohm plus 4 kilo ohm or V test times $1/5$.

So, $V_A - B$ which is V_A minus V_B is V test times $1/6$ minus $1/5$ this turns out to be V test times minus $1/30$ basically the point is it is a negative number times V test. So, now, this $V_A - B$ is a negative number times V test, this means that A should be positive and B should be negative. Because finally, when you have the op amp in the circuit and you have some difference V_d . So, for it to be in negative feedback V_d will have some component of V out in it and this number should be negative.

Now, $V_A - B$ is a negative number times V test which stands for the output voltage of the op amp, we removed the op amp and placed V test started output. So, this V_d should be equal to $V_A - B$, $V_A - B$ had to come out be some positive number times V test, this V_d would have to be minus $V_A - B$. In this case, the difference voltage of op amp must be equal to be $V_A - B$ which means that A is the positive terminal and B is the negative terminal and that is what is given as the answer here.

(Refer Slide Time: 07:06)

3) In the figure below, determine the constants in the output. The output can be written as $\alpha V_1 + \beta V_2$ as given in the figure. Assume that the opamps are ideal and in negative feedback. (The answers show the numerical values of α and β)

1 point

Value of $\alpha =$

4) Value of $\beta =$

1 point

In this case we have to analyze an op amp circuit it is given that the op amps are operating in negative feedback. So; that means, that you can apply virtual short principle for every op amp then we have to find this output voltage, typically op amp circuit analyzes is very easy when ideal op amps are given, because first of all this is 0 volts.

Now, the voltage at this node here this is V_1 , so this node is also at V_1 and then finally, here this node here is at V_2 . So, this op amp which is also a negative feedback has 0 volt across it is inputs, so this is also at V_2 . Now, all we have to do is write Kirchhoff current law equations at the op amp input terminals no current flows into the op amp. So, the current that is flowing here is V_1 divided by 1 kilo ohm, because V_1 is across the 1 kilo ohm resistor and the same thing flows through this also.

So, the voltage across this is V_1 divided by 1 kilo ohm times 2 kilo ohms or 2 times V_1 . And if you want to write the voltage at the output of the first op amp it will be whatever voltages at that node plus the voltage dropped across the resistor in this polarity which happens to be 3 times V_1 . Similarly, we do it with the other op amp the current flowing in this direction is V_2 minus V_{out} divided by 1 kilo ohm nothing flows into the input of the op amp, so all of this flows there. So, the voltage drop across this is V_2 minus V_{out} by 1 kilo ohm times 1 kilo ohm which is V_2 minus V_{out} .

So, the voltage at this node will be voltage here which is V_2 plus the voltage dropped in this polarity which is V_2 minus V_{out} . So, here we have V_2 plus V_2 minus V_{out} and

we have already calculated the voltage here to be $3V_1$ that has to be equal to this one. So, $3V_1$ should be equal to V_2 plus V_2 minus V_{out} , so from this we get the expression for V_{out} to be 2 times V_2 minus 3 times V_1 or minus 3 times V_1 plus 2 times V_2 which is αV_1 plus βV_2 . So, α is minus 3 and β is 2 α is minus 3 and β is 2 .

(Refer Slide Time: 10:06)

The screenshot shows a circuit diagram with two operational amplifiers (op-amps) and various resistors. The circuit is annotated with handwritten notes and equations. The top right corner contains the equation $V_{AB} = 0 = \left(-\frac{V_{test}}{3}\right) = \left(+\frac{1}{3}\right)V_{test}$. The bottom left corner contains the equation $V_{out} = \alpha V_1 + \beta V_2$. The circuit diagram shows two op-amps, one labeled A1 and the other A2. The input terminals are labeled A1, B1, A2, and B2. The output terminal is labeled V_{out}. The circuit includes resistors of 2kΩ and 1kΩ, and voltage sources V₁, V₂, and V_{test}. The handwritten notes indicate that the circuit is in negative feedback.


Now, the next question is to find the signs of the op amp terminals. So, that they are indeed in negative feedback, we solved the previous problem by assuming that it is in the negative feedback. Now, we will see how to assign the signs of the op amp, so that it is in negative feedback, we can start with either one. So, let me start with this is OPA 1, so let me remove this op amp and I have to measure V_{AB} just for simplicity I call it be V_{AB} these terminals are A1 and B1 what I have to do is apply a test voltage here and null the independent sources, so V_1 equals 0 and V_2 equals 0. So, this gets shorted into ground that gets shorted to ground.

So, now, this V_{test} will go through some circuit as usual V_{AB} is proportional to V_{test} if V_{AB} is a positive number times V_{test} then A1 is negative and B1 is positive, if V_{AB} is a negative number times of V_{test} then A1 is positive and then B1 negative. So, now, first we will try assuming that this op amp is already in negative feedback so; that means, that this is at 0 volts, this is also at 0 volts.

So, then the current flowing here would be V_{test} divided by 1 kilo ohm, the same current will flow through the resistor, see there is actually no contradiction here, because the current flowing here can flow through there, sometimes when there is no feedback around this op amp then you will end up with some contradiction, but in this case it is perfectly fine to assume that this op amp has negative feedback, then we do not have naught worry about the signs of this.

So, then the voltage here is this current V_{test} by 1 kilo ohm times 1 kilo ohm, so that is also V_{test} . Now, because this is 0 volts and we have a V_{test} drop across it at this point we get minus V_{test} and here if I call this V_A that is 0 volts, because it is shorted to ground and this V_B is this V_{test} divided by whatever ratio comes out of this resistor divider which is 1 kilo ohm divided by 1 kilo ohm plus 2 kilo ohms. So, V_B will be minus V_{test} divided by 3. So, this $V_A B$ in this polarity is 0 minus minus V_{test} by 3 or plus 1 by 3 times V_{test} , so it is a positive number times V_{test} . So, what it means is that A_1 has to be negative terminal of the op amp. So, then that is what is given over there. So, for the first op amp A_1 is the negative terminal.

(Refer Slide Time: 13:35)

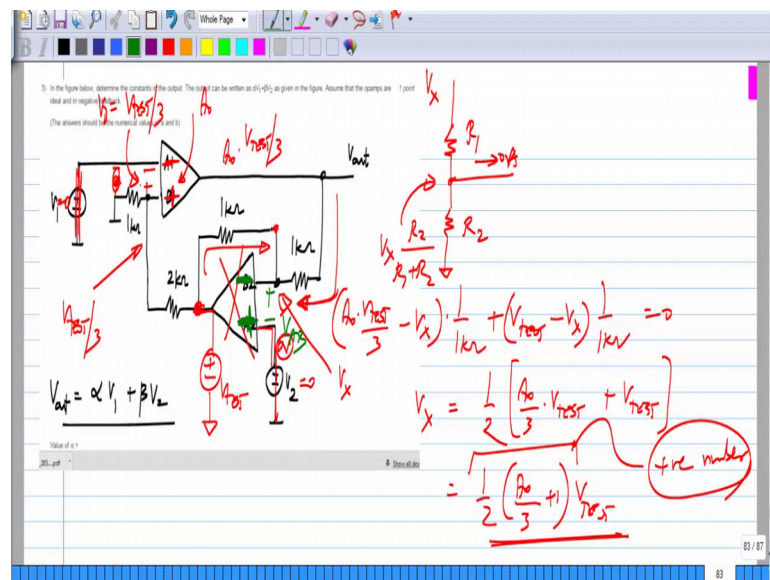

Let us now repeat the exercise for the second op amp, we already know that this is negative terminal, this is the positive terminal as usual we null the sources V_1 equal 0, V_2 equal 0 and I remove this op amp and apply V_{test} . So, now, again first we can try assuming that this op amp has negative feedback, so its inputs are at virtual ground, but

if you do assume that this is at 0 volts, because this is at 0 volts then you have a contradiction, because no current flows into the op amp we apply V_{test} here due to this voltage divider this 2 kilo ohm and 1 kilo ohm are in series I call it a voltage divider when you have 2 resistance in series and there is no other current flowing anywhere.

So, then if you apply V_x here we will get V_x times, let us say this is R_2 and R_1 R_2 by R_1 plus R_2 . So, we would have to get V_{test} divided by 3 over there, but that is the problem, because now the virtual ground concept is saying that this is 0 volts, this is really means that you cannot use the virtual ground idea or the fact that this op amp is in negative feedback.

Now, this is not surprising, because it turns out that this op amp will be negative feedback only when this op amp is present. So, now, we cannot use that model, so what we have to use is that this has a certain gain A_{naught} it does not matter what it is it is A_{naught} critical. So, now, this terminal here is that V_{test} by 3 and we know that it is plus minus this way the voltage that way is V_{test} by 3. So, the output voltage will be A_{naught} times V_{test} divided by 3, because this is the this voltage here is the difference input of the op amp V_d , so it is A_{naught} times V_{test} by 3.

So, we can calculate what voltage appears here. So, let me call this V_x the other terminal anyway is at 0 volts, if I call this V_x then there is a certain current flowing here which is A_{naught} times V_{test} by 3 minus V_x times 1 by 1 kilo ohm basically it is a voltage drop this voltage minus that voltage divided by 1 kilo ohm. And also in this direction there is another current flowing, which is V_{test} the voltage here minus V_x divided by 1 kilo ohm.

So, the sum of currents entering this node has to be 0 because nothing is connected there. So, V_{test} minus V_x 1 kilo ohm equals 0, so from this I will find V_x , so V_x will turn out to be 1 half of A_{naught} by 3 times V_{test} plus V_{test} which is half A_{naught} by 3 plus 1 times V_{test} and this is a positive number. Now, because this is a positive number let me call this $V_{A B}$. So, if this is a positive number; that means, that this has to be the negative terminal and that has to be the positive terminal. So, B 2 is the negative terminal and that is what is indicated in the answer over there.

(Refer Slide Time: 17:47)

7) In the figure below, determine the highest amplitude V_p which can be used such that the opamp is not saturated. (The answer should be the numerical value of the voltage in volts/V) (If the answer is 5V, write 5) (If the answer is 5mV, write 0.005 etc.)

Handwritten notes on the whiteboard:

- $V_i = 1V \cos \omega t$
- $V_o = -4V_i = -4V \cos \omega t$
- $V_o = -4(1V + V_p \cos \omega t)$
- $= -4V - 4V_p \cos \omega t$
- $-10V < -4V - 4V_p \cos \omega t < +10V$
- $-6V < -4V_p \cos \omega t < 14V$
- $1.5V > V_p \cos \omega t > -3.5V$

So, next question there is this op amp which the operating from 10 volts applies it what it really means is that the op amps output will be saturated to the power supply values it cannot go above plus 10 volts or go below minus 10 volts, the input is given to be 1 volt plus $V_p \cos \omega t$ and we know that this is an inverting amplifier even if you do not know it by assuming the virtual ground concept this is at 0 volts, this is V_i by 1 kilo ohm flows that way, the same current flows there because nothing flows into the input of the op amp, the voltage drop here is V_i by 1 kilo ohms times 4 kilo ohms or V_i times 4.


So, this voltage here is minus 4 times V_i it is 0 volt minus the drop across the 4 kilo ohm resistor. So, V_o is minus 4 times 1 volt plus $V_p \cos \omega t$ or minus 4 volt minus 4 $V_p \cos \omega t$. Now, this voltage here minus 4 volt minus 4 $V_p \cos \omega t$ has to be between minus 10 volts and plus 10 volts. Now, I will shift this four to this side and also to that side it says that minus 4 $V_p \cos \omega t$ should be smaller than 14 volts if I take it on this side and minus 6 volts if I take it on that side and if I divide every side by minus 4 first of all the sign of the inequalities the direction inequalities will be reversed and I will have 1.5 volts greater than $V_p \cos \omega t$ greater than 14 by 4 which is minus 3.5 volts.

So, now, there are through two different limits, first of all we know that $V_p \cos \omega t$ goes between plus V_p and minus V_p and it is limited by 1.5 volts on the upper side and minus 3.5 volts much larger value on the negative side, so; obviously, the

relevant limit is on the upper side. So, $\cos \omega t$ has the maximum value of one, so V_p has to be smaller than 1.5 volts and that what is given there.

Because, the input has an off set of 1 volt, the output will have negative off set of minus 4 volts. So, it will clip more easily on one side than on the other side. But, if it is clipped on one side then that side you cannot do anything useful with amplifier its output is not a linear multiple of the input. So, the maximum input amplitude V_p you can apply to this circuit without the op amp going into saturation is 1.5 volts.

(Refer Slide Time: 21:19)

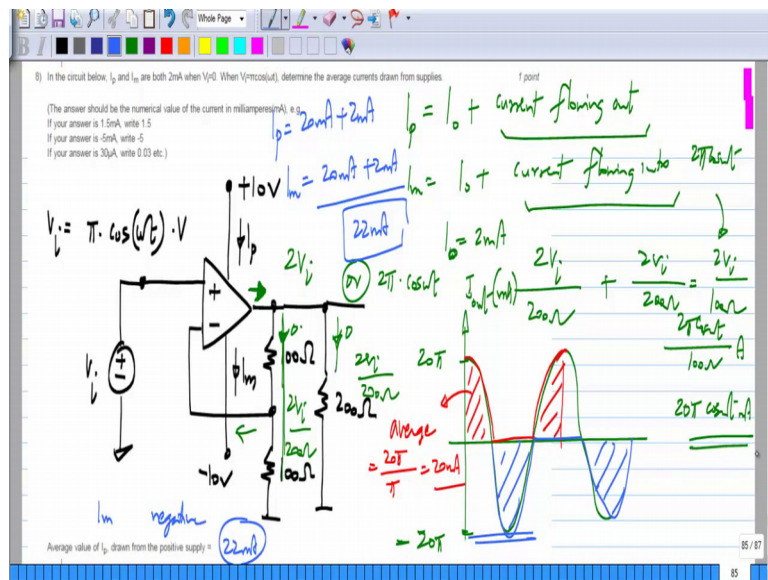

In this again there is a non inverting amplifier this resistance equals that resistance. So, the output is 2 times V_i this you should know by now otherwise you can refer to the lectures and there is also some load resistance connected to the output and this question is about the currents drawn by the op amp from the supply voltages, first of all it tells you that V_i when V_i is 0 when this is 0 the current I_p and I_m are both 2 milli amps. So, when V_i is 0 what happens is this is at 0 volts, so the current here is 0 and the current there is 0.

So, the output current of the op amp is 0 so; that means, that we know that the model for both I_p and I_m is I_p is some fixed value I_{naught} plus current flowing out of the op amp if the current is flowing out and I_m is I_{naught} plus current flowing into the op amp, if the current is flowing in, so if the current is flowing in I_p will be just equal to I_{naught} and if the current is flowing out I_m will be just equal to I_{naught} .


Now, when V_i equals 0 no current is flowing out of the op amp, so this means that this I_{naught} value is 2 milli amps, because no current is flowing out of the op amp then I_p is I_{naught} and I_m is also I_{naught} . So, this says that I_{naught} is 2 milli amps and the input is $\pi \cos \omega t$ when the input is $\pi \cos \omega t$ the output will be $2 \pi \cos \omega t$.

So, now, the current flowing out of the op amp is the output voltage $2 V_i$ divided by this resistance, this series combination of resistances no current flows here. So, the current flowing this way is $2 V_i$ divided by 200 ohms and the current flowing that way is also $2 V_i$ divided by 200 ohms. So, the total current flowing out of the op amp is $2 \text{ times } V_i$ divided by 200 ohms plus $2 \text{ times } V_i$ divided by 200 ohms or $2 \text{ times } V_i$ divided by 100 ohms.

So, if the input is $\pi \cos \omega t$ the output voltage will be this will be $2 \pi \cos \omega t$ and the current will be $2 \pi \cos \omega t$ divided by 100 ohm this many amperes or basically $20 \pi \cos \omega t$ milli amperes. So, the total current is a sinusoidal who peak value is 20π milli amperes, now during these part of the cycle the current will be flowing out of the opamp and this will contribute to I_p . And if you calculate the average of this, you know this from other basic mathematics that the value of this half wave rectifier sign wave, now value of the half sign wave will be 1 by π times the peak value. So, the average value here which is what is asked for is 20π divided by π which is 20 milli amperes. And similarly for the negative half cycle we have this it has a peak value of this 20π and the average values again 20π divided by π or 20 milli amperes.

So, the average value of I_p will be 20 milli amperes due to the signal dependent current plus a fixed current of 2 milli ampere and similarly for I_m we have 20 milli amperes due to the sinusoidal current plus 2 milli amperes. So, both are equal to 22 milli amperes. So, the average value of I_p drawn from the positive supply is 22 milli amperes and the same is true for I_m from the negative supply.

(Refer Slide Time: 26:16)

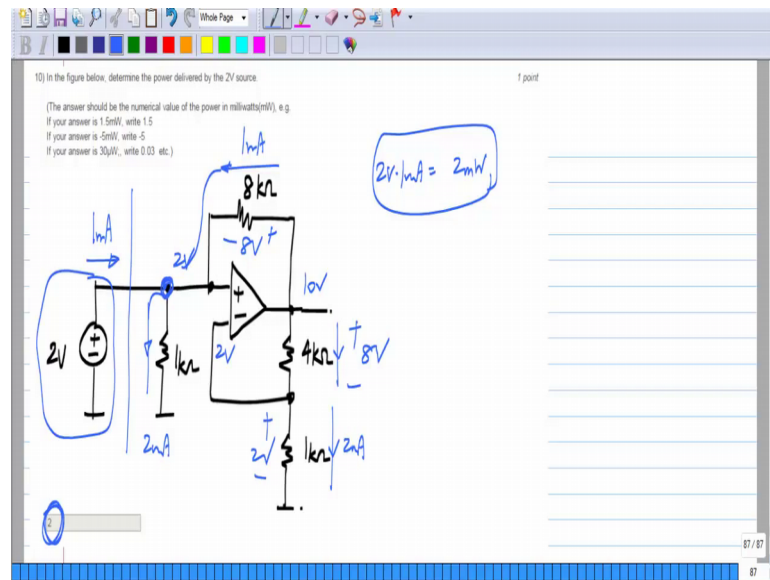

The last question here talks about power delivered by the 2 volt source essentially to do that you have to calculate the amount of current flowing there and that is not difficult first of all 2 volts supplied here and you can recognize that if the op amp is ideal and then negative feedback this will be 2 volts and you can verify that it is indeed in negative feedback. So, the current here is 2 volts divided by 1 kilo ohm which is 2 milli ampere, the current there is 2 milli amperes as well. So, the voltage here is 2 milli amperes times 4 kilo ohm which is 8 volts.

So, the total voltage here is 2 volt plus 8 volt which is 10 volts, so what happens is there is a current flowing this way which is 2 volts divided by 1 kilo ohm which is 2 milli amperes and there is a current flowing that way which is 10 minus 8 that is 8 volts divided by 8 kilo ohm which is 1 milli ampere. So, we are applying KCL at this node you will see that the current driven from the 2 volt sources 1 milli ampere. So, the power delivered is 2 volts times 1 milli ampere which is 2 milli watts. So, and that is the answer, so that concludes the solutions for the assignment for the 8th week.