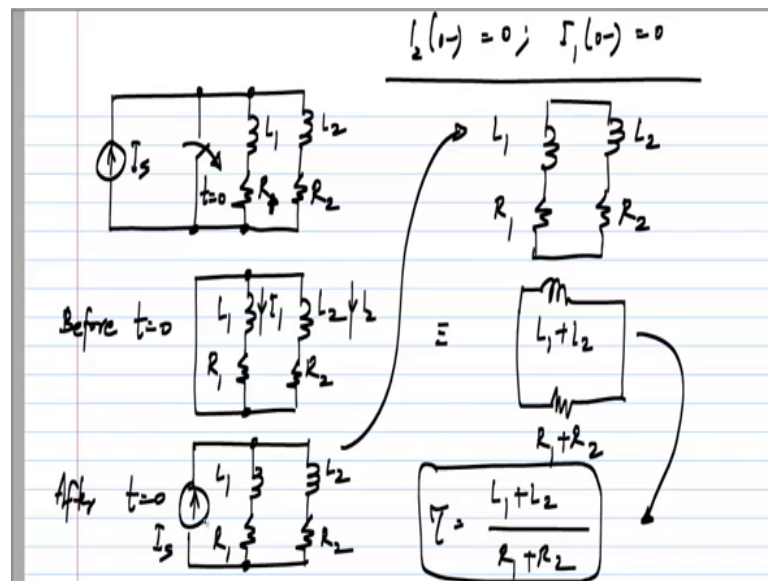


Basic Electrical Circuits
Dr Nagendra Krishnapura
Department of Electrical Engineering
Indian Institute of Technology Madras

Lecture – 130

Now, we will look at an example of a circuit with inductors where inductors currents can undergo instantaneous changes.

(Refer Slide Time: 00:12)



Let say we have a current I_s and we have a space like this as a mention before if you have switching action that could be equivalent to stepping the values of currents or voltages in the circuits. And let say this switch is initially short circuited and it opens at t equal to 0 and let say we have these two inductors of first order all will determine the order of the circuit, that will come soon.

Now, before t equal to 0 this switch is short circuited and all of this current flows in to the short circuit and all we have effectively is a circuit like this and after t equal 0 we have the current source driving this two parallel branches. So, that is say the value of this is I_s , so we can think of basically solving this particular circuit, because a won't you solution for t greater than 0 and in some initial conditions some values of L_1 and L_2 , R given at t equals 0.

Let me for simplicity assume that the current through L_1 and the current through L_2 are both 0 just before the step current is applied like said opening this switch is like a

applying step current to this particular circuit. So, first of all, what is the order of the circuit, so if I take the source free circuit that is with the current source open circuited, what do I have I have the single loop $R_1 R_2, L_1 L_2$. And this is the of course, equivalent to we can see that these two inductors are in series these two resistors are in series. So, we have L_1 plus L_2 as a single inductor of L_1 plus L_2 across that we have a single resistor R_1 plus R_2 .

We know that, if you have a single inductor in a circuit it is a first order circuit and the time constant of the circuit is value of the inductors divided by the value of the resistance, which is across it. So, this will give you the time constant, which is equal to L_1 plus L_2 divided by R_1 plus R_2 . So, this is the way calculate the time constant we will, now the valued formally and verify that this is the indeed the case.

(Refer Slide Time: 04:02)

Time constant

$$L_1 \frac{di_1}{dt} + R_1 I_1 = L_2 \frac{d(I_s - I_1)}{dt} + R_2 (I_s - I_1)$$

$$(L_1 + L_2) \frac{dI_1}{dt} + (R_1 + R_2) I_1 = L_2 \frac{dI_s}{dt} + R_2 I_s$$

$$\frac{L_1 + L_2}{R_1 + R_2} \frac{dI_1}{dt} + I_1 = \frac{L_2}{R_1 + R_2} \frac{dI_s}{dt} + \frac{R_2}{R_1 + R_2} I_s$$

So, let me copy over the this part of the circuit and write the different equation now will choose I_1 as the variable I_1 is the current through well L_1 and by Kirchoff current law here and these node I know that in the current through L_2 is I_s minus I_1 . Now, what is the circuit equation i going to it these three branches are in parallel in particular L_1 and R_1 the series branches parallel with the series branches L_2 and R_2 .

So, the voltage across these branch and that branch are exactly the same and that is say equation I going to write you can write any way we want you can write the KVL around this 2.1. Now, the voltage across L_1 and R_1 will be L_1 time derivative of I_1 plus R_1 times I_1 and that is the exactly equal to L_2 times the time derivative of the current

through L_2 , which is I_s minus I_1 plus R_2 times the current, which is I_s minus I_1 . So, if I group all the terms containing the variable I_1 to the left hand side this is what I will and on the right hand side left with.

I will normal said, so that the term without the deli derivative the 0 of term on the left hand side as a coefficient of a unity. So, that lets me read of the time constant, so I divided all terms by $R_1 + R_2$. So, now, this is in the standard form and if this coefficient is unity the coefficient here is the time constant is exactly, what we calculated earlier. that is the time constant.

(Refer Slide Time: 07:00)

$$\frac{L_1 + L_2}{R_1 + R_2} \frac{dI_1}{dt} + I_1 = \frac{L_2}{R_1 + R_2} \frac{dI_s}{dt} + \frac{R_2}{R_1 + R_2} I_s$$

$I_s(t) = I_0$ at $t=0$

$\frac{dI_s}{dt}$: impulse @ $t=0$

@ instant of the step

$$\frac{L_1 + L_2}{R_1 + R_2} \int_{0^-}^{0^+} \frac{dI_1}{dt} dt = \frac{L_2}{R_1 + R_2} \int_{0^-}^{0^+} \frac{dI_s}{dt} dt$$

The equation also tells us a number of other things like a said what we have the circuit in which, this current I_s is being step at t equal 0 it goes from 0 to some value, let me call that I_{naught} . So, if a think about is I_s as a time function it goes from 0 to I_{naught} , so the derivative of I_s is an impulse at t equals 0. Now, I do not want to introducing impulses in to or calculation in and so on and it is not necessary also just to find out what we will not we can simply appreciate the fact that the first derivative of I_s is an impulse, so this is an impulse were has this quantity with just as I_s is finite.

This already tells you that this I_1 cannot be continues I_1 also must have a jump, because if a I_1 is continues than the slope of I_1 will be finite everywhere and we can never impulse on the right hand side with only finite quantities on the left hand side. So, the only way for this equation is to satisfied is for I want to have a step, which means that the first derivative of I_1 , dI_1 by dt also an impulse. So, this part which is an impulse

balances this part, which is also an impulse.

So, that is balance by that one and this part, which is finite will balance that part which is also finite which is just at the instant of the step. So, at the instant of the step we have L_1 plus L_2 by R_1 plus R_2 times dI_1 by dt to be equal to L_2 by R_1 plus R_2 times dI_s by dt . Now, this means that this just the instead of the step if I integrate both sides with respective time this will be equal to each other between the same limits 0 minus and 0 plus.

(Refer Slide Time: 10:02)

$$\textcircled{a} \text{ instant of the step}$$

$$\frac{L_1 + L_2}{R_1 + R_2} \int_{0^-}^{0^+} \frac{dI_1}{dt} dt = \frac{L_2}{R_1 + R_2} \int_{0^-}^{0^+} \frac{dI_s}{dt} dt$$

$$\frac{L_1 + L_2}{R_1 + R_2} [I_1(0^+) - I_1(0^-)] = \frac{L_2}{R_1 + R_2} [I_s(0^+) - I_s(0^-)]$$

$$[I_1(0^+) - I_1(0^-)] = \frac{L_2}{L_1 + L_2} [I_s(0^+) - I_s(0^-)]$$


So, if I do this, this quantity with nothing but, I_1 of 0 plus minus I_1 of 0 minus and this quantity here is nothing but, I_s of 0 plus minus I_s of 0 minus and I will of course, have the same scaling factors on the two sides. So, what this tells you is that R_1 plus R_2 in the denominator will cancel allowed. So, we will have the change in current across the step across the instead of the step will be L_2 by L_1 plus L_2 times the change in the source current.

Now, this is similar to what we have to capacitors if you apply a voltage step across a series combination of capacitors than across each capacitor we will have some capacitor will ratio times the input step. Similarly, if you apply a step current to a parallel combination of inductors than them each inductors you will have step current and the size of the step in each will be related to ratios of inductors.

So, this you can calculate and again just like in case of capacitors when we applied Kirchhoff's current law at the instant of the step we could ignore the resistors, because if

you had infinite currents in capacitors and finite current through the resistors the resistors do not contribute anything and we can kind of neglect them. And; that is what we have done mathematically here I would try to balance the left and right sides separately for the impulses and the finite quantities.

(Refer Slide Time: 12:14)

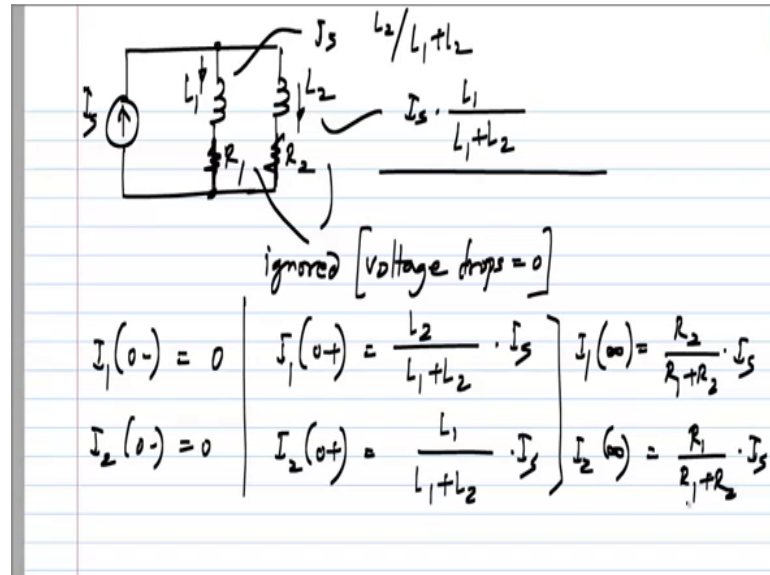


So, just like we ignored resistors in parallel with capacitors in this case we can ignore resistors and series with inductors. So, just for the calculation of current steps whatever R_1 we had here and R_2 we had here these two are ignored while writing KCL; that means that the voltage drops across them equal 0; that is they are short circuited. And these makes and again, because if you have a step change and inductor current across the inductor you have an infinitely large voltage and this is finite voltage across the resistor, so we neglected similar to how a neglected resistive currents in circuits were capacitors current were infinite.

We have L_1 and L_2 and we have I_s and you clearly see that the current divides in inverse ratios of inductors. So, through L_1 we would have I_s times L_2 by L_1 plus L_2 and through L_2 we will have I_s times L_1 by L_1 plus L_2 . Just like we said that in a series combination of capacitors that R cannot go anywhere from the intermediate plate the total charge there has to remain the same here also we can state a similar rule were the total flux in case will remain the same in the inductors just across the step.

Remember all of these calculations are valued just calculate the inductor currents immediately after the step after that the resistor voltages will be significant and we have

to go from there. So, I_1 , which is the current through L_1 at 0 minus was 0 and I_2 as 0 minus was also 0 and just after the application the current step this will be L_2 by L_1 plus L_2 times I_s and I_2 of 0 plus is L_1 by L_1 plus L_2 times I_s .

(Refer Slide Time: 14:38)

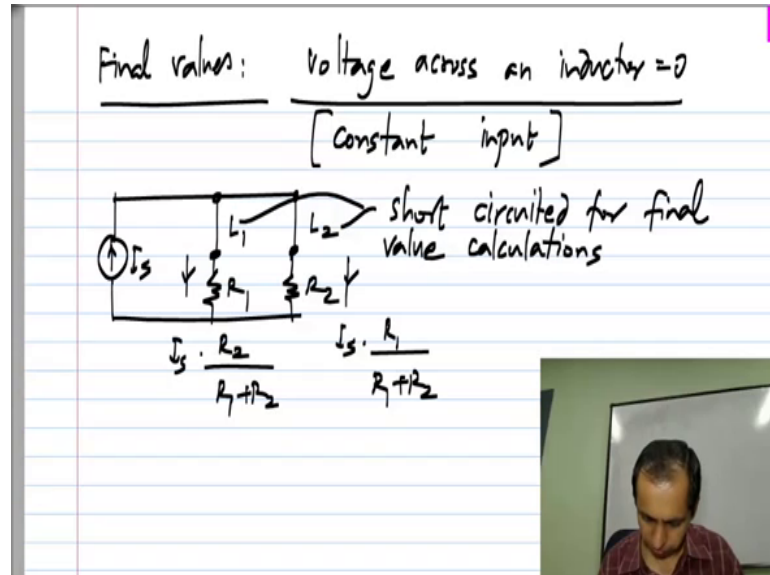

So, from these and the final values, which can also be calculated quite easily for the final values in an inductor circuit, what is that we no voltage across an inductor equals 0 this is of course, assuming constant are fees wise constant in inputs this is for a constant input. Because, than the inductor current also has to be constant and if they inductor current is constant the voltage across it, which is the time derivative of the current will also be 0.

So; that means, that all inductors can be short circuited for the final value calculations when you have constant inputs. So, we have I_s and I will short circuit L_1 and also short circuit L_2 and we have R_1 and R_2 , so this is the resistive circuit, so we know that the final values will be I_s times R_2 by R_1 plus R_2 over there and I_s times R_1 by R_1 plus R_2 over there. So, this also we know, we know the time constant, so we can construct the final solution very easily.

So, I_1 of infinity will be R_2 by R_1 plus R_2 times I_s and I_2 of infinity would be R_1 by R_1 plus R_2 times I_s . So, from these and the time constant we can write down the functions for both I_1 and I_2 .

(Refer Slide Time: 16:43)

$\tau = \frac{L_1 + L_2}{R_1 + R_2}$

Solutions:

$$I_1(t) = I_1(\infty) + [I_1(0+) - I_1(\infty)] \cdot \exp\left(-\frac{t}{\tau}\right)$$

$$= \frac{R_2}{R_1 + R_2} \cdot I_s + \left[\frac{L_2}{L_1 + L_2} I_s - \frac{R_2}{R_1 + R_2} I_s \right] \cdot \exp\left(-\frac{t}{\tau}\right)$$

$$I_2(t) = I_2(\infty) + [I_2(0+) - I_2(\infty)] \exp\left(-\frac{t}{\tau}\right)$$

$$= \frac{R_1}{R_1 + R_2} \cdot I_s + \left[\frac{L_1}{L_1 + L_2} I_s - \frac{R_1}{R_1 + R_2} I_s \right] \cdot \exp\left(-\frac{t}{\tau}\right)$$

I assume 0 initial conditions, so I_1 of t , which is I_1 of infinity plus I_1 of 0 plus minus I_1 of infinity times exponential minus t by tau term, which this is the of course, the general form for any first of the circuit and I_1 of infinity we found was R_2 by R_1 plus R_2 times I_s and I_1 of 0 plus is L_2 by L_1 plus L_2 times I_s minus I_1 of infinity, which is R_2 by R_1 plus R_2 times I_s exponential minus t by tau I will written the symbol tau, but we know that tau equals L_1 plus L_2 divided R_1 plus R_2 , so this is the expression for I_1 of t .

I_2 of t is of course, the same general form I_2 of infinity plus I_2 of 0 plus minus I_2 of infinity exponential minus t by tau, tau is of course, the same and I_2 of infinity is R_1 by R_1 plus R_2 times I_s plus L_1 by L_1 plus L_2 times I_s minus R_1 by R_1 plus R_2 times I_s exponential minus t by tau. So, these are the solutions for I_1 and I_2 as the function of time and if we have numerical values we can substitute these and also we assume 0 initial condition just before the step is applied if we do have non 0 initial conditions than its a still quite easy.

(Refer Slide Time: 19:00)

Handwritten mathematical derivation on lined paper:

② instant of the step

$$\frac{L_1 + L_2}{R_1 + R_2} \int_{0^-}^{0^+} \frac{dI_1}{dt} dt = \frac{L_2}{R_1 + R_2} \int_{0^-}^{0^+} \frac{dI_2}{dt} dt$$
$$\frac{L_1 + L_2}{R_1 + R_2} [I_1(0^+) - I_1(0^-)] = \frac{L_2}{R_1 + R_2} [I_2(0^+) - I_2(0^-)]$$
$$[I_1(0^+) - I_1(0^-)] = \frac{L_2}{L_1 + L_2} [I_2(0^+) - I_2(0^-)]$$

All we have to do substitute the right values for I_1 of 0 minus over there, so from there we can calculate everything. So, that is how we calculate currents for any other quantity in a circuit where the inductor current can have step changes.