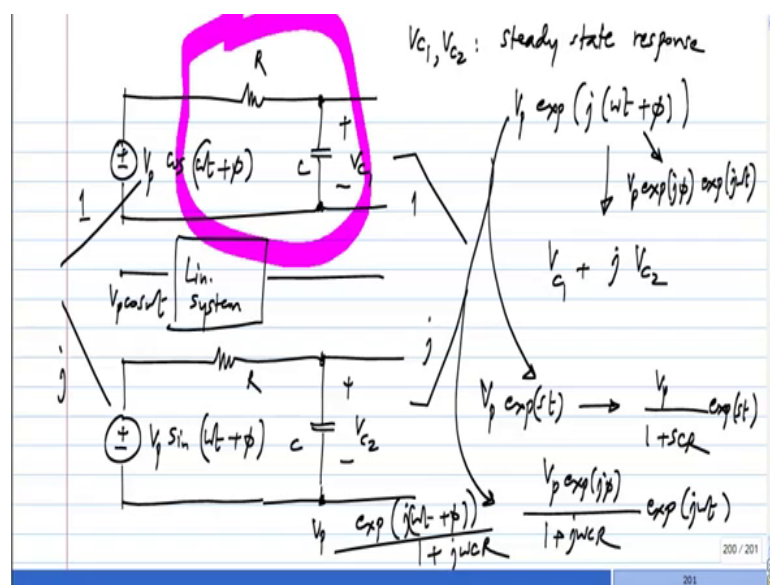


**Basic Electrical Circuits**  
**Dr Nagendra Krishnapura**  
**Department of Electrical Engineering**  
**Indian Institute of Technology Madras**

**Lecture – 134**

It turns out that there is an even more elegant way of finding the force response of a linear circuit to a sinusoidal input, given that we know the solution to exponential  $s t$  and we also know that these are linear circuits.

(Refer Slide Time: 00:17)



I will show an R c filter here, but this applies to any linear system of any order. I will continue with this example, but it could be, some way I could think of a general system here, where I apply  $V_p \cos \omega t$  to some linear system. So, I will get some let say  $V_c 1$ . So, here I am only considering the steady state response parts, so let say this  $V_c 1$  is the steady state and  $V_c 2$  is the steady state response. So,  $V_c 1$  is the steady state responds to  $V_p \cos \omega t + \phi$ ,  $V_c 2$  is the steady state responsively  $V_p$  times  $\sin \omega t + \phi$  and we know that, this follows super position. So, the steady state responses follow super position.


So, what should I do now? What could I do? Let say I could weight this by some number and this by some other number and add up, that will be the response to weighting this by some number and weighting this by this number. Is not it or if I imagine this R c filter with  $\alpha$  times this as the input and  $\beta$  times that as the input, the steady state response will be  $\alpha$  times  $V_c 1$  plus  $\beta$  times  $V_c 2$ . Is it part convincing? This is

just straight forward super position.

So, the interesting thing is now let say this is 1 and this is j, I will take  $V_p \cos \omega t + \phi$  plus  $j$  times  $V_p \sin \omega t + \phi$ , this is all in your head. I mean do not worry about how we get  $j$  times  $V_p$  as the voltage. So, what is the actual input that you are applying? This is equivalent to applying an input of  $V_p$  exponential  $j \omega t + \phi$  and the response to that is... Now, the solution to this is I already know. What is it? What is the steady state solution to  $V_p$  exponential  $j \omega t + \phi$  for this particular circuit?

I have two linear systems, the first one has an input  $V_p \cos \omega t + \phi$ , second one has an input  $V_p \sin \omega t + \phi$ , the first one has the response  $V_{c1}$ , second one has the response  $V_{c2}$ . So, if I apply to a third system, so maybe I will show those pictures.

(Refer Slide Time: 03:39)

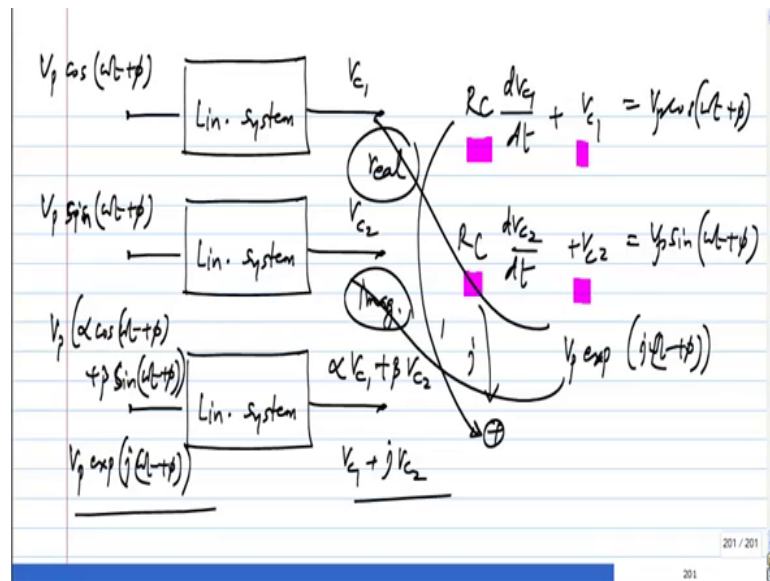

So, let say the response is  $V_{c1}$  to  $V_p \cos \omega t + \phi$  and the response is  $V_{c2}$  to  $V_p \sin \omega t + \phi$  and so if I have  $V_p$  times  $\alpha \cos \omega t + \phi$  plus  $\beta$  times  $\sin \omega t + \phi$ . The steady state response would be  $\alpha V_{c1} + \beta V_{c2}$  that is. So, clearly this falls for any  $\alpha$  and  $\beta$ , so I will use  $\alpha$  equal to 1 and  $\beta$  equals to  $j$ . So, the response to  $V_p$  exponential  $j \omega t + \phi$  would be  $V_{c1} + j V_{c2}$ .

So, what is the response of R circuit to  $V_p$  ((Refer Time: 05:10)) exponential  $j \omega t + \phi$ ? What is the response to  $V_p$  exponential  $s t$ ? What was it, the study state

response?  $V_p$  by  $1 + sCR$  exponential  $s t$ . So, this is nothing but,  $V_p$  exponential  $j\omega t + \phi$  exponential  $j\omega t$ . So, the solution to this is  $V_p$  exponential  $j\omega t + \phi$  by  $1 + j\omega CR$  exponential  $j\omega t$  and I can put the  $\phi$  back to there, I can write it as also  $V_p$  exponential  $j\omega t + \phi$  by  $1 + j\omega CR$ .

The answer I already know that is the advantage here, I did the super position, the input turns out to be  $V_p$  exponential  $j\omega t + \phi$  and answer to that I already know, then what.

Student: ((Refer Time: 06:20))

If I write the differential equation separately, this one is  $R \frac{dv_c}{dt} + v_c = V_p \cos \omega t + \phi$  and  $R \frac{dv_c}{dt} + v_c = V_p \sin \omega t + \phi$ , the key here is these coefficients are all real, if those coefficient for imaginary which is a perfectly valid linear differential equation we could not do this, then you would get cross them, I mean this can give you that and so on.


The only place we get this square root of minus 1 is where we do the super position, we multiply this by 1 and we multiply this by  $j$  and then we add it up. So, the only place where this  $j$  appears is when it multiplies this one, because of that when you compute the response to  $V_p$  exponential  $j\omega t + \phi$ , the real part is the response here and the imagine part is the response there. The key thing here is that, this is the liner system whose differential equation has only real coefficients.

Now of course, any circuit will follow that because all our component values are real, but it is possible to construct differential equations with I mean I can just put a  $j$  here, we can find the solution to that. But, then you cannot say that the real part is coming from there, because you could also get a complex part just because of  $j$  that inside the system. So, this is the real part and this is the imaginary part, is this fine. So, this is just a way of superposing cos and sin to get complex exponential and the solutions to complex exponential in general are simpler, algebraically compare to the solutions to sinusoidal.

There is the same solution of course, in a spirit, but the formulas look a little more messy, because I had this  $\alpha \cos \omega t + \beta \sin \omega t$  and then I have to find constants and so on. Now, this is an easier way of doing it of course, while doing this you will get the same answer. So, I strongly urge you to try all three methods, this is first of all a very, very simple circuit. So, you put a solution as  $\alpha \cos \omega t + \beta \sin \omega t$ , find the constants, you decompose the cos as exponential plus  $j\omega$  exponential minus  $j$


omega, find the solution. And finally, you do this you will get the solution. What is the solution then? What is  $V_c$  (Refer Time: 08:44)? What is the force response? What is the real part of this?

(Refer Slide Time: 08:50)

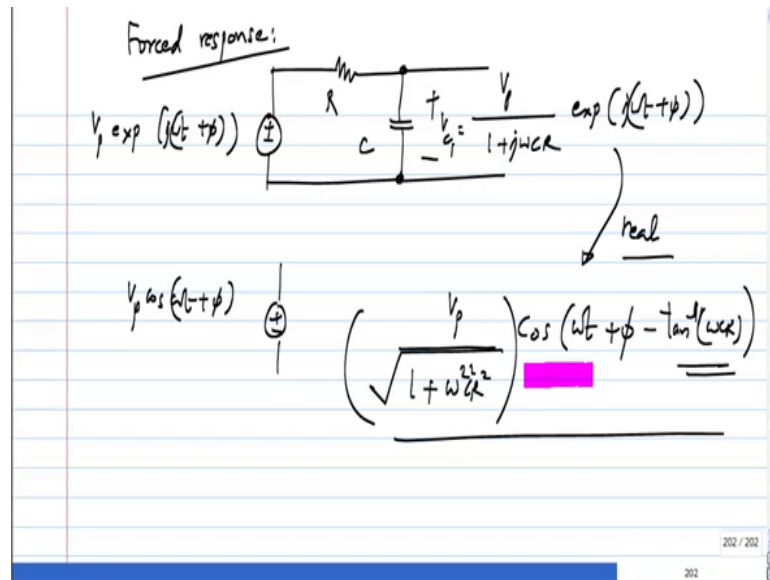

If this is the source R and C, the solution is  $V_p$  by  $1 + j\omega c R$  exponential  $j\omega t + \phi$ , this is the force response again we are only talking about the force response here and if you had  $V_p \cos \omega t + \phi$  as the excitation, the response would be the real part of this. So, what is the real part of this?

(Refer Slide Time: 09:38)

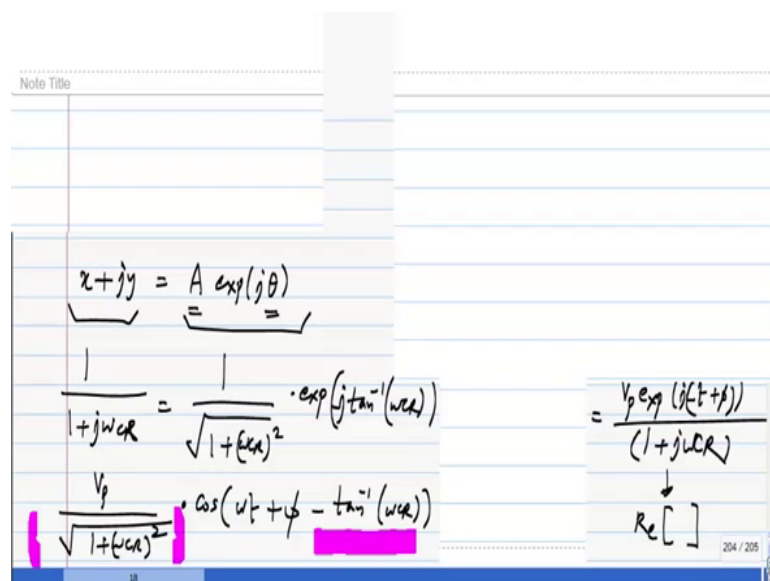

The real part of this and what is that many ways to do it, first of all I assume we are

already pretty comfortable with calculations involving complex numbers, there are two forms of complex numbers, this is not as a rectangular form, where review the x and y coordinates of the complex number or the polar form it is here to amplitude and the argument or the angle.

Now, both representations say useful clearly this is more convenient for adding complex numbers, this is more convenient of multiplying complex numbers. So, if I use this here what do I have  $1 + j\omega c R$ . What is the amplitude of this?

Student: ((Refer Time: 10:29))

Amplitude.

Student: ((Refer Time: 10:32))

And that is the amplitude and the argument is  $\tan^{-1} \omega c R$ . There are so many ways of doing it. ((Refer Time: 10:52)) So, you get the real denominator and then a complex numerator and so on. So, finally, the response to this turns out be  $V_p$  by square root of  $1 + \omega c R^2$  and  $\cos(\omega t + \phi - \tan^{-1} \omega c R)$ .

So, you apply a sinusoidal to a linear system, what you get out with this, a sinusoidal with exactly the same treatment  $c$ , the amplitude will be deep changed and the face will be change. How much the amplitude will be change and then how much the face will be change depend on the circuit? So, this is the amount of face says and this is the factor by which the amplitude is change. So, that clearly depends on the circuit as well as frequency.

So, you can also once you have capacitors into the picture or inductors you can have frequency selective circuits that is circuits which behave differently and different frequencies. Clearly you can see from this expression itself that the  $\omega$  is very large the amplitude of the output will be very small and if  $\omega$  is very small, amplitude is the same as the input and very small is compare to  $1 + R c$ . So, if  $\omega c$  had is much smaller than 1 the output amplitude is  $V_p$  is much smaller than 1 it inversely proportional to  $\omega$  ((Refer Time: 12:20)).

So, the response the real part of this as a cosine  $\cos$  amplitude is  $V_p$  divided by square root of  $1 + \omega^2 c^2 R^2$  and whose argument is  $\omega t + \phi - \tan^{-1} \omega c R$ . Most important thing you notice here is that if you apply a

sinusoidal to a linear system, the force response will be a sinusoidal of the exactly the same frequency, you cannot generate any new frequency from the linear system, you applied  $\cos$  of  $\omega t$  you are only going to get  $\cos \omega t$ , it is amplitude is change it is phase is change that is all. But, this is the very, very important concept of linear systems that will be useful for everything both for analysis and measurement and testing.