



Now, we already discuss this we have  $V_c$  and its derivative we can have some trigonometry function here either sign or cos we have sign the derivative will be cos and we have cos the derivative will sign. So, in general  $V_c$  itself has to be linear combinations of sign and cos, so that this equation can be satisfied. So,  $V_c$  is let say some  $\alpha \cos \omega t + \beta \sin \omega t$ .

Now of course, this  $\omega$  is exactly the same as that one, because when you differentiate it this  $\omega$  will not change. So, you have to take this same frequency for this sinusoid as well. So, now, let us use this in the left hand side and try to balance the terms.

(Refer Slide Time: 03:25)

$$RC \frac{dv_c}{dt} + v_c = V_p \cos(\omega t + \phi)$$

$$RC [\beta \omega \cos \omega t - \alpha \omega \sin \omega t] + [\alpha \cos \omega t + \beta \sin \omega t] = V_p \cos(\omega t + \phi)$$

$$\beta(\omega RC) + \alpha = V_p \cos \phi$$

$$\beta - \alpha(\omega RC) = -V_p \sin \phi$$

$$\alpha = \frac{V_p \cos \phi + (\omega RC) V_p \sin \phi}{(\omega RC)^2 + 1}$$

$$\beta = \frac{(\omega RC) V_p \cos \phi - V_p \sin \phi}{(\omega RC)^2 + 1}$$

$$v_c(t) = \alpha \cos \omega t + \beta \sin \omega t = \sqrt{\alpha^2 + \beta^2} \cdot \cos(\omega t - \tan^{-1} \frac{\beta}{\alpha})$$

So, what we will get is this is, what we have on left side and the first of these term this will give you  $RC$  times  $\beta \omega \cos \omega t - \alpha \omega \sin \omega t$  and this term will give plus  $\alpha \cos \omega t + \beta \sin \omega t$ . And finally, on the right side we have  $V_p \cos \omega t + \phi$ . So, that has to be equal to  $V_p \cos \phi \cos \omega t - V_p \sin \phi \sin \omega t$ .

Now, you have  $\cos \omega t$  and  $\sin \omega t$  on the right hand side as well and left hand side, so the  $\cos \omega t$  has to be balanced by  $\sin \omega t$ , similarly  $\sin \omega t$  has to be balanced by  $\cos \omega t$ . So, we have two equations this plus that gives you that one that one and this plus that gives you that one. So, we have  $\beta \omega RC + \alpha = V_p \cos \phi$  and  $\beta - \alpha \omega RC = -V_p \sin \phi$ .

We have two unknowns alpha and beta we have two equations and we can solve for this, so solve for this yourself solving these two equations will get alpha to be  $V_p \cos \phi$  plus  $\omega C R$  times  $V_p \sin \phi$  times  $1$  over  $\omega C R$  square plus  $1$  and beta is  $\omega C R$  times  $V_p \cos \phi$  minus  $V_p \sin \phi$  and divided by  $\omega C R$  square plus  $1$ . Now, so the solution is we know it is  $\alpha \cos \omega t$  plus  $\beta \sin \omega t$ , which can also be written as square root of alpha square beta square that will be amplitude of the sin square times  $\cos \omega t$  and there will be a phase shift, which is minus tan inverse beta by alpha and these are alpha and beta.

(Refer Slide Time: 07:19)

$$\sqrt{\alpha^2 + \beta^2} = \frac{V_p}{\sqrt{1 + (\omega CR)^2}}$$

$$-\tan^{-1} \frac{\beta}{\alpha} = \phi - \tan^{-1}(\omega CR)$$

$$v_c(t) = \frac{V_p}{\sqrt{1 + (\omega CR)^2}} \cdot \cos(\omega t + \phi - \tan^{-1}(\omega CR))$$

$$v_s = V_p \cdot \cos(\omega t + \phi)$$


Again I will let you compute this square root of alpha square to beta square and tan inverse beta by alpha it turns out that square root of alpha square plus beta square is  $V_p$  divided by square root of  $1 + \omega C R$  square and minus tan inverse beta by alpha equals  $\phi$  minus tan inverse  $\omega C R$ . So, finally you will find that the steady state response is  $V_c$  of  $t$  is  $V_p$  by square root  $1 + \omega C R$  square  $\cos \omega t$  plus  $\phi$  minus tan inverse  $\omega C R$ , now the input  $v_s$  was  $V_p \cos \omega t$  plus  $\phi$ .

So, you can see that the output has the same frequency as the input  $\omega$  and what is happened is that there is an extra phase shift the phase has been modified by that much the input phase was  $\phi$  this is  $\phi$  minus tan inverse  $\omega C R$  the input amplitude was  $V_p$  the output amplitude  $V_p$  divided by some thing. So, this is in general true for any linear time variant system excited by sinusoid steady state responses will be sinusoid at the same frequency, but with the different amplitude phase.

Now, we can consider the second method using complex exponentials, which I outlined that is that if we have  $V_p \cos(\omega t + \phi)$  exciting the first order system in general I will take the R C circuit as an example we want to find the steady state part of the responses. Now, we can think of this  $\cos \sin$  as  $V_p / 2$  exponential  $j\omega t + \phi$  plus exponential minus  $j$  times  $\omega t + \phi$ . Now, if we are finding out only the steady state part of response we can use super position you can think as combination of two sources exponential of plus  $j\omega t + \phi$  exponential of minus  $j\omega t + \phi$ .

So, if we have  $V_p / 2$  exponential  $j\omega t + \phi$  it is very easy to write down steady state responses, what is  $V_c$  we know that for an input of  $V_p$  exponential  $s t$  the steady state responses is  $V_p / (1 + j\omega CR)$  exponential  $s t$ . And it is exactly the same thing we have here the input is  $V_p / 2$  exponential  $j\phi$  remember the argument here is proportional to time, so that part will isolate. So, this is equivocate to exponential  $j\phi$ , which is multiple factor to exponential  $j\omega t$ .

So, the steady state response corresponding to this is  $s$  here basically  $j\omega t$  over there. So, we will have this part of it, which is  $V_p / 2$  exponential  $j\phi$  whatever the amplitude is divided by  $1 + j\omega CR$  times exponential  $j\omega t$ . Similarly, if we have  $V_p / 2$  exponential minus  $j$  times  $\omega t + \phi$  as our input, which can be written as  $V_p / 2$  exponential minus  $j\phi$  exponential minus  $j\omega t$  response would be  $V_p / 2$  exponential minus  $j\phi$  divided by  $1 - j\omega CR$  exponential minus  $j\omega t$ , so all I do is in this solution I have to put  $s$  equals minus  $j\omega$  that is all. So, the steady state response is simply the sum of this and that one.

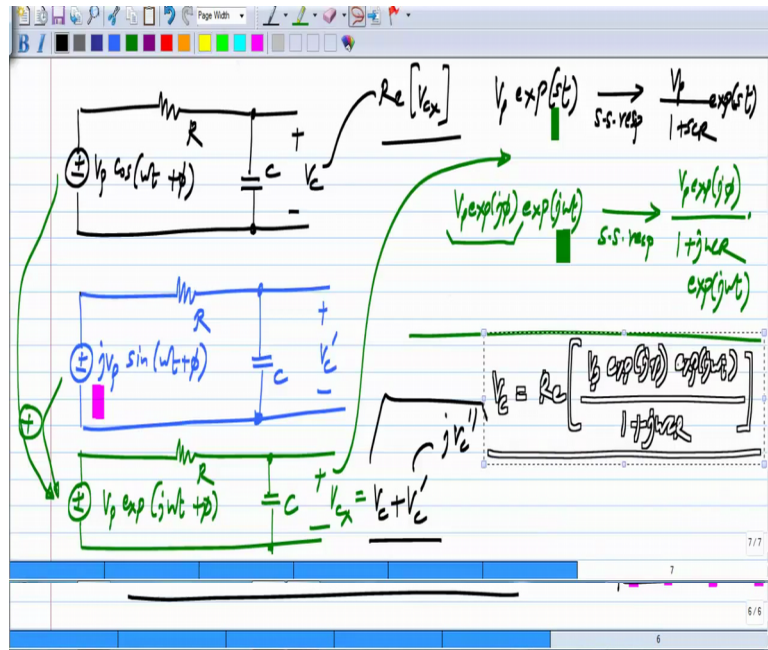

(Refer Slide Time: 09:20)

This is simply  $V_p \cos(\omega t + \phi)$  divided by  $1 + j\omega RC$  plus  $V_p \sin(\omega t + \phi)$  divided by  $1 - j\omega RC$  times exponential minus  $j\omega t$ . And this part you can do the simplification yourself you will find that the answer is  $V_p \cos(\omega t + \phi - \tan^{-1}(\omega RC))$ . Now, to be able to do this you have to flow into the usage of complex numbers in particular changing complex numbers from a polar to rectangular form and so on.

So, when you use the complex numbers you use something known as rationalization of the denominator to add up fractions. So, that you have a real number in the denominator and also you need to know rectangular to polar form conversion; that is we can express a complex number as  $x + jy$  or  $r \exp(j\theta)$ . So, this is the real part, this is imaginary part, this is the amplitude and this is phase any of them can be used and you too use them frequently.

Now, this two methods are expected give same answer but I have already talked about the other method, which is most convenient I have  $V_p \cos(\omega t + \phi)$  going into RC of an RC circuit and I want to find response  $V_c$  let us imagine another circuit to, which we apply  $jV_p \sin(\omega t + \phi)$  in c and let me call this  $V_{c'}$ . Now, if I take a third circuit and apply  $V_p \exp(j\omega t + \phi)$  I will get some response I will call that  $V_{c_x}$  that is the steady state responses.

We see that this case here exponential  $j\omega t + \phi$  is clearly a super position of these two cases. So, this  $V_c x$  is nothing but, because if I add this two  $V_p \cos(\omega t + \phi) + j \sin(\omega t + \phi)$  at  $V_p \exp(j\omega t + \phi)$ , so  $V_c x$  is simply  $V_c \cos(\omega t + \phi) + j V_c \sin(\omega t + \phi)$ . Now, everywhere we have only real coefficient real  $R$  real  $C$  the only place, where  $j$  a square root of minus 1 appears is over them.

So, in this  $V_c x$  we have  $V_c$ , which is purely real and  $V_c \cos(\omega t + \phi)$ , which is purely imaginary  $V_c \sin(\omega t + \phi)$  will be  $j$  times some  $V_c$  the whole prime and the answer we want to find as  $V_c \cos(\omega t + \phi)$  and that can be easily found us real part of  $V_c x$ . Now, the reason to do it as usual because the responses to an exponential is very easily determined for a linear differential equation. So, you do it with the particular kind of coefficient with  $j\omega$  instead of sinusoid of  $\omega$  and then, you find the real part and that is a solution this even easier than the previous case, where the super post two complex exponential.

We do not even need 2 1 is enough the response of this can be written down again quite easily, because we know that  $V_p \exp(s t)$  has a steady state responses remember I am only talking about steady state responses here  $V_p$  by  $1 + s C R$  times exponential  $s t$ . Now, this here, which is  $V_p \exp(j\phi) \exp(j\omega t)$  as a steady state responses they cannot exponential  $j\phi$  to be short of part the multiplying factor I will have  $V_p \exp(j\phi)$  divided by  $1 + j\omega C R$ .

So,  $s = j\omega$  that is all  $s$  is  $j\omega$  over that, so this times exponential  $j\omega t$ . So, what is  $V_c$  after all  $V_c$  is real part of  $V_p \exp(j\phi) \exp(j\omega t)$  by  $1 + j\omega C R$  like I said you have to be fluent with converting from rectangular to polar format 1 I will, so that here how it is useful, so this is the solution.

(Refer Slide Time: 15:14)

The image shows a handwritten derivation on a digital whiteboard. The derivation starts with the expression for the voltage  $V_c$  as the real part of a complex fraction:

$$V_c = \text{Re} \left[ \frac{V_p \exp(j\phi) \exp(j\omega t)}{1 + j\omega RC} \right]$$

Next, the denominator is converted to polar form:

$$\frac{1}{1 + j\omega RC} = \frac{1}{\sqrt{1 + (\omega RC)^2}} \exp(-j \tan^{-1}(\omega RC))$$

This is then substituted back into the expression for  $V_c$ , and the real part is taken:

$$\text{Re} \left[ \frac{V_p}{\sqrt{1 + (\omega RC)^2}} \exp(j(\omega t + \phi - \tan^{-1}(\omega RC))) \right]$$

The expression is then simplified to a cosine function:

$$\equiv \frac{V_p}{\sqrt{1 + (\omega RC)^2}} \cdot \cos(\omega t + \phi - \tan^{-1}(\omega RC))$$

The derivation also shows the addition of two complex numbers in rectangular form:

$$\begin{aligned} x_1 + jy_1 &+ A_1 \exp(j\theta_1) \\ x_2 + jy_2 &+ A_2 \exp(j\theta_2) \\ \hline x_1 + x_2 + j(y_1 + y_2) &+ A_1 A_2 \exp(j(\theta_1 + \theta_2)) \end{aligned}$$

So, first of all this rectangular form right, let us say you have complex number it is most convenient when you want to add them because the real parts add and the imaginary parts also add with each other to give you the final real part, so addition is very easy with the rectangular form. On the other hand the polar form makes it very easy to carry out multiplication. So, the product of these two products of  $A_1 A_2 \exp(j(\theta_1 + \theta_2))$ , so this is why you need to know both and go back and forth between them.

So, I have this part in the rectangular form I know that  $1 / (1 + j\omega RC)$  has an amplitude, which is  $1 / \sqrt{1 + (\omega RC)^2}$  and phase, which is  $-\tan^{-1}(\omega RC)$  because this is in the denominator. So, if I use that in here all the amplitudes get multiplied together after different complex numbers and all the phases get added together. So, this transfer to be real part of  $V_p / \sqrt{1 + (\omega RC)^2} \exp(j(\omega t + \phi - \tan^{-1}(\omega RC)))$ .

So, it will be  $\cos(\omega t + \phi - \tan^{-1}(\omega RC))$  and taking a real part of something like this, this is very easy we have a single complex exponential inside, which means that the real part of it is  $\cos$  of the same argument without this  $j$ . So, this is nothing but,  $V_p / \sqrt{1 + (\omega RC)^2} \cos(\omega t + \phi - \tan^{-1}(\omega RC))$ . So, again exactly the same answer as before as we should expect it is the same circuit with the same input, but this third method is most convenient. So, that why is used all the time.