

Basic Electrical Circuits
Dr Nagendra Krishnapura
Department of Electrical Engineering
Indian Institute of Technology Madras

Lecture – 139

We have spent a quit a bit time in first order circuits, but we also generalize some principles from there, which will be applicable to high order circuits. Now, everything that we set so far with that you can analyze any circuits with a single capacitor or a single inductor. And I say single capacitor or inductor, let us assume that you have done all the parallel series combinations possible with the source being null, with the source being null you will effectively get a single capacitor or single inductor; that is a first order circuit.

So, that, all of that you can analyze now with what we have. Is that okay? There will be one time constant that you can find by finding the Thevenin resistance across the terminals of the capacitor or the inductor. Now, what we have not done so far is to put both the inductors and capacitors together, so let us do that and see what happens.

(Refer Slide Time: 00:59)

Second order circuits; e.g: RLC

Diff. equation in terms of V_c

$$LC \frac{d^2 V_c}{dt^2} + RC \frac{dV_c}{dt} + V_c = V_s$$

Natural response: $V_s = 0$

$$LC \frac{d^2 V_c}{dt^2} + RC \frac{dV_c}{dt} + V_c = 0$$

$$V_c = V_0 \exp(\gamma t) \quad (LC \cdot p^2 + RC \cdot p + 1) V_0 \exp(\gamma t) = 0$$

Characteristic eq. of the D.E

So, far we have only resistors and inductors or resistors and capacitors, now we will have everything together. Now, we have some current in the loop, the way I have chosen the circuit is to put all three elements in series of course, not necessary we can have it in different ways and we have a single loop with a loop current and we have a number of variables V_R , V_L

and V_C . So, first of all please write down the differential equation in terms of V_C , please do that.

Student: I will also derive the differential equation; you can compare your answer to what I get.

You do get second order differential equation, which is...

Student: $L C$ times second derivative of V_C plus $R C$ times time derivative of V_C plus V_C equals V_S .

So, you get that and all you do is, KVL around this loop V_R plus V_L plus V_C equals V_S and then, express V_R and V_L in terms of V_C . This is V_R , C times $d v_c / d t$ is the current and that times R is the voltage across the resistor and this L times derivative of that is the voltage across the inductor. For that we can write the differential equation for the circuit in terms of V_R or V_L . What could be it in terms of V_R ? What would we get?

Student: Again please derive the differential equation in terms of V_R and compare it to what I get. You will get exactly the same terms on the left hand side, because the circuit is the same $L C$ times second derivative of V_R with respect to time plus $R C$, first derivative of V_R with respect to time plus V_R equals $R C$ times first derivative of V_S , the Source Voltage.

As usual you get the same homogeneous part of the question. So, only the right hand side that is changed and if you do it, if you try to V_L you will again get the exact same thing; that is the left part is the same, the differential equation and the right hand side will be different. So, what it means of course, is that the natural response will have the same form for any quantity in the circuit and you can also write it in terms of I , which is also very easy, I is simply V_R divided by R . So, you just divide this by R and you will get the differential equation in terms of y .

So, this is the differential equation governing the circuit and as usual, first we will find natural response or the solution to the homogeneous equation and what is that. What you have to do? Set V_S to 0, so we will be left with...

Student: $L C$ times second derivative of V_C with respect to time plus $R C$, first derivative of V_C with respect to time plus V_C equals 0.

What is the form of the response expected from this? Exponential, I mean that is the standard solution to any linear differential equation; that simply, because the derivative of an exponential is an exponential. So, you sum up any number of derivatives together, you expect that all of them will have some exponential as a function of time, so the only way I will cancel is by having all the coefficients in the appropriate values. So, if I do assume that V_C is something; that means p times t here and just for keeping dimensions correct I will use V node, but that will cancel out anywhere. So, what do I have? What is the first term?

Student: If I substitute this V_C in to the differential equation.

LC times p square plus RC times p plus 1 times V naught exponential p t equals 0 . The only way this is going to happen is, if that quadratic equation equals 0 . I think we have done things of this type, this is known as the characteristic equation of the differential equation. When we did it for the first order circuit, we did not do it directly like this. We manipulated the variables to get a homogeneous equation and from there we got the answers, but exactly the same procedure will work.

(Refer Slide Time: 06:50)

The image shows handwritten notes on a digital whiteboard. At the top, the differential equation for a first-order circuit is given as $RC \frac{dV_C}{dt} + V_C = 0$. A note indicates $p = -\frac{1}{RC}$ for a first-order circuit. Below this, the assumed solution $V_C = V_0 \exp(pt)$ is substituted into the differential equation, leading to the characteristic equation $(RC \cdot p + 1) \cdot V_0 \exp(pt) = 0$. The term $(RC \cdot p + 1)$ is highlighted in pink. Below this, the characteristic equation for a second-order circuit is shown as $(LC \cdot p^2 + RC \cdot p + 1) V_0 \exp(pt) = 0$, with $(LC \cdot p^2 + RC \cdot p + 1)$ highlighted in pink and labeled as the characteristic equation of the D.E. The roots of this equation are given as $p = \frac{-RC \pm \sqrt{(RC)^2 - 4LC}}{2LC} = -\frac{R}{2L} \pm \sqrt{\left(\frac{R}{2L}\right)^2 - \frac{1}{LC}}$. The date 207/207 is visible in the bottom right corner of the whiteboard.

Because, what was the differential equation in that case.

Student: RC times first derivative of V_C plus V_C equals 0 .

This was the homogeneous equation and if I assume V_C is V naught exponential p times t , I would get RC times p plus 1 V naught exponential p t equals 0 . So, values of p which satisfy

this whole thing equal 0 will satisfy the differential equation; obviously, p is minus 1 by R C. What are the dimensions of p? Frequency, exponential p t is the argument of the exponential should be dimensionless. So, p times t is dimensionless, p is frequency.

So, if you solve the characteristic equation you get possible frequencies of the exponential. So, similarly here you have a quadratic equation you will get two solutions and, what are the solutions, so this part has to be equal to 0. So, at two ails of p whatever.

Student: We get the standard solution to the quadratic equation, which is minus R C plus or minus square root of R C square minus four times L C divided by two times L C which can also be written as minus R by 2L plus minus square root of R by 2L whole square minus 1 by L C.

So, you can write it in either form, so there are two values of p that' is satisfy this, what is the mean for the natural response there are two modes two natural modes for the circuit. So, p 1 and p 2 and both are possible exponential p 1 t and exponential p 2 t and actual natural response will be some linear combination of the 2. Because, for the linear differential equation of two possible solution any linear combination as also a solution, so in general. So, let us say a one exponential p 1 t plus a 2 exponential p 2 t those are the solutions to this homogeneous differential equations and how do you find a 1 and a 2 initial condition.

(Refer Slide Time: 10:14)

Two possible solutions: p_1, p_2 $\exp(p_1 t)$ & $\exp(p_2 t)$ are possible solutions.

In general: solution (Natural response) = $A_1 \exp(p_1 t) + A_2 \exp(p_2 t)$

$$LC p^2 + RC p + 1 = 0$$

$$p_{1,2} = \frac{-RC \pm \sqrt{(RC)^2 - 4LC}}{2LC} = -\frac{R}{2L} \pm \sqrt{\left(\frac{R}{2L}\right)^2 - \frac{1}{LC}}$$

$p_{1,2}$: real & distinct: $(RC)^2 > 4LC \Rightarrow \frac{R^2}{C} > \frac{4}{L}$ $A_1 \exp(p_1 t) + A_2 \exp(p_2 t)$

There are some conditions that you have to further check, so now we have a coordinate

equations, so what are the possibilities for the roots. So, both p_1 and p_2 are real in which, case you simply get this two distinctive exponentials, so that is the solution in that case and you find a_1 and a_2 from initial conditions. And then, it is possible that p_1 and p_2 are identical and real and finally, p_1 and p_2 are complex conjugate each other.

Now, you can also have p_1 and p_2 to be complex conjugate each other. So, in p_1, p_2 real and distinct this is the natural response and when does this happen when will they real understand $R^2 C^2 > 4 L C$ or in other words $R^2 > 4 L / C$. So, in general they will be two explanations.

Student: Sir, in the natural response, now you we to considered to other cases as well when p_1 and p_2 are real and identical and when their complex conjugates of each other, we will first in another lesson look at a second order system as a scatted of two first order systems and come back to these issues, because that will help us understand the solutions even better.