

Basic Electrical Circuits
Dr Nagendra Krishnapura
Department of Electrical Engineering
Indian Institute of Technology Madras

Lecture - 142

We have taken a specific second order circuit and set of the differential equation and analyzed it. Now, we will look at the second order differential equation with normalized coefficients. So, that any other kind of circuit can also be easily analyzed.

(Refer Slide Time: 00:16)

Diff. equation: $LC \cdot \frac{d^2V_c}{dt^2} + RC \frac{dV_c}{dt} + V_c = V_s$ p_1, p_2

$\omega_n = \frac{1}{\sqrt{LC}}$

ω_n : natural frequency

ζ : zeta: damping factor

Q : quality factor

$Q = \frac{1}{2\zeta}$; $\zeta = \frac{1}{2Q}$

$\frac{d^2V_c}{dt^2} + \frac{R}{L} \frac{dV_c}{dt} + \frac{V_c}{LC} = \frac{V_s}{LC}$

$\frac{d^2V_c}{dt^2} + 2\zeta \omega_n \frac{dV_c}{dt} + \omega_n^2 V_c = \omega_n^2 V_s$

$\frac{d^2V_c}{dt^2} + \frac{\omega_n}{Q} \frac{dV_c}{dt} + \omega_n^2 V_c = \omega_n^2 V_s$

So, we have the differential equation as this I will write the homogeneous equation like this, this can also of course, be written as I do this just to normalized things in the way it is normally done. I think this part you probably already are familiar with from the spring mass system. All I did was to divide everything by LC that is all and I could of course, write it for the case with the input Vs by LC. Now, this can be written as d square Vc by dt square plus 2 zeta omega n d Vc by dt plus omega n square Vc equals omega n square Vs.

I mean I just put out all these things this omega n square is 1 by LC it has dimensions of frequency square 1 by LC has dimensions of frequency squared. So, this omega n and omega n is called the natural frequency and this R by L you know that it has dimensions of frequency and that happens to be defined as this two times this zeta, which is the damping factor damping factor times omega n first derivative of Vc and so on.

So, this is one possible way of defining the constants and sometimes you do it slightly

differently $d^2 V_c / dt^2 + \omega_n / Q dV_c / dt + \omega_n^2 V_c = \omega_n^2 V_s$. So, what this kind of normalization let us do is first of all do you have written for an LC circuit, but if you normalize the constants like this, if you define the constants like this it applies to any second order system that is why we do it that way that is all.

In this case this Q is known as the quality factor and; obviously, $Q = 1 / (2 \zeta)$ or $\zeta = 1 / (2Q)$ is fine. Now, from the characteristic polynomial we can find the values of p_1 and p_2 and exponential $p_1 t$ and exponential $p_2 t$ will be in general the natural responses. Now, we can classify the types of natural responses, we have already found those types, there are three types one where you have a combination two exponentials, one you have a single exponential multiplied by $A_1 + A_2 t$ and the third one where you have an exponentially modulated sinusoid that is you have a sinusoid $\cos \omega_n t + \phi$ multiplied by exponential something.

So, these constants the natural frequency ω_n and the damping factor ζ or the natural frequency ω_n and the quality factor Q are some properties of the system, just like for a first order system we say something is the time constant what is the time constant, it is what appears in the exponential. So, similarly here this ω_n is some constant, it is a second order differential equations. So, we have two constants we can either leave the constants as they are in terms of component values or in a more general way we can define this natural frequency ω_n and the damping factor.

We could also instead of this just use the values of p we could simply use p_1 and p_2 . So, this is a little more general way of associating with any other second order system that is all. So, there is nothing special here all I did was to redefine variables in this page if you look at it all I have done is that.

(Refer Slide Time: 04:52)

Characteristic polynomial: $LC \cdot p^2 + RC \cdot p + 1 = 0$

$$p_{1,2} = \frac{-R}{2L} \pm \sqrt{\left(\frac{R}{2L}\right)^2 - \frac{1}{LC}}$$

$$p^2 + 2\zeta \cdot \omega_n p + \omega_n^2 = 0$$

$$p^2 + \frac{\omega_n}{Q} p + \omega_n^2 = 0$$

$$Q = \frac{1}{R} \sqrt{\frac{L}{C}} = \frac{1}{2\zeta} \Rightarrow \zeta = \frac{R}{2} \sqrt{\frac{C}{L}}$$

$$p_{1,2} = \omega_n \left[-\frac{1}{2Q} \pm \sqrt{\left(\frac{1}{2Q}\right)^2 - 1} \right]$$

Real & distinct	$Q < 1/2, \zeta > 1$	$A_1 \exp(p_1 t) + A_2 \exp(p_2 t)$
Real, repeated	$Q = 1/2, \zeta = 1$	$(A_1 + A_2 t) \exp(p_1 t)$
Complex conj	$Q > 1/2, \zeta < 1$	$(2A_1) \exp(\sigma t) \cos(\omega_d t + \phi)$

Now, what were the conditions the characteristic polynomial was LC times p squared plus RC times p plus 1 equals 0 which alternately could also be written as 2 times ζ times ω_n times p plus ω_n squared is 0 . I divide by LC that is all and we get we know that $p_{1,2}$ what are they, what was the values $\frac{-R}{2L}$ plus or minus square root of $\left(\frac{R}{2L}\right)^2 - \frac{1}{LC}$ in terms of this new constant what is that ω_n by $2Q$ that is one way of doing that plus or minus what do you have ω_n by $2Q$ square minus ω_n square.

So, now, you can kind of take this ω_n outside plus minus square root of or if you express it in terms of damping factor, what is it I mean you can see the convenience already this ω_n which is the frequency that comes out and then whether the roots are real or repeated or complex conjugate or determined only by this damping factor ζ or the quality factor Q .

So, we already saw that this real and distinct roots when does this happen, when $\frac{R}{2L}$ whole squared is more than $\frac{1}{LC}$ like by the way what is the expression for this quality factor Q in terms of LC and so on. In this case it is $\frac{1}{R} \sqrt{\frac{L}{C}}$ quality factor and the damping factor is $\frac{R}{2} \sqrt{\frac{C}{L}}$. So, you can see that if the value of R becomes larger and larger for the same L and C you will have higher damping factor or lower quality factor.

Now, real and distinct roots this corresponds to what in terms of quality factor what is that when do you have real and distinct roots in terms of quality factor Q less than half or

equivalently the damping factor greater than 1 that is why it is called the damping factor and then you have real and repeated roots if the quality factor is equal to half or damping factor exactly equals 1 and finally, the complex conjugate roots when Q is more than half and the damping factor is less than 1.


So, this damping factor and quality factor are normally used constants. That is why I defined both of them. So, in this case you will get a response of the type $A_1 e^{p_1 t}$ plus $A_2 e^{p_2 t}$, where p_1 and p_2 can also be expressed in terms of ω_n and Q or zeta like this. So, these are the values of p_1 and p_2 and in this case you will have $A_1 + A_2 t e^{p_1 t}$ I will just call that P_1 both roots are p_1 and in this we will have we can call it $2 A_{naught}$ or is a single constant A_{naught} it does not matter it is the point is that there is some constant there $e^{p_r t} \cos p_i t + \phi$.

So, you have to find this constant I mean I could as well call this some A_1 or something ((Refer Time: 10:02)) two it does not have any significance, you have to find the multiplying factor for this whole thing that is all. So, now, what is the value of p_r minus zeta ω_n many ways to express it minus R by $2L$ this p_r if this part is negative the square root is purely imaginary and then this is the real part and this p_r is negative that is the point.

So, what happens what is the kind of response you have, the exponential will decay. So, it will be a sinusoid, but whose amplitude will go on decaying. And then if you examine this p_1 . What is the value of p_1 ? If zeta equals 1 minus zeta ω_n it will be some negative number also I mean it is the same minus R by $2L$. So, then also the responsible eventually will decay and finally, for this real and distinct case you can evaluate that both roots will be negative.

So, when you have this negative sign both terms are negative; obviously, the result is negative, when you have this positive sign you have some negative number and another positive number which is smaller than that, so you will have both negative roots. So, this circuit is also always stable. So, in this case also the natural response raised on with time let us now examine the roll of the damping factor in the natural response of the second order system.

(Refer Slide Time: 11:32)

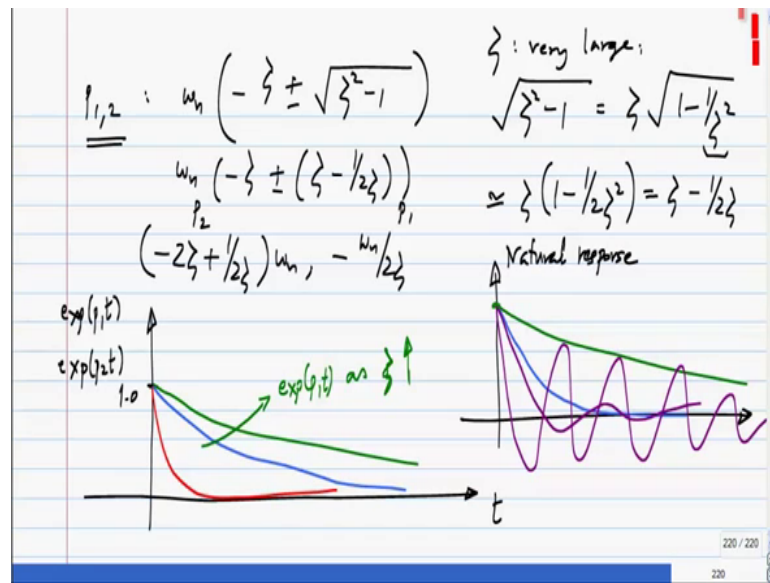

The roots will be $\omega_n \left(-\zeta \pm \sqrt{\zeta^2 - 1} \right)$. Now, if ζ is very large then what happens is that this square root of $\zeta^2 - 1$ can be written as $\zeta \sqrt{1 - \frac{1}{\zeta^2}}$, where this $\frac{1}{\zeta^2}$ is a small number. So, this is approximately $\zeta \left(1 - \frac{1}{2\zeta^2} \right)$, you know this approximation square root of $1 + x$ is $1 + \frac{x}{2}$ which is $\zeta - \frac{1}{2\zeta}$. So, these roots can be approximated as $\omega_n \left(-\zeta \pm \zeta - \frac{1}{2\zeta} \right)$. The two values will be basically when it is minus minus $2\zeta \omega_n + \frac{\omega_n}{2\zeta}$ and $-\frac{\omega_n}{2\zeta}$. I will set ζ is very large. So, that part is small what is the other root minus ω_n by 2ζ .

So, these are the two roots and let say on the same axis I plot let us say I call this V_2 and this is $V_1 \exp(p_1 t)$ and $\exp(p_2 t)$ what will I look like relatively let say I start both of them with unity exponential $p_1 t$ and exponential $p_2 t$ what will they look like, it will up to start from 1 and decay to 0, but how will that do that which one will go to 0 or pick up p_2 . So, exponential $p_2 t$ would do that and exponential $p_1 t$ would do that.

For a given ω_n the larger of the value of ζ this exponential $p_1 t$ gets keeps getting slower and slower as ζ increases. So, we will have two exponentials in the natural response one of them will die out very quickly, other one will take a very long time to die out this is fine. So, what happens is, so let say you start with I mean you look at the natural response and for large values of ζ it will be dominated by this exponential $p_1 t$. So, it will be very, very slow it will almost like a single exponential that is very slow as the damping factor reduces and when you reach critical damping you get some nice response like that.

Now, what happens when zeta becomes very small? So, what will happen is that it will go to go out quickly like that, but then it will ring back and forth. And then, if zeta becomes very, very small what happens is that it becomes just as bad as the other case when zeta is very large. So, it will go rapidly, but then it will start doing this, because what is the real part of p_1 and p_2 when they are complex conjugates by ω and ζ .

So, when zeta becomes very small; that means, that $\zeta\omega$ in this very small number and that is the exponential that is modulating the sinusoid. So, that exponential is dying out very, very slowly. So, if you are looking for a clean settling critically damp response the one to look for, in many cases you look for the system to have a critically damp response of course, it depends on what system it is, but that is the reason.

So, for a given ω a very large value of zeta means that it will not ring like this, but it will be ((Refer Time: 16:14)) it will settle very slowly and for a very small value of zeta it will thought of changing very rapidly, but then this sinusoidal part will stay for long time. On the other hand if you have critically damp stuff it just goes down and then settles cleanly. So, it gives you short of the cleanest settling, so if you look for damping factors which are around the critically damped value in many cases.