

Basic Electrical Circuits
Dr Nagendra Krishnapura
Department of Electrical Engineering
Indian Institute of Technology Madras

Lecture - 44
Structure of the Conductance Matrix

(Refer Slide Time: 00:28)

Nodal analysis equations

node 1

$$[G] \underline{V} = \underline{I}$$

a_{ij} : i^{th} row and j^{th} column

diagonal elements a_{ii} : Total conductance at node i

$\underline{V} = [G]$

We have looked at how to set up nodal analysis equations. We write down Kirchhoff current law equations at $N - 1$ nodes of the circuit; and in each term of the equation, we use voltages which refer to the reference node of the circuit, and element relationships from the resistors in the circuit. And also we saw how to put it in matrix form. For this particular circuit, we have got the nodal analysis equation to be $G_1 V_1 + G_{12} V_2 - G_{12} V_3 = I_1$, $-G_{12} V_1 + (G_{12} + G_{23}) V_2 - G_{23} V_3 = 0$, and $-G_{13} V_1 - G_{23} V_2 + (G_{13} + G_{23}) V_3 = I_3$. And of course, this can be written as the conductance matrix G times the vector of node voltages V equals the vector of independence sources I . So, this is the nodal analysis equations setup and of course, we can solve for V by using matrix inversion with which we are familiar $G^{-1} I$.

Basically, this is saying that we have three simultaneous linear equations, and three variable V_1, V_2, V_3 and we solve for it. And we solve for it, we are basically doing matrix inversion. Now we will briefly look at techniques and matrix inversion later that is only for hand analysis, things that you all ready know. The important part a setting up

of the equations, there are many techniques for matrix inversion and especially for a large circuits lot of work has been done to figure out efficient ways of inverting matrix on the computer. So, the important part for us now is to understand the structure of the G matrix and be able to set of the equation for circuits of any size. Of course, for circuits of small sizes such as once with may be 3 or 4 nodes, you should be able to invert the matrix by hand and solve the circuit.

Let us look at the structure of this conductance matrix. First let us focus on the diagonal elements of the matrix. What do you see let me remind you that the first row is node 1 and the first column here corresponds to whatever is multiplying V_1 . If you look at the element a_{11} of the matrix where use the standard notation a_{ij} corresponds to i th row and j th column, we have $G_{11} + G_{12}$. Similarly if we look at a_{22} , that is the second row and second column, we have $G_{12} + G_{23} + G_{22}$, and finally, a_{33} is $G_{23} + G_{32} + G_{33}$. You easily notice that the diagonal elements are basically some of conductance connected to particular nodes. The first row correspondence to node 1 and the diagonal element in that element a_{11} is basically the total conductance connected to node 1, so this is node 1, we have 2 resistance R_{11} and R_{12} connected to it. So, the total conductance would be the conductance of this G_{11} plus the conductance of that G_{12} .

Similarly, if you look at node 2, there are resistors connected G_{12} , G_{23} and G_{22} . So, all of them are summed up and appear as diagonal element in the second row. And finally, node 3 has G_{23} and G_{32} connected to it and the sum of that appear all there. So, the diagonal elements, if you look at a_{ii} that is diagonal elements in the i th row then this has the total conductance at node i so that should be pretty obvious. Now if you look at the half diagonal elements this is element a_{12} , so if you look at element a_{12} what is that we have node 1 over here and node 2 over there, and we have a resistance R_{12} connected between them the conductance of that is G_{12} .

So, basically the element a_{12} of the matrix is nothing but the negative of the conductance connected between node 1 and node 2. So, you can go through the remaining entrees of the matrix and easily verify that is a case. For instance the element a_{23} is the negative of conductance connected between nodes 2 and 3. And there is a reason for it which is pretty obvious also; when you write Kirchhoff current law equation here and look at the term for the current through this resistance R_{23} , what we have we are writing currents and flowing away from this node. So, current flowing away from

this node 2 or 2 3 would be V_2 minus V_3 times G_{23} . So, obviously we will have V_2 times V_2 that appears in the diagonal, and then minus V_3 times V_2 and this happens for every node.

So, if you look at any half diagonal term, it will have basically negative of the conductance connected to that node and that is exactly what we have. And also another thing that you observe is that matrix is symmetric; clearly we have minus G_{12} here and minus G_{12} , there minus G_{23} there and minus G_{23} , and similarly zero and zero this zero is because there is no conductance directly connected between node 1 and node three. So, there is zero conductance connected between them. Now it is also obvious why do is matrix because this is element a_{12} , which should have negative of conductance between nodes 1 and 2, and this is element a_{21} which should have the negative of conductance between nodes 2 and 1 which is the exactly the same as the conductance between nodes 1 and 2. So, the matrix is symmetric as well.

(Refer Slide Time: 09:13)

$(N-1) \times (N-1)$ for an N node circuit
Conductance matrix: Resistances (conductances) and current sources
 * Diagonal terms a_{ii} : Sum of conductances connected to node i
 * Symmetric: $a_{ij} = a_{ji}$: negative of conductance connected between nodes i and j .

So to just summarize the structure of the conductance matrix, firstly, we will have the diagonal terms a_{ii} to be the sum of conductance's connected to node i , and it is quite clear why this happens, because again we are summing all of the currents flowing out of a let say node 2, now there are three currents here through G_{12} through G_{23} and through G_{23} . Now all of them will have V_2 in them the current trough G_{12} is V_2 minus V_1 times V_1 2; currents V_2 2 is V_2 minus zero times V_2 2 and current through G_{23} is V_2 minus V_3 G_{23} . So, all of them will have V_2 . So, the sum of all conductance to connected to a node will appear in the diagonal. And of course, the

matrix itself is symmetric and the terms a_{ij} or a_{ji} which will be equal to each other corresponds to the negative of conductance connected between nodes i and j .

So, this is the structure of the conductance matrix. Let me also add that for an N node circuit, the conductance matrix will be N minus 1 times N minus 1, it is a square matrix. And also these properties, we have written, they are for the specific kind of circuit we have been considering, which consist of only resistances or conductance, and current sources. As we add more elements, we see that some of these properties may be modified. So, we will look at those things later. This structure will be obvious when we consider examples of what happens when we make some changes to the circuit, so that is the structure conductance matrix for a circuit consisting only resistors and current sources. This will become clearer when I take an example circuit and then modify into certain ways and see how the conductance matrix changes.