

Basic Electrical Circuits
Dr Nagendra Krishnapura
Department of Electrical Engineering
Indian Institute of Technology Madras

Lecture - 61
Mesh Analysis with Current Controlled Voltage Sources

(Refer Slide Time: 00:01)

$i_x = i_1 - i_3$

Mesh analysis for circuits with CCVS

mesh #1: $i_1(R_{11} + R_{12} + R_{13}) - i_2 R_{12} - i_3 R_{13} = V_1$

mesh #2: $i_1(R_{12}) + i_2(R_{12} + R_{22} + R_{23}) - i_3 R_{23} = 0$
 $+ R_m(i_1 - i_3)$

mesh #3: $i_1(-R_{12} + R_m) + i_2(R_{12} + R_{22} + R_{23}) - i_3(R_{23} + R_m) = 0$

mesh #3: $-i_1 R_{13} - i_2 R_{23} + i_3(R_{23} + R_{33}) = 0$

Now, we will see how to carry out mesh analysis for circuits which have a current controlled voltage source. What I have done is I have taken the same circuit as before, but replace the second voltage source by a current controlled voltage source - R_m times I_x , and I_x is this current. Now clearly this control voltage source is in the second mesh and it is going to effect the equation only for the second mesh. So, for the first mesh equation is the same as what we had earlier that is I_1 times R_{11} plus R_{12} plus R_{13} minus I_2 times R_{12} minus I_3 times R_{13} equal V_1 . Now for the second mesh, the independent voltage source in the second mesh is zero, so in the right hand side will just I have a zero. The left hand side, if I ignore the control source, I will have I_2 times R_{12} plus R_{22} plus R_{23} minus I_3 times R_{23} , these are the contributions from the resistors, and I will also have I_1 times minus R_{12} . So, these are the contribution from the resistors in the second mesh.

So, this is what I have but this is not complete because I have to also additionally take this voltage drop which is R_m times I_x . So, on the lefty hand side, I will have plus R_m times I_x . Now I_x I do not want use another variable here, I know that this I_x here in

this branch equals I_1 minus I_3 . So, instead of I_x , we have I_x to be I_1 minus I_3 , so we will have plus R_m times I_1 minus I_3 . So, if I rearrange it, while grouping the current variables I have I_1 minus R_{12} plus R_m plus I_2 times R_{12} plus R_{22} plus R_{23} minus I_3 times R_{23} plus R_m . So, this is what I will have, and you will see that this R_m because I_x is here, and I_x equal I_1 minus I_3 , R_m adds to the coefficient of I_1 and subtraction from the coefficient of I_3 . And for mesh number three nothing has changed I just have I_1 R_{13} minus I_2 R_{23} plus I_3 times R_{13} plus R_{23} plus R_{33} to be equal to 0.

(Refer Slide Time: 03:59)

Mesh analysis with CCVS

$$\begin{bmatrix} R_1 + R_{12} + R_{13} & -R_{12} & -R_{13} \\ -R_{12} + R_m & R_{12} + R_{22} + R_{23} & -R_{23} - R_m \\ -R_{13} & -R_{23} & R_{13} + R_{23} + R_{33} \end{bmatrix} \begin{bmatrix} i_1 \\ i_2 \\ i_3 \end{bmatrix} = \begin{bmatrix} V_1 \\ 0 \\ b \end{bmatrix}$$

~ Nodal analysis with CCS

So, if I put this in matrix form, I will have R_{11} plus R_{12} plus R_{13} minus R_{12} minus R_{13} . Here I will have minus R_{12} plus R_m , which is the contribution of the current controlled voltage source, then R_{12} plus R_{22} plus R_{23} and minus R_{23} minus R_m ; and the third one is the same as before minus R_{13} minus R_{23} R_{13} plus R_{23} plus R_{33} i_1 i_2 and i_3 , and in this whole thing equals V_1 0 0 . So, these are the mesh analysis equations, and this is analogous to the case of nodal analysis with a voltage controlled current source. What we have here is mesh analysis with a current controlled voltage source and that is analogous to nodal analysis with the voltage controlled voltage source. You can write the three node equations now the matrix becomes asymmetric, as you can see this element is not equal to that element.