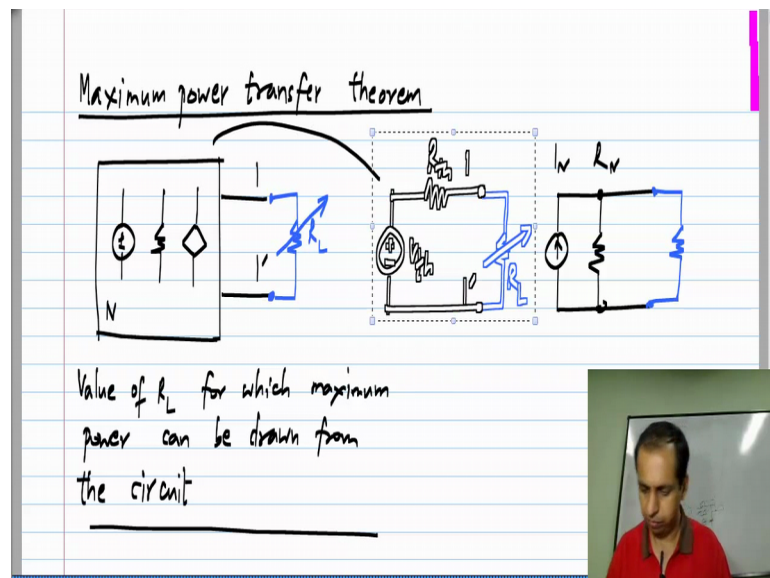


Basic Electrical Circuits
Dr Nagendra Krishnapura
Department of Electrical Engineering
Indian Institute of Technology Madras

Lecture – 77

In this lesson, we will discuss the maximum power transfer theorem, it is a theorem of great practical importance. If you have a circuit with a number of independent sources and other linear components, such as resistors and control sources and you have access to it is terminals, the question is how do you extract the maximum power by connecting a resistor, a load between these two terminals. So, what we will work out is the condition for maximizing the power that can be drawn from these terminals.

(Refer Slide Time: 00:36)



It is known as the maximum power transfer theorem; I have a network N with independent sources, linear resistors and linear control sources, self content. So, all the controlling quantities are within the same circuit N and we have access to two of it is terminals 1 1 prime. We can connect a resistance R_L between 1 and 1 prime and there all out vary R_L and we are required to find out at what value of R_L we can draw the maximum power from the circuit; that is, at what value of R_L will maximum power be dissipated in R_L and how much that power is.

Now, we know that every network, every circuit for which two terminals are accessible can be modeled by either the Thevenin equivalent, a voltage source V_{th} in series with resistance R_{th} or the Norton equivalent, a current source I_N in parallel with a

resistance R_N . So, we will use these models, we do not want to deal with the specifics of the circuit, but we know that all these circuits can be reduced to this model or that model. So, we will consider one of these models to find the condition for maximum power transfer, we can use either one, the answer will be exactly the same with either case.

So, now if you have a voltage source V_{th} in series with R_{th} , this part is fixed anyway, because what we are allowed to vary is the load R_L . So, as R_L is varied, when does it draw the maximum power; that is what we want to find.

(Refer Slide Time: 03:23)

$$P_L = V_{th}^2 \cdot \frac{R_L}{(R_L + R_{th})^2}$$

$$\frac{dP_L}{dR_L} = V_{th}^2 \cdot \frac{(R_L + R_{th})^2 - R_L \cdot 2 \cdot (R_L + R_{th})}{(R_L + R_{th})^4}$$

$$= V_{th}^2 \cdot \frac{(R_L + R_{th})(R_{th} - R_L)}{(R_L + R_{th})^4}$$
 Zero when $R_L = R_{th}$


Now, what is the power dissipated in R_L ? P_L will be equal to the voltage across R_L times the current through R_L . The voltage across R_L from voltage divider expression is V_{th} times R_L by R_L plus R_{th} , the current through R_L we have V_{th} across R_{th} plus R_L , so it will be just V_{th} by R_L plus R_{th} . The power P_L which is the product of the two will be $V_{th}^2 R_L$ by R_L plus R_{th} square. Now of course, to maximize the function we know that we can differentiate the function and set it to 0; at least that will find the extremes of the function, whether it is maximum or minimum and by finding the second derivative, you can figure out whether it is maximum or minimum.

Now, by differentiating this with respect to R_L which is our variable here, which is what we are allowed to vary, we have V_{th}^2 which is the constant as far as we are concerned and the denominator will be square. We have denominator times the derivative of the numerator, which turns out to be R_L plus R_{th} square times the derivative of R_L which is 1 minus the numerator R_L times the derivative of the denominator, which is 2

times R_L plus R_{th} .

So, this whole thing turns out to be V_{th}^2 times R_L plus R_{th} , R_{th} minus R_L and here we have R_L plus R_{th} to the power of 4. Now, it is very easy to see that, this goes to zero when R_L equals R_{th} and R_L equals R_{th} the derivative goes to zero. So, that is fine, the extreme has occurred and it turns out that is the maximum.

(Refer Slide Time: 06:15)

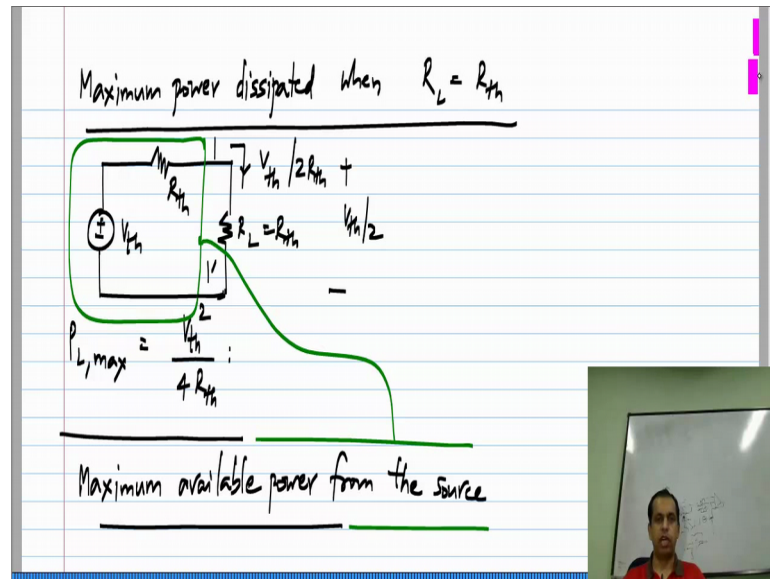

What does it say, if the load resistance equals the Thevenin's resistance seen across the two terminals 1 1 prime, then it draws the maximum amount of power, this condition is known as matching of the load to the source. The source has some internal resistance which is R_{th} ; that is the equivalent resistance, terminal resistance of the source and if you have a load which is the exactly the same value, then you draw the maximum power. Now, how much is that the power?

So, if this is the case, the current here will be V_{th} by $2R_{th}$ and the voltage across this will be just V_{th} by 2. So, the maximum power that can ever be dissipated in R_L as you vary R_L for a given source is the product of this voltage and current which is V_{th}^2 square by $4R_{th}$. Note is that, this is the property of just the circuit, the load when it is arranged to draw maximum power, its resistance will be equal to the source resistance.

So, the maximum power that is dissipated in the load will be equal to V_{th}^2 square by $4R_{th}$ and this is known as the maximum available power from the source. By source I mean, this part the combination of V_{th} and R_{th} which could be by itself like that, that is you could have a voltage source and series with the resistance or it could be a

representation of a very complicated circuit. We know that any complicated circuit can be represented in this form, a voltage source and series with the resistance.

So, whatever it is the maximum available power from the source is this much; that is, if you do all you can to maximize the amount of power drawn from the source, this is what you will be able to draw. So, in summary if you have a source which is represented by a voltage source V_{th} in series with the resistance R_{th} , then to draw maximum power from that you should connect a load resistance which is exactly equal to R_{th} ; that is, you should match the load to the source and the amount of power you can draw which will be the maximum available power from the source is V_{th}^2 by $4 R_{th}$.

(Refer Slide Time: 09:29)

Maximum power transfer theorem
For a given source (V_{th} , R_{th}), maximum power can be drawn from it when the load resistance equals the source resistance ($R_L = R_{th}$) & the max. power drawn (available power of the source) = $\frac{V_{th}^2}{4R_{th}} = P_{av}$.

So, here is the statement of the maximum power transfer theorem. For a given source, when I say given source the Thevenin voltage and the Thevenin resistance are given, maximum power can be drawn from it when the load resistance equals the Thevenin resistance of the source. I will call it the source resistance R_L equals R_{th} and the maximum power drawn, which is defined to be the available power of the source equals V_{th}^2 by $4 R_{th}$, this is the available power.

Now, I made some implicit assumptions here, I assume that R_{th} was positive and R_L is also positive; that is this is the case with many sources such as antenna. An antenna can be represented as a voltage source and series with some resistance, which constitutes the impedance of the antenna and then, the load it is always dissipative, so it also is a positive resistor. So, under these conditions when you make R_L equals R_{th} , you draw

maximum power.

(Refer Slide Time: 11:50)

$$P_L = V_{th}^2 \cdot \frac{R_L}{(R_L + R_{th})^2} = \frac{V_{th}^2}{R_{th}} \cdot \frac{R_{th} R_L}{(R_{th} + R_L)^2} = \frac{V_{th}^2}{R_{th}} \left[\frac{\sqrt{R_{th} R_L}}{R_{th} + R_L} \right]^2$$

$$= \frac{V_{th}^2}{R_{th}} \frac{1}{\left(\sqrt{\frac{R_{th}}{R_L}} + \sqrt{\frac{R_L}{R_{th}}} \right)^2}$$

Maximum P_L (minimum denominator)
 when $\sqrt{\frac{R_L}{R_{th}}} = 1$, $R_L = R_{th}$

$\left(x + \frac{1}{x} \right)^2$
 minimum when $x = 1$

This can also be delivered in a slightly different way, the expression for the power was V_{th}^2 by R_L plus R_{th} square times R_L which can be rewritten as V_{th}^2 by $R_{th} R_L$ by $R_{th} + R_L$ square and I will further rewrite this as V_{th}^2 by R_{th} times square root of $R_{th} R_L$ by $R_{th} + R_L$ this whole thing square. And finally, taking the square root term in to the denominator we will get V_{th}^2 by R_{th} 1 by square root R_{th} by R_L was square root R_L by R_{th} square.


Now, if you observe the denominator that is this one it is of the form x plus 1 by x square, now this form x plus 1 by x may be familiar to you. Now, as x increases the first one increases and the second one decreases and if you try to minimize the value of this, you will find that the minimum will occur when x exactly equals 1 . So, this has a minimum when x equals 1 , when x tends to 0 this one goes towards to infinity, when x tends to infinity this one goes towards infinity in the middle some were it will reach minimum and it turns out that it will be 1×1 equals 1 , you can work this out for yourself.

Now, if you see the denominator of this expression it is of this form x plus 1 by x squared. Now, to maximize this function the power in the load we have to minimize the denominator remember R_L is only in the denominator, now were else in the expression. So, we have to minimize the denominator and that will be minimum when x equals 1 that is each of these terms equals 1 , you can think of one of them as x and other one is 1 by x .

In other words, in the maximum of the L which occurs when the denominator is at, it is

minimum when square root R_L by R_{th} as 1 or R_L equals R_{th} . So, it is another way of deriving the same result.

(Refer Slide Time: 15:27)

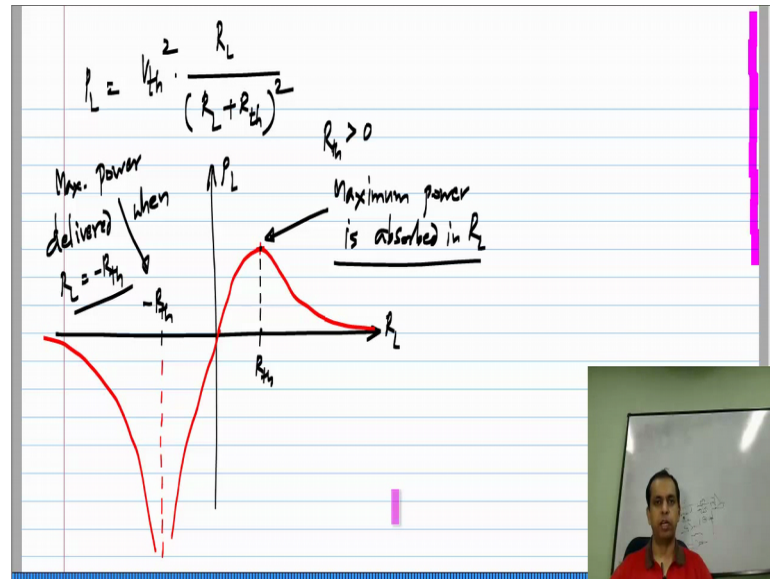

Now, let us explore this a little bit further this expression P_L being V_{th}^2 times R_L by R_L plus R_{th} squared you plot P_L of the function R_L . This is what you will see, if R_{th} is positive and R_L is restricted to be positive, then this function will be maximum when R_L equals R_{th} and then for both R_L equal to 0 and R_L equal to infinity the powers of all to 0 for R_L equal to 0 the load is a short circuit there can be no voltage across it and it does not draw any power, it does not dissipate any power.

Similarly, when R_L equals infinity it is an open circuit that can be no current through it and again there is no power through R_L . Now, if you allowed R_L to be negative what happens is that when R_L equals minus R_{th} you have a short circuit across the voltage source, the series combination gives you 0 resistance. So, that gives you the maximum possible current that is infinite current through R_L and in fact R_L will be delivering power instead of observing power.


The power actually goes to infinity when R_L equals minus R_{th} when it becomes more negative than minus R_{th} it again comes back to 0. So, here I assume that R_{th} is more than 0 and then this will be even maximum power is observed in R_L . If you say maximum power observed or delivered by R_L , the maximum power of the delivered when R_L equals minus R_{th} , but of course, this not a very use full result because this means that R_L itself is delivering power and to R_{th} for that R_L cannot be physical

resistor, but equivalent of some complicated circuits with sources inside and so on.

So, this is not a very useful result, but I just wanted to highlight that it is possible to have infinite power also, but then it will be infinite power being delivered by R_L , when R_L exactly equals minus R_{th} , the current in the loop goes to infinity and you have infinite power as well of the result of real significance is this when R_L equals R_{th} and you have the maximum power observed and example of this happens when you have an antenna, antenna can be represented by as a voltage source and series with resistance many standers antennas have a 50 ohm internal resistance.

So, you have a voltage source in series with the 50 ohms resistance and to draw maximum power form that your circuit must appear like a 50 ohm resistance, again even this load resistance is a representation of the input of your circuit it may or not be a physical resistance, it is a physical resistance power will be dissipated unit, if it is the equivalent of something power will go elsewhere, but to draw the maximum power from antenna which has a 50 ohm internal resistance your circuits should also present 50 ohm resistance and those of you will go on to study R F circuit later you find that a lot of effort is expended on by in trying to make the input of the circuit look like 50 ohms.

(Refer Slide Time: 19:42)

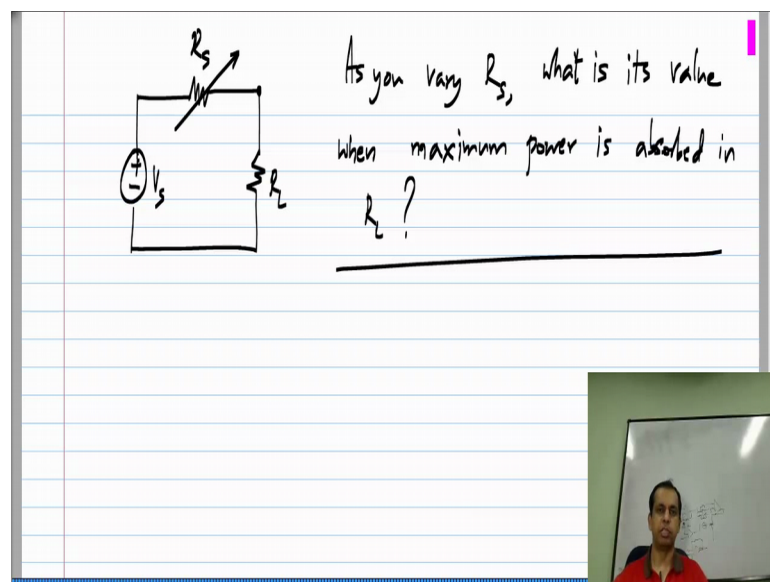

As the very last think I just want to touch up on something I won't discuss is in detail this scenario is sometimes confuse with the scenario that we all ready discussed that is let say we have a source V_s and it is source resistance R_s and you connect a load to it, exactly the same situation is before I simply change the symbols around that is all. Now, let us

say that we vary R_s not R_L as you vary R_s , what is its value, when maximum power is observed in R_L I won't work this out you can do it yourself and you can do it by differentiation or by thinking about it in any other way. Of course, you can for now assume that all resistances are positive they are non negative, think about it answer is very simple, but do not confuse this situation with the other one where varying R_L and trying to find when the maximum power is observed in R_L .