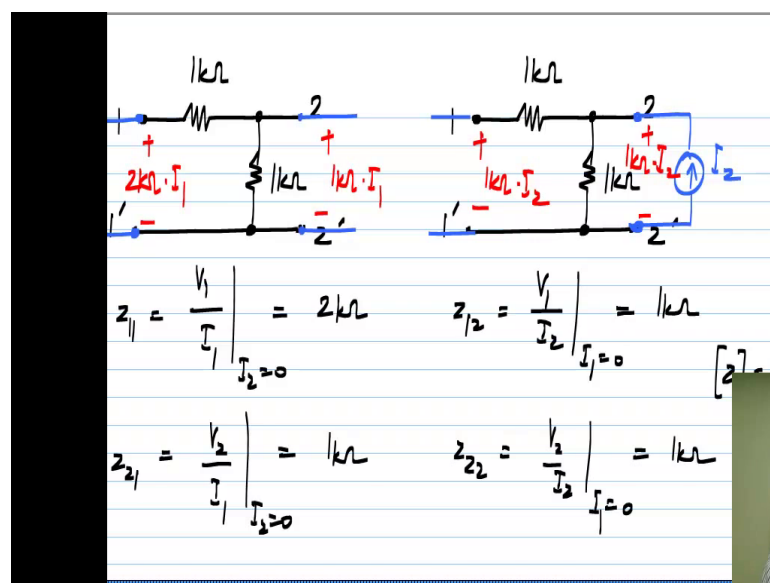


Basic Electrical Circuits
Dr Nagendra Krishnapura
Department of Electrical Engineering
Indian Institute of Technology Madras

Lecture – 84

Now I will take an example circuit and calculate its z parameters. I will take the same circuit that I took for the y parameter example, so that you can relate different parameter sets for the same circuit.

(Refer Slide Time: 00:17)




So, this is the circuit I took and I have two cases for measurement, one in which port 2 is left open circuited and a current source is connected to port 1 and in the other case, where port 1 is left open circuited and a current source is connected to port 2, so extremely simple circuit, very easy to analyze. So, I_1 flows through these two resistors, so the voltage here across port 1 is the series combination of these two resistors 2 kilo ohms times I_1 , whereas the voltage across port 2 is I_1 times this resistor 1 kilo ohm.

In this circuit, no current flows through this 1 kilo ohm, because it is in series with an open circuit. So, the voltage drop across this is also zero, all of these I_2 flows into 1 kilo ohm, giving you a port 2 voltage of 1 kilo ohm times I_2 and the same voltage appears here and that is 1 kilo ohm times I_2 . So, from the first circuit in which we have port 2 open circuited will get z_{11} , which is V_1 by I_1 with port 2 open circuited I_2 equal to 0 to be 2 kilo ohms and we also get z_{21} , which is V_2 by I_1 with port 2 open circuited to be equal to 1 kilo ohm.

So, z_{11} is nothing but, the resistance looking into port 1 with port 2 open circuited and if you look into port 1, you will see the combination of these two resistors in series which gives you a 2 kilo ohm resistance. Or let us go to the other circuit and from this we will get z_{12} , which is V_1 by I_2 with port 1 open circuited which gives you 1 kilo ohm and z_{22} , which is V_2 by I_2 with port 1 open circuited, which is also 1 kilo ohm.

So, these are the four z parameters and z_{22} here is nothing but, the resistance looking into port 2 with port 1 open circuited. If you look into port 2, you will see this 1 kilo ohm and this 1 kilo ohm which is hanging, so it does not contribute anything. So, the looking in resistance into port 2 is just 1 kilo ohm and that is what we see. So, the z parameter set of this particular circuit is 2 kilo ohm, 1 kilo ohm, 1 kilo ohm and 1 kilo ohm and you can verify for yourselves, that this z matrix is the inverse of the y matrix which you derived for the same circuit in the earlier example.

(Refer Slide Time: 04:04)

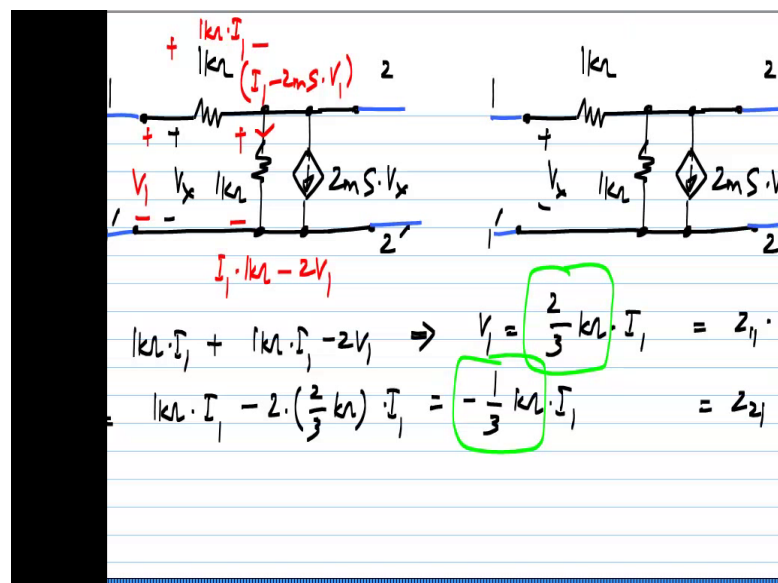

Now, let us make the circuit slightly more complicated by adding a control source, again I will take the exact same example I took earlier, so that you can relate different parameter sets for the same circuit port 1, port 2, 1 kilo ohm, 1 kilo ohm and 2 Millisiemens. So, I will go through this analysis quickly, because circuit analysis by now is familiar to you, so you can work this out yourselves and compare your answers to what I derived.

So, again I need two cases, one in which port 2 is open circuited, a current is applied to port 1 and another case, where port 1 is open circuited and a current is applied to port 2.


So, now, we have a slightly more complicated situation with the controlled source. Now, if you observe this circuit, I_1 flows through this 1 kilo ohm, then the parallel combination of these two. So, the voltage drop across this is 1 kilo ohm times I_1 , a current through this resistor is I_1 minus whatever current is flowing through the current source, which is I_1 minus 2 Millisiemens times V_x and in this circuit, you see that V_x equals V_1 , because the voltage here is V_1 .

So, V_x is the same as V_1 , so I will write this as I_1 minus 2 Millisiemens times V_1 , so that is the current flows over there. So, the voltage drop across this is this current times 1 kilo ohm, which is I_1 times 1 kilo ohm minus 2 Millisiemens times 1 kilo ohms times V_1 , which is minus 2 V_1 and also the voltage V_2 is nothing but, the voltage drop across this 1 kilo ohm resistor. So, I will write these two equations. First of all V_1 equals the sum of voltage drops across this one and that one, which is 1 kilo ohms times I_1 plus 1 kilo ohms times I_1 minus 2 V_1 .

From this we see that V_1 is $\frac{2}{3}$ kilo ohms times I_1 and we know that, V_2 is the voltage drop across this. So, v_2 is 1 kilo ohm times I_1 minus 2 V_1 and V_1 we have already calculated. So, it is $\frac{2}{3}$ kilo ohms times I_1 , which is basically minus $\frac{1}{3}$ kilo ohm times I_1 and with port 2 open circuited, we know that V_1 is nothing but, $z_{11} I_1$ and V_2 is nothing but, $z_{21} I_1$. So, z_{11} is this quantity and z_{21} is that quantity.

So, we need a little more calculation and I went through it quickly, but the analysis of the circuit with the current source I_1 applied is routine by now. So, you should be able to do this yourselves and I will do it for the other case as well. Let me copy over this part of the circuit.

(Refer Slide Time: 08:15)

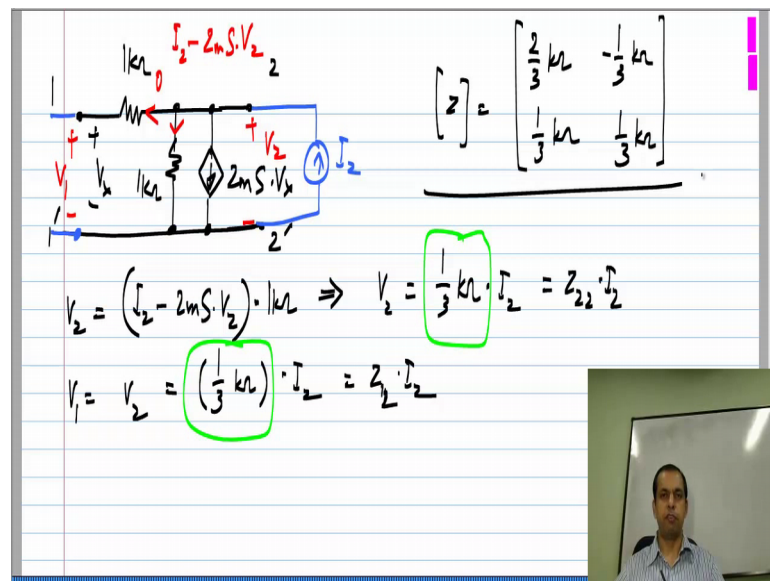

Port 1 is open circuited, now again the current through the 1 kilo ohm resistor is zero and V_2 equals V_1 in this particular circuit, this is not true in general of course, and also V_x happens to be equal to V_1 . So, now, the current through this 1 kilo ohm resistor, by the way through this it is zero and through this vertical 1 kilo ohm resistor is I_2 minus whatever current is flowing through the controlled source, which is I_2 minus 2 Millisiemens times V_x , which is the same as V_1 which is also the same as V_2 . So, I am going to write that right away.

So, now, this voltage drop V_2 is the current through this 1 kilo ohm resistor times the 1 kilo ohm resistance. So, V_2 we get it to be I_2 minus 2 Millisiemens times V_2 times 1 kilo ohms and from this, we get V_2 to be 1/3rd of a kilo ohm times I_2 and we also said, V_1 is the same as V_2 which is also 1/3rd kilo ohm times I_2 . And we know that, with port 1 open circuited V_2 is nothing but, $Z_{22} I_2$ and V_1 is nothing but, $Z_{12} I_2$.

So, this is Z_{12} and that is Z_{22} , the Z parameter matrix for this circuit turns out to be 2/3rd kilo ohms minus 1/3rd kilo ohms, 1/3rd kilo ohm and 1/3rd kilo ohm. Again, you can go back to the old or y parameter example and verify that, this is the inverse of the y matrix for this circuit.