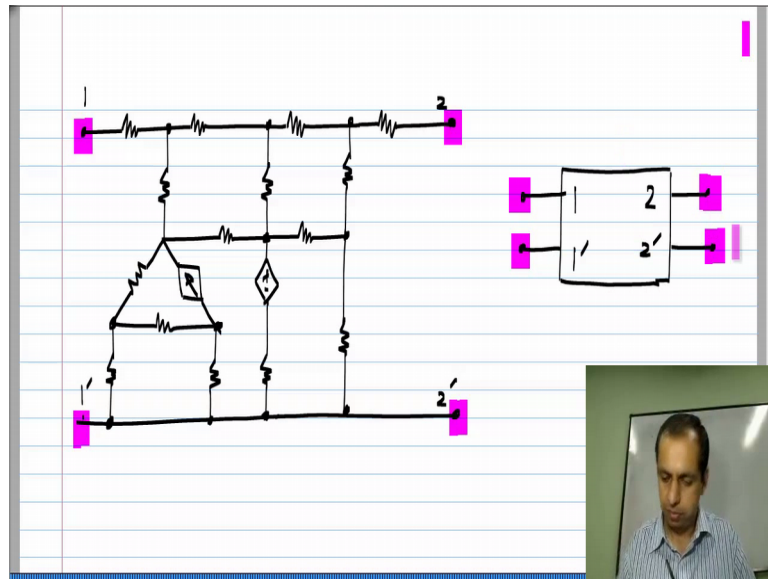


Basic Electrical Circuits
Dr Nagendra Krishnapura
Department of Electrical Engineering
Indian Institute of Technology Madras

Lecture - 89
Calculations with a two port element


(Refer Slide Time: 00:08)



In this lesson, we will look at the utility of these two port parameters. Let say we have a complicated circuit something like this; and it could be even more complicated than this; it could have hundreds of components. Now I have marked these ports 1, 1 prime and 2 2 prime, let say you are allowed to make connections only to these. So, then in that case, so I will represent this is as the box and you are allowed to make connections only to these terminals. So, in that case, you do not need to analyze this circuit over and over, you can imagine that analyzing such a circuit is quite a job, it is complicated. And like I said it could be lot bigger than this, this is only limited by what I could draw in a short time, it could have hundreds of components.

As long as you are allowed to make connections only to a two ports then the whole thing can be reduced to a set of two port parameters, and it can be anything, it could choose y parameters, z parameters, h parameters or g parameters. Once that is done, any calculation that you need to make with this circuit, you can make with the two parameters set. Now what are the possible calculations that you could be asked to make, I will show you an example.

(Refer Slide Time: 01:37)

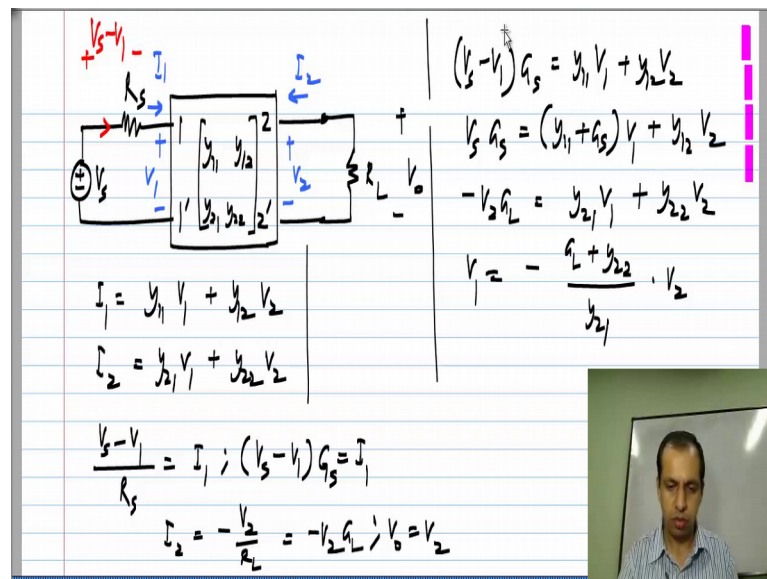

For instance let say you had a circuit whose y parameters are given or you have calculated them already. Now, I could connect the source like this; V_s in series with the resistance R_s , and I could have a load resistance to this side. And I define the voltage across the load resistance be V_{naught} . I need to calculate V_{naught} by V_s . Now I took the scenario, because this is a common one involving amplifiers on one side; you connect the source, the source could be imperfect; so it has the series resistance and on the other side you connect a load. So, now, again like I said we do not need to know what is inside, they could it could have hundreds of components. You need to do the calculation only once to determine these y parameters and after that you can simply use the y parameters.

So, I am going to show an example. Now the y parameters relates V_1, I_1, V_2 and I_2 ; and those relations we know which is I_1 is $y_{11} V_1$ plus $y_{12} V_2$; and I_2 is $y_{21} V_1$ plus $y_{22} V_2$. And now there are constraints imposed by whatever we have connected on the two sides. Firstly, let us take the circuit connected to port 1, we have V_s and R_s connected. So, the voltage drop across R_s is V_s minus V_1 that is pretty obvious considering Kirchhoff's voltage law around this loop. And the current through R_s is this current I_1 , so clearly V_s minus V_1 divided by R_s is I_1 . And let me write this in terms of conductance, it is a little more convenient. So, V_s minus V_1 times G_s is I_1 , where G_s is $1/R_s$. And if you look at the output side this V_2 is the voltage across R_L , and I_2 is the current through R_L , but in the upwards direction. So, you see that I_2 is nothing but minus V_2 by R_L or minus $V_2 G_L$. And V_{naught} is nothing but V_2 , because V_{naught} is defined across this and that is the same as V_2 .

So, now from these, we have two equations relating the voltages and currents of the two port. This is the a generic relationship for the two port. And whatever we connect on the outside imposes some constraints, we add to that and solve for V_1 by V_2 or V_2 in terms of V_1 . We eliminate all of the intermediate variables V_1 , V_2 , I_1 and I_2 we have enough equations to do that. So, let us go about doing that thing. So, I will first substitute this into the first equation, I have V_1 minus V_2 times G_1 to be $y_{11} V_1$ plus $y_{12} V_2$. So, this gives you V_1 to be $y_{11} V_1$ plus G_1 times V_2 plus $y_{12} V_2$. And I will substitute this I_2 equals minus $V_2 G_L$ in the second equation, which gives me minus $V_2 G_L$ is $y_{21} V_1$ plus $y_{22} V_2$ and this gives you V_1 to be minus G_L plus y_{22} divided by y_{21} times V_2 .

(Refer slide Time: 06:49)

The whiteboard shows the following steps:

$$(V_1 - V_2)G_1 = y_{11}V_1 + y_{12}V_2$$

$$V_1 G_1 = (y_{11} + G_1)V_1 + y_{12}V_2$$

$$-V_2 G_1 = y_{21}V_1 + y_{22}V_2$$

$$V_1 = -\frac{G_1 + y_{22}}{y_{21}} V_2$$

$$V_1 G_1 = -\frac{(y_{11} + G_1)(y_{22} + G_1)}{y_{21}} V_2 + y_{12}V_2$$

$$\frac{V_1}{V_2} = \frac{y_{12}}{G_1} = \frac{-y_{21}}{(y_{11} + G_1)(y_{22} + G_1) - y_{12}y_{21}}$$

So, let me copy those over, and from these two, I need to eliminate V_1 , so that I have a relationship between V_1 and V_2 ; and V_2 is nothing but V_{out} the output voltage that I am interested. So, putting this into that one I will get V_1 to be $y_{11} V_1$ plus G_1 times V_2 plus $y_{12} V_2$. Now by manipulating this, I can get V_1 by V_2 which is the same as V_2 by V_1 to be minus y_{21} divided by $y_{11} + G_1$ plus y_{22} plus G_1 minus $y_{12} y_{21}$. So you can take the module of the circuit module of the two ports in terms of the two port parameters and analyze the whole circuit. We do not need to look at the insides of the circuit that is the advantage. And of course, the two port parameters could be Z, G or H instead of y. In this case, I took y as an example, but it could be described by any other set of parameters. You can do the calculations in that particular set of parameters or you can convert them into one of the other sets if that

happens to be more convenient. So, this is the one of the kind of calculations that you could do.