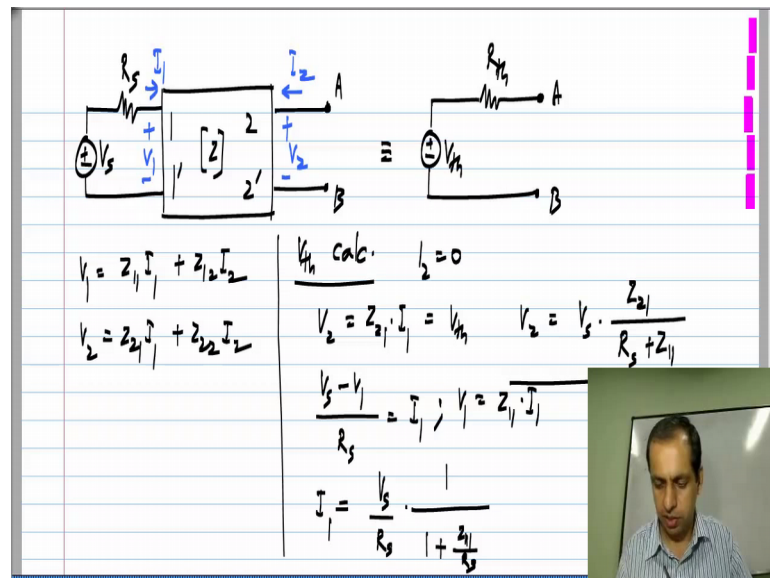


Basic Electrical Circuits
Dr Nagendra Krishnapura
Department of Electrical Engineering
Indian Institute of Technology Madras

Lecture – 90

(Refer Slide Time: 00:01)



Now, I will show you another one, these cases could be lot more complicated, but for simplicity I will use something similar to what I had earlier. Let say you are given this whole circuit and you are asked to find the Thevenin equivalent between the terminals A B, that is we need to find the Thevenin voltage and the Thevenin resistance between A and B and that also can be done in terms of the two port parameters. So, in this case let me assume that, the two port is described by Z parameters instead of y parameters.

So, what will I have? I have this V_1, I_1, V_2, I_2 and I know that V_1 is $Z_{11}I_1 + Z_{12}I_2$, V_2 is $Z_{21}I_1 + Z_{22}I_2$. I need to find the Thevenin voltage, that is I do not connect anything between A and B, I have an open circuit and find V_2 . In this particular circuit, if you have an open circuit between A and B, I_2 will be 0. Now, this is not necessarily always the case, this is the case in this particular example. So, for V_{th} calculation, in this circuit I_2 happens to be 0 that may not always be the case.

For instance we could have some load connector here, in which case I_2 will not be 0. So, V_2 will be simply $Z_{21}I_1$ and that is V_{th} , the open circuit voltage that appears here. Now, what is I_1 , that we can find out from this side. We know that $V_s - V_1$ divided by R_s is I_1 and also we know that V_1 is $Z_{11}I_1$, because I_2 is 0. So, putting

these two things together, we will get I_1 to be V_s by R_s times 1 by 1 plus Z_{11} by R_s . So, this is what comes out of the calculation and V_2 will be simply Z_{21} times this value. So, it is V_s times Z_{21} divided by R_s plus Z_{11} . In this particular case, it happens to be V_s times Z_{21} by R_s plus Z_{11} .

(Refer Slide Time: 03:51)

The slide contains a circuit diagram and several equations. The circuit shows a resistor R_s in series with a two-port network represented by Z-parameters. The input terminals are labeled 1 and 1', and the output terminals are labeled 2 and 2'. A current source I_{test} is connected across the output terminals. The voltage across the resistor is V_1 and the voltage across the two-port network is V_2 . The current entering terminal 1 is I_1 and the current leaving terminal 2 is I_2 .

The equations written on the slide are:

$$R_{th} = \frac{V_2}{I_2}$$

$$= \left[Z_{22} - \frac{Z_{21}Z_{12}}{Z_{11} + R_s} \right]$$

$$V_1 = Z_{11}I_1 + Z_{12}I_2 \quad -I_1R_s = Z_{11}I_1 + Z_{12}I_2$$

$$V_2 = Z_{21}I_1 + Z_{22}I_2 \quad I_1 = -\frac{Z_{12}}{Z_{11} + R_s} \cdot I_2$$

$$V_1 = -I_1R_s \quad V_2 = -\frac{Z_{21}Z_{12}}{Z_{11} + R_s} I_2 + Z_{22}I_2$$

Now, we also have to find the Thevenin resistance, for that we set the independent source V_s to 0. We have R_s and we have to find the resistance looking back in to this one that is for instance this is v_2 and this is I_2 . We can think of injecting either a voltage or a current source, this has nothing to do with what parameters set we choose. This is described by Z parameters, but I could apply a voltage source on this side.


It is only for measuring the parameters that we apply a current source in case of Z parameters. So, let say I do apply a current source I_{test} , clearly you see that I_2 is exactly equal to I_{test} . So, what I need to find is the ratio v_2 by I_2 , that is the resistance looking back between the terminals A and B, I also have this V_1 and I_1 over there. Now, again we have V_1 is $Z_{11}I_1$ plus $Z_{12}I_2$ and v_2 is $Z_{21}I_1$ plus $Z_{22}I_2$.

Now, because we have this resistance here, we have a relationship and force between V_1 and I_1 by ohms law. So, V_1 is minus I_1 times R_s , this is because of the direction of variables chosen; I_1 is flowing out this, whereas V_1 is defined with this polarity. Remember, we need to find V_2 by I_2 ; that means, we have to eliminate V_1 and I_1 from these two equations. So, if I substitute this I will get minus I_1R_s is $Z_{11}I_1$ plus $Z_{12}I_2$ and from this, I get I_1 to be minus Z_{12} divided by Z_{11} plus R_s times I_2 and

I will substituted in the other equation.

I will get V_2 to be Z_{21} times I_1 , which is minus $Z_{21} Z_{12}$ by Z_{11} plus R_s times I_2 plus Z_{22} times I_2 and the Thevenin resistance which is nothing but, V_2 by I_2 . I_2 is the same as the I_{test} and V_2 is the voltage developed, wherever you apply I_{test} . This will come out to be Z_{22} minus $Z_{21} Z_{12}$ divided by Z_{11} plus R_s . So, that is what we are going to have.

(Refer Slide Time: 07:15)

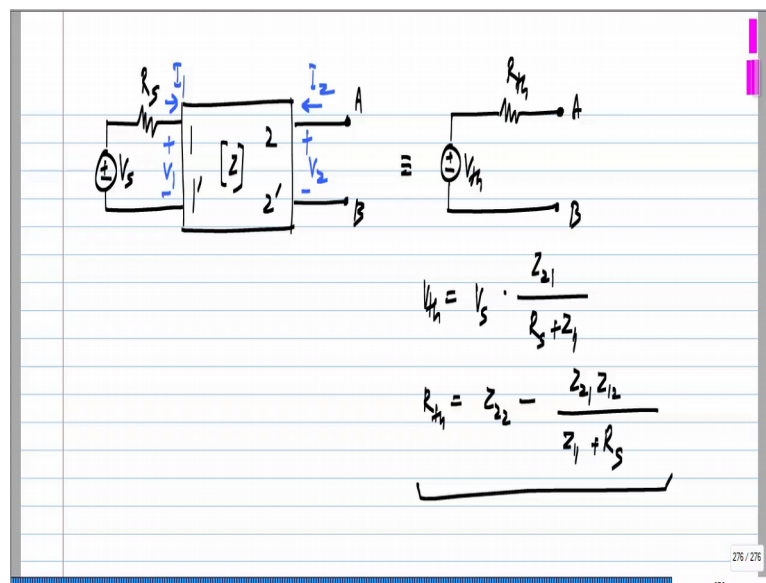

So, this whole thing, it could even be lot more complicated than this, it is equivalent to a Thevenin source and series with the Thevenin resistance, where the Thevenin voltage source is given by V_s times Z_{21} by R_s plus Z_{11} . We see that it is depended on this network as well as the voltage source and resistance connected to it and R_{th} is Z_{22} minus $Z_{21} Z_{12}$ divided by Z_{11} plus R_s . So, we can have a two ports and some circuit using the two ports and the whole thing can be represented as by it is Thevenin equivalent circuit.

So, there are many more calculations you can do, the principle is always the same. You use the two port parameter and the relationship implied by them that is, you have the voltages and currents for the two port and you have some relationship between the voltages and currents. And also the circuitry that you connect outside of the two ports will impose some relationship between some of these variables by solving for all of these equations and eliminating some variables, you can find whatever you want.