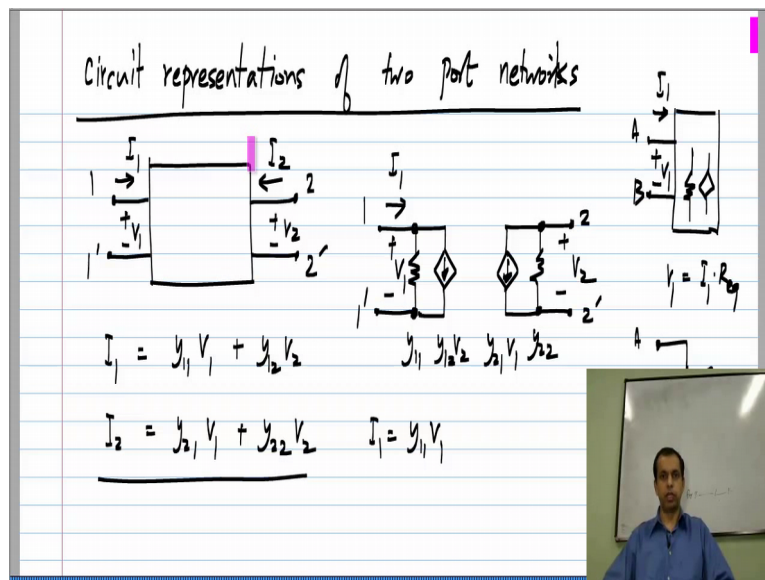


Basic Electrical Circuits
Dr Nagendra Krishnapura
Department of Electrical Engineering
Indian Institute of Technology Madras

Lecture – 93

So, far we have described the two ports using the relationships between the port currents and port voltages, they turn out to be linear combinations. In some contexts, it is useful to have a circuit representation for the same relationships; that is what we going to look at in this lesson.

(Refer Slide Time: 00:21)



So, let say we have a two port and we choose to use y parameters that says that I_1 is $y_{11} V_1 + y_{12} V_2$ and I_2 is $y_{21} V_1 + y_{22} V_2$. It would be useful to have an equivalent circuit which realizes these equations, this is analogous too, let say you are given a box with linear elements inside. Then, you could provide the relationships algebraically, V_1 equals I_1 times R equivalent or equivalently you can say, let say this is terminal A and terminal B. You could say that between A and B you have this equivalent resistance; you could show this picture instead. What we are going to do is similar to this; instead of showing the equations we will show the picture.

So, for each of these terms there will be a corresponding element, let say this is port 1, we have V_1 across it. The current flowing into port 1 is a sum of two parts $y_{11} V_1 + y_{12} V_2$. First look, let us look at this $y_{11} V_1$. So, it is flowing into port 1 and it is also related to the voltage between the same two terminals 1 and 1 prime. Clearly, if you


had just this part, let us say I_1 equals y_{11} times V_1 that would correspond to a conductance or a resistance.

So, if I have a conductance whose value is y_{11} , it will draw a current, which is y_{11} times V_1 , because it is placed across V_1 , across this conductance we have a voltage V_1 . Now, we have the second part y_{12} times V_2 , so this is y_{12} and V_2 is over there, so there is a current drawn in port 1 in response to a voltage in port 2. So, this is clearly a dependent source or a voltage controlled current source, whose value is given by $y_{12} V_2$.

Similarly, if you look at the second equation we have I_2 equals y_{22} times V_2 ; that is one part of it and that is the relationship between the voltage on port 2 and the current in port 2, so it is represented by a conductance whose value is y_{22} . And this last part y_{21} times V_1 is represented by a controlled source like this, it is I_2 . So, it is the current drawn from port 2 and it is proportional to V_1 ; that is voltage elsewhere in the circuit. So, it is model y , a voltage controlled current source and its value is $y_{21} V_1$.

So, this picture with these four elements 2 conductance's and 2 controlled sources says exactly the same thing as, what this equation is saying. Sometimes, when you are analyzing circuits, it is useful to put down this picture instead of the two port and sometimes some of these relationships becomes very obvious when you put down the picture instead of manipulating equations. Now, similar things exist for all four types of parameters; that is, what we are going to look at.

(Refer Slide Time: 05:07)

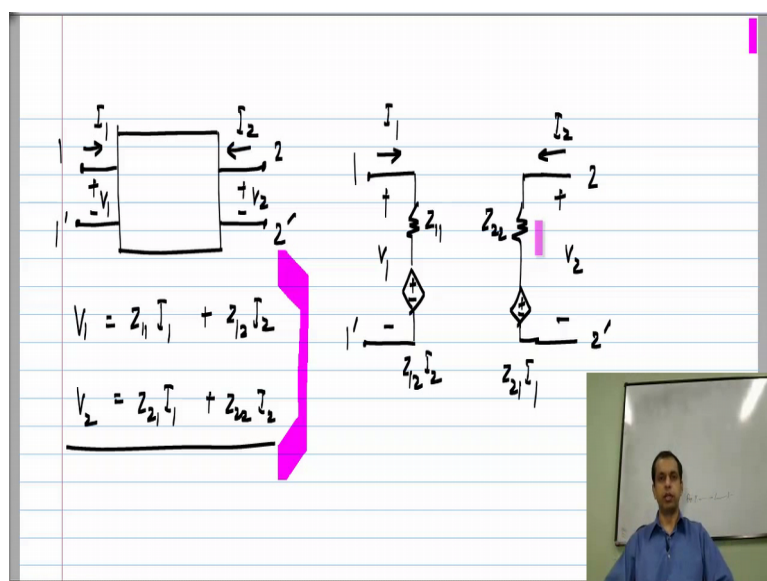


Now, we consider the z parameter representation to the two port, which gives you V_1 and V_2

2 as linear combinations of I_1 and I_2 . So, again let say this is port 1 and a current I_1 flows into that port and we have V_1 across it. We see that V_1 is the sum of two quantities so; that means that, there should be some two voltage drops in series to realize this sum. Now, the first one is z_{11} times I_1 ; that is a voltage drop which is proportional to the current flowing through the port. So, if I have a resistance whose value is z_{11} , the voltage across that will be z_{11} times I_1 , because I_1 is flowing through z_{11} .

Now, second part of it z_{12} times I_2 , it depends on the current elsewhere in the circuit that is in port 2. So, we have the second port V_2 across it and I_2 through it, so in series with this resistance of value z_{11} we will have $z_{12} I_2$. And similarly, for the second equation we have a series combination of two voltage drops, one which is z_{21} times I_1 , because it depends on the current elsewhere in the circuit. We have a current controlled voltage source, whose value is z_{21} times I_1 and in series with that we have a resistance z_{22} , because I_2 is flowing through that z_{22} , it creates a voltage drop $z_{22} I_2$.

So, again this equivalent circuit enforces the same relationships between the port voltages and port currents as do these set of equations. Sometimes, instead of using these equations it is useful to write this picture and then, may be add in whatever else comes from the rest of the circuit and proceed with your calculations.

(Refer Slide Time: 07:20)

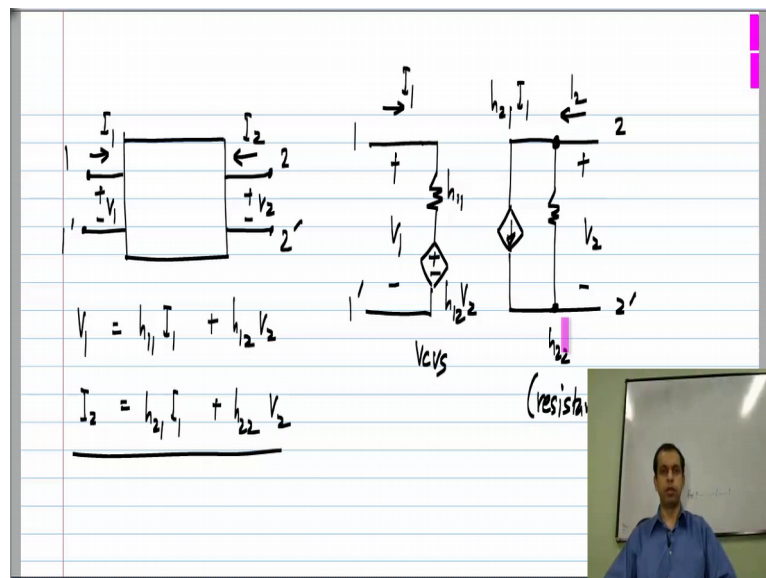


Now, we will look at the h parameter representation of the two ports. Here, again we have two equations, V_1 is the sum of two quantities since the voltage is the sum of two quantities. We can think of each of these as individual voltage drops, which appear in series to form V_1 .

And in the second equation I_2 , a current is sum of two quantities since these two currents sum up to give this you can think of these two as parallel branch currents, which add up to give I_2 . So, as you expect from the name hybrid parameters, the equivalent circuit will also be hybrid, on one side it will have series branches and on the other side parallel branches.

So, let say this is port 1 with V_1 across it and I_1 through it and this is port 2 with V_2 across it and I_2 through it. So, V_1 is a sum of these two drops, so we have a resistance whose value is h_{11} and we have a controlled source is V_1 depends on V_2 . So, this is a voltage controlled voltage source, whose proportionality constant is h_{12} or whose value is h_{12} times V_2 . For the second equation we need parallel branches, because we need to add currents, so we have $I_2 = h_{22} V_2$, so I_2 is proportional to V_2 , so this is a conductance and the conductance is h_{22} or the resistance value is $1/h_{22}$.

Finally, we have a current controlled current source, because I_1 is a current the resultant I_2 is also a current. So, this term is created using a current control current source on the gain of the current control current sources h_{21} . So, this is the, what we have on port one we have series branches on port on port two parallel branches.

(Refer Slide Time: 10:00)

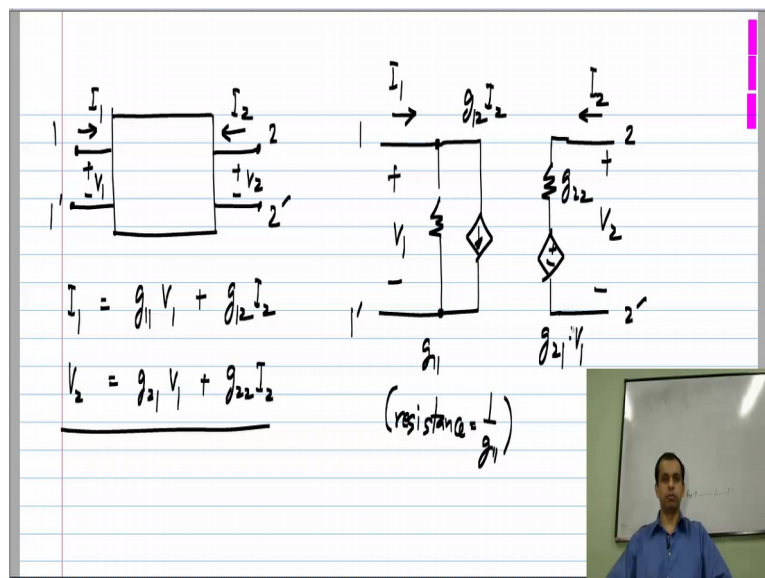

Finally, we will look at g parameters again we have two equations each with sum of two terms the first equation result in a current, which is the sum of two currents. So, we need parallel branches to implement this, the second equation is the voltage, which is the sum of two other voltages, so we need a series combination to implement that one. So, port 1 we have the voltage V_1 and the current I_1 and port 2 with voltage V_2 and current I_2 . So, the

first one is a current, so we have sum of two branches g_{11} and V_1 that represent the conductance of g_{11} or a resistance of $1/g_{11}$, the second one gives the dependence of I_1 on I_2 , so this is the current controlled current source whose gain is g_{12} or whose value is g_{12} times I_2 .

Now, on the other side or the other port we have the voltage or the sum of two other voltages V_2 equals $g_{22} I_2$ voltage proportional to current, which is obtained using a resistor whose value is $1/g_{22}$ and in series with this is the voltage controlled voltage source V_2 equals $g_{21} V_1$, so it is a voltage controlled of gain g_{21} . So, this is equivalent circuit for the g parameter two port. So, like I said any network can be represented by any set of parameters of course, sometimes some of these parameters are infinite valued in which case you do not use them, but in general you could use any one of them.

Similarly, you could use any one of these equivalent circuits, now again, which one you choose is based on convenience. Exactly like either choosing to calculate with resistances or conductance's here we do have more choices, because we have ports more variables and so on.