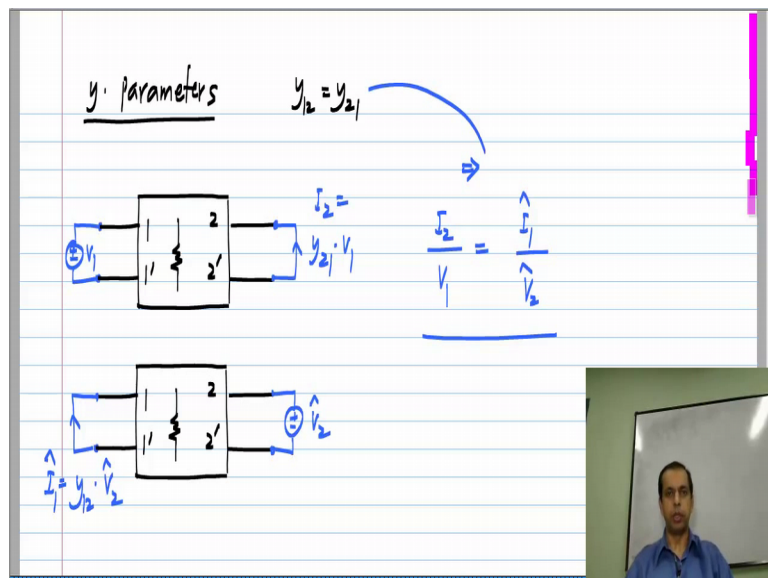


Basic Electrical Circuits
Dr Nagendra Krishnapura
Department of Electrical Engineering
Indian Institute of Technology Madras

Lecture - 97
Reciprocity in Terms of different Two Port Parameters

In this lesson, we will consider the implications of reciprocity in resistive network. We have stated reciprocity and also derived it in terms of two port parameters, but two port parameters really refer to the ratios of some electrical quantity to some other electrical quantity under certain conditions. We can talk about reciprocity even without talking about any particular two port parameter sets. So, in this lesson, we will look at what reciprocity in terms each of the two port parameters implies and also how it is useful.

(Refer Slide Time: 00:41)



So, let us first take y parameters reciprocity says that y_{12} equals y_{21} . So, if I have a resistive network and two ports, what is that mean let say I connect V_1 to the first side and short circuit the second side, the current here would be by definition y_{21} times V_1 . And on the other hand, if I connect V_2 had to the second port, short circuit the first port the current here would be I_1 hat which is equal to y_{12} times V_2 hat. And by the way let me define this current as I_2 . So, in this form, in terms y parameters it is says that the ratio of short circuit current in one port to the apply voltage is the same as the short circuit current in port one to the voltage applied at port two. So, this what it implies is short circuit current in port two ratio of that to voltages apply at port one, this is y_{21}

will be equal to I_1 hat divided by V_2 hat. The reason I am pointing does how it is different two port parameters have different implications in terms of exactly what you are measuring and also in different circumstances, you will have ratio of voltages or currents or voltages across open circuits and currents to short circuits and so on. So, you should be able to use reciprocity for all those situations.

(Refer Slide Time: 02:48)

Reciprocity: $\left\{ \begin{array}{l} \text{Ratio of short circuit current in port 2 to} \\ \text{the applied voltage at port 1} \\ = \\ \text{Ratio of short circuit current in port 1 to} \\ \text{the applied voltage at port 2} \end{array} \right.$

resistive networks

Reciprocity means ratio of short circuit current in port two to the applied voltage at port one equals ratio of short circuit current in port one to the applied voltage at port two now this is of course, true for purely resistive networks. So, this is one particular statement of reciprocity in terms of short circuit currents.


(Refer Slide Time: 04:06)

Z-parameters $Z_{12} = Z_{21}$

$\frac{V_2}{I_1} = \frac{V_1}{I_2}$


Now, similarly let say what it means in terms of z parameters which is z_{12} equals z_{21} . So, when you are measuring z_{21} you will apply a current port one and measure the open circuit voltage at port two and when you are measuring z_{12} you apply current two port two and measure the open circuit voltage at port one and this statement our reciprocity means that V_2 by I_1 equals V_1 hat by I_2 hat. So, here the ratio open circuit voltage to the applied the current is the same whether you applied the current at port one and measure the voltage at port two or you applied the current at port two and measure the current at port one.

(Refer Slide Time: 05:31)

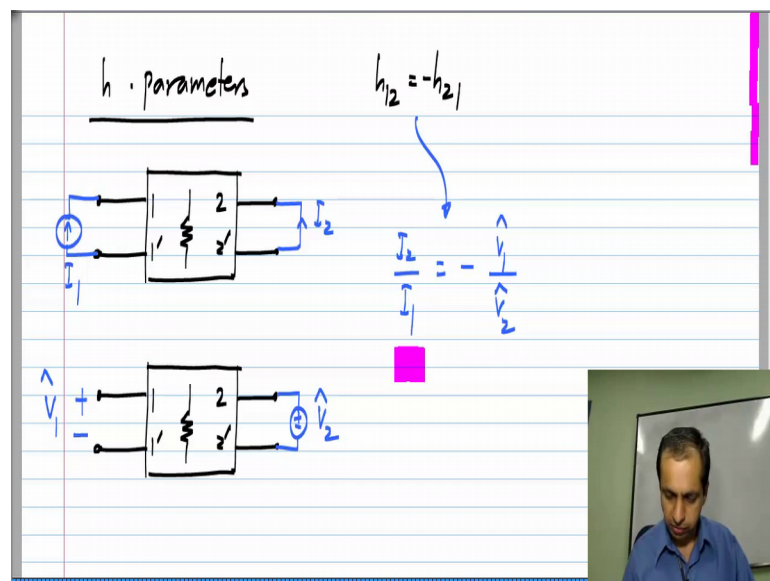


It we do it with h parameters you will have h_{12} equal h_{21} and this is my resistive two port when you are measuring h_{21} you will apply like a current two port one terminate port two with short circuit and measure the current in port two and when you measuring the h_{12} will apply a voltage to port two and have an open circuit across port one and measure the voltage across that open circuit this of course, implies that I_2 by I_1 equals minus V_1 hat by V_2 hat. So, basically the current again from port one to port two which is port given by this is the negative of the voltage gained from port two to port one, so you get this negative sign. If you choose the direction of currents, I show on here I you had chosen the current to be in the opposite direction you want get that, but we always choose the current direction consistent with the two port parameter definitions. So, we get this I_2 by I_1 2 be minus V_1 hat by V_2 hat.

(Refer Slide Time: 07:23)

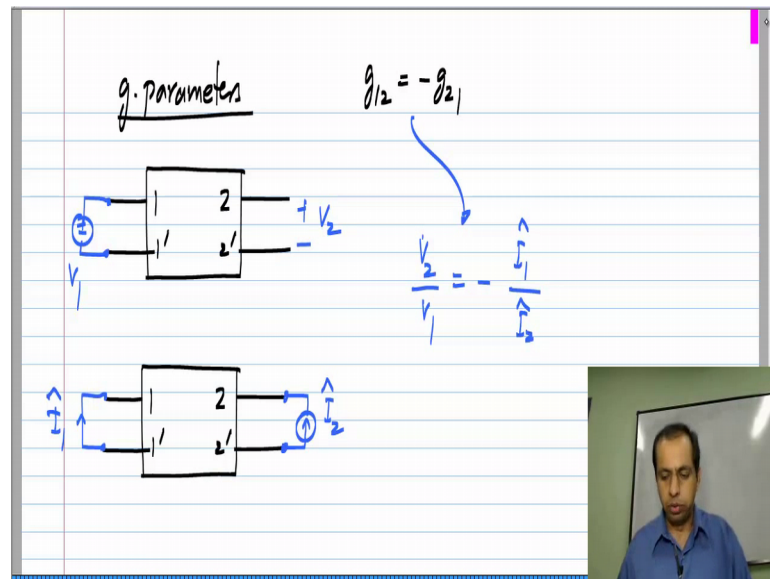

g parameters, we have exactly the same thing g_{12} is minus g_{21} and I have my two port. When I measuring g_{21} I will apply a voltage to port one and measure the open circuit voltage across port two, and when I measuring g_{12} I will apply a current to port two and measure the short circuit currents through port one. And this implies that the voltage gain from port one to port two, and this voltage gain is measured with an open circuit termination equals the negative of the current gain port two to port one which of course, is measured with short circuit termination. These are all the implication reciprocity in terms of two port parameters we have defined.

(Refer Slide Time: 08:52)

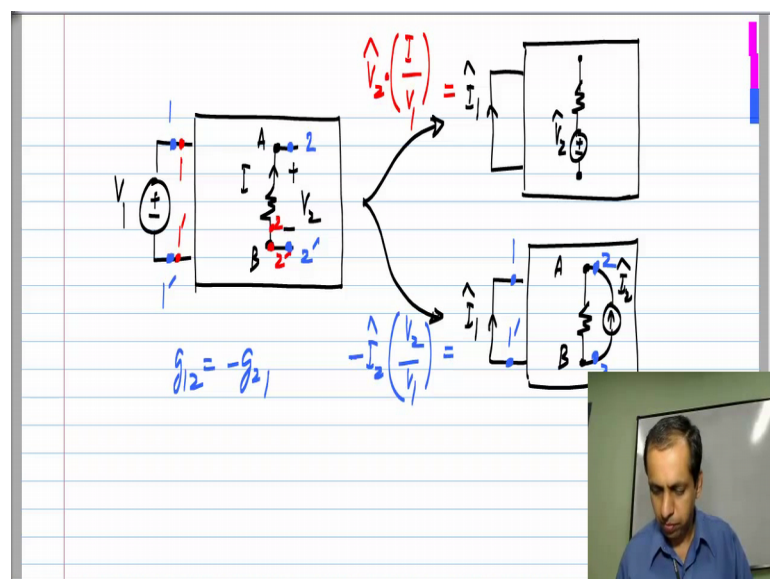

But the main use of reciprocity is that let say you already know some result, with the

particular source. So, let say the network and it consist of resistors and let say I have the single independent source some where I will consider that to voltage source. Let say you already solve for this case that is I know that if I apply V_1 here between these two nodes I get particular V_2 what reciprocity theorem enables to do is let say you have alternative scenario where for instance let me call node a node b and between node a there is resistor. So, let say we have alternative scenario where the voltage source V_1 replays by for circuit and between nodes a node b. We have the resistance in series with that we have voltage source let me call that V_2 hat now I already know the result one V_1 is apply certain V_2 appears across a and b and; obviously, you also know this current which flows through the resistor.


So, now, let say you have the scenario or an alternative scenario where a still have a short circuit were the voltage source was and between a and b, I have a current source in a parallel, let me call the I_2 hat. And I want know how much current this I_1 hat here or I_1 hat in this case I do not need to solve for the circuit again I can use reciprocity from this one to get these result because in the first case essentially what I am doing is I am defining let say this is port one and this link here is port two then you can think of the original case as the case with port to be short circuit at and this current.

I have marked this really the current port two I marked it top of the resistor, but now the resistor part of the two port it is really the port current. So, now, clearly this V_2 hat applies to the second port over there and the first port short circuit at. So, I_1 hat I can find out without doing any further calculations is the same as V_2 hat times the ratio of the hat here which is I_1 by V_1 I_1 by V_1 would be nothing but y_{21} with this as the first port and that as the second port.

Similarly, in this case I can relate this case to the original case by defining something else as two ports let me call this port one which is same as before and now I will call this between node a and b define the second port two. So, now, if you do that we can see that basically these V_2 by V_1 is nothing, but g_{21} this port two is open circuit at here nothing else connected there and now this port one which is short circuited and this is port two to which this current I_2 hat is applied. So, again using reciprocity in terms of g parameters I can find out I_1 hat and I_1 hat would be equal to negative of I_2 hat times V_2 by V_1 this negative sign comes because g_{12} is minus g_{21} and this V_2 by V_1 here is nothing, but g_{21} between these two ports shown in blue and here what I want is g_{12} that is nothing, but the negative of g_{21} .


So, this is the point of the reciprocity theorem, we do not have to be presented with something that is defined at the two port network. You could be ask question like this that you apply voltage here and you gets something ales there and in other case the voltage apply on this side and what response appear from that side you can use reciprocity by defining your on two port.

(Refer Slide Time: 13:57)

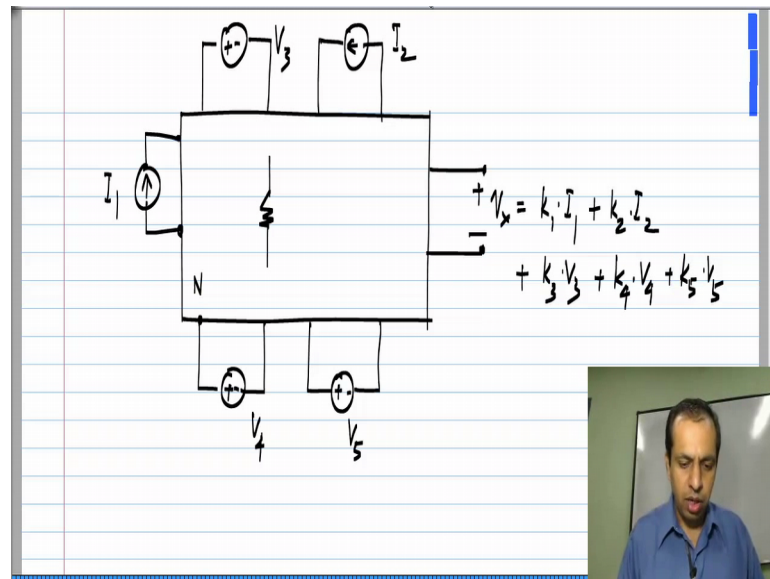

In the case and which can be particularly useful. So, let say we have these two points and measuring the voltage and then we have only resistor in this circuits let say we have number of sources connected both current sources and voltage sources let say this is the circuit we have multiple sources and we have the output now you are required to find out the contribution all of these things to the output. So, let me call this V 2, V 3, V 4, V 5. So, now, we have to find out this V x from all of these sources, now sometimes it could be easier turn this problem around and realize that the transfer from I 1 to this even all these us other sources are will be the same as this point to that and so on. So, now, we this V x clearly be linear combination of all of these sources. So, let me call that k 1 times I 1 plus k 2 times I 2 plus k 3 times V 3 plus k 4 time V 4 plus k 5 times V 5 naturally because this is the voltage and these two are currents k 1 and k 2 will have dimension of resistance, and k 3, k 4, k5 will be dimension less constants.

(Refer Slide Time: 16:14)

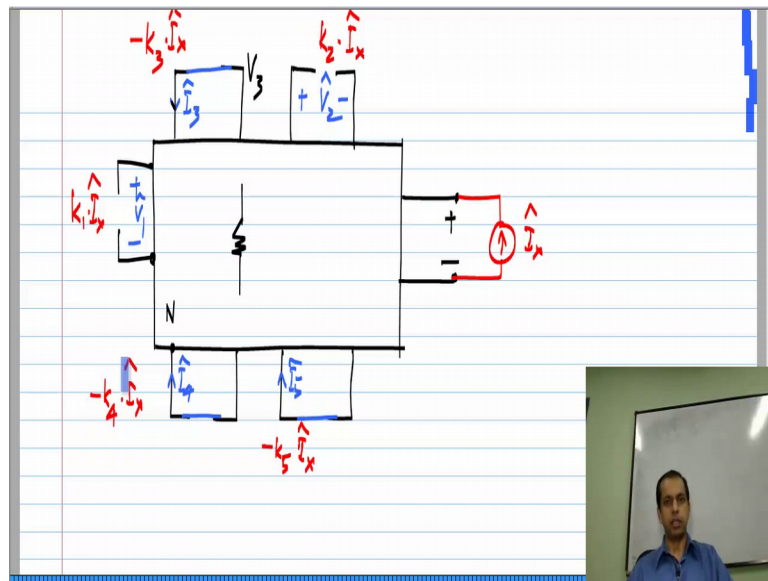

Now how do we use reciprocity in a situation like this. What we do is we deactivate all these sources that is short circuits all the voltage sources and we open circuit all of the current sources let me define this is I_3 hat I_4 hat I_5 hat and this V_1 and this is V_2 these directions are consistent with that two port convention that I have already use the current sources and voltage sources that on a implies. Now because in the original circuit, this is terminated in open circuit, I will apply a current source i_x hat and do the analysis. Now the advantage of this is that we have single source in the analysis and this is many times easier to carry out now is given hat would be k_1 times I_x hat this V_2 hat would be k_2 times I_x hat and this I_3 hat would be minus k_3 times I_x hat, this I_4 hat would be minus k_4 I_x hat and I_5 hat would be minus k_5 times I_x hat.

What I did was the first consider this and that as the two port, and use the z parameters version then this and the that as the two port use to the z parameters version, then this and the that as the two port and use the g parameter version and so on. So, I get these ratios. The point is by analyzing the circuit with single source, I get these coefficients of the linear combination k_1, k_2, k_3, k_4, k_5 . So, this is the advantage of using reciprocity in certain situations. Now it turns out that in circuit analysis in particular we have something known as noise analysis every resistor in the circuit in general any component in the circuit trades noise and you need to calculate the transfer function from every noise source to the output and multiply that by the actual noise would be created to find output noise.

Now in this case in terms out the particular simple to turn the whole picture around and

apply an excitation at the output and find what appears in place of each of the resistors that should be the transfer function which is also the same as the transfer function from the resistor to the output. And by using this reciprocity the simulator is able to calculate the noise as functions very easily so that is the application of it.