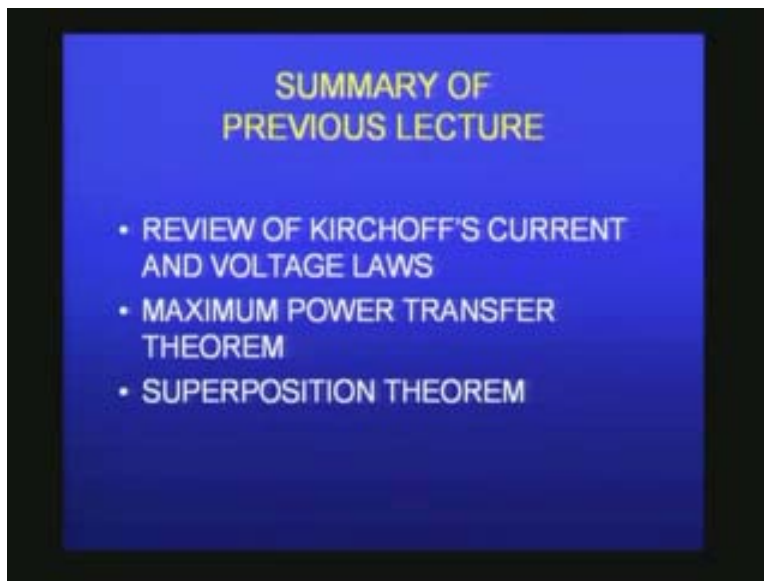


**BASIC ELECTRONICS  
PROF. T.S. NATARAJAN  
DEPT OF PHYSICS  
IIT MADRAS**

**LECTURE-5  
SOME USEFUL THEOREMS IN  
BASIC ELECTRONICS**

Hello everybody! In our series of lectures on basic electronics let us now move onto the next lecture. Before we do that let us recall what we discussed in the previous lecture.

[Refer Slide Time: 1:36]




In the previous lecture we were looking at some of the well known theorems and laws which are very useful in electronics. We just reviewed the Kirchoff's law of current and voltage and then we also looked at some detail the maximum power transfer theorem which says when maximum power will be transferred from a given circuit to the load. We found that when internal resistance of the source is matched by the external load resistance there is maximum power transfer. We also saw some demonstration of the same. Lastly we also saw the most important network theorem that is superposition theorem. When we have more than one source, current sources or voltage sources how do we solve for a current or voltage across any of the given resistors. We saw the conditions to be satisfied, how the whole thing has to be looked at as a superposition. So this superposition theorem is very useful in solving network problems.

Today we will look at two more very important theorems of network basically Thevenin's theorem and Norton's theorem. These two are also very, very useful in simplifying very complicated circuits and trying to understand the working of different circuits in electricity and electronics. Let us now take first Thevenin's theorem. We

actually had a brief idea about Thevenin's, Norton's theorem in the previous lecture at the end of the lecture. Thevenin's theorem is very useful by which a complex circuit can be reduced to an equivalent series circuit consisting of a single voltage source which is called  $V_{TH}$  and a single series resistance which is called  $R_{TH}$  resistance of the Thevenin's and a load resistance  $R_L$  which any way is there in the circuit.


[Refer Slide Time: 3:58]

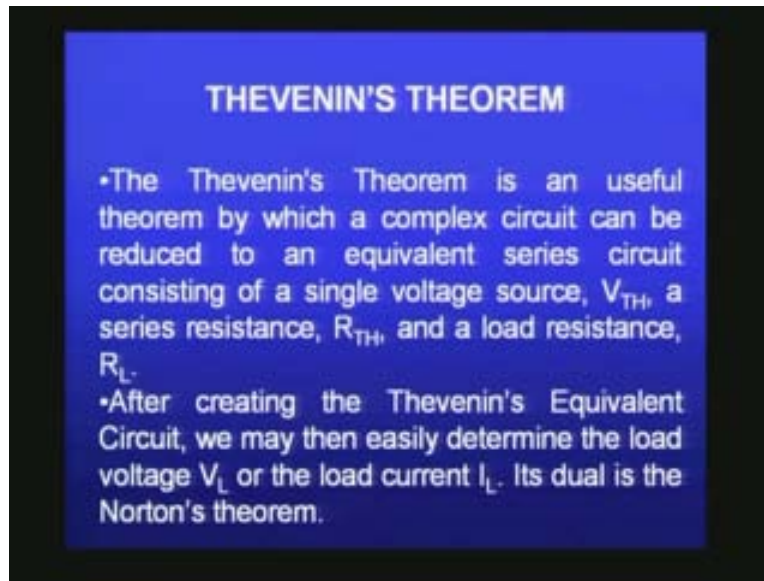

So any complicated circuit having any number of sources and resistors can be simplified by just having only one Thevenin's source, a voltage source and one Thevenin's resistors equivalently. So that becomes much simpler to solve once we have this type of an arrangement and you can see that it becomes very simple to solve such a theorem. There is also another theorem, the second theorem which is called the Norton's theorem which is a dual of Thevenin's voltage theorem. In the Norton's theorem instead of looking at voltage sources which we will do in Thevenin's theorem, we look at current sources. That means any complicated circuit can be equivalently considered as having one single Norton's current source and Norton's resistance. So these two theorems are very useful in solving many problems in electronics and electricity.

On the screen you can see there is a black box where there could be any circuit with number of DC sources and resistances and that is connected to one  $R_L$ , the load resistance at the terminals A and B output terminals of this black box. What Thevenin says is that the entire set of resistors and sources that you have in this box can be equivalently considered with only just two devices. One is Thevenin's voltage source  $V_{TH}$  and other is the Thevenin's resistance  $R_{TH}$ . One has to obtain the value of  $V_{TH}$  and value of  $R_{TH}$  corresponding to any given circuit and then the simplified circuit will just have only three components; the Thevenin's voltage source, the Thevenin's resistance and the external  $R_L$  that is being connected.


[Refer Slide Time: 6:10]

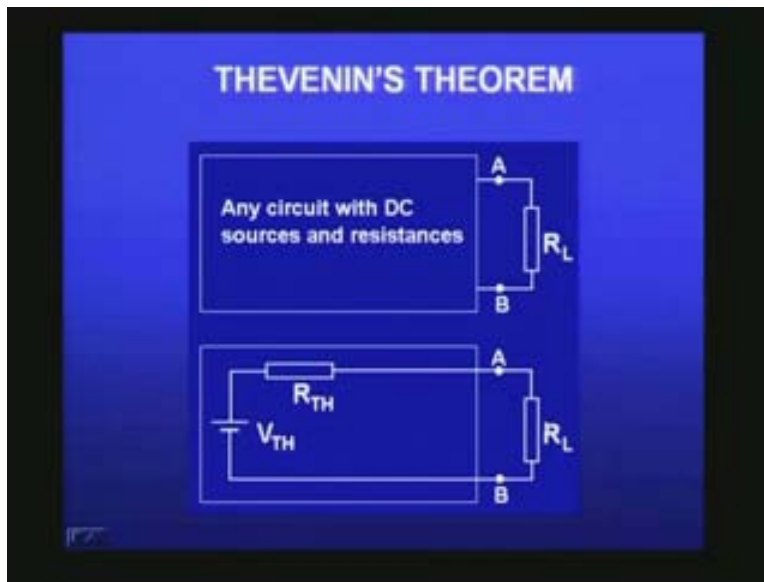

Then it becomes very simple. It becomes a simple potential divider. If you want to know the voltage across  $R_L$ , it is just a question of finding out what percentage or what proportion or what fraction of voltage  $V_{TH}$  is appearing across  $R_L$  which is a very simple problem which we have already solved.

Now let me take an example of a circuit which has got three internal resistors  $R_1$ ,  $R_2$  and  $R_3$  and  $R_L$  is the external resistance between the terminals A and B.


[Refer Slide Time: 6:41]

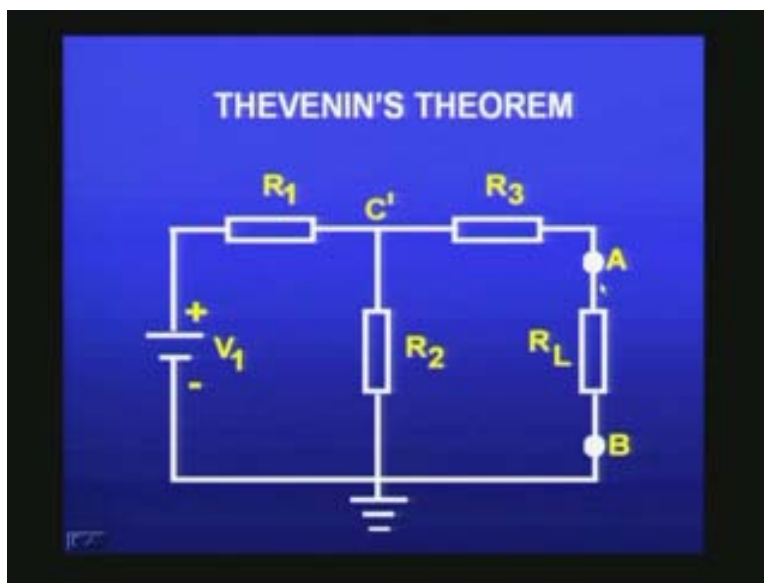

You have only one source because to start with the example will be very simple with one voltage source and just three resistors connected as shown in the figure. Our job is now to


find out how to solve these using Thevenin's theorem so that we should be able to obtain ultimately an equivalent Thevenin's voltage and equivalent Thevenin's resistance which will replace all these voltage sources  $V_1$  and  $R_1$ ,  $R_2$ ,  $R_3$  combination. We will see what the theorem says. The theorem says that you can measure the Thevenin's voltage in two ways.

[Refer Slide Time: 7:24]

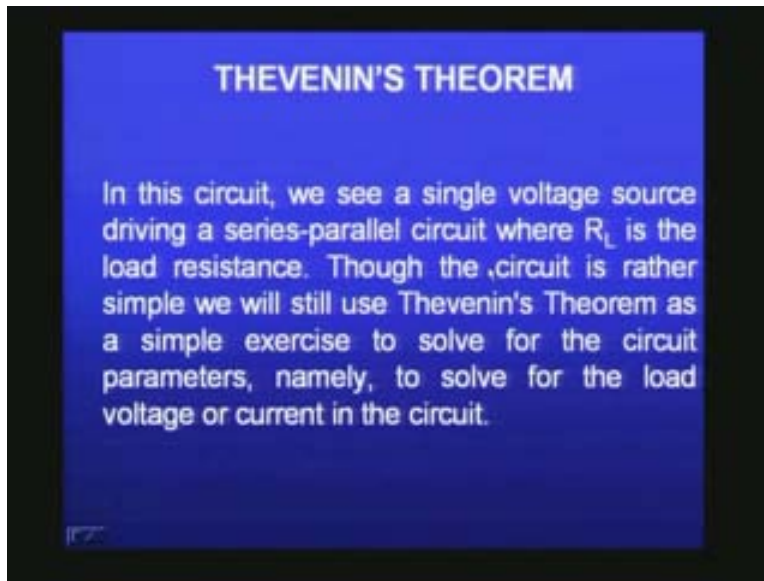

One is by actual measurement. The other one is looking at it in an analytical way. Let us see how we go about doing this. The first thing is we want to find out what is  $V_{TH}$ .

[Refer Slide Time: 7:39]

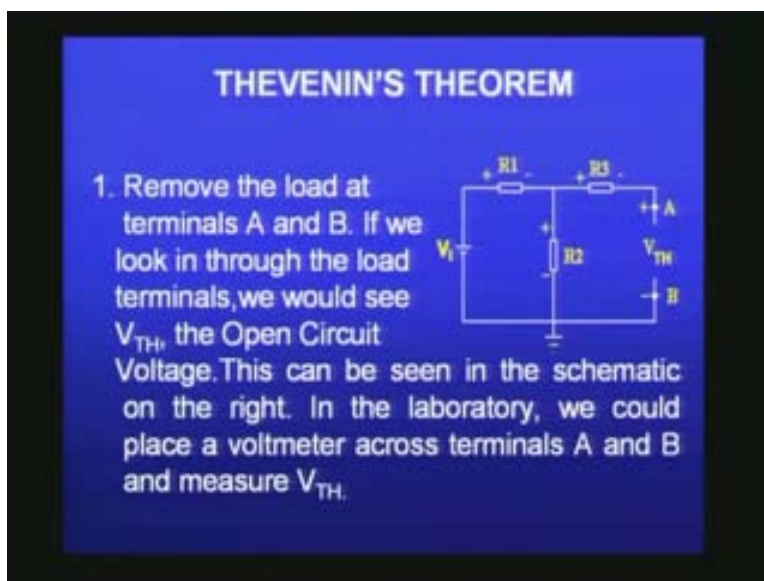


Then all that we have to do is remove the load. That is what you can see in the picture now. The load  $R_L$  is removed here and you just connect the terminals A and B to a voltmeter and measure the open circuit voltage. It is an open circuit now because the circuit is open at this point. You have removed  $R_L$ . So the circuit is open. That means infinite resistance here and if you measure using a digital multimeter the voltage between the points A and B is the effective Thevenin's voltage appearing at the output. So if you want to measure it is very simple. Open the circuit. That is remove the  $R_L$  from the circuit and use a multimeter to measure the voltage across the output terminals A and B under open condition. That gives you the  $V_{TH}$ .

Let us look at analytically how we calculate the Thevenin's voltage.

[Refer Slide Time: 8:48]

**THEVENIN'S THEOREM**

- Since the circuit is open at terminals A and B, no current flows through  $R_3$ .
- With no current through  $R_3$ , there is no voltage drop across  $R_3$ .
- Therefore,  $V_{TH} = V_{R_2}$   
( the voltage across  $R_2$  )
- This we can calculate easily.



Since the circuit is open between A and B you can see there will not be any current through the resistance  $R_3$  because the circuit here is infinite resistance. The entire current will be flowing only through  $R_1$  and  $R_2$  and therefore whatever voltage you want between A and B will be the same as the voltage across  $R_2$ , for example. The voltage across  $R_2$  will therefore be the voltage Thevenin,  $V_{TH}$ . That is what shown is shown here on the screen.  $V_{TH}$  is equal to  $V_{R_2}$ , the voltage across  $R_2$ . This we can easily calculate from this circuit because you can see you have a voltage source, you have two resistors and you want to find out what is the voltage that has to be developed across one of the resistors.

[Refer Slide Time: 9:38]

### THEVENIN'S THEOREM

- Since the circuit is open at terminals A and B, no current flows through R3.
- With no current through R3, there is no voltage drop across R3.
- Therefore,  $V_{TH} = V_{R2}$   
(the voltage across R<sub>2</sub>)
- This we can calculate easily.

It is a simple potential divider and therefore you know  $V_{TH}$  will have to be  $V_1$  multiplied by  $R_2$  divided by  $R_1 + R_2$  which is nothing but a simple potential divider arrangement and you are trying to measure the proportional voltage across  $R_2$ , one of the resistors.

[Refer Slide Time: 10:00]

### THEVENIN'S THEOREM


The equation for  $V_{TH}$  is:

$$V_{TH} = V_1 \cdot \frac{R_2}{R_1 + R_2}$$

We now have the Thevenin Equivalent Voltage,  $V_{TH}$ , and must determine the Open Circuit Resistance,  $R_{TH}$  (Thevenin Equivalent Resistance).

So we can see this is the  $V_{TH}$  and this will be the effective equivalent voltage source that we should ultimately use after we simplify the circuit. We have now got  $V_{TH}$ . Next step is to obtain  $R_{TH}$ . How do we get  $R_{TH}$ ?  $R_{TH}$  can also be easily measured by just measuring the resistance across the output terminal with  $R_L$  removed; that is the open circuit resistance. How do we do that? Before you measure the resistance, remove all source voltages and replace them with a short while retaining any internal source resistance.

[Refer Slide Time: 10:47]

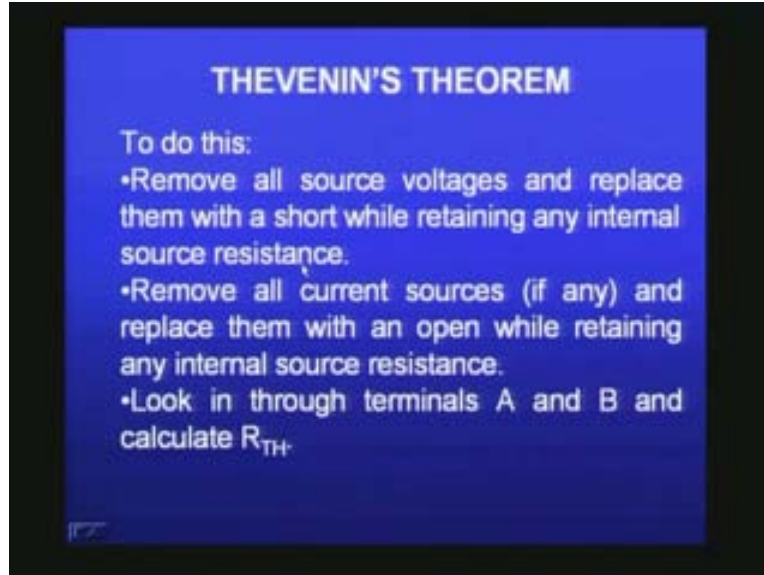

So if you have a voltage source, you just remove the voltage source from the circuit; connect a short in its place or because we assume the voltage source to be ideal if the voltage source you know has got an internal resistance then include only the resistance and remove the voltage source. Similarly if it contains current sources then you have to open the current source and if the current source has got internally very large resistance include the resistance in the circuit. So you will have only resistances in the circuit. You would remove all the sources, whether it is voltage source or current source. After removing all the sources look in through the terminals A and B, the output terminals, where the load was and measure the resistance. That resistance is equivalent to  $R_{TH}$ , the Thevenin's equivalent resistance. You can see in the circuit that is what I have done. I have removed the voltage source which was here previously and I replaced it with a short. So this point is connected to the ground because we assume that voltage source is an ideal voltage source; almost nil internal resistance and therefore you are left with only the three resistors  $R_1$ ,  $R_2$  and  $R_3$  and  $R_L$  is removed here and you have A and B terminal which is an open circuit situation and therefore now if I measure using a multimeter, the resistance between the two terminals A and B, that resistance will be the equivalent Thevenin's resistance.

[Refer Slide Time: 12:27]

### THEVENIN'S THEOREM

If we look in terminals A and B of the circuit on the right, we see the Thevenin Equivalent Resistance. Let us see what type of resistance connections we have in the circuit.

We have seen how we can measure the Thevenin's voltage and the Thevenin's resistance. We can also calculate in this simple circuit which contains only three resistors  $R_1$ ,  $R_2$  and  $R_3$  the equivalent resistance. I am sure every one of you knows about it. You can see  $R_{TH}$  is actually  $R_3$  plus the parallel combination of  $R_1$  and  $R_2$ . Let me go back and show you, you can see  $R_1$ ,  $R_2$  are now coming in parallel because these ends are the same for the two resistors; these ends are also the same  $R_1$   $R_2$  are coming in parallel,  $R_3$  is in series with this combinations of  $R_1$  and  $R_2$ . The equivalent Thevenin's resistance can now be written  $R_{TH}$  is equal to  $R_3$  plus  $R_1$  multiplied by  $R_2$  divided by  $R_1$  plus  $R_2$ .

[Refer Slide Time: 13:31]

### THEVENIN'S THEOREM

The equation for  $R_{TH}$  is:

$$R_{TH} = R_3 + \frac{R_1 \cdot R_2}{R_1 + R_2}$$

We could also measure this resistance in the laboratory with an ohmmeter by replacing the source with a short and placing the ohmmeter across terminals A and B.



This is the effective resistance of the parallel combination of  $R_1$  and  $R_2$ , to add it along because it is in series with  $R_3$  this effective resistance is added with  $R_3$  to obtain the total effective Thevenin's resistance,  $R_{TH}$ . This can be also be measured by using a multimeter. We would see that later on. Let us take an example. On the same circuit I have just given some values to the various resistors. For example  $R_1$  is 3.9 K; that is 3900 ohms.  $R_2$  is 8.2 K ohms,  $R_3$  is 4.7 K ohms and  $R_L$  is 3.3 ohms and  $V_1$  the voltage source is 10V.

[Refer Slide Time: 14:20]

**THEVENIN'S THEOREM**

As an example let us calculate  $V_{RL}$  using Thevenin's Theorem for the following circuit parameters:

$R_1 = 3.9k$ ;  $R_2 = 8.2k$ ;  
 $R_3 = 4.7k$ ;  $R_L = 3.3k$ ;  
 $V_1 = 10V$ .

Now let us calculate the Thevenin Equivalent Voltage

I have just given some numbers for the resistors and the voltage. We will now try to solve numerically what will be  $V_{TH}$ , what will be  $R_{TH}$  and with the  $R_{TH}$  and  $V_{TH}$  position let us draw a simplified diagram and calculate what will be the output voltage across the load  $V_L$ . So that is what we are going to now do as an illustration. So you can see the circuit diagram now with all the values shown.  $R_1$  is 3.9K,  $R_2$  is 8.2K,  $R_3$  is 4.7K and we want  $V_{TH}$ . Therefore you know what we have to do.

[Refer Slide Time: 15:00]

### THEVENIN'S THEOREM

- Now we will solve the circuit using Thevenin's theorem.

We have to just bring voltmeter and connect between A and B and measure if you have got a voltmeter. Otherwise we can also do by actually working out, calculating the  $V_{TH}$  by the method that we already mentioned to you.

[Refer Slide Time: 15:17]

### THEVENIN'S THEOREM


- Remove the load at terminals A and B. The  $V_{TH}$  is the open circuit voltage between A and B. We can measure the voltage  $V_{TH}$  using a multimeter.

If you want to calculate the  $V_{TH}$  at the output, you know  $R_3$  will not contribute anything because this is in series with an infinite resistance here because you have now open circuit.  $R_L$  is not there and therefore the voltage across  $R_2$  is the Thevenin's voltage with  $V_1$  connected to  $R_1$  and  $R_2$  in series and therefore all that you have to calculate the  $V_{TH}$  which is equivalent to the voltage across  $R_2$ .

[Refer Slide Time: 15:52]
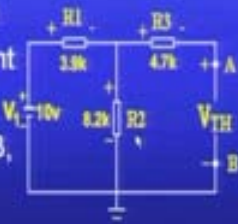
### THEVENIN'S THEOREM

- Since the circuit is open at terminal A and B, No current flow through R3.
- With no current through R3, There is no voltage drop across R3.
- Therefore  $V_{TH} = V_{R2}$  (Voltage across R<sub>2</sub>)




Let us do that.  $V_{TH}$  therefore will be equal to  $V_1$  the applied voltage which is here 10V multiplied by  $R_2$  divided by  $R_1 + R_2$  because  $R_1$   $R_2$  form a potential divider and so  $V_{TH}$  is equal to 10V because  $V_1$  is 10V and  $R_2$  is 8.2 K. Therefore 8200 divided by 3900 which is the value of  $R_1$  plus 8200 which is  $R_2$  and if you simplify this we get  $V_{TH}$  to be 6.78 V.

[Refer Slide Time: 16:25]

### THEVENIN'S THEOREM

$$V_{TH} = V_1 \cdot \frac{R_2}{R_1 + R_2}$$

$$V_{TH} = 10V \cdot \frac{8200}{3900 + 8200}$$

$$V_{TH} = 6.78V$$


You can verify it with a calculator. So  $V_{TH}$  we have calculated to be 6.78 for this circuit which contains a very simple scheme of three resistors and a voltage source. Now that we have got the  $V_{TH}$  we should now measure or calculate  $R_{TH}$  which is the open circuit resistance across the load.

[Refer Slide Time: 16:49]

### THEVENIN'S THEOREM


- We now have the Thevenin Equivalent Voltage,  $V_{TH}$ , and must determine the Open Circuit Resistance,  $R_{TH}$  (Thevenin Equivalent Resistance).
- Remove all source voltages and replace them with a short while retaining any internal source resistance.
- Remove any current sources and replace them with an open while retaining any internal source resistance.
- Look in through terminals A and B and calculate  $R_{TH}$ .

For this, what we have to do? I have already explained to you. Replace the voltage sources with the short, current sources with open and include any internal resistance that may be present along with the voltage source. We generally assume the voltage sources to be ideal for this case and therefore just remove the voltage source, connect a short and there you have a very simple scheme of only resistors and we will now calculate the effective resistance,  $R_{TH}$  between the two terminals A and B at the output. That is exactly what we have done here. You can see on this picture,  $R_1$  is 3.9 K,  $R_3$  is 4.7 K and  $R_2$  is 8.2 K. We have replaced the voltage  $V_1$  by a short.

[Refer Slide Time: 17:39]
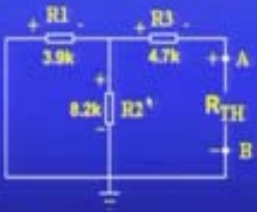
### THEVENIN'S THEOREM

- If we look in terminals A and B of the circuit on the right, we see the Thevenin's Equivalent Resistance.
- We can see  $R_1$  and  $R_2$  are in parallel and are in series with  $R_3$ .



We want to measure what is this? You can measure by using a multimeter in ohms range that will directly give you the Thevenin's resistance. The other way to do is to calculate

from this circuit. This circuit is a very simple circuit. Again you can see  $R_1$ ,  $R_2$  are coming in parallel and the combination is coming in series with  $R_3$ . Therefore Thevenin's equivalent resistance can be very easily calculated. It is shown on the screen.  $R_{TH}$  is equal to  $R_3$  plus  $R_1$  into  $R_2$  divided by  $R_1$  plus  $R_2$ ; we have already seen that.

[Refer Slide Time: 18:11]

**THEVENIN'S THEOREM**

The equation for  $R_{th}$  is

$$R_{TH} = R_3 + \frac{R_1 \cdot R_2}{R_1 + R_2}$$

$$R_{TH} = 4700 + \frac{8200 \cdot 3900}{8200 + 3900}$$


$$R_{TH} \approx 7343 \text{ Ohms}$$

In this case  $R_3$  is 4700 ohms, 4.7K plus  $R_1$ ,  $R_2$  combination is 8200 multiplied by 3900 divided by 8200+3900 and the effective resistance when you do simplification is around 7.3K. So this is the  $R_{TH}$ . So we have calculated  $V_{TH}$ . We have also calculated  $R_{TH}$  once we do that we can simplify the original circuit by just having the  $V_{TH}$  here as you can see and you have the  $R_{TH}$  which you have now calculated for this example and just you have connect the  $R_L$  which is the alternate load resistance we want to apply.

[Refer Slide Time: 18:56]
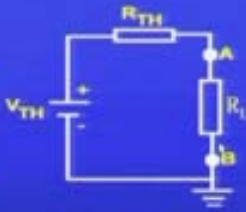
### THEVENIN'S THEOREM

- Now that we have determined the Thevenin's Equivalent Resistance and the Thevenin's Equivalent Voltage.



- We redraw the simplified circuit as a series circuit consisting of  $V_{TH}$  and  $R_{TH}$ . Make sure that the polarity of  $V_{TH}$  in the series circuit is the same as the polarity of the open circuit voltage. Reconnect the load,  $R_L$  to terminals A and B.


You can see all the complicated circuit has been removed and replaced with a very simple scheme of one source and one internal resistance of the source which can be equivalently ..... (19:12). Now we have to calculate the voltage across the load; that is what the problem started with. So you can again see because you have only two resistors now  $R_{TH}$  and  $R_L$  with one single voltage source the problem becomes very simple.

[Refer Slide Time: 19:29]

### THEVENIN'S THEOREM

Now, calculate the load voltage.

The equation for  $V_L$  is:

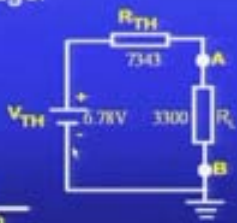


$$V_L = V_{TH} \cdot \frac{R_L}{R_{TH} + R_L}$$

$$V_L = 6.78V \cdot \frac{3300}{7343 + 3300} = 2.1 V$$

We have to just look at the voltage across the  $R_L$ .  $V_L$  is therefore  $V_{TH}$  multiplied by the potential divider arrangement  $R_L$  divided by  $R_{TH}$  plus  $R_L$ . With the values substituted  $V_{TH}$  we calculated to be 6.78 multiplied by 3300 which is the load resistance 3.3K divided by the Thevenin's resistance 7.3K plus 3.3K of the load resistance and when you simplify this you get the value of about 2.1V.

You can see we have simply replaced very complicated circuit with a Thevenin's equivalent circuit and that becomes very simple to solve. Let us try to simulate this whole measurement. I am going to show you on the screen a simple simulation of the experiment. You can see a breadboard coming over here and the same circuit is put there. There is one 3.9K; there is another 4.7K which is  $R_3$  and the  $R_2$  is 8.2K and your load resistance is 3.3K. That is connected to a voltage source on this side and the output is connected to a multimeter on this side and the circuit also for reference is shown here at the bottom corner.

[Refer Slide Time: 20:53]

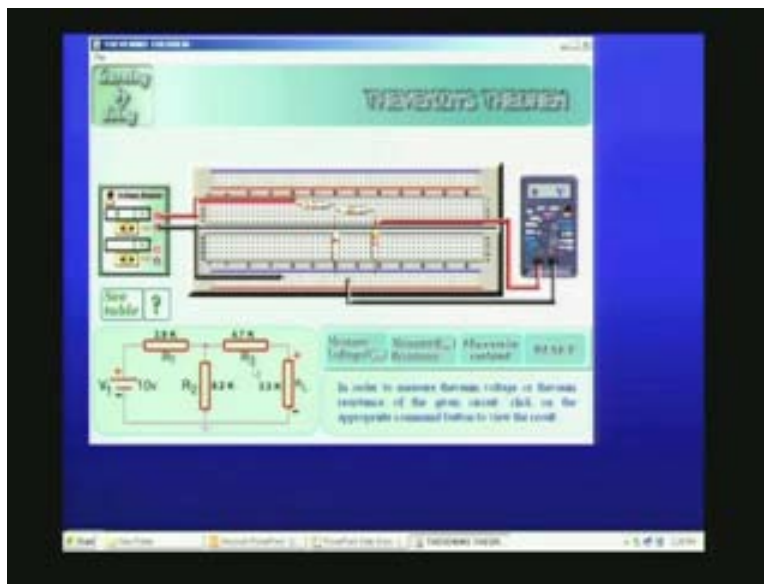


Now you have to measure the Thevenin's. We will do both. We will measure and we will also calculate. Let us measure Thevenin's voltage. Once I click you know what we have to do. We have to open circuit. That means we have to remove the  $R_L$ . So I go there and click on the  $R_L$ ,  $R_L$  is gone. Now I will have to measure the voltage using the voltmeter. Before that I should switch on the power supply. So I switch on the power supply; switch on the multimeter. Now start applying voltage by using this increase button. I will apply 10V because that is what we started with. I apply now 10V for this circuit and measure the voltage across the load terminal after removing the load and you can see the voltage on the multimeter is 6.78 which is what we calculated in the previous slides. So the Thevenin's equivalent resistance is very simple. Just remove the load, connect a voltmeter; switch on the power supply and measure you find it is 6.78. If you want to see how it comes you can go and look at here; you can see the whole thing. If I apply 5V, the Thevenin's equivalent voltage will be 3.39. When you apply 10V the Thevenin's equivalent is 6.78.

Now you will switch off the voltage sources. We will go ahead to measure the Thevenin's resistance,  $R_{TH}$ . We will have to calculate  $R_{TH}$ . We know the rule. The rule is replace the power supply with a short. So when I click here you find this point is connected to the ground by using a shorting wire and the power supply is disconnected.

Now I have only the three resistors. The  $R_L$  is removed; under the open circuit condition I will measure the resistance here.


[Refer Slide Time: 22:54]

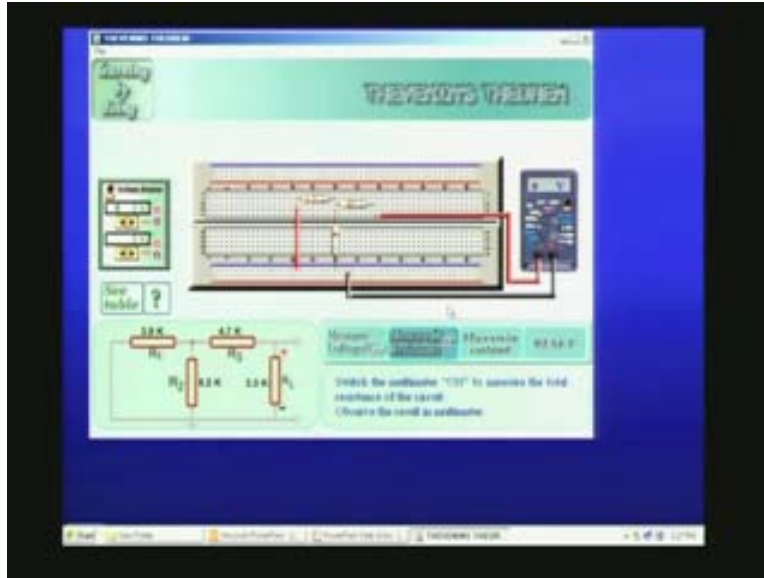

I will switch on only the resistance. I will switch on the multimeter. Immediately you can see it comes into resistance mode and it measures about 7.343ohms. So this is the Thevenin's equivalent resistance and the calculation is shown here.  $R_{TH}$  is nothing but  $R_3$  and  $R_1R_2$  in parallel combination. So now we have measured both the Thevenin's resistance and Thevenin's voltage. Now we have to measure the Thevenin's output across the load. The circuit now is simplified. You can see the voltage is connected here and there is only this 7.343 that is the Thevenin's resistance; this is the Thevenin's voltage source. Now we will have to set it for 6.78V. This is the load resistance 3.3K. Now we will switch on the power supply source and then you will increment. Immediately voltage comes out to be 6.78 which is the Thevenin's voltage we have set; we have measured and therefore I set this for 6.78 and I just measure the output voltage across the load to be 2.1V which is what we calculated in the previous example. You can see that the output voltage is also shown in the table. You can see that is about 2.1V.


[Refer Slide Time: 24:22]



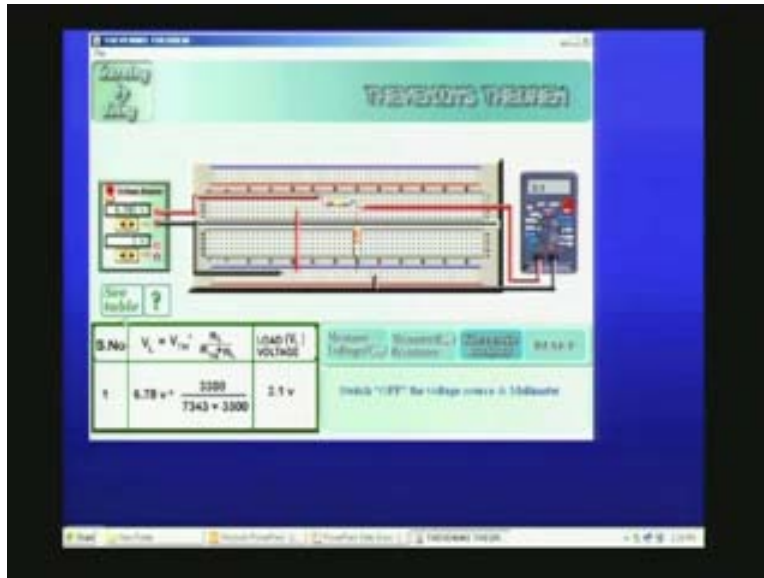

Now we will switch off the power supply and multimeter. We are ready to go and try the actual experiments. We will perform the experiment and then do the same measurement. Here I have the power supply. Red and black lines are connected to this circuit. For simplicity I have shown the circuit here. You have same circuit which we just now did. This is the voltage supply  $V_1$ . We will set up 10V here and the three resistors  $R_1$  3.9K,  $R_2$  8.2K and  $R_3$  4.7K. The same resistors are shown here. This is  $R_1$ ; this is  $R_2$ ; this is  $R_3$  and this is the load resistance which is 3.3K and this is the load resistance.

[Refer Slide Time: 25:31]

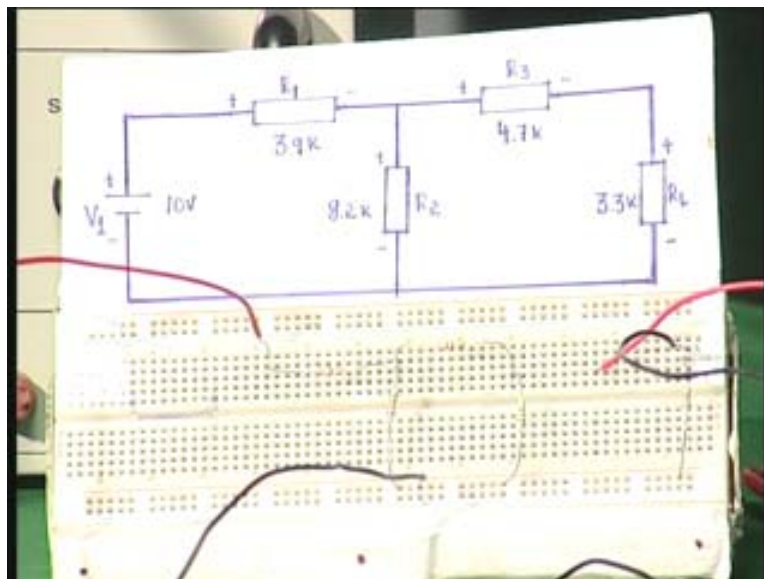

The red wire is connected to this end that is this point and the black is connected to the ground line, common line at the bottom and therefore the input is connected from the voltage source. I have to set this for 10V and I should remove this and measure the

voltage across this point using this multimeter in voltage range. Then I will be able to measure the Thevenin's equivalent voltage. Let us do that. For that I remove the load resistance. Therefore under open circuit condition I have the multimeter; I will connect the one end to the ground. I will take the other end and connect it to the point where  $R_3$  is coming. This is the multimeter. I will switch on the multimeter to voltage range. I have connected to voltage range; put it in volts and connect it to DC. Now it is reading zero because I have not switched on the power supply. I am going to switch on the power supply and it is set for about 10V. So this is around 10V as you can see on the screen and 10V is applied with the three resistors. I have removed the load resistance and measuring the output voltage. Output voltage is around 6.89 or so. We actually calculated the value of 6.78. We see here it is around 6.9.

[Refer Slide Time: 27:27]



The difference is because these resistors are not the exact values as mentioned here. They have some 5% or 10% tolerance and therefore the actual resistance value will be slightly different from the value that I have specified here and therefore you will get the actual voltage corresponding to this combination. But you can see it is very close to what we actually discussed and this is the Thevenin's voltage because I removed the load and measuring the voltage output using the multimeter. So this is the Thevenin's voltage  $V_{TH}$  that we have measured.

The next point is to measure the Thevenin's resistance. For that what we have to do? I will first switch off and I should remove the voltage source and connect it by short. I will take as small short wire. I will remove this red wire. I will connect that point where the voltage source is connected with a short. This is the shorting wire which has come in place of the voltage source and I have to now measure, after removing the load which I have already done, the resistance. I should now change the multimeter to resistance range and see how much is the resistance? I will move it resistance range; I will press here. Now I have done that. So three resistors are there and I am measuring the resistance using

this multimeter and I hope you can see the reading here is about 7.19K ohms or 7.2K ohms.


[Refer Slide Time: 29:12]



We calculated something close to 7.3K ohms. We are getting here as 7.2 K ohms. That is why there was a difference also in the output voltage.

We have actually calculated the Thevenin's voltage; we have also calculated the Thevenin's resistance. Now I have to connect the load resistance and measure how much is the thing. So I will again remove this short. I will connect the load resistance 3.3K once again which I removed previously. Now I will connect the power supply back. I have connected the load resistance 3.3K. In the same circuit I have connected this power supply also back after removing the short. Now I switch on and measure the load resistance. I want to just measure the load resistance. I want to push it into voltage. I have connected voltmeter back to DC voltage and I have switched on. This is again around 10V and the output voltage across the load  $R_L$ ,  $V_L$  is around 2.13V as you can see and therefore the load voltage is now 1.3V under the condition of all the resistors in place.


[Refer Slide Time: 30:50]

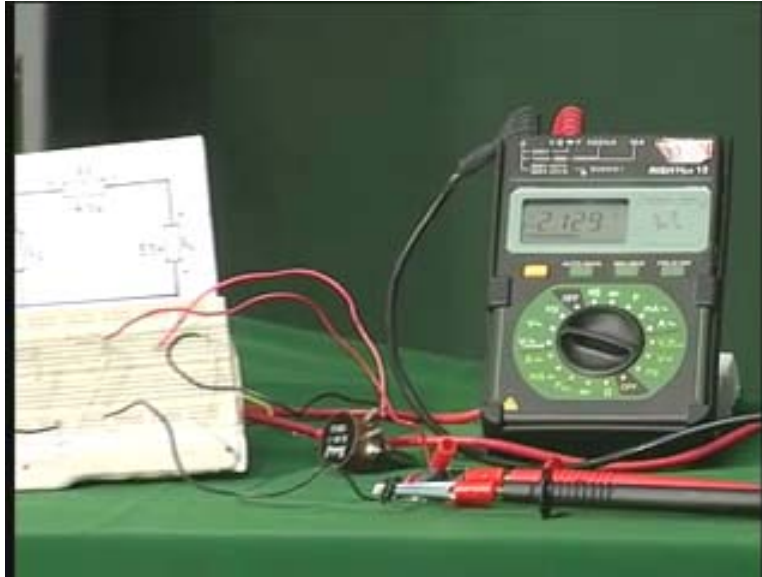

We have calculated  $V_{TH}$ ; we have calculated the  $R_{TH}$ . Therefore now I am going to introduce the  $V_{TH}$ ,  $R_{TH}$  only and put the load resistance and measure the output voltage. If again I get 2.1 then we have solved the circuit. So let us now try to do that. What I am going to do now is take this power supply out and set here 6.2V. I have set it up. I have here a resistor which is a potentiometer, a variable resistor. Let us first measure the resistance of that potentiometer. I will take the multimeter in resistance mode and calculate the resistance. Now it is around 7.8. I can adjust it to some smaller value. So it is around 7.5K. We calculated the Thevenin's resistance to be 7.3 or so. Let us make it to 7.3 by moving the potentiometer knob. So it is around 7.3K; right. We have now set Thevenin's resistance by using a potentiometer. We have set the voltage source to give an output voltage which is equivalent to Thevenin's voltage. Now I will connect this across the simplified circuit and now I will measure the output voltage using the voltmeter. I have connected the voltmeter across the load 3.3K. This is the Thevenin's resistance; this is the Thevenin's voltage source. I have discarded the original earlier circuit and I have got only two resistors; one is the potentiometer which I have set equivalent to Thevenin's resistance near about and this is the load resistance which is again 3.3K and voltage source which is 6.2.


Now we will have to measure the voltage. You can see the voltage is around 2V. We calculated it to be 2.1V in the actual situation and therefore it comes very close to that and I already explained to you that the difference is because these resistors that we have used are not exactly equivalent to whatever the color code says. There is a tolerance variation. Therefore you can see the Thevenin's equivalent circuit also gives about 2V; this circuit also gave 2V when I applied 10V here and then measure the voltage across the load and therefore you can see the whole circuit can be replaced by an equivalent Thevenin's resistance and Thevenin's source and we will be able to simplify the whole circuit in an easy way.

[Refer Slide Time: 34:43]

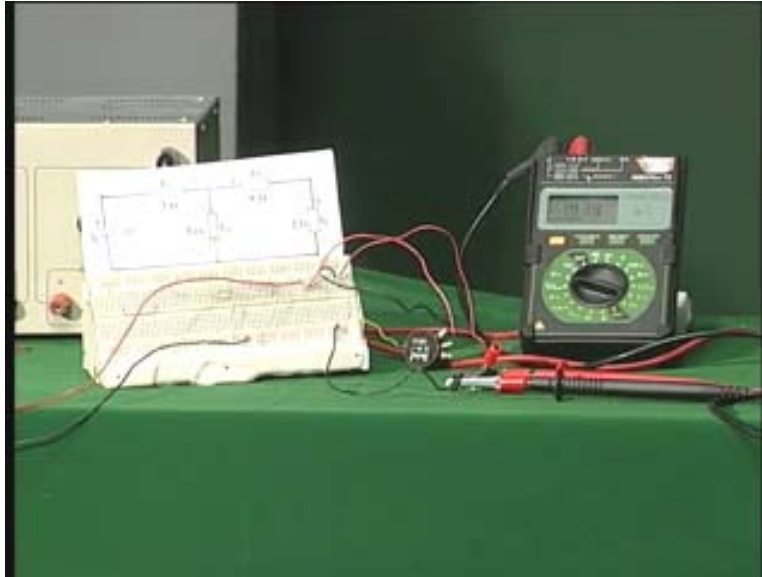

We have seen a very simple scheme in which I have used only one voltage source and three resistors. We can also take examples which involve more than one voltage source and several resistors. So I have now considered the second example which is more complicated as you can see here. It has got two sources.

[Refer Slide Time: 35:15]

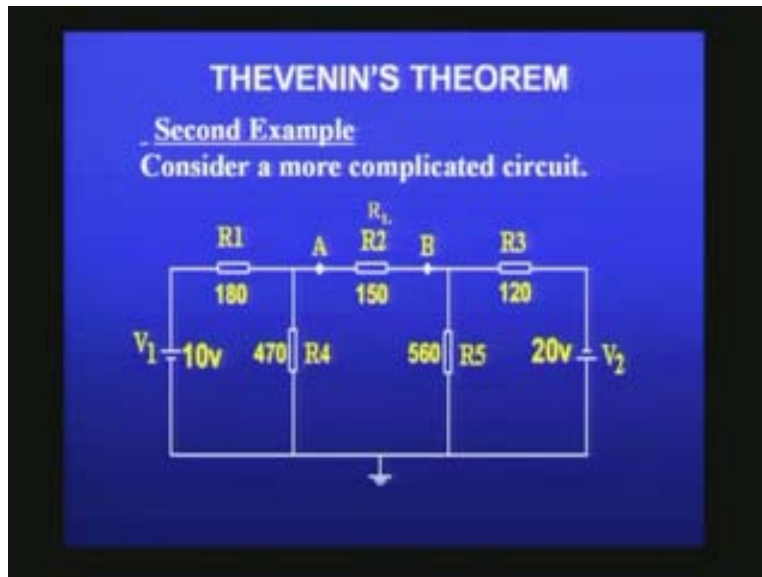

There is  $V_1$  here 10V and  $V_2$  here 20V and you can see the polarity is also changed here and you have number of resistances  $R_1$ ,  $R_2$ ,  $R_3$ ,  $R_4$  and  $R_5$  and this  $R_2$  is actually  $R_L$  I assume. Therefore what we want to do now is find out the voltage across  $R_2$ , A and B.  $R_2$  is our  $R_L$ ; I have shown here. We want know the voltage across this. That means I have to replace the entire block around this  $R_2$  by simply using two devices. One is  $V_{TH}$ , the Thevenin's voltage and  $R_{TH}$ , the Thevenin's equivalent resistance. That is what we

should do. How do we go about it? There are number of ways to do that. You find with reference to  $R_2$  there is some circuit on the right side with one voltage source and two resistors and on this side there is another voltage source and two resistors. If you look at this side you can see it is similar to what we saw in the previous example and there are two parts of the circuit; the left part and the right part. So we can try to see whether we can solve the Thevenin's equivalent circuit for the right side of the circuit and for the left side of the circuit and then combine them together and then find the total equivalent Thevenin's circuit. That is how we will do that.

What we have to do is we have to remove the load. I have removed the load here; open circuit condition and I should measure using a multimeter in the voltage range the voltage between terminals A and B. That will give me the Thevenin's equivalent voltage. By measurement it is very simple. Just remove the load; measure the voltage across the terminals of the load using a multimeter. That is all. That is the Thevenin's equivalent voltage and similarly measurement of Thevenin's resistance also is very simple. Remove the voltage source by a short, this voltage source also by a short and measure the resistance between A and B using a multimeter in resistance range. As simple as that.

[Refer Slide Time: 37:37]

**THEVENIN'S THEOREM**


- Remove the load at terminals A and B. If we look in through the load terminals, we would see  $V_{TH}$ , the Open Circuit Voltage. This can be seen in the schematic on the right. In the laboratory, we could place a voltmeter across terminals A and B and measure  $V_{TH}$ .

We will go ahead and then try to see how we can measure? I have already mentioned to you that we will consider this in two parts, left part and the right part. Let us look at for example  $V_{TH1}$  corresponding to the left part,  $V_{TH2}$  corresponding to the right part. Consider together separately and then combine the two together. Now you have here the left part alone, left half of the circuit and so now you can immediately see  $V_{TH}$  can be obtained because there are only two resistors; they are forming a potential divider. Therefore I can calculate the  $V_{TH}$  corresponding to this simple circuit on the left side.  $V_{TH1}$  is equal to  $V_1$  which is 10V in this case multiplied by  $R_4$  divided by  $R_1+R_4$  because  $R_1$ ,  $R_4$  forms the potential divider arrangement. When I put the value of resistor 470 ohms, 180 ohms and 470 ohms I get a Thevenin's equivalent voltage of 7.23V.

[Refer Slide Time: 38:45]

### THEVENIN'S THEOREM

- The circuit on the right is the left half of the open circuit above. The equation for  $V_{TH}$  is:


$$V_{TH} = V_1 * \frac{R_4}{R_1 + R_4}$$
$$V_{TH} = 10V * \frac{470}{180 + 470} = 7.23V$$


So this is the Thevenin's equivalent voltage for the left side. Now we have to find out what is the Thevenin's equivalent resistance  $R_{TH}$  for the left side. For that we remove the voltage source; replace it with a short and measure the resistance. You can see in the circuit shown I have removed the voltage source and connected with a simple wire and I just have only two resistors and these two resistors are coming in parallel and therefore  $R_{TH}$  is nothing but a parallel combination of  $R_1$  and  $R_4$ .

[Refer Slide Time: 39:21]

### THEVENIN'S THEOREM

- If we look in the terminals of the circuit on the right, we see the Thevenin Equivalent Resistance. For this example, all we see is a simple parallel circuit. We could measure this resistance in the laboratory with an ohmmeter by replacing the source with a short and placing the ohmmeter across terminals A and ground.




So  $R_{TH}$  is equal to  $R_1$  multiplied by  $R_4$  divided by  $R_1 + R_4$  and by substituting the values 180 ohms and 470 ohms and simplifying you can see  $R_{TH}$  is about 130 ohms.

[Refer Slide Time: 39:38]

### THEVENIN'S THEOREM

- The equation for  $R_{TH}$  is:

$$R_{TH} = \frac{R_1 * R_4}{R_1 + R_4}$$
$$R_{TH} = \frac{180 * 470}{180 + 470}$$
$$R_{TH} = 130 \text{ , Ohms}$$


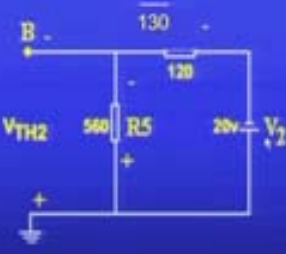
Therefore we have solved the left side of the circuit.  $R_{TH}$  is about 130 ohms and Thevenin's voltage is 7.23V. That is what we measured.

Let us move on to the right side. In the right you have  $R_3$ ,  $R_5$  and the 20V power supply.

[Refer Slide Time: 40:01]

### THEVENIN'S LAW

- Now let us look at the right half of the circuit and apply Thevenin's Theorem. We will calculate  $V_{TH2}$  and  $R_{TH2}$ . The circuit on the right is the right half of the open circuit above.




We have to calculate the equivalent  $V_{TH}$  and  $R_{TH}$  in this side. You can see that  $V_{TH}$  is again very simple because there are only two resistances  $R_3$  and  $R_5$  coming in the circuit and so  $V_{TH2}$  is  $V_2$  into  $R_5$  divided by  $R_3+R_5$ .



[Refer Slide Time: 40:21]

### THEVENIN'S THEOREM

- The equation for  $V_{TH}$  is:


$$V_{TH} = V_2 \cdot \frac{R_5}{R_3 + R_5}$$
$$V_{TH} = \frac{-20V \cdot 560}{120 + 560}$$
$$V_{TH} = -16.47V$$


This is -20V because the polarity is reversed compared to the other one; multiplied by 560 divided by 120+560. That is the potential divider arrangement we have and the value is around -16.5V. That is the Thevenin's voltage. To measure the Thevenin's resistance, again you go by the same rule. You replace the voltage source with a short and then calculate the resistance across the terminal where you connect the load. You can see in the circuit here I replaced voltage source with a short and I have to measure the resistance between these two terminals and this is nothing but the parallel combination of  $R_3$  and  $R_5$ .

[Refer Slide Time: 41:12]

### THEVENIN'S THEOREM

- If we look in the terminals of the circuit on the right, we see the Thevenin Equivalent Resistance. For this example, all we see is a simple parallel circuit. We could measure this resistance in the laboratory with an ohmmeter by replacing the source with a short and placing the ohmmeter across terminals B and ground.



$R_3$  is 120 ohms,  $R_5$  is 560 ohms. So  $R_{TH2}$  for the right side is  $R_3$  multiplied by  $R_5$  divided by  $R_3+R_5$ .


[Refer Slide Time: 41:22]

### THEVENIN'S THEOREM

- The equation for  $R_{TH2}$  is:

$$R_{TH2} = \frac{R_3 * R_5}{R_3 + R_5}$$

$$R_{TH2} = \frac{120 * 560}{120 + 560}$$

$$R_{TH2} = 99 \text{ Ohms}$$


With the values of resistors substituted it comes to around 99 ohms. We have solved for the right side of the circuit the equivalent Thevenin's voltage and Thevenin's resistance. Now what we have to do to is we have to combine the two. Left side and the right side we should combine them together. So that is what we are doing here. Here you can see this is  $R_{TH1}$  and  $V_{TH1}$  and this side  $R_{TH2}$  and  $V_{TH2}$ . I combine them and that will be the equivalent Thevenin's circuit.


[Refer Slide Time: 41:58]

### THEVENIN'S THEOREM

- Now reattach the grounds from the left and right equivalent circuits. We will see the complete circuit on the right.
- Notice we have a series circuit consisting of two voltage sources and two resistances. Since the two sources are connected series aiding, we can combine them into a single voltage source:

$$V_{TH} = V_{TH1} + V_{TH2}$$

$$V_{TH} = 7.23V + 16.47V$$

$$V_{TH} = 23.70V$$


$V_{TH}$  is  $V_{TH1} + V_{TH2}$ ; algebraically you should add. This is 7.23; this is -16.47 in this case. But they are actually aiding each other. It is like a series connection and therefore the total resistance will be 23.7 V. Similarly resistance I should connect them together; 130 ohms and 99 that correspond to 229 ohms.


[Refer Slide Time: 42:24]

### THEVENIN'S THEOREM

- Connect the  $V_{TH}$  so that the negative terminal of the source is ground. We will also connect node B to ground.
- Now calculate  $R_{TH}$ , the two Thevenin Equivalent resistances connected in series.

$$R_{TH} = R_{TH1} + R_{TH2}$$

$$R_{TH} = 130 + 99$$

$$R_{TH} = 229 \text{ Ohms}$$


Therefore I can replace the entire circuit combination of both the right side and the left side with a very simple  $R_{TH}$  and  $V_{TH}$  resistors and this case  $R_{TH}$  and  $V_{TH}$  are 23.7V and 229 ohms. Finally to obtain the voltage across the load  $R_L$ , we will put all the things together;  $V_{TH}$ ,  $R_{TH}$  and measure the voltage across AB.


[Refer Slide Time: 42:56]

### THEVENIN'S THEOREM

- Now we have simplified our Thevenin Equivalent circuit, reconnect the load,  $R_L$  to terminals A and B. We now have the circuit on the right. Now, calculate the load voltage.

The equation for  $V_L$  is:


$$V_L = V_{TH} * \frac{R_L}{R_{TH} + R_L}$$

$$V_L = 23.7V * \frac{150}{150 + 229} = V_L = 9.38V$$


$V_L$  the load voltage is equal to  $V_{TH}$  which is 23.7V multiplied by the potential divider  $R_L$  divided by  $R_{TH}+R_L$  and when you do the simplification, it is around 9.38V. We can actually put the circuit on a breadboard and measure once again as we have done in the previous case. We have taken two examples; one a very simple example, another one slightly more complicated with two sources and multiple resistors and we have seen how the equivalent Thevenin's circuit can be obtained for this complicated circuit. This is the final circuit with the  $V_{TH}$  and  $R_{TH}$  shown.


We will move on to the next theorem which is Norton's theorem which is a dual of Thevenin's theorem. Only difference is you make all the complicated circuits of the network that you have got by replacing it with a current source instead of a voltage. In the case of Thevenin you replaced it with the voltage source. In the case of Norton's you replace it with an equivalent current source and there will also be equivalent Norton's resistance just as you have a Thevenin's resistance. I have shown on the screen any circuit with several DC sources and linear resistances. It can be simplified with a single current source  $I_N$  corresponding to Norton's current source and a resistance  $R_N$  which in this case is connected in parallel. Therefore we look at it as conductance  $G_N$  if you want to consider.

[Refer Slide Time: 44:35]

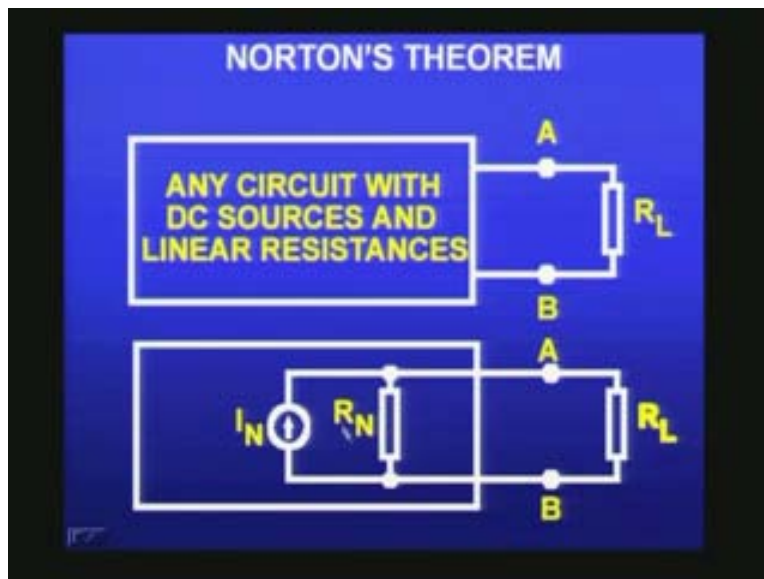

$R_N$  is the resistance value of this parallel resistance and this  $R_L$  is anyway there. The problem now is how to get  $I_N$  and  $R_N$  by measurement and by calculation. I take a very similar example as we did in the previous case with three resistors  $R_1$ ,  $R_2$ ,  $R_3$  and one current source  $IS_1$  to start with.

[Refer Slide Time: 45:00]

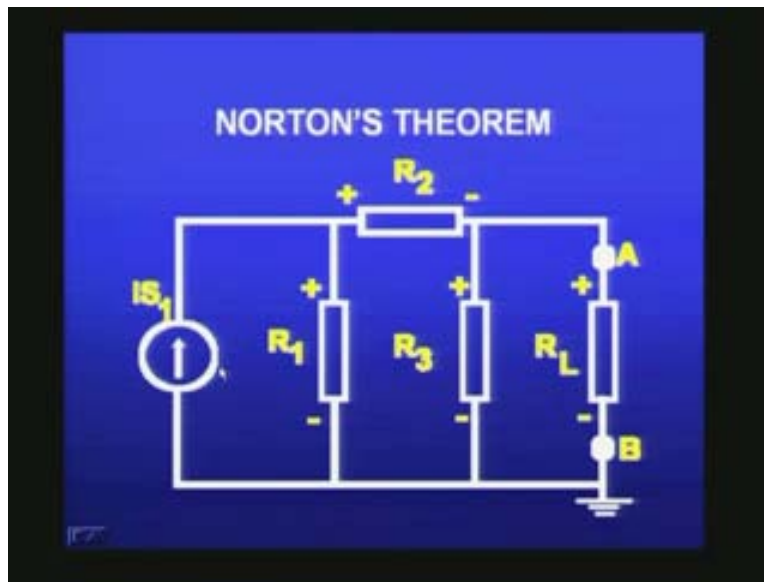

You have  $R_L$  here connected between the terminals A and B. How do we apply Norton's theorem and obtain the equivalent Norton's circuit.

[Refer Slide Time: 45:11]

The slide, titled "NORTON'S THEOREM", contains the following text: "Consider the circuit above. Norton's Theorem states that the current in any conductance or resistor connected to a network is the same if the conductance or resistance was connected to a current source where:"

What do we do? In this case if you want to measure the equivalent Norton's current source all that you have to do is remove the load resistance and connect it with a short and measure the short circuit current. Therefore what we have to do is remove  $R_L$  and connect a current meter in its place. The current meter will measure the current flowing through that terminal now. Because there is no resistance it is called a short circuit. Current meters are assumed to have zero resistance and therefore what you measure is the short circuit current across the load terminal and that gives you the Norton's current. In


the other case, in the Thevenin's case you will measure the open circuit voltage across the load terminal after removing the  $R_L$ . Here you remove  $R_L$ , connect it by a short and measure the current flowing through that short and that is the Norton's equivalent current source. If you want to measure the resistance all that you have to do is open circuit  $R_L$ . Remove  $R_L$  and measure the resistance across the terminals. That means  $R_N$  is equal to Thevenin's resistance,  $R_{TH}$ . Both are equal.  $R_{TH}$  and  $R_N$  are equivalent because method of measurement is also the same.

In this circuit I have short circuited the load. I have removed the load and connect it with a short wire. We have to find out the current here. Because I have shorted here this  $R_3$  is parallel to  $R_L$ . Because I have got a short here  $R_3$  will have no current at all.

[Refer Slide Time: 47:11]

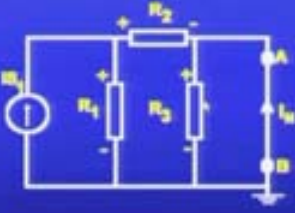**NORTON'S THEOREM**

- Since the load terminal is shorted, no current flows through  $R_3$ .
- $I_N$  is  $I_{R_2}$ , the current flowing through  $R_2$ . This current may be calculated using the current divider theorem:



$$(I_{S1} R_1) R_2 = I_N R_2$$

$$I_N = I_{S1} \cdot \frac{R_1}{R_1 + R_2}$$


All the current will go through the zero resistance path rather than the  $R_3$  and therefore  $R_3$  is not to be considered at all. Because  $R_3$  is not effectively in the circuit you find  $I_{S1}$ , the Norton's current source is actually dividing here into two current components; one here and one here. The parallel resistors divide current and that is what we see here. I have written the equation here and so you can calculate the short circuit  $I_N$  which is actually the Norton's current source is obtained from the  $I_{S1}$ , the source multiplied by  $R_1$  divided by  $R_1 + R_2$ . This is the equivalent Norton's current. If this is called  $I_N$ , this current will be  $I_{S1} - I_N$ . Whatever is the difference that will be flowing here multiplied by  $R_1$  the voltage across this should be equal to the voltage across  $R_2$  and  $R_2$  is  $I_N$  multiplied by  $R_2$ , that is the voltage across  $R_2$ . From this simplification you get  $I_N$  is equal to  $I_{S1}$  into  $R_1$  divided by  $R_1 + R_2$  by using the current divider theorem if you wish to remember that. Parallel resistors divide current. So we have now got Norton's equivalent current and we must measure Norton's equivalent resistance or conductance. For that what we do? We open circuit all current sources and short all voltage sources. We do not have any voltage sources in the circuit and measure the resistance across the terminal  $R_L$  after  $R_L$  is removed, A B.

[Refer Slide Time: 48:55]
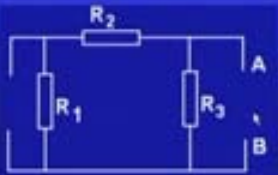
### NORTON'S THEOREM

We now have the Norton Equivalent Current, and we must determine the Norton Equivalent resistance (or conductance). To accomplish this we:

- Open all current sources retaining any source resistance
- Short all voltage sources while retaining any source resistance.



The diagram shows a circuit with three resistors: R<sub>1</sub>, R<sub>2</sub>, and R<sub>3</sub>. R<sub>1</sub> is on the left vertical branch. R<sub>2</sub> is on the top horizontal branch. R<sub>3</sub> is on the right vertical branch. The right terminals are labeled A and B.

This is equivalent to the earlier Thevenin's consideration. That is what we have done now. We can see R<sub>1</sub> R<sub>2</sub> are coming in series and it is parallel with R<sub>3</sub>.

[Refer Slide Time: 47:11]

### NORTON'S THEOREM

We can measure this resistance in the laboratory with an ohmmeter by replacing the source with an open, removing the load resistance, measuring the resistance at the terminals.

The equation for R<sub>N</sub> is:

$$R_N = \frac{R_3 * (R_1 + R_2)}{R_1 + R_2 + R_3}$$

The equivalent resistance therefore will be R<sub>3</sub> multiplied by R<sub>1</sub> R<sub>2</sub>. They are coming in series therefore together I should take them, divided by R<sub>1</sub>+R<sub>2</sub>+R<sub>3</sub>. This is the equivalent Norton's resistance. We have determined Norton's resistance, Norton's current source and therefore we can put the R<sub>L</sub> and complete the whole circuit. We can calculate the load current when R<sub>L</sub> is also in place.

[Refer Slide Time: 49:50]

**NORTON'S THEOREM**

Now, calculate the load current. The equation for  $I_L$  is:

$$I_L = I_N \cdot \frac{R_N}{R_N + R_L}$$

OR

$$I_L = I_N \cdot \frac{G_L}{G_N + G_L}$$

That can again be obtained by the current division.  $I_L$  is actually coming from  $I_N$  through resistances. Two resistances is coming in parallel  $R_N$  and  $R_L$  and therefore  $I_L$  is  $I_N$  into  $R_N$  divided by  $R_N+R_L$  by the current division theorem or  $I_L$  is  $I_N$  into  $G_L$  by  $G_N+G_L$  which is using the conductance, the reciprocal of the resistances.

We will take an example which will perhaps illustrate this very simply.

[Refer Slide Time: 47:11]

**NORTON'S THEOREM**

For example let us find the load current of the given problem using Norton's theorem. Where in this problem the following datas are given:  
 $R_1 = 270\Omega$  ;  $R_3 = 100\Omega$  ;  $I_{S1} = 10\text{mA}$  ;  $R_2 = 220\Omega$  ;  $R_L = 100\Omega$

Using the relation

$$I_N = I_{S1} \cdot \frac{R_1}{R_1 + R_2}$$

I have taken  $R_1$  to be 270 ohms,  $R_2$  is 220 ohms,  $R_3$  is 100 ohms and  $I_{S1}$  is 10 milliamperes.  $I_N$  we know is  $I_{S1}$  into  $R_1$  by  $R_1+R_2$ . If you substitute the values 10



milliamperes multiplied by 270 divided by 270 ohms + 220 ohms gives me an  $I_N$  of 5.5 milliamperes. This will be the short circuit current across the terminals of the circuit where  $R_L$  was originally. We have to find out  $R_N$ .

[Refer Slide Time: 51:02]

**NORTON'S THEOREM**

We find the value of  $I_N$  to be

$$I_N = 10 \text{ mA} \cdot \frac{270 \Omega}{270 \Omega + 220 \Omega}$$

$$I_N = 5.5 \text{ mA}$$

Then we have to find the value of  $R_N$  using the formula :

$$R_N = \frac{R_3 \cdot (R_1 + R_2)}{R_1 + R_2 + R_3}$$


$$R_N = \frac{100 \Omega \cdot (270 \Omega + 220 \Omega)}{270 \Omega + 220 \Omega + 100 \Omega} = 83.4 \Omega$$

For finding  $R_N$ , you know  $R_3$  and  $R_1+R_2$  together in series are coming in parallel. Therefore  $R_3$  multiplied  $R_1$  plus  $R_2$  divided by  $R_1$  plus  $R_2$  plus  $R_3$  and if you substitute the values of resistances we have taken in example you get an equivalent resistance of about 83 ohms. I have now got the equivalent Norton's circuit. The Norton's equivalent current is 5.5 milliamperes, we have calculated.

[Refer Slide Time: 51:34]

**NORTON'S THEOREM**

$I_N = 5.5 \text{ mA}$   
 $R_N = 83.4 \Omega$   
 $R_L = 100 \Omega$



Now we have to calculate the load current and load voltage.

The Norton's resistance is 83.4 ohms that is connected in parallel to the current source and  $R_L$  is also connected in parallel to the entire circuit.  $R_L$  is 100 ohms. We have to calculate the load current, load voltage, etc.

[Refer Slide Time: 51:52]

**NORTON'S THEOREM**


Now using the values of  $I_N$  and  $R_N$  we have to find the load current. The formula is

$$I_L = I_N * \frac{R_N}{R_N + R_L}$$
$$I_L = 5.5\text{mA} * \frac{83.4 \Omega}{83.4 \Omega + 100 \Omega}$$
$$I_L = 2.50 \text{ mA}$$

Thus the load current value is obtained using Norton's theorem.

Again by using the current division  $I_L$  is equal to  $I_N$  into  $R_N$  by  $R_N + R_L$ . We know all the values 5.5 milliamperes is Norton's current multiplied by 83.4 which is the Norton's equivalent resistance divided by 83.4 plus  $R_L$  which is 100 ohms here and the current is 2.5mA. Thus the load current value is obtained using Norton's theorem. This is the actual final circuit where I have shown the value of the Norton's current source 5.5mA, Norton's equivalent resistance it is 83.4 ohms and the load resistance  $R_L$  and  $I_L$  flowing through the load is 2.5mA. Out of 5, 2.5mA flows through that; rest of the 3mA will flow through that. So if 2.5mA is flowing through the load resistance  $R_L$  you can also calculate the voltage across the load which is nothing but the product of these two and the product is about 2.5 into 100 which is 2500mV. Because it is milliamperes it is equivalent to 0.25V.


[Refer Slide Time: 53:09]

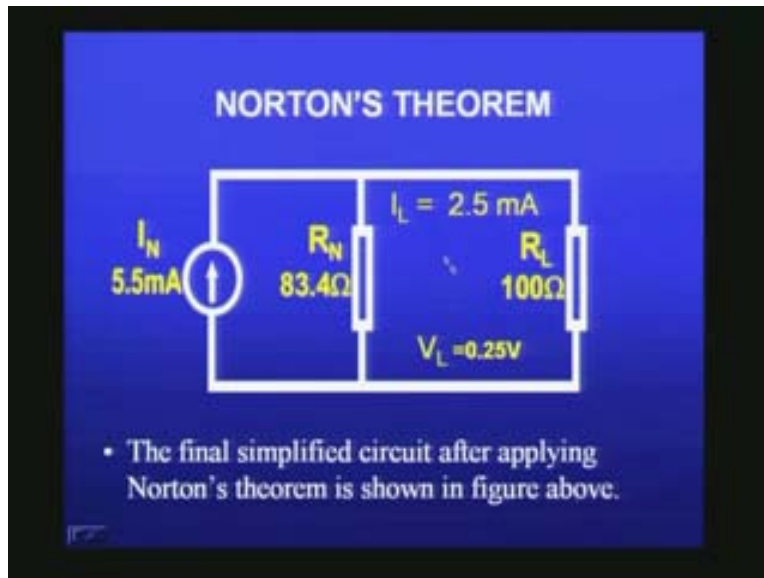

So you can calculate the voltage across the load, the current through the load and all information regarding the circuit. It is very easy by using Norton's theorem.

Let me quickly go through the simulation for this. Here I have the same circuit. You have different resistances. 270 ohms; here you have 220 ohms; here you have 100 ohms  $R_3$ ; this is your  $R_L$  100 ohms. You have a multimeter, you have a current source here and the circuit is also shown here.


[Refer Slide Time: 53:50]

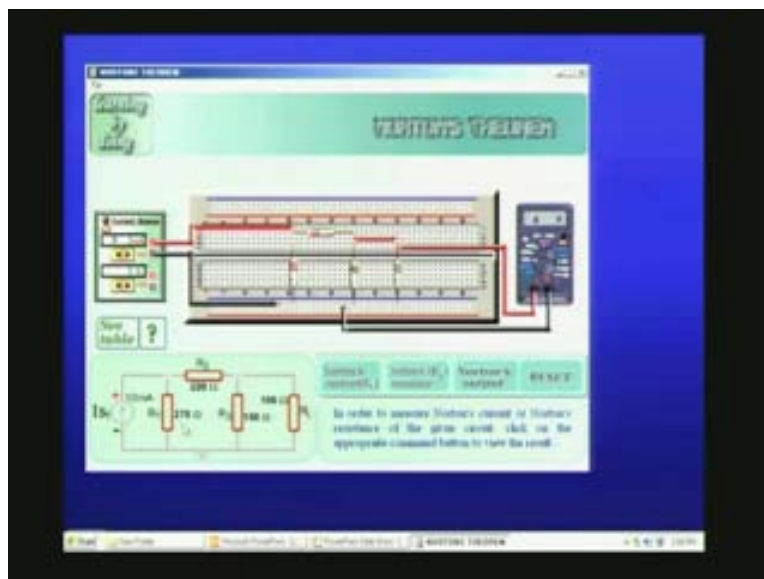

We have to measure the Norton's current which is the short circuit current and the Norton's resistance. We will do that in the simulation. To measure Norton's current we have to short the load. Therefore we remove the load. Click here, the load is removed


and in its place I have got the multimeter in the milliampere range, in the current range and I have the current source here. Let us switch on the current source and the multimeter.

[Refer Slide Time: 54:24]

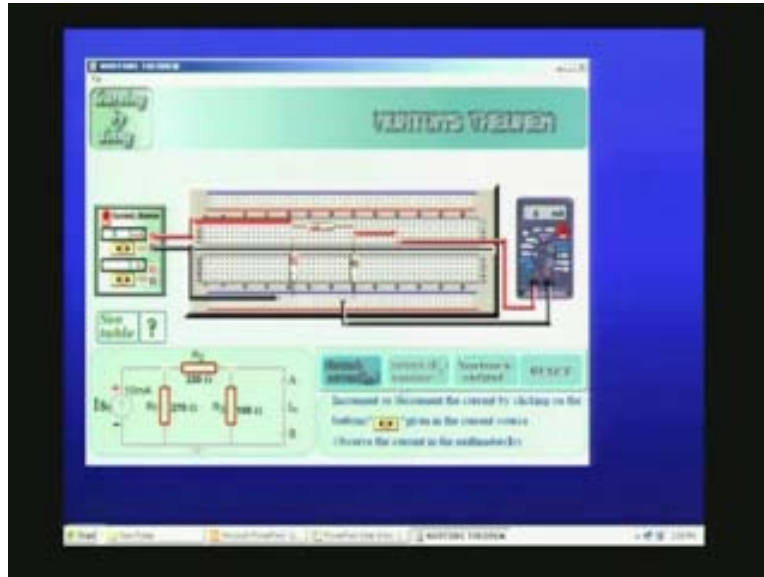


Increase the current to 10mA because that is the current value  $I_{S1}$ . Now I have 10mA current and you can see the short circuit current is 5.51 as measured by multimeter. If you want to look at the calculation it is shown here.  $I_N$  is  $I_{S1}$  into  $R_1$  by  $R_1 + R_2$  which is 5.51, which we already calculated. We have obtained the Norton's equivalent current source. Now we have to obtain the Norton's equivalent resistance. For that if I have current source I should open circuit. Therefore when I click here the connection to the current source is removed. That means it is open circuit here and I just have the three resistors and I should make use of the multimeter in resistance mode and measure the resistance. Let me switch on the multimeter it comes in ohms range and it is measuring 83.4 ohms. So this is the Norton's equivalent resistance. If you want to look at the value you can see.  $R_3$  coming in parallel to  $R_1$  and  $R_2$  and therefore the equivalent resistance is 83.4 ohms. We have calculated the Norton's current; we have calculated the Norton's equivalent resistance. Then we have to get the complete circuit with the load connected. This is the Norton's equivalent resistance 83.4. I will set here the Norton's current and I will measure the current through the load resistance. You can see the circuit here. Now I will switch the current source, I will switch the multimeter and you would find if I connect here I get 5.51milliampere as a source and the series current measured by this is 2.5mA which is the value we obtained previously. The calculation can be seen in the screen 5.51 multiplied by 83.4 divided by 83.4+100 ohms gives me 2.5mA. That is what we got. So by simulation we were able to do the Norton's equivalent circuit. This is the final circuit that we have got here.

[Refer Slide Time: 56:50]

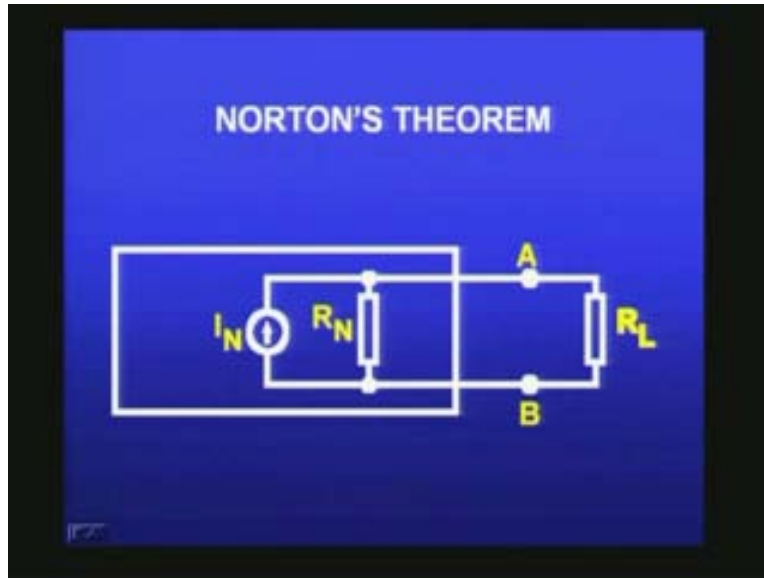


The entire block is removed and replaced by one Norton's source and one Norton's resistance and they are connected in parallel to  $R_L$ , the load resistance. We have already mentioned that the Thevenin's and Norton's are the dual of each other.

[Refer Slide Time: 57:08]

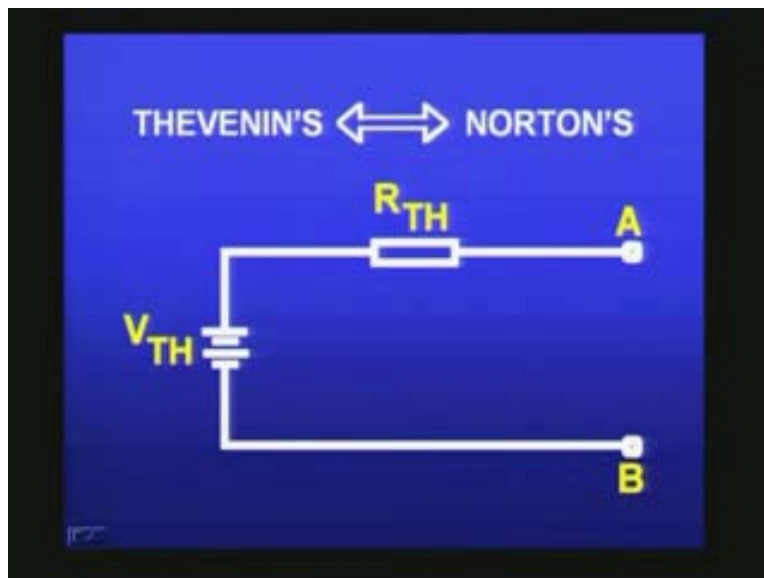


In Thevenin's we have got the voltage source,  $V_{TH}$  and a series resistance  $R_{TH}$ . In Norton's you have got a current source  $I_N$  and a resistance  $R_N$  in parallel.

[Refer Slide Time: 57:19]

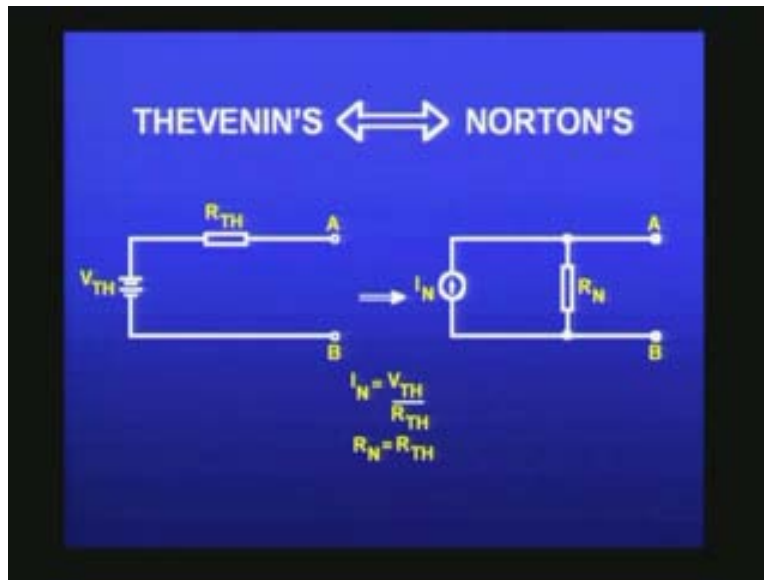

Now you can see how to convert from Thevenin's to Norton's and from Norton's to Thevenin's. Then you can see the relation between the Thevenin's and Norton's values.  $I_N$  is nothing but  $V_{TH}$  by  $R_{TH}$  and  $R_N$  is equal to  $R_{TH}$ . That I already mentioned to you. So the two circuits are equivalent. Similarly if I want  $V_{TH}$  if I know  $I_N$  and  $R_N$  I should multiply  $I_N$  by  $R_N$ . That will give me  $V_{TH}$  and  $R_{TH}$  is anyway equal to  $R_N$ . Therefore you can see the circuits are all equivalent.

[Refer Slide Time: 57:55]

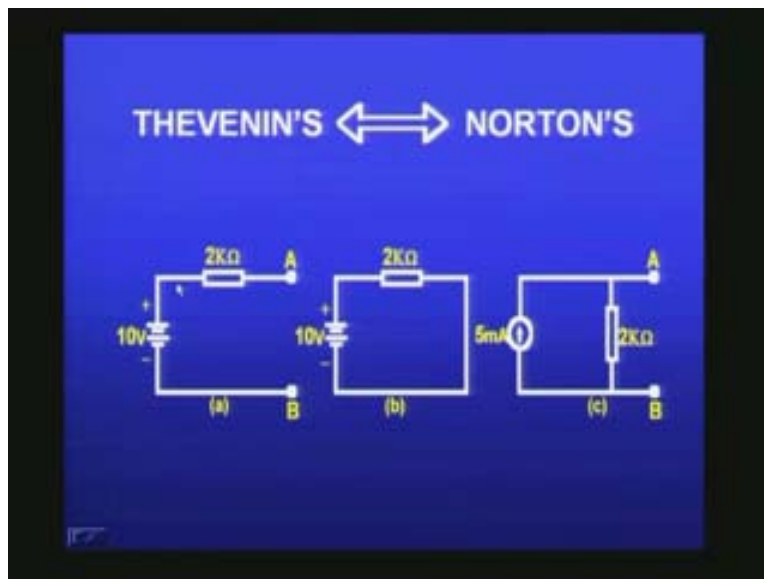

In our case for example if I have 10V and 2K then if I want the corresponding Norton's current I should short circuit and measure;  $10V$  by  $2K$  which is around 5mA.

So 5mA is the Norton's current and 2K is the Thevenin's resistance. That is what I have shown here. So Norton's and Thevenin's can be easily converted from one to the other and therefore both the theorems are very useful in solving different problems in networks.

We will conclude this lecture at this stage and we have seen two important theorems in this lecture. One is the Thevenin's theorem and the other one is Norton's theorem. In the next lecture we will look at one of the important passive devices namely semiconductor diode and its different types and how it will be very useful in many applications in electronics. Thank you very much.