

PSG COLLEGE OF ARTS & SCIENCE  
(AUTONOMOUS)  
BSc DEGREE EXAMINATION DECEMBER 2018  
(Third Semester)

Branch - MATHEMATICS WITH COMPUTER APPLICATIONS

DIGITAL ELECTRONICS

Time : Three Hours

Maximum : 75 Marks

SECTION-A (20 Marks)

Answer ALL questions

ALL questions carry EQUAL marks (10x2 = 20)

- 1 Write the digital signals.
- 2 Define frequency.
- 3 Draw the OR gate with truth table.
- 4 Write the commutative law.
- 5 Draw the truth table of binary subtraction.
- 6 Draw the diagram of half adder.
- 7 What is meant by flip flop?
- 8 Write short note on ring counter.
- 9 What are types of D/A converter?
- 10 Define Accuracy of A/D converters.

SECTION - B (25 Marks!)

Answer ALL Questions

ALL Questions Carry EQUAL Marks (5x5 = 25)

- 11 a Write short notes on ASCII codes with example.

**OR**

b Convert  $(34.562)_{10} = ( )_2$ .

- 12 a Explain the operation of AND gate with pin diagram.

**OR**

b Discuss about the duality theorem.

- 13 a Describe the full subtractor with neat diagram.

**OR**

b With neat diagram, explain the demultiplexer.

- 14 a Explain about JK flip flop with necessary diagram.

**OR**

b What is meant by shift register? Explain the serial in serial out shift register.

- 15 a Write the resolution of D/A convertor.

**OR**

b Define A/D convertor and explain the simultaneous conversion method.

SECTION - C (30 Marks)

Answer any THREE Questions

ALL Questions Carry EQUAL Marks (3x10 = 30)

- 16 Write the following (i) GRAY Code (ii) Parity Code.
- 17 Explain the Demorgan's theorem.
- 18 Explain the decoder with neat diagram.
- 19 With neat diagram, explain the synchronous counter.