

PSG COLLEGE OF ARTS & SCIENCE  
(AUTONOMOUS)  
BSc DEGREE EXAMINATION MAY 2017  
(Third Semester)

Branch - ELECTRONICS

**ELECTRONIC CIRCUITS**

Time : Three Hours

Maximum : 75 Marks

**SECTION-A (20 Marks)**

Answer ALL questions

ALL questions carry EQUAL marks (10 x 2 = 20)

- 1 What is called filter?
- 2 Draw the circuit for  $n$  filter.
- 3 Write any two characteristics of CC amplifier. "
- 4 Write any two types of transistor biasing.
- 5 Draw the input and output signal for class B amplifiers.
- 6 Write any two difference between class A and class C amplifier.
- 7 Draw the block diagram of feedback.
- 8 Define negative feedback.
- 9 Draw the block diagram for oscillator.
- 10 Write any two difference between Hartley oscillator and colpits oscillator.

**SECTION - B (25 Marks)**

Answer ALL Questions

ALL Questions Carry EQUAL Marks (5 x 5 = 25)

- 11 a With a circuit diagram the function of clipping circuit.  
OR  
b Explain the function inductor filter.
- 12 a Explain the method of transistor biasing.  
OR  
b Explain the operations of multistage amplifier.
- 13 a Write a short note about class C amplifier.  
OR  
b Explain the stage efficiency and current drain of power amplifiers.
- 14 a Explain the effects of negative feedback on gain stability and bandwidth.  
OR  
b Explain the operation of current shunt feedback.
- 15 a Explain the working of Hartley oscillator.  
OR  
b Explain about Schmitt trigger.

**SECTION - C (30 Marks!)**

Answer any THREE Questions

ALL Questions Carry EQUAL Marks (3 x 10 = 30)

- 16 Draw a circuit diagram and explain the function of bridge rectifier.
- 17 Explain in detail the frequency response of RC coupled amplifier.
- 18 Describe the function of class AB amplifier.
- 19 With a neat circuit diagram explain the function of voltage series feedback and current series feedback.
- 20 Briefly explain the function of phase shift oscillator. '