

BSc DEGREE EXAMINATION MAY 2017
(Third Semester)

Branch- **ELECTRONICS**

DIGITAL PRINCIPLES & APPLICATIONS

Time : Three Hours

Maximum : 75 Marks

SECTION-A (20 Marks)

Answer **ALL** questions

ALL questions carry **EQUAL** marks (10x2 = 20)

- 1 What is the base of following number systems?
i) Binary ii) Hexadecimal
- 2 Find the Gray code equivalent for the following binary codes.
i) 11001101 ii) 10101010
- 3 Draw the logic symbol and truth table of EX-NOR gate.
- 4 i) $A + A = ?$ ii) $A \cdot 1 = ?$ *
- 5 What is a multiplexer?
- 6 Perform the following addition $101101 + 111100$.
- 7 What is a counter?
- 8 Draw the truth table of D- flipflop.
- 9 Mention the major advantage and disadvantage of successive approximation ADC.
- 10 Define the accuracy of a DAC.

SECTION - B (25 Marks!)

Answer **ALL** Questions .

ALL Questions Carry **EQUAL** Marks (5x5 = 25)

- 11 a Explain decimal to hexadecimal conversion with an example.
OR
b Explain BCD and Excess-3 codes with suitable examples.
- 12 a Draw the logic symbol and truth tables for the following logic gates.
i) OR ii) EX.OR iii) NOR iv) AND v) NAND.
OR
b State and prove DeMorgan's theorem.
- 13 a Explain the function of a half subtractor.
OR
b Draw the logic diagram of a 1- to - 4 demultiplexer and explain its functions.
- 14 a Describe the functionality of a D-flipflop.
OR
b Explain the working of a 4-bit ring counter.
- 15 a Draw the circuit of a 4-bit weighted resistor D/A converter and explain its working.
OR
b Explain simultaneous A/D conversion method.

SECTION - C (30 Marks)

Answer any **THREE** Questions

ALL Questions Carry **EQUAL** Marks (3x10 = 30)

- 16 Perform the following conversions:
a) $(349)_{10} =$ b) $(ACB4)_{16} =$ c) $(1476)_8 =$ d) $(1011101101)_2 =$
- 17 Minimize the following logic function using k-map
 $f(A,B,C,D) = \sum m(2, 3, 7, 10, 11, 14) + \sum d(1, 5, 15)$
- 18 Perform the following subtractions using 2's complement arithmetic,
a) $(34)_{10} - (29)_{10}$ b) $(41)_{10} - (53)_{10}$
- 19 Explain the operation of a 4-bit binary ripple counter.
- 20 Draw the logic diagram of a dual slope A/D converter and explain its operation.