

PSG COLLEGE OF ARTS & SCIENCE
(AUTONOMOUS)
BSc DEGREE EXAMINATION DECEMBER 2017
(Fourth Semester)

Branch - ELECTRONICS

DIGITAL AND LINEARS IC'S

Time : Three Hours

Maximum : 75 Marks

SECTION-A (20 Marks)

Answer **ALL** questions

ALL questions carry **EQUAL** marks (10 x 2 = 20)

- 1 Write use of insulating layer in IC fabrication.
- 2 Expand LSI and VLSI.
- 3 What is Totem pole output?
- 4 What is differential amplifier?
- 5 Define bandwidth.
- 6 What is differentiator and integrator?
- 7 Define comparator.
- 8 Mention two applications of comparator.
- 9 What is the operating voltage and drive load current timer 555?
- 10 Write two applications of PLL.

SECTION - B (25 Marks)

Answer **ALL** Questions

ALL Questions Carry **EQUAL** Marks (5 x 5 = 25)

- 11 a Explain the epitaxial growth method.
OR
b Explain Silicon wafer preparation methods.
- 12 a Explain the integrated injection logic.
OR
b Explain the operation of DTL basic NAND gate.
- 13 a Explain the working of Op-amp Adder circuit.
OR
b Explain the working of Op-amp integrator circuit.
- 14 a Explain the working of sine wave generator using Op-amp.
OR
b Explain Op-amp as comparator.
- 15 a Explain 555 in monostable mode.
OR
b Explain the operation of PWM circuit with waveform.

SECTION - C (30 Marks)

Answer any **THREE** Questions

ALL Questions Carry **EQUAL** Marks (3 x 10 = 30)

- 16 Explain fabrication of transistors and resistors in monolithic IC with proper sketch.
- 17 Explain the open collector TTL NAND gate circuit with diagram.
- 18 Explain the working of instrumental amplifier and derive its formula for gain.
- 19 Explain the function of Monostable multivibrator with suitable waveforms.

O A Uvnloin fiirtirmal hlock diagram of IC555.