

PSG COLLEGE OF ARTS & SCIENCE
(AUTONOMOUS)

MSc DEGREE EXAMINATION MAY 2024
(First Semester)

Branch - CHEMISTRY

BASIC ELECTRONICS FOR CHEMISTS

Time: Three Hours

Maximum: 75 Marks

SECTION-A (10 Marks)

Answer ALL questions

ALL questions carry EQUAL marks (10 × 1 = 10)

- 1 Tell pentavalent impurity has Valence electrons.
a) 3 b) 5 c) 4 d) 6
- 2 Tell n-type semiconductor is
a) Positively charged b) Negatively charged
c) Electrically neutral d) None of the above
- 3 Tell monostable multivibrator has $R = 120k\Omega$ and the time delay $T = 1000ms$, calculate the value of C?
a) $0.9\mu F$ b) $1.32\mu F$ c) $7.5\mu F$ d) $2.49\mu F$
- 4 Which among the following can be used to detect the missing heart beat?
a) Monostable multivibrator b) Astable multivibrator
c) Schmitt trigger d) None of the mentioned
- 5 Which of the following options comes under the non – saturated logic family in Digital Electronics?
a) Emitter – coupled Logic b) High-Threshold Logic
c) Integrated – injection Logic d) Diode – Transistor Logic
- 6 What is a switching function that has more than one output called in Digital Electronics?
a) Multi-gate function b) Multi-output function
c) Multiple-gate function d) Multiple-output function
- 7 What is the advantage of using flash type A/D converter?
a) High speed conversion b) Low speed conversion
c) Nominal speed conversion d) None of the mentioned
- 8 Drawback of counter type A/D converter.
a) Counter clears automatically b) More complex
c) High conversion time d) Low speed
- 9 Which technique separates charged particles using electric field?
a) Hydrolysis b) Electrophoresis
c) Protein synthesis d) Protein denaturing
- 10 Electrophoresis was developed by
a) Tswett b) Tsvedberg c) Tiselius d) Sanger

Cont...

SECTION - B (35 Marks)Answer **ALL** questions**ALL** questions carry **EQUAL** Marks (5 × 7 = 35)

- 11.a. Explain about Zener voltage regulator.
(OR)
- 11.b. Describe short note on Semiconductor devices.
- 12.a. Show the function Inverting amplifier.
(OR)
- 12.b. Explain about monostable multivibrator.
- 13.a. Describe the JK Master and Slave Flipflop.
(OR)
- 13.b. Sketch the NAND and NOR gates with Truth table.
- 14.a. Sketch The Binary up/down counter.
(OR)
- 14.b. Show the Ring Counter.
- 15.a. Explain about Conductivity bridge.
(OR)
- 15.b. Bring out on Spectrophotometer.

SECTION -C (30 Marks)Answer **ANY THREE** questions**ALL** questions carry **EQUAL** Marks (3 × 10 = 30)

- 16 Enumerate the feature of intrinsic and Extrinsic semiconductor .
- 17 Identify Point out the integrator and differentiator with neat diagram.
- 18 Compare with JK Flipflop and master slave Flipflop.
- 19 Justify the D/A and A/D Converter.
- 20 Classify about pH Meter.

Z-Z-Z

END