

PSG COLLEGE OF ARTS & SCIENCE
(AUTONOMOUS)
PG DEGREE EXAMINATION DECEMBER 2023
(Third Semester)
TRANS DISCIPLINARY COURSE
(Common to PG Programmes)

BASIC ELECTRONICS

Time: Three Hours

Maximum: 50 Marks

SECTION-A (5 Marks)

Answer ALL questions

ALL questions carry EQUAL marks

(5 x 1 = 5)

- 1 Identify the answer for 100 K Ω resistor colour code -----.
(i) Brown black red (ii) Brown black yellow
(iii) Brown black green (iv) Brown black orange
- 2 Choose the following for Ohms law parameter V= -----.
(i) IR (ii) IP
(iii) RL (iv) RC
- 3 Match the negatively charged particle -----.
(i) proton (ii) neutron
(iii) electron (iv) atom
- 4 Which is the correct answer for gray to binary conversion of 1011-----.
(i) 1101 (ii) 0101
(iii) 1001 (iv) 0111
- 5 Identify the complement gate -----.
(i) AND (ii) OR
(iii) NAND (iv) NOT

SECTION - B (15 Marks)

Answer ALL Questions

ALL Questions Carry EQUAL Marks

(5 x 3 = 15)

- 6 a State voltage definition.
OR
b Classify power and energy.
- 7 a Justify Ohms law.
OR
b Illustrate the current divider rule.
- 8 a Sketch the structure of the atom.
OR
b Explain the energy band.
- 9 a Solve the given problem to find Excess 3 code 2 4.
OR
b Apply the Commutative law.
- 10 a Analyze the NOR gate operation with its truth table.
OR
b Discuss the associative law.

Cont...

SECTION -C (30 Marks)

Answer ALL questions

ALL questions carry EQUAL Marks

(5 x 6 = 30)

- 11 a Criticize resistor connected in series and parallel.
OR
b Assess the inductor connected in series and parallel.
- 12 a Enumerate the Kirchhoff's voltage law.
OR
b Predict the maximum power transfer theorem.
- 13 a Criticize the V I Characteristics of zener diode.
OR
b Enumerate the insulator.
- 14 a Predict the A9F5 and 72DE into octal number.
OR
b 6723 and 5146 solve the octal number into binary.
- 15 a Elucidate Demorgan's theorem.
OR
b Assess the EX-NOR gate with its truth table.

Z-Z-Z

END