PSG COLLEGE OF ARTS & SCIENCE (AUTONOMOUS)

BSc DEGREE EXAMINATION MAY 2025

(Third Semester)

Branch - INFORMATION TECHNOLOGY

FUNDAMENTALS OF DIGITAL COMPUTERS

Time: Three Hours Maximum: 75 Marks

SECTION-A (10 Marks)

Answer **ALL** questions

ALL questions carry EQUAL marks

 $(10 \times 1 = 10)$

Madel-	O4'	ALL questions carry EQUAL marks (10	× 1 = 10	,
Module No.	Question No.	Question	K Level	CO
1	1	The representation of octal number (532.2)8 in decimal is a) (346.25)10 b) (532.864)10 c) (340.67)10 d) (531.668)10	K1	CO1
	2	2's complement of 11001011 is a) 01010111 b) 11010100 c) 00110101 d) 11100010	K2	CO1
2	3	DeMorgan's theorem states that a) (AB)' = A' + B' b) (A + B)' = A' * B c) A' + B' = A'B' d) (AB)' = A' + B	K1	CO2
	4	The expression Y=AB+BC+AC shows the operation. a) EX-OR b) SOP c) POS d) NOR	K2	CO2
3	5	Total number of inputs in a half adder is a) 2 b) 3 c) 4 d) 1	K1	CO3
	6	Which is the major functioning responsibility of the multiplexing combinational circuit? a) Decoding the binary information b) Generation of all minterms in an output function with ORgate c) Generation of selected path between multiple sources and a single destination d) Encoding of binary information	K2	CO3
4	7	A latch is an example of a a) Monostable multivibrator b) Astable multivibrator c) Bistable multivibrator d) 555 timer	K1	CO4
	8	The only difference between a combinational circuit and a flip-flop is that a) The flip-flop requires previous state b) The flip-flop requires next state c) The flip-flop requires a clock pulse d) The flip-flop depends on the past as well as present states	K2	CO4
5	9	The instruction used in a program for executing them is stored in the a) CPU b) Control Unit c) Memory d) Microprocessor	K1	CO5
	10	a) NAND and OR gates b) NOR and decoder c) Decoder and OR gates d) NAND and decoder	K2	CO5

Cont...

SECTION - B (35 Marks)

Answer ALL questions

ALL questions carry EQUAL Marks

 $(5 \times 7 = 35)$

Module No.	Question No.	Question	K Level	СО
1	11.a.	Explain the characteristics of octal and hexadecimal numbers.		
	(OR)			CO1
	11.b.	Describe compliments and its types with suitable example.		
**	12.a.	Analyse the working principles of canonical forms.	K4	CO2
2		. (OR)		
-	12.b.	Inspect the characteristics of AND, OR and NOT gates.		
	13.a.	Identify the working pattern of full adder with diagram.		
3	-	(OR)		CO3
•	13.b.	Develop the procedure to identify the internals of decoder with diagram.		
	14.a.	Construct the truth table for SR flip-flop and explain the table with circuit diagram.		
4		(OR)		CO4
	14.b.	Demonstrate the working principles of ripple counters.		
5	15.a.	Examine the hierarchy of memory.		
		(OR)		CO5
	15.b.	Analyse auxiliary memory with diagram.		

SECTION -C (30 Marks)

Answer ANY THREE questions

ALL questions carry EQUAL Marks

 $(3\times10=30)$

Module No.	Question No.	Question	K Level	СО
1	16	Analyse any two binary codes with suitable example.	K4	CO1
2	17	Examine the principles of k-map and don't care condition with suitable example.	K4	CO2
3	18	Inspect the functions of subtractors with example.	K4	CO3
4	19	Analyse shift register with neat diagram.	K4	CO4
5	20	Evaluate the working principles of cache memory.	K4	CO5