

PSG COLLEGE OF ARTS & SCIENCE (AUTONOMOUS)

MSc DEGREE EXAMINATION DECEMBER 2025
(First Semester)

Branch- APPLIED ELECTRONICS

POWER ELECTRONICS AND CONTROL SYSTEMS

Time: Three Hours

Maximum: 75 Marks

SECTION-A (10 Marks)

Answer ALL questions

ALL questions carry **EQUAL** marks

$$(10 \times 1 = 10)$$

Cont...

SECTION - B (35 Marks)

Answer ALL questions

ALL questions carry EQUAL Marks

(5 × 7 = 35)

Module No.	Question No.	Question	K Level	CO
1	11.a.	Describe the theory, construction, and working of an SCR with neat diagram. (OR)	K2	CO1
	11.b.	Illustrate the operation of PUT along with its typical applications.		
2	12.a.	Apply the concept of static switching to design and explain a single-phase AC static switch using SCRs. (OR)	K3	CO2
	12.b.	Explain the operation of a single-phase bidirectional AC voltage controller with inductive load.		
3	13.a.	Differentiate between Buck and Boost regulators in terms of circuit configuration, voltage conversion ratio, and practical applications. (OR)	K4	CO3
	13.b.	Analyze the differences between a three-phase half-wave controlled converter and a three-phase fully controlled converter.		
4	14.a.	Justify the need for a closed-loop control system over an open-loop system in terms of accuracy, stability, and disturbance rejection. (OR)	K5	CO4
	14.b.	Evaluate the role of Mason's Gain Formula in determining the overall transfer function of a system.		
5	15.a.	Propose a PID control scheme for a temperature control system. (OR)	K6	CO5
	15.b.	Explain the concept of stability in control systems with suitable examples.		

SECTION - C (30 Marks)

Answer ANY THREE questions

ALL questions carry EQUAL Marks

(3 × 10 = 30)

Module No.	Question No.	Question	K Level	CO
1	16	Describe about different TRIAC triggering circuits and their significance in power control.	K2	CO1
2	17	Explain the operation of a single-phase cycloconverter in both step-up and step-down modes.	K4	CO2
3	18	Analyze the working of a three-phase inverter. Compare its performance with that of a single-phase bridge inverter in terms of efficiency.	K4	CO3
4	19	Critically evaluate the Force-Voltage analogy for modeling mechanical systems.	K5	CO4
5	20	Design a PI controller for a second-order system to improve steady-state error while maintaining system stability.	K6	CO5