

**PSG COLLEGE OF ARTS & SCIENCE
(AUTONOMOUS)**

MSc DEGREE EXAMINATION DECEMBER 2025
(First Semester)

Branch- CHEMISTRY

ELECTRONICS FOR CHEMISTS

Time: Three Hours

Maximum: 75 Marks

SECTION-A (10 Marks)

Answer ALL questions

ALL questions carry **EQUAL** marks

$$(10 \times 1 = 10)$$

Cont...

SECTION - B (35 Marks)

Answer ALL questions

ALL questions carry EQUAL Marks $(5 \times 7 = 35)$

| Module No. | Question No. | Question | K Level | CO |
|------------|--------------|---|---------|-----|
| 1 | 11.a. | Name the different configurations of a transistor and state their features. (OR) | K1 | CO1 |
| | 11.b. | List the applications of Zener diode as a voltage regulator. Explain its working principle with diagram. | | |
| 2 | 12.a. | Compare the operation and transfer functions of an ideal op-amp integrator and an ideal op-amp differentiator. (OR) | K2 | CO2 |
| | 12.b. | Describe the basic function of an Analog-to-Digital Converter (ADC) and a Digital-to-Analog Converter (DAC). | | |
| 3 | 13.a. | Illustrate the effect of noise on measurement signals with a neat sketch. (OR) | K3 | CO3 |
| | 13.b. | Ascertain the dependability requirements of an instrumentation system with examples. | | |
| 4 | 14.a. | Differentiate between pneumatic actuators and hydraulic actuators with examples of their uses. (OR) | K4 | CO4 |
| | 14.b. | Explain the basic structure and functions of a control system with neat diagrams. | | |
| 5 | 15.a. | Interpret the working principle of a pH meter with diagram. (OR) | K5 | CO5 |
| | 15.b. | Conclude the significance of auto titrators in reducing manual errors in titration processes. | | |

SECTION -C (30 Marks)

Answer ANY THREE questions

ALL questions carry EQUAL Marks $(3 \times 10 = 30)$

| Module No. | Question No. | Question | K Level | CO |
|------------|--------------|--|---------|-----|
| 1 | 16 | Describe in detail Kirchoff's Laws with examples and circuit diagrams. | K2 | CO1 |
| 2 | 17 | Construct and illustrate the working of a summing amplifier. Classify its applications in analog computing. | K3 | CO3 |
| 3 | 18 | Classify temperature sensors and distinguish their working principles. | K3 | CO3 |
| 4 | 19 | Explain the functions and applications of directional control valves and flow control valves in control engineering. | K4 | CO4 |
| 5 | 20 | Interpret the working of an electronic balance by explaining its construction and key components. | K5 | CO5 |