

PSG COLLEGE OF ARTS & SCIENCE (AUTONOMOUS)

BSc DEGREE EXAMINATION DECEMBER 2025
(Third Semester)

Branch - ELECTRONICS

DIGITAL AND LINEAR IC's

Time: Three Hours

Maximum: 75 Marks

SECTION-A (10 Marks)

Answer ALL questions

ALL questions carry **EQUAL** marks

$$(10 \times 1 = 10)$$

Cont.

SECTION - B (35 Marks)

Answer ALL questions

ALL questions carry EQUAL Marks

 $(5 \times 7 = 35)$

Module No.	Question No.	Question	K Level	CO
1	11.a.	Classify the function of epitaxial growth. (OR)	K2	CO1
	11.b.	Illustrate the method of the monolithic transistors.		
2	12.a.	Provide a detailed explanation of the function of RTL. (OR)	K2	CO2
	12.b.	Summarize the process of CMOS.		
3	13.a.	Examine the working principle of a non-inverting Amplifier. (OR)	K4	CO3
	13.b.	Discover the working function of the integrator.		
4	14.a.	Organize the role of the schmitt trigger. (OR)	K3	CO4
	14.b.	Identify and explain the concepts of the wien bridge oscillator.		
5	15.a.	Distinguish and explain the monostable mode and its application. (OR)	K4	CO4
	15.b.	Assume the operation of the digital Phase detector.		

SECTION -C (30 Marks)

Answer ANY THREE questions

ALL questions carry EQUAL Marks $(3 \times 10 = 30)$

Module No.	Question No.	Question	K Level	CO
1	16	Interpret the operation of the photolithography.	K1	CO1
2	17	Assess the working principle of TTL with a neat diagram.	K2	CO2
3	18	Identify the principles of instrumentation amplifier with their applications.	K3	CO3
4	19	Classify the operation of the astable multivibrator and its advantage and disadvantage.	K3	CO4
5	20	Explain the operation of the 8038 function generator with suitable examples.	K4	CO4