

**PSG COLLEGE OF ARTS & SCIENCE
(AUTONOMOUS)**

BSc DEGREE EXAMINATION DECEMBER 2025
(First Semester)

Branch - ELECTRONICS

ELECTRIC CIRCUITS

Time: Three Hours

Maximum: 75 Marks

SECTION-A (10 Marks)

Answer **ALL** questions

ALL questions carry **EQUAL** marks

$$(10 \times 1 = 10)$$

Cont...

SECTION - B (35 Marks)

Answer ALL questions

ALL questions carry EQUAL Marks (5 × 7 = 35).

Module No.	Question No.	Question	K Level	CO		
1	11.a.	Discuss the term power energy.	K2	CO1		
	(OR)					
	11.b.	Explain the principle of RLC circuits with diagrams.				
2	12.a.	Explain the super position theorem with examples.	K3	CO2		
	(OR)					
	12.b.	Describe the Norton's theorem.				
3	13.a.	Show and explain the sine wave equation.	K3	CO3		
	(OR)					
	13.b.	Construct a phasor diagram in detail.				
4	14.a.	Write the function of series resonance.	K4	CO4		
	(OR)					
	14.b.	Conclude the function of resonance frequency for a tank circuit.				
5	15.a.	Compare the single phase and 3- phase voltages.	K4	CO5		
	(OR)					
	15.b.	Explain the principle of Power measurements in 3-phase circuits.				

SECTION -C (30 Marks)

Answer ANY THREE questions

ALL questions carry EQUAL Marks (3 × 10 = 30)

Module No.	Question No.	Question	K Level	CO
1	16	Examine the Kirchhoff's law with diagrams.	K4	CO1
2	17	Explain the Millman's power transform theorem with neat sketch.	K4	CO2
3	18	Justify the RL and RC parallel circuits with diagrams.	K5	CO3
4	19	Conclude the Q factor in parallel resonance with examples.	K4	CO4
5	20	Develop a circuit for generation of 3- phase voltage.	K5	CO5