

PSG COLLEGE OF ARTS & SCIENCE
(AUTONOMOUS)

MSc DEGREE EXAMINATION DECEMBER 2025
(First Semester)

Branch - PHYSICS

INTEGRATED ELECTRONICS

Time: Three Hours

Maximum: 75 Marks

SECTION-A (10 Marks)

Answer ALL questions

ALL questions carry EQUAL marks

(10 × 1 = 10)

| Module No. | Question No. | Question | K Level | CO |
|------------|--------------|--|---------|-----|
| 1 | 1 | The binary addition of $(1011)_2$ and $(1101)_2$ is _____ a) $(11000)_2$ b) $(10100)_2$ c) $(11100)_2$ d) $(10010)_2$ | K1 | CO1 |
| | 2 | The 1's complement of $(101100)_2$ is _____ a) 101011 b) 010011 c) 110011 d) 010100 | K2 | CO1 |
| 2 | 3 | The output of a NOT gate is _____ a) Always 0 b) Always 1 c) Same as input d) Complement of input | K1 | CO2 |
| | 4 | A 3-variable K-map contains how many cells? a) 4 b) 6 c) 8 d) 16 | K2 | CO2 |
| 3 | 5 | A de-multiplexer can be used as _____ a) Data distributor b) Data selector c) Encoder d) Comparator | K1 | CO3 |
| | 6 | The invalid condition of an SR flip-flop occurs when _____ a) S = 0, R = 0 b) S = 1, R = 0 c) S = 1, R = 1 d) S = 0, R = 1 | K2 | CO3 |
| 4 | 7 | The basic logic family that uses diodes and transistors is called _____ a) Transistor-Transistor Logic (TTL) b) Complementary Metal Oxide Semiconductor (CMOS) c) Emitter Coupled Logic (ECL) d) Resistor-Transistor Logic (RTL) | K1 | CO4 |
| | 8 | The propagation delay in transistor logic circuits is mainly caused by _____ a) Input voltage levels b) Transistor switching time c) Diode resistance d) Power supply voltage | K2 | CO4 |
| 5 | 9 | The input impedance of an ideal op-amp is _____ a) Infinite b) Zero c) Very low d) Equal to output impedance | K1 | CO5 |
| | 10 | The common-mode rejection ratio (CMRR) of an ideal op-amp is _____ a) 0 b) 1 c) 100 d) Infinite | K2 | CO5 |

Cont...

SECTION - B (35 Marks)

Answer ALL questions

ALL questions carry EQUAL Marks

 $(5 \times 7 = 35)$

| Module No. | Question No. | Question | K Level | CO |
|------------|--------------|---|---------|-----|
| 1 | 11.a. | Explain binary addition and subtraction with suitable examples. (OR) | K2 | CO1 |
| | 11.b. | Estimate the X value of the following: (i) $277_{10} = X_2$ (ii) $10110_2 = X_{10}$ | | |
| 2 | 12.a. | Construct the truth table for a logic circuit having inputs A and B connected to an NAND gate. Draw the logic diagram and write the Boolean expression. (OR) | K3 | CO2 |
| | 12.b. | Use a Karnaugh map to simplify the logic expression $Y = A(BC + \bar{B}\bar{C}) + A\bar{B}C$. | | |
| 3 | 13.a. | Examine 2-to-1 multiplexer with circuit representation, truth table and logic diagram. (OR) | K4 | CO3 |
| | 13.b. | Explain J-K Master-Slave flip flops with neat diagram. | | |
| 4 | 14.a. | Summarize any five characteristics of digital logic families. (OR) | K5 | CO4 |
| | 14.b. | Measure the Transistor-Transistor Logic (TTL) characteristics. | | |
| 5 | 15.a. | Evaluate the gain, input and output impedances of Non-inverting Operational Amplifier. (OR) | K5 | CO5 |
| | 15.b. | Explain Digital to Analog conversion system. | | |

SECTION - C (30 Marks)

Answer ANY THREE questions

ALL questions carry EQUAL Marks

 $(3 \times 10 = 30)$

| Module No. | Question No. | Question | K Level | CO |
|------------|--------------|--|---------|-----|
| 1 | 16 | Explain the process of obtaining the 1's and 2's complement of a binary number with an examples. | K2 | CO1 |
| 2 | 17 | Apply Karnaugh map, to convert (i) $Y = \bar{B}\bar{C} + \bar{A}\bar{B} + ABC$ into its product-of-sum (POS) equation. (ii) $Y = (A+B)(\bar{B}+C)$ into its sum-of-product (SOP) equation. | K3 | CO2 |
| 3 | 18 | Illustrate the four-bit ring counter and shift counter with timing waveforms. | K4 | CO3 |
| 4 | 19 | Interpret the performance characteristics of various logic families. | K5 | CO4 |
| 5 | 20 | Evaluate the waveforms of OP-AMP Astable multivibrator and determine its frequency. | K5 | CO5 |