

PSG COLLEGE OF ARTS & SCIENCE  
(AUTONOMOUS)

MSc DEGREE EXAMINATION MAY 2022  
(Second Semester)

Branch – PHYSICS

ANALOG DIGITAL ELECTRONICS AND MICROPROCESSORS

Time: Three Hours

Maximum: 50 Marks

SECTION-A (5 Marks)

Answer ALL questions

ALL questions carry EQUAL marks  $(5 \times 1 = 5)$

1. A JFET is a \_\_\_\_\_ device.  
(a) Current driven device  
(c) rectifier device
2. Multiplex means \_\_\_\_\_.  
(a) many to one  
(c) one to one
3. A ring counter resembles a \_\_\_\_\_ register.  
(a) left or right  
(c) shift right
4. When in a negative scalar, both  $R_1$  and  $R_f$  are reduced to zero, the circuit functions as \_\_\_\_\_.  
(a) integrator  
(c) comparator
5. Microcontrollers are used for \_\_\_\_\_ applications.  
(a) un control  
(c) control

SECTION - B (15 Marks)

Answer ALL Questions

ALL Questions Carry EQUAL Marks

$(5 \times 3 = 15)$

6. a. Describe the construction and working of a FET.  
OR  
b. Explain the working of p-n junction diode under forward and reverse biasing.
7. a. Convert  $Y = AB + AC + BC$  into standard SOP form.  
OR  
b. What is demultiplexer? Explain the working of a 1 : 4 demultiplexer.
8. a. Explain the operation of the clocked RS flip flop with a diagram and truth table.  
OR  
b. Explain the operation of shift register with block diagram and waveform diagram.
9. a. Analyze the characteristics of an ideal OPAMP.  
OR  
b. With a neat circuit diagram, discuss the working of a monostable multivibrator.

Cont...

- 10 a Write any five instructions in data transfer group. Explain their function with examples.

OR

- b Explain Memory mapped I/O scheme and I/O mapped I/O scheme.

**SECTION -C (30 Marks)**

Answer ALL questions

ALL questions carry EQUAL Marks (5 x 6 = 30)

- 11 a Analyze an experiment to determine the characteristics of a transistor in a common emitter mode.

OR

- b Describe the construction and working of MOSFET with a neat circuit diagram.

- 12 a Discuss the method of three variable Karnaugh map simplification with necessary diagram.

OR

- b What is decoder? Explain the function of BCD to 7 segment decoder with a neat diagram.

- 13 a Explain the operation of the master slave flip flop with a neat diagram and give its timing diagram.

OR

- b Outline the operation of D flip flop with a diagram and truth table.

- 14 a Describe the construction and working of Schmitt trigger using OPAMP.

OR

- b With the circuit diagram, explain the working of OPAMP as triangular waveform generator. Give the expression for its frequency.

- 15 a Discuss the addressing modes of 8085 microprocessor with examples.

OR

- b Draw the block diagram of the architecture of 8085 microprocessor and explain the function of each block

Z-Z-Z

END