

**PSG COLLEGE OF ARTS & SCIENCE  
(AUTONOMOUS)**

**MSc DEGREE EXAMINATION MAY 2018  
(First Semester)**

**Branch - APPLIED ELECTRONICS**

**ANALOG & DIGITAL CIRCUIT DESIGN**

Time : Three Hours

Maximum : 75 Marks

**SECTION -A (30 Marks)**

Answer ALL questions

ALL questions carry **EQUAL** Marks ( 5 x 6 = 30)

- 1 a What is an integrator and explain its operation?  
OR  
b Describe briefly about the working of PLL.
- 2 a Write a short note on saw tooth generators.  
OR  
b Describe the operation of high voltage regulators.
- 3 a Explain with an example about the working of parity generator.  
OR  
b What is a decoder and explain its concept of working?
- 4 a Define the working of mealy machine.  
OR  
b Write short note on synchronous and sequential logic circuits.
- 5 a What are the types of FPGA and list them?  
OR  
b Write short note on Input / Output Block (IOB).

**SECTION -B (45 Marks)**

Answer any **THREE** questions

ALL questions carry **EQUAL** Marks ( 3 x 15 = 45)

- 6 Explain briefly about the working of Log and Anti log amplifier with circuit diagrams.
- 7 Describe working of IC 723 voltage regulator with neat circuit diagram.
- 8 Explain briefly about operation of multiplexer and demultiplexer with suitable examples.
- 9 Discuss in detail about the concept of state table minimization.
- 10 Explain briefly about the analysis and digital circuit using OrCAD.