#### ATX XIVIU

# PSG COLLEGE OF ARTS & SCIENCE

(AUTONOMOUS)

### **BSc DEGREE EXAMINATION DECEMBER 2019**

(Fifth Semester)

#### Branch-PHYSICS

# PRINCIPLES OF DIGITAL ELECTRONICS

Time: Three Hours Maximum: 75 Marks

## **SECTION-A (20 Marks)**

Answer ALL questions

ALL questions carry EQUAL marks (10x2 = 20)

- 1 Define Boolean Algebra.
- 2 State Demorgan's theorem.
- 3 What is multiplexer?
- 4 Define Ascii code.
- 5 Solve the following:  $(101)_2 + (110)_2$
- 6 What is 2's complement arithmetic method give example.
- 7 What are modulus counter?
- 8 What is the function of serial in serial out shift registers?
- 9 Distinguish between ROM and RAM.
- 10 What is D/A and A/D conversion.

#### **SECTION - B (25 Marks!**

Answer ALL Questions

ALL Questions Carry EQUAL Marks (5x5 = 25)

11 a Explain the OR operation with truth table and circuit diagram.

OR

- b State and explain Boolean laws.
- 12 a Solve the following: i) 10010<sub>2</sub> to Decimal ii) DE5<sub>16</sub> to Decimal OR

b Explain the seven segment decoder with a suitable diagram.

13 a What are flip flops? Describe the working of D flip flop with a neat diagram.

OR

- b State and explain Schmitt trigger.
- 14 a Explain about serial in parallel out shift registers.

 $\cap \mathbb{R}$ 

- b Discuss about synchronous counter.
- 15 a Define PROM & EPROM and explain it with its applications.

OR

b Explain about continuous A/D conversion.

#### SECTION - C (30 Marks)

Answer any **THREE** Questions

**ALL** Questions Carry **EQUAL** Marks  $(3 \times 10 = 30)$ 

- State and explain about sum of product method using kamaugh Map. with their truth table and examples.
- Distinguish between multiplexer and demultiplexer Discuss 1 to 16 decoders with diagram.
- Explain the construction and working of RS flip flop and clocked RS flip flop.
- With a suitable diagram, explain the working of parallel in serial out and