

**PSG COLLEGE OF ARTS & SCIENCE**  
(AUTONOMOUS)  
**BSc DEGREE EXAMINATION MAY 2019**  
(Third Semester)

**Branch - MATHEMATICS WITH COMPUTER APPLICATIONS**

**DIGITAL ELECTRONICS**

Time : Three Hours

Maximum : 75 Marks

**SECTION-A (20 Marks)**

Answer **ALL** questions

**ALL** questions carry **EQUAL** marks (10x2 = 20)

- 1 Define the Analog Vs Digital.
- 2 What is meant by Duty Cycle?
- 3 Write the Associative Law.
- 4 Draw the symbol of NAND gate with truth table.
- 5 Write the truth table of Binary Addition.
- 6 Draw the diagram of Half Subtractor.
- 7 Define Shift Register.
- 8 Write short notes Decade Counter.
- 9 Define Binary Ladder D/A Converter.
- 10 What are types of A/D converter? '

**SECTION - B (25 Marks)**

Answer **ALL** Questions

**ALL** Questions Carry **EQUAL** Marks (5 x 5 = 25)

- 11 a Write the Excess - 3 code with example.  
OR  
b Convert  $(1110100011010110)_2 = ()_6$ .
- 12 a Explain the operation of NAND gate with pin diagram.  
OR  
b Discuss about the Distributive Laws.
- 13 a With a neat diagram, explain the Full adder.  
OR  
b Explain 1's and 2's compliment with example.
- 14 a What is meant by flip flop? Explain the RS Flip flop.  
OR  
b Explain the Ring Counter with neat diagram.
- 15 a Write the resolution of D/A converter.  
OR  
b Define A/D converter and explain the simultaneous conversions.

**SECTION - C (30 Marks)**

Answer any **THREE** Questions

**ALL** Questions Carry **EQUAL** Marks (3 x 10 = 30)

- 16 Write the following : (i) GRAY code (ii) Parity code.
- 17 Explain the Demorgan's theorem.
- 18 Explain the Decoder with neat diagram.
- 19 With neat diagram, explain the synchronous counter.
- 20 Describe the Binary ladder D/A Converter.