

PSG COLLEGE OF ARTS & SCIENCE  
(AUTONOMOUS)

BSc DEGREE EXAMINATION MAY 2019  
(Fifth Semester)

Branch – PHYSICS

**PRINCIPLES OF DIGITAL ELECTRONICS**

Time : Three Hours

Maximum : 75 Marks

**SECTION-A (20 Marks)**

Answer ALL questions

ALL questions carry EQUAL marks (10 x 2 = 20)

- 1 State the Boolean laws for the AND operation.
- 2 What do you understand by the terms sum-of-products and product-of-sums? Give one example for each.
- 3 What is the acronym for ASCII Code? What is its purpose?
- 4 Convert  $FFA0H = ( )_2 = ( )_8 = ( )_{10}$ .
- 5 The 1's complement of  $(11001011)_2 = ?$   
The 2's complement of  $(10110010)_2 = ?$
- 6 How many gates are involved in a half subtractor? What are their actions?
- 7 Which shift register performs both shift left and shift right operations? Give one example for this operation.
- 8 How many flip flops are required for constructing MOD – 5 counter? How many states are skipped during the operation? Why?
- 9 What is the difference between ROM and PROM? How you can signify both?
- 10 Which hardware components is best suited for digital to analog conversion? Why? How?

**SECTION - B (25 Marks)**

Answer ALL Questions

ALL Questions Carry EQUAL Marks (5 x 5 = 25)

- 11 a What does AND, OR and NOT operations represent in the digital logic circuits? Explain with their truth tables and symbolic representations.  
OR  
b State and prove DeMorgan's theorem.
- 12 a What is meant by Demultiplexing? Explain a 16-1 demultiplier.  
OR  
b Convert  $(945)_{10} = ( )_8 = ( )_{16}$ .  
Convert  $(11010110)_2 = ( )_{10} = ( )_{16}$   
Convert to excess 3 code =  $(1011)_2 = ( )_{\text{excess 3}}$   
Convert to Gray Code  $(10110110)_2$   
Convert to binary  $(01110110)$  gray code.
- 13 a How to perform a 3-bit arithmetic addition and subtraction? Explain using Full adder and subtrator circuits.  
OR  
b What is the purpose of a Schmitt Trigger? Explain its working with the necessary circuit diagram.
- 14 a With a neat logic circuit diagram explain a 4-bit serial IN serial OUT shift register.  
OR  
c What is the action of decoding gates in asynchronous counters and synchronous counters? Explain.

Cont...

- 15 a What does EPROM signify? How does it work? Explain with proper diagrams.

OR

- b Explain the counter method of A/D conversion. Draw circuits wherever required.

**SECTION - C (30 Marks)**

Answer any **THREE** Questions

**ALL** Questions Carry **EQUAL** Marks (3 x 10 = 30)

- 16 State the various boolean laws and theorems. Apply the laws to simplify the following expression by Karnaugh mapping, draw AND – OR logic gates.

$$Y = A \bar{B} \bar{C} \bar{D} + \bar{A} B \bar{C} \bar{D} + \bar{A} \bar{B} C \bar{D} + \bar{A} \bar{B} \bar{C} D$$

- 17 What are Encoders, Parity generators/checkers? Explain with examples.
- 18 What is a Flip Flop? Explain a RS flip flop and a JK master /slave flip flop with suitable circuits and truth tables.
- 19 Explain the action of a 8-bit ring counter. Draw a neat logic diagram and wave form representation.
- 20 Draw the binary ladder network for the digital to Analog conversion and explain the ladder in steps.

Z-Z-Z

END