

CORE ELECTIV – I : SEMICONDUCTOR ELECTRONICS

Time : Three Hours

Maximum : 75 Marks

SECTION-A (20 Marks)

Answer ALL questions

ALL questions carry EQUAL marks

(10 x 2 = 20)

- 1 What are N-type extrinsic semiconductors?
- 2 Define ripple factors.
- 3 What are the three important static characteristics of transistor?
- 4 What is the need for biasing a transistor?
- 5 State any two advantages of negative feedback.
- 6 Explain the summing point of an OPAMP.
- 7 Give the frequency of oscillation of a Hartley oscillator.
- 8 What is the advantage of frequency modulation over amplitude modulation?
- 9 What is clipping circuit?
- 10 What is a bistable multivibrator?

SECTION - B (25 Marks)

Answer ALL Questions

ALL Questions Carry EQUAL Marks (5 x 5 = 25)

- 11 a Explain the volt-ampere characteristics of p-n junction.
OR
b Discuss the voltage regulation of a zener diode.
- 12 a Discuss the input and output characteristics of a common base transistor.
OR
b Discuss the operation of a push pull amplifier.
- 13 a Describe the working of an emitter follower circuit.
OR
b Discuss the effects of negative current feedback.
- 14 a Discuss in detail the working of a Hartley oscillator.
OR
b What are the different types of Modulation? Explain amplitude modulation.
- 15 a What are clipping and clamping circuits?
OR
b Discuss the switching action of a transistor.

SECTION - C (30 Marks)

Answer any THREE Questions

ALL Questions Carry EQUAL Marks (3 x 10 = 30)

- 16 Explain in detail the working of a full wave rectifier.
- 17 With a neat circuit discuss the working of RC coupled amplifier.
- 18 Give the characteristics of an ideal OPAMP. Discuss the applications of OPAMP as Integrator and differentiator.
- 19 Discuss the stages of a super heterodyne receiver.
- 20 Explain the construction, working and characteristics of FET.